Wireless World

FEBRUARY 1952 · TWO SHILLINGS

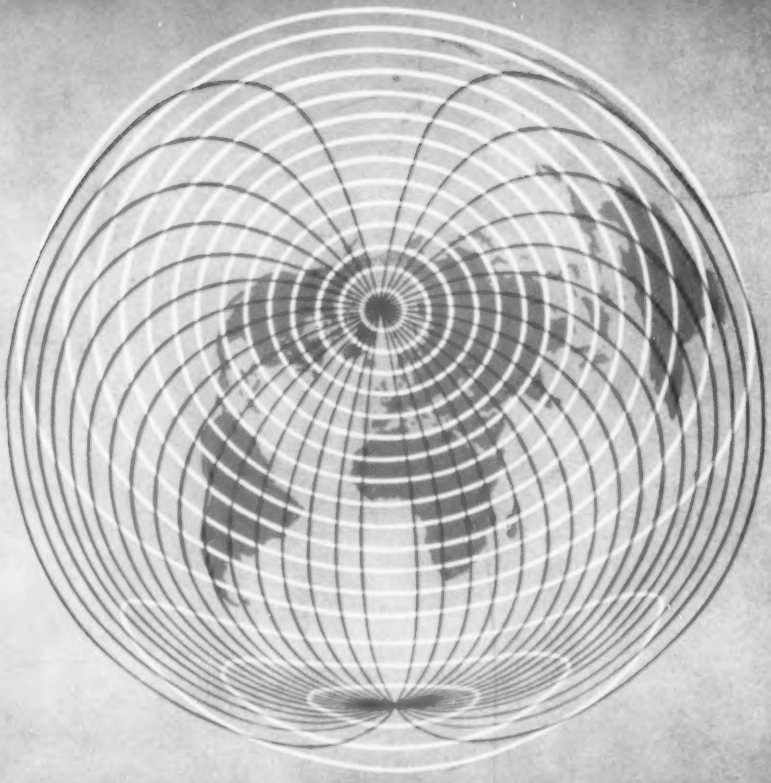

RADIO, TELEVISION AND ELECTRONICS

B.B.C. INSTALL
BICC R.F. CABLES
IN LIME GROVE T/V STUDIOS

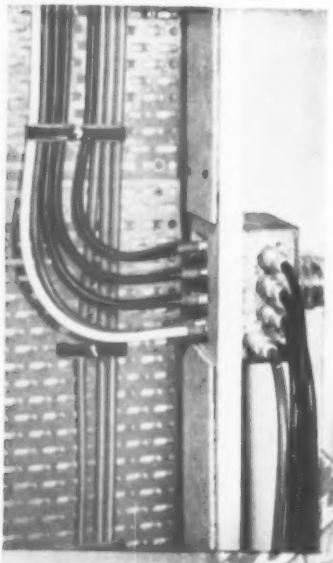

These double screened co-axial BICC Radio Frequency Cables were recently installed by the BBC in their new T.V. Studios at Lime Grove, Shepherds Bush, London. They are used in the distribution network carrying television picture and other video wave forms to studios and control rooms throughout the building. For identification purposes BICC supplied these Radio Frequency Cables in seven colours.

This is another example of BICC service to suit individual requirements.

B.I. Callender's

RADIO FREQUENCY CABLES

BRITISH INSULATED CALLENDER'S CABLES LIMITED
NORFOLK HOUSE, NORFOLK STREET, LONDON, W.C.2

Model 8

UNIVERSAL AVOMETER

20,000 ohms per volt *plus* AUTOMATIC Overload Protection

Produced in response to a demand for a high sensitivity version of the world-famous Universal AvoMeter, this model incorporates the traditional design features of its predecessors, so highly valued for simplicity of operation and compact portability.

It has a sensitivity of 20,000 ohms per volt on all D.C. voltage ranges and 1,000 ohms per volt on A.C. ranges from 100V. upwards. A decibel scale is provided for audio frequency tests. In addition, a press button has been incorporated which reverses the direction of current through the moving coil, and thus obviates the inconvenience of changing over test leads when the current direction reverses. It also simplifies the testing of potentials, both positive and negative, about a common reference point. A wide range of resistance measurements can be made using internal batteries, separate zero adjustment being provided for each range.

It is of importance to note that this model incorporates the "AVO" automatic cut-out for protection against inadvertent overloads.

Size 8¼" x 7½" x 4½"
Weight 6½lbs. (including leads)

£19 . 10s.

The following accessories are available to widen still further the ranges of the instrument:— A Resistance Range Extension Unit to extend the limits of measurement from 0.025 ohms to 200MΩ, a 10kV. D.C. multiplier and a number of A.C. current transformers.

D.C. VOLTAGE	D.C. CURRENT	A.C. VOLTAGE	A.C. CURRENT	RESISTANCE	
2.5V.	50μA.	2.5V.	100mA.	*First indication 0.5Ω.*	
10V.	250μA.	10V.	1A.	*Maximum indication 20MΩ.*	
25V.	1mA.	25V.	2.5A.	0—2,000Ω	using internal batteries
100V.	10mA.	100V.	10A.	0—200,000Ω	
250V.	100mA.	250V.	—	0—20MΩ	
1,000V.	1A.	1,000V.	—	0—200MΩ	using external batteries
2,500V.	10A.	2,500V	—		

THE AUTOMATIC COIL WINDER & ELECTRICAL EQUIPMENT CO. LTD.
WINDER HOUSE • DOUGLAS STREET • LONDON S.W.1 *Telephone* VICtoria 3404—9

A 1 A 8/1

A QUESTION FOR DESIGNERS

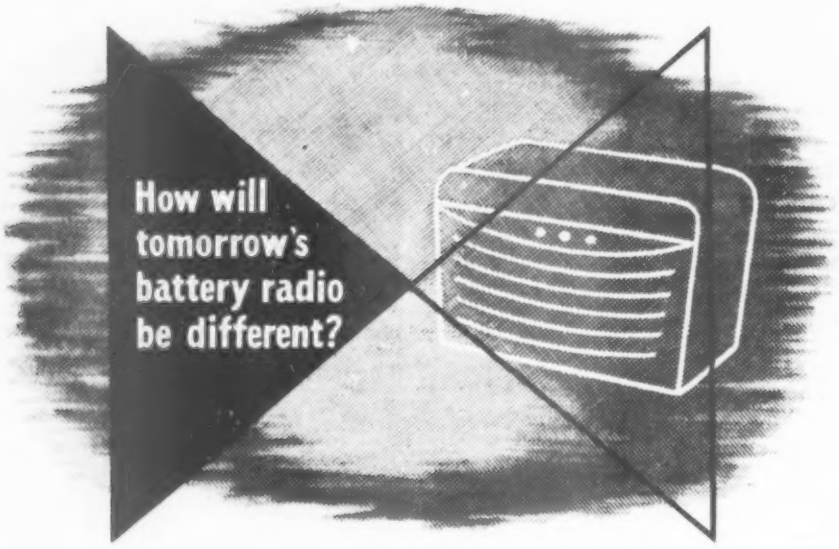

Circuits progress; new cases will evolve from new materials and techniques — but the one outstanding feature of tomorrow's battery radio is here today —

VENNER *Lightweight Accumulators*

One third the weight and half the size of standard accumulators of comparable capacity, these revolutionary miniature storage batteries *maintain a steady 1.5 volt output on load throughout their discharge period.*

Thus they eliminate the need for constant replacement due to voltage drop, which is the failing of all other conventional L.T. batteries.

In addition, Venner Lightweight Accumulators are completely non-spillable, are unharmed by high charge and discharge rates and may be left in discharged condition without damage.

The services of our technical department are freely at your disposal in investigating the many operational advantages of these accumulators.

For full technical data please write for leaflet VAO11/WW

VENNER *ACCUMULATORS LTD*

(Distributors for London and Home Counties :—
THE DART TRADING CO., (ENGINEERING) LTD.,
173 SLOANE STREET, LONDON, S.W.1. Tel.: SLOane 8532)

KINGSTON-BY-PASS, NEW MALDEN, SURREY. *Telephone:* MALden 2442 *(6 lines)*

ACTUAL SIZE

A High-Slope Low-Noise R.F. Pentode with low power consumption

The combination of good slope to capacity ratio, low noise factor, and low power consumption makes this new Mullard R.F. pentode an ideal valve for use in all types of communications equipment operating at V.H.F. Its slope to capacity ratio approaches unity, and this makes it specially suitable for use in Wide Band Amplifiers.

Used as a neutralized triode, and followed by a grounded grid stage (cascode), the EF95 has a typical noise factor of 3.5 when operated at 180 Mc/s.

With a heater current of only 0·175A., this valve shows a large saving in power consumption over previous valves of a similar class. This saving in power is emphasized in applications where large numbers of R.F. stages are involved.

The EF95 has identical characteristics to the American 6AK5 and may be used as a direct replacement for this valve.

For full technical information on this and other valves in the Mullard range please write to the address below.

Heater		Capacitances	
V_h	6.3 V	c_{in}	4.0 μμF
I_h	0.175 A	c_{out}	2.8 μμF
		c_{g1-g3}	0.02 μμF
Characteristics			
V_a	120 V		
V_{g2}	120 V	**Limiting Values**	
V_{g1}	−2.0 V	V_a max.	180 V
I_a	7.5 mA	p_a max.	1.7 W
I_{g2}	2.5 mA	V_{g2} max.	140 V
g_m	5.0 mA/V	p_{g2} max.	0.5 W
r_a	0.34 MΩ	I_k max.	18 mA

Base B7G

Mullard

MULLARD LTD COMMUNICATIONS AND INDUSTRIAL VALVE DEPARTMENT · CENTURY HOUSE · SHAFTESBURY AVENUE · LONDON · WC2

MVT 11

MANNING BRITAIN'S RADAR DEFENCES

There's a place for YOU..

in the PART-TIME R·A·F

In building up Britain's air defences the Royal Air Force needs a large, fully trained reserve of men and women on whom it can rely in any emergency. On their skill the whole fighting efficiency of the R.A.F. hinges—and there's a place for you among them. In the cheerful atmosphere of the part-time R.A.F. you will find yourself doing work that is vital and fascinating, among people you will be proud to call your friends. You can get full particulars by posting the coupon now.

TO : ROYAL AIR FORCE (W.D.715) , VICTORY HOUSE, LONDON, W.C.2

Please send particulars of part-time service with the R.A.F. (*Applicants from British Isles only*)

NAME _____ ADDRESS _____

(*If ex-R.A.F. or ex-W.A.A.F. give rank, trade and No.*)

★ IF YOU ARE BETWEEN 14 AND 17—AND KEEN—JOIN THE A.T.C. ★

PREMIER RADIO Company

(REGD.) RADIO — B. H. MORRIS & CO. (RADIO) LTD. — ESTAB. 40 YRS. TELEVISION

Now being Delivered!

PREMIER MAGNETIC TAPE RECORDING KIT

£29 · 8 · 0 *Including ALL parts, Valves, Cabinet, Loudspeaker, etc., but excluding Microphone.*

(Carriage and Packing 15/-)

The kit incorporates the **LANE TAPE TABLE** already assembled and ready for use, a **6 VALVE SPECIALLY DESIGNED AMPLIFIER KIT including Bias and Erase Oscillator for use with the above unit, a WELL MADE WALNUT FINISHED TABLE CABINET** is Supplied to house the complete unit. Outside dimensions when closed: Height 13¼in., Length 17in., Depth 13¼in.

SPECIAL FEATURES of the Amplifier include separate Bass and Treble lift controls, high and low gain Input Sockets, Record Playback indicator, etc. May be fed from Microphone, pick-up or directly from the Speaker terminals of your radio. Chassis size 14" x 9" x 2½".

SPECIFICATION of the LANE TAPE TABLE:—

HEAVY FLYWHEEL. Made to high standards and incorporating a heavy flywheel ensuring true running and low level of "Wow" and "Flutter" throughout the full length of tape.

FAST RE-WIND. Provision is made for fast re-wind and the mechanical action is simple, ensuring reliability through long life.

HEAVY DUAL MOTOR. The Motor is **HEAVY DUTY** model with **AMPLE RESERVE** of power.

HIGH FIDELITY RECORD PLAYBACK (1 hour approx. playing). The Table is fitted with High Fidelity record playback and separate erase heads, both of which are enclosed in **MU-METAL** shields. The heads are half track size allowing app. 1 hour playing from standard 1,200ft. reel of tape. All standard heads are wound to high impedance.

TAPE SPEED 7½in. sec. A.C. 200-250 50 Cycles only.

Moving Coil Microphones suitable for use with the above are available from stock £5. 12s. 6d.

As is usual in all PREMIER KITS every single item down to the last nut and bolt is supplied. The chassis is punched and lay-out diagrams and theoretical circuits are included. EACH UNIT MAY BE PURCHASED SEPARATELY:

LANE TAPE TABLE £16 10s. 0d., 7/6 packing and carriage.

PREMIER AMPLIFIER KIT INCLUDING 8in. SPEAKER £7 19s. 6d. 2/6 packing and carriage.

CABINET £4 18s. 6d., 5/- packing and carriage.

INSTRUCTIONAL BOOKLET 2/6

This is credited if a complete Kit of the Tape Recorder is ordered.

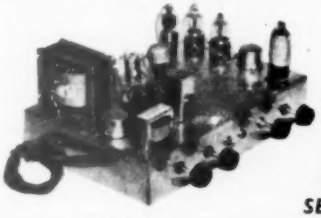

The above Recording Outfit has been designed for use with M.C.-1-111 SCOTCH BOY Magnetic Tape. With this high quality tape a frequency range of 50 c.p.s. to 9,000 c.p.s. at tape speed of 7½in. sec. can be readily achieved.

1,200 ft. reels 35/-.

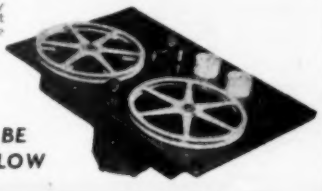

WORKING MODELS MAY BE SEEN AT THE ADDRESS BELOW

THIS IS OUR ONLY ADDRESS

207 · EDGWARE ROAD · LONDON · W·2

TERMS OF BUSINESS: Cash with order or C.O.D. over £1. Please add 1/- for Post. Orders under 10/-, 1/6 under 40/- unless otherwise stated.

Telephones: AMBassador 4033, PADdington 3271/2

OPEN UNTIL 6PM ON SATURDAYS

PREMIER RADIO Company

REGD. RADIO — E. H. MORRIS & CO. (RADIO) LTD. — ESTD. 40 YRS. TELEVISION

BRAND NEW R1155 RECEIVERS
In original cases, complete with 10 valves. £12 10 -
7/6 packing and carriage.

BRAND NEW R1355 RECEIVERS
In original cases, as specified for the "Inexpensive Television," complete with 11 valves. £2 15 -, 7/6 packing and carriage.

HEADPHONES
Balanced Armature Low Resistance
Type 1 5 11 pair. Type 3, 7 11 pair
High Resistance
12 6 pair
Moving Reed
Type 3, 8 11 pair
Lightweight High Resistance
14 6 pair

TRANSMITTER RECEIVER TYPE TR9H
Consists of Transmitter type T1196 and Receiver R1139 in one case. This is a 9 valve Battery operated Unit covering 4.3 M. to 6.6 M/s. Crystal controlled, complete with valves. 50 -, plus 7/6 packing and postage.

TANNOY HAND MICROPHONES
With switch in handle. 4 11.

MOVING COIL MICROPHONE INSERTS
A moving coil loudspeaker or microphone unit, 1¼in. dia. 3 -.

CRYSTAL MICROPHONE
An entirely insulated crystal microphone which can be safely used on A.C./D.C. amplifiers. High impedance. No background noise, really natural tone. The ideal Mike for tape, wire and disc recording and sound projectors. Price 22 6.

PREMIER BABY ALARM KIT

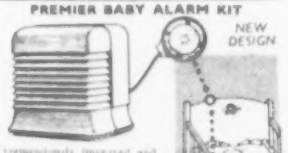

NEW DESIGN

A tremendously improved and re-designed version of the famous Premier Baby Alarm Kit, consisting of a Kit of Parts in Plastic Cabinet to construct a device to enable Baby's cries, or even breathing, to be heard in any selected room in the house. Consists of a 2-valve Amplifier (A.C. mains operated 200/250 volts), with a Midget Telephone used as a Microphone. A 3½in. loud speaker is now incorporated in the Kit which, together with other improvements in the design, have resulted in tremendously improved sensitivity and quality of reproduction. Complete with valves Circuit and Instructions. Price 69 6.

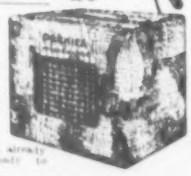

PREMIER De Luxe BABY ALARM
This is a completely wired and tested amplifier housed in a grey resin-covered cabinet. Entirely self-contained for use on A.C. or D.C. mains supply of 200/250 volts already assembled and ready to plug in.
Reduced price £8 5 -, plus 7/6 p. & p.

MAINS NOISE ELIMINATOR KIT
Two specially designed chokes with three smoothing condensers with circuit diagram. Cuts out all mains noise. Can be assembled inside existing receiver. 6 - complete.

BUILD A PROFESSIONAL LOOKING RADIO AT LESS THAN HALF TO-DAY'S PRICE
We can supply all the parts to help you.

Bakelite Cabinet (Brown or Ivory)	17 6
Packing and insurance	2 6
Punched chassis, 3-valve plus rectifier T.R.F.	3 9
Engraved Glass Dials, 180-550 and 800-2,200 m.	1 6
With station names, new wavebands	
T.R.F. Coils, 180-550, 800-2,200 metres, pair	6 6
Drum (12in. diam.)	1 6
Driving cord	1 6
Double pointer	4d
Spring	3d
Nylon cord (yard)	6d
Dial Pencil Plate	2 6

SEND 1 6 FOR EASY TO FOLLOW POINT TO POINT DIAGRAMS AND CIRCUIT DIAGRAM which shows how YOU can build the Receiver illustrated above.

THE COMPLETE KIT
to construct a 3 valve plus rectifier TRF Receiver for use on 200/250 v. A.C. mains can be supplied at £6 9 6 plus 2/6 packing and carriage.

Each Kit is complete in every detail, nothing has to be made or improvised. Easy to follow point to point diagrams are supplied, making construction very simple. The Dial is illuminated and the Receiver housed in a Bakelite Cabinet size 12in. x 9in. x 6in. presents an attractive appearance. The valve line-up is 7S7A—H.F. Pentode VR116—Detector. ATP4—Output, and Metal Rectifier. Waveband coverage is for the medium and long bands. Choice of Walnut or Ivory coloured Cabinet.

DULCI MIDGET RECEIVER

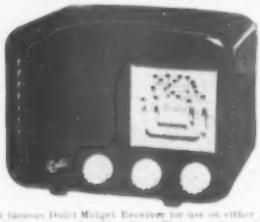

The famous Dulci Midget Receiver for use on either A.C. or D.C. mains, 200/250 volts. This is a 2-waveband 4 v. Superhet Receiver covering the short waveband from 13.5 metres to 50 metres, and the medium waveband from 200-500 metres. Can be supplied in either ivory or brown bakelite cabinet.
Size: 7½in. length, 6in. height, 5¼in. depth.
This receiver is fully covered by the manufacturer's guarantee. Price £8 15 -, carriage paid.

BATTERY CHARGER KITS
All incorporate metal rectifiers. Transformers are suitable for 200-250 v. A.C. 50 cycle MAINS

Cat. No.		
2001	Charges 6 volt accumulator at 1 amp. Resistance supplied to charge 2 v. accumulator	£1 2 6
2003	Charges 12 volt accumulator at 1 amp.	£1 7 6

ACCUMULATORS
Ex world-famous maker. 2 volt 10 a. 4/11.

IMPORTANT ANNOUNCEMENT: All prices quoted in our advertisements are those ruling at the time of submitting advertisement copy, and are subject to alteration without notice.

H.T. ELIMINATOR AND TRICKLE CHARGER KIT
All parts to construct an eliminator to give an output of 120 volts at 20 m.A., and 2 volts to charge an accumulator. Uses metal rectifier. £2.

THREE-PIECE AERIAL
Ex-U.S.A. 12ft. 6 sft. screw-in sections of copper-plated steel, highly flexible with non-stick screw fits, tapering ¾in. to ¼in. *Brand new* in container. 6 9, packing and carriage 1 6. Insulated Base 2 6.

EX-U.S.A. U.H.F. AERIAL
with matched detector stage, consisting of V.R. 92 valve, etc. Brand new, in carton 5 -.

ADJUSTABLE BENCH LAMP
Complete with flex, lampholder and reflector. 25 -. Post and insurance 2 -.

BURGOYNE SOLDER GUNS, 75/-

TUNING CONDENSERS
4-Gang .0005 mfd. Ceramic insulation, ¼in. spindle, 5 - | 3-Gang .0005 mfd., ¼in. spindle 7 6.

GERMANIUM CRYSTAL DIODES
Wire ends, midget size. The ideal Crystal Detector. G.E.C. or B.T.H. 4 6

PREMIER SUPERHET COILS
16-50, 180-550, 800-2,000 metres, set with circuit. 10 6

METAL RECTIFIERS—FULL WAVE
6 v. 1 amp. 4 - | 12 v. 1 amp. 8 -.
E.H.T. Pencil Type:
Output, 650v. 1 m.A. 4 7 each, 1,000v. 1 m.A., 6 - each

CAR BATTERIES—*BRAND NEW*

6 v. 11 plate—WALKER
Hght. 6¾in., Lgth. 7¾in., Dpth. 6¼in. Price 77 6.
6 v. 15 plate—READING
Hght. 7¾in., Lgth. 9¼in., Dpth. 7¼in. Price 95 -.
6 v. 15 plate—DELCO-REMY. Hght. 7¾in., Lgth. 9¼in., Dpth. 7¼in. Price 97 6.
6 v. 23 plate—DELCO-REMY. Hght. 9¾in., Lgth. 13¾in., Dpth. 7¼in. Price 110 -.
12 v. 9 plate—WALKER
Hght. 8¾in., Lgth. 17¾in., Dpth. 6¾in. Price 110 -.
6 v. 170 amp. Tank Case: Hght. 13¼in., Lgth. 15¾in., Dpth. 7¾in. Price 110 -.
ALL PRICES PLUS 7/6 CARR. & PACKING.

FRACTIONAL H.P. MOTOR
A 50 v. 3 phase A.C. motor, 1/40th h.p. by famous maker. Supplied complete with resistor, condenser and circuit diagram to convert the motor to ¼ h.p. for use on 240 v. single phase A.C. mains. Brand new 25 -, plus 2 6 carriage and packing.

SPECIAL OFFER of
ADMIRALTY REFLEX-RE-ENTRANT P.A. LOUDSPEAKERS

W/coil 7 ohms. Matching transformers 4.5-1 and 6-1 ratios with volume control at max. Very sensitive and directional. Single Unit, 55 -. Twin Units, 75 -. Plus 3 - carriage and packing.

SUPER QUALITY TELEVISION MAGNIFYING LENS
To suit 9in., 6in. or 7in. Tubes. Increase picture size considerably. 25 - each.

WHITE RUBBER MASK
For 6in. Tube, 5 6.

P.M. MOVING COIL LOUDSPEAKERS
(3 ohm voice coils)

7in. Goodmans	15 -	6in. Truvox	12 6
8in. Plessey	15 -	8in. Plessey	14 6
5in. Plessey	12 6	10in. P.M.C.	27 6
5in. Truvox	12 6	12in. Truvox	70 -
5in. Rola	13 6		

THIS IS OUR ONLY ADDRESS

207 · EDGWARE ROAD · LONDON · W.2

TERMS OF BUSINESS:
Cash with order or C.O.D. over £1. Please add 1/- for Post Orders under 10/-, 1/6 under 40/- unless otherwise stated.

Telephones: AMBassador 4033, PADdington 3271/2

OPEN UNTIL 6PM ON SATURDAYS

IMPORTANT ANNOUNCEMENT: WE CANNOT ACCEPT RESPONSIBILITY FOR, NOR CAN WE GUARANTEE ANY—

PREMIER RADIO Company

(REGD.) ESTAB. 40 YRS.

S. H. MORRIS & CO. (RADIO) LTD.

RADIO

PREMIER TABLE RADIOGRAM CABINET (WALNUT FINISH)

Outside dimensions: 24in. high, 14in. deep, 14½in. wide. Price £2 5/- plus 5/- carriage and packing.

Special Offer—**AT ALMOST HALF PRICE PLESSEY GRAMOPHONE UNITS**

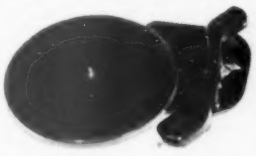

The Motor, Tone arm, and Magnetic Pick-up is in one Unit, with Automatic stop and start.
For use on 200/250 v. A.C. mains 50 cycles. Limited quantity only. **£4 19 6**, plus 5/- packing and carriage.

RADIO CABINET (WALNUT FINISH)

Outside dimensions: 18½in. high, 11½in. deep, 16½in. wide

Price **£2 2 6**, plus 7/6 carr./pkg.

GRAMOPHONE UNITS

Collaro RC500 Autochanger Unit, single speed, 78 r.p.m., already mounted on metal frame, ready to drop into cabinet.	£16 10 0
Collaro Autochanger 3-speed Unit, including Crystal Head for long playing and standard recordings	£18 14 1
Connoisseur 2-speed Gramophone Unit. LE88 Pick-up	£22 18 8
Pick-up and 2 heads for above	£10 0 8
Conrad Rim Drive Gramophone Unit. Less Pick-up arm, 78 r.p.m.	£4 3 10
Ditto, 33 r.p.m.	£4 7 5
Decca 3-speed Rim Drive Gramophone Unit. LE88 Pick-up	£7 3 4
Decca Single-speed Rim Drive. LE88 Pick-up, 78 r.p.m.	£3 14 4
Ditto, 33 r.p.m.	£3 14 4
Decca Pick-up with 2 heads, one long playing and one standard	£7 0 0
Plessey Autochanger 3-speed magnetic head, plays mixed records	£23 13 0
Collaro Rim Drive Magnetic Unit, 78 r.p.m.	£6 11 4

Plus Packing and Carriage.

ALL THE ABOVE ARE FOR USE ON A.C. MAINS ONLY.

PX25 AMPLIFIERS

A superb push pull 15 watt model with all the latest refinements, extended tone control range, 3in. moving coil panel meter for current and distortion checks, oil filled condensers, fuses in circuits, two smoothing chokes and although in a steel case the front panel extends to fit on a 19in. standard rack. The high gain circuit of latest design will give full volume from the smallest input. 500 ohm output. Less valves. **£5 5/-** plus **£1/1/-** carriage, packing and insurance.

PREMIER 3-BAND COIL PACK

Consists of a wired and aligned Coil Pack of the most Modern Type incorporating such features as Air Dielectric Trimmers, Litz wound medium wave coils. Tuned R.F. stage, covers 13-14, 40-129, 200-557 metres. Dimensions of pack: 6in. × 4½in. × 2½in. Complete circuit is supplied. Price **29 6**.

PREMIER 4-BAND COIL PACK

Consists of a fully wired and calibrated Coil Pack of the latest type. 5 Position switch includes a Gram. position. Wavebands covered: 13.8-32 metres (22-8.8 Mcs.) 51-190 metres (5.9-1.57 Mcs.), 190-540 metres and 900-2100 metres. Air Dielectric Trimmers on all Short wave Coils. Unit consists of 3 Screened Sections, Aerial, R.F. and Oscillator. Dimensions of Pack, 6in. × 4½in. × 2½in. Price with circuit diagram, **£4 11 8**.

PREMIER TELEVISOR CABINET FOR 12in. TUBE TELEVISOR

A handsome walnut finished cabinet. Primarily designed for our own Kits. They are quite suitable for most of the kits published in the various Radio periodicals. For this reason the holes for control knobs have not been drilled. A baffle board suitable for a 10in. Loudspeaker is provided. Outside dimensions 23½in. high, 20½in. deep, 16in. wide **£9 9/-**, plus 7/6 packing and carriage.

CORRECT ASPECT WHITE RUBBER MASK

For 12in. Round or Flat faced Tube. **16 11**.

TELEVISION

RADIO CABINET (WALNUT FINISH)

Outside dimensions: 18½in. high, 9in. deep, 17in. wide

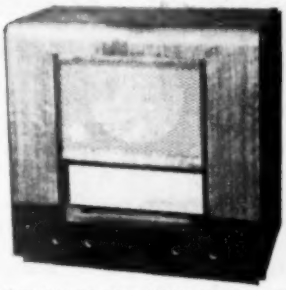

A beautifully made cabinet. **£3 10/-**, plus 7/6 carr./pkg.

5-VALVE SUPERHET RADIO CHASSIS

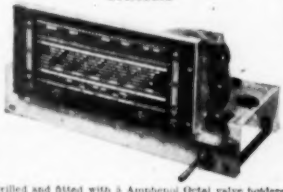

Drilled and fitted with 5 Amphenol Octal valve holders, aerial, earth and gramophone sockets, necessary cut-outs for all control mountings, mains transformer and 500 PF tuning gang condenser. Fitted with Full Vision Drive assembly consisting of unbreakable Perspex 3-coloured scale for long, medium and short wave-bands. Calibrated in metres, kilocycles and station names. Price **39 6**.

AS A SPECIAL OFFER—CABINET ILLUSTRATED ABOVE AND CHASSIS, TOGETHER £5. 5. 0. Plus 7/6 Carr. Pkg. & Insurance.

RADIO CABINET (WALNUT FINISH)

Outside dimensions: 17in. high, 11in. deep, 16in. wide.

Price **£2 2 6**, plus 7/6 carr./pkg.

THIS IS OUR ONLY ADDRESS

207 · EDGWARE ROAD · LONDON · W.2

TERMS OF BUSINESS:
Cash with order or C.O.D. over £1. Please add 1/- for Post. Orders under 10/- 1/6 under 40/- unless otherwise stated.

Telephones: AMBassador 4033, PADdington 3271/2

OPEN UNTIL 6PM ON SATURDAYS

—KIT OR COMPONENT SOLD AS A PREMIER PRODUCT BY FIRMS OTHER THAN OURSELVES

HIRE PURCHASE SPECIALISTS

TRADE & EXPORT ENQUIRIES INVITED

RADIO & TELEVISION
ELECTRICAL APPLIANCES
ELECTRIC TOOLS
KITS

RADIO CENTRE

TEST EQUIPMENT
HI-FI REPRODUCTION
TAPE RECORDERS
AMPLIFIERS

Presenting . . .

The "BURGOYNE"

Magnetic Recording Head

FOR SUPERIOR PERFORMANCE AT LOWER COST

Record/Playback and Erase Heads giving first-class frequency response

★ HIGH IMPEDANCE ★ POSITIVE FIXING METHOD ★ HALF TRACK WIDTH
★ TOTALLY ENCLOSED WITH TAPE GUIDE ★ WIDE FREQUENCY RANGE

A competitively priced Head equal to the best. *Ample supplies in stock for manufacturers etc.*

★ DISTRIBUTED EXCLUSIVELY BY M·O·S ★

ONLY **39/6** Post Free

Record/Playback or Erase Head

The "LANE" Tape Tables *and accessories*

"LANE" Tape Table

£16. 10s. (Carr. Pkg. 10/-)

130/- deposit and 12 monthly payments of 20/-.

Incorporating features ensuring low level of "wow" and "flutter" for full length of tape, the LANE Tape Table is precision built and uses a heavy duty motor with ample reserve of power. Provision is made for fast re-wind. The LANE uses half track high fidelity heads enclosed in metal shields, and of high impedance.

● Tape speed 7½in. per second ● Size 11½in. x 15½in. x 7in. ● Heavy flywheel ● Circuit diagram included ● Take up spool supplied ● For use on A.C. mains.

Hundreds of satisfied customers have purchased the Tape Table described above and NOW we have every confidence in presenting an entirely new LANE production on which we can accept orders for early delivery:—

Take up and fast re-wind control

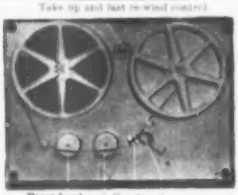

Erase head Capstan
Record playback head Pinch roller

"VERDIK" Tape Table

£25 (Carr. Pkg. 10/-)

£9 deposit and 12 monthly payments of 30/-.

THE "VERDIK" TAPE TABLE

● 3 motors specially designed for use in this Table with ample reserve of power ● Fast forward facilities to allow rapid selection of any desired portion of tape ● Fast re-wind facilities ● Tape is handled ONLY to change spools ● 2 Tape speeds: 7½in. per second and 3¾in. per second ● Heavy precision balanced flywheel ● Heads mounted in one unit, ensuring perfect alignment ● Half track width heads ● Negligible "wow" and "flutter" ● Take up spool included ● Circuit diagram enclosed ● For use on A.C. mains.

LANE OSCILLATOR UNIT. Constructed on a small chassis and providing variable r.f. for bias and erase. Output is ample to erase the most difficult signals from modern tapes, and each unit is checked for waveform.
OC.1. Erase and bias generator unit complete with valve **£3.10.0.** Deposit 10/- and 12 monthly payments of 8/4.

OC.2 OSCILLATOR COILS
As used in OC 1 r.f. generator. For use with high or low impedance heads 10/- each.

THE TAMSA SERIES OF RECORDING HEADS ARE STILL AVAILABLE: RECORD PLAYBACK—PLAYBACK—ERASE. ALL 59/6 Post Free. TAMSA OSCILLATOR COIL 10/6.

BSR

3-Speed Gramophone Unit Type GU4, with high fidelity lightweight Crystal Head.

★ 33⅓-45-78 r.p.m. speeds by switching ★ 4 pole induction motor ★ Transcription quality ★ Automatic stop ★ 16in. heavy pressed steel turntable fitted with removable rubber mat

£9.19.11 Cash or Dep. £2.10s. and 12 mthly. paym'ts of 16/-.

All other units advertised by BSR and many others available from stock.

RECORD/PLAYBACK AMPLIFIER KIT TYPE A4

Designed for use with high impedance record playback heads, this amplifier solves the problems of the home constructor.

In the Record position, the amplifier has provision for microphone and gramophone inputs, and a mixer circuit allows fading and balancing between them. A Radio tuner may also be used in place of the gramophone. In the Record position, provision is made for monitoring on headphones, the material being recorded. The use of headphones eliminates feedback problems usually associated with speaker monitoring.

In the Playback position the circuit is re-arranged to form a stable high gain amplifier. The playback pre-amplifier stage uses an EF37A giving extremely high signal to noise ratio, complete freedom from microphony, and negligible hum. Pre-set equaliser circuits are included, and further tonal adjustment is given by a variable tone control.

The microphone circuit is terminated in an impedance satisfactory for crystal microphones, the Acos MIC 22-2 (at **£6.6.0**) being particularly recommended. There is sufficient output to modulate all types of tape.

As with all M.O.S. kits, a fully detailed and comprehensive manual gives the fullest details, the kit being complete including pre-drilled chassis, nuts, bolts, solder tags, and solder, etc.

KIT COMPLETE with Instruction Manual **£6.19.6**

Instruction Manual only 3/9

HIRE PURCHASE Kit as above Deposit £3.0.0 12 monthly payments of 11/6.

Complete Lane Tape Table, Oscillator Unit and A4 Record/Playback Amplifier CASH £25.19.6 or DEPOSIT £6.19.6 12 monthly payments of 35/-.

MICROPHONES

ACOS Mic 22-2	£6 6 0
RESLEY Ribbon R1 A	£7 10 0
GRAMPIAN M.C.	£5 17 6

H.P. terms available.

TAPE

	Per reel
EMI High or Low Coercivity 1200ft	35/-
SCOTCH BOY 1200ft.	35/-
PHILIPS	40/-
WEARITE grade P	45/-

All other makes of tape available.

LOUDSPEAKERS Specialists in all makes of high fidelity Loudspeakers, we welcome your enquiries for all types. We list below some available from stock.

	Cash Price	H.P. Deposit	12 monthly payments of
WHARFEDALE			
W10CB	£8 10 0	£2 10 0	13 4
GOLDEN CSB	£5 12 6	£1 17 6	9 6
BRONZE 10in.	£3 2 6	£1 0 0	6 8
SUPER SC8	£4 7 6	£1 7 6	8 4
BRONZE 8in.	£2 6 6	—	—
GOODMANS			
AUDIOM 60	£8 12 6	£2 12 6	13 4
AXIOM 150	£10 5 6	£2 5 6	16 8

	Cash Price	H.P. Deposit	12 monthly payments of
W.B.			
CONCENTRIC DU-PLEX with trans	£7 15 0	£2 5 0	12 6
DITTO less trans	£6 15 0	£2 5 0	10 9
BAKER			
12in. TRIPLE CONE	£8 5 0	£2 15 0	12 6
12in. SINGLE CONE	£6 15 0	£2 15 0	10/-
VITAVOX K12/10	£8 10 0	£3 0 0	12 6

M·O·S

MAIL ORDER SUPPLY, *The* RADIO CENTRE
Dept. WW, 33, TOTTENHAM COURT ROAD, LONDON, W.1.

MUSeum 6667

RADIO & TELEVISION
ELECTRICAL APPLIANCES
ELECTRIC TOOLS
KITS

RADIO CENTRE

TEST EQUIPMENT
HI-FI REPRODUCTION
TAPE RECORDERS
AMPLIFIERS

Press-button soldering!
The "BURGOYNE" 7 second
SOLDER GUN
A.C. ONLY 200-250v.
No current used unless actually making a joint, no element to burn out; heats in 7 seconds; no constant retinning. Two years guarantee.
Spare bits, 10/6 to 7/8
79/6
Post free

TEST EQUIPMENT SPECIALISTS

A NEW RANGE OF TEST GEAR BY TAYLOR

The reliable Windsor range has been considerably extended and we can offer prompt deliveries on all models with easy Hire Purchase terms.

Model	Cash Price £ s. d.	H.P. Deposit £ s. d.	12 monthly payments of £ s. d.
65A Signal Generator	22 10 0	7 0 0	1 10 0
65C Signal Generator	17 15 0	5 15 0	1 3 6
70A Universal meter 1,000 opv.	12 10 0	4 10 0	17 0
75A Universal meter 20,000 opv.	15 0 0	5 0 0	1 0 0
71A Universal meter 1,000 opv.	11 11 0	3 11 0	16 8
72A Universal meter 1,000 opv.	15 15 0	5 15 0	1 9 0
77A Universal meter 20,000 opv.	15 0 0	5 0 0	1 0 0
120A Universal meter 20,000 opv.	9 0 0	3 10 0	12 6
170A Electronic Test Meter	24 0 0	8 0 0	1 10 0
260A TV Wobbulator	36 15 0	12 0 0	2 8 0
450 Valve Tester	24 0 0	8 0 0	1 10 0
50A Oscilloscope	33 10 0	12 10 0	2 0 0
88A P Universal Meter 20,000 opv.	19 10 0	6 10 0	1 5 0

A selection of the latest releases from the Windsor range is illustrated

OTHER TEST GEAR IN STOCK

Model	Cash Price £ s. d.	H.P. Deposit £ s. d.	12 monthly payments of £ s. d.
Wee Megger 250 V.	19 2 6	5 2 6	1 6 9
Hunts Bridge	18 18 0	4 18 6	1 6 10
Pullin Universal Meter, Series 100	11 11 0	2 0 0	1 0 0
Amplion Testmeter	5 0 0	1 10 0	9 2
Cossor Double Beam Oscilloscope 1035	85 0 0	25 0 0	5 11 2
Cossor Telecheck	27 0 0	8 0 0	1 15 0
BPL Foundation Meter, 1 mA.	3 10 0	1 0 0	7 6
Advance E2 Signal Generator	28 0 0	8 0 0	1 16 8

The AVO range

Needs no introduction from us. We can however, supply from stock most instruments in the range for cash or on attractive Hire Purchase terms.

Valve Characteristic Meter, £50. Deposit £16, 12 monthly payments of 65/-.

Electronic Test Meter, £40. Deposit £12, 12 monthly payments of 52/6.

Wide Range Signal Generator (Mains or Battery), £30. Deposit £10, 12 monthly payments of 47/6.

Universal Bridge, £26. Deposit £9, 12 monthly payments of 32/6.

Model	Cash Price £ s. d.	H.P. Deposit £ s. d.	12 monthly Payments of £ s. d.
Electronic Test Unit	19 10 0	6 0 0	1 5 6
Model "7" "8" or "9" Avometer	19 10 0	6 0 0	1 5 6
Heavy Duty Motor	15 0 0	5 0 0	1 0 0
Universal Avominor	10 10 0	3 10 0	15 0
D.C. Avominor	5 5 0	1 15 0	9 2

"VIEWMASTER" TELEVISION

We are able to resume our offer of Viewmaster Components, Valves and Cathode Ray Tubes on Hire Purchase, with an extended range of equipment.

This is available for any service area, i.e., London, Sutton Coldfield, Holme Moss and Kirk o'Shotts, etc., which you must, of course, specify in your order. Send for our Schedule "D," which details the breakdown of components into their various groupings. In addition we detail below the complete kits of various types, together with their terms.

A special feature which we are now introducing is the Tallon series of cabinets, supplied in break-down form and which can be assembled easily with a screwdriver only. These cabinets have polished French walnut panels and are fitted with genuine Armourplate Glass. The Console model has ball-bearing castors.

	Deposit £ s. d.	12 monthly payments of £ s. d.
Table model, less valves and tube	9 15 6	1 18 4
Table Model with valves, less tube	11 15 6	2 9 4
Table model with 9" tube, less valves	14 15 6	2 19 2
Table model with 12" tube, less valves	14 15 6	3 7 11
Table model, with 9" tube and valves	16 15 6	3 10 7
Table model, with 12" tube and valves	16 15 6	3 19 4
Console model, less valves and tube	10 5 6	2 11 8
Console model, with valves, less tube	12 5 6	2 13 8
Console model, with 9" tube, less valves	15 5 5	3 2 6
Console model with 12" tube, less valves	15 15 6	3 11 3
Console model, with 9" tube and valves	17 5 6	3 13 11
Console model, with 12" tube and valves	17 5 6	4 2 8
Set of 12 valves only	2 0 0	11 5

TALLON CABINETS

	Cash Price £ s. d.	Deposit £ s. d.	12 monthly payments of £ s. d.	Overall Size	Weight
12" or 9" Console	13 15 0	3 15 0	1 0 0	41" × 20½" × 20"	55 lbs.
12" Table Model	7 14 0	2 14 0	11 8	17½" × 21½" × 20½"	25 lbs.
9" Table Model	6 3 9	2 3 9	10 0	15½" × 20½" × 16½"	20 lbs.

Carriage and Packing 10/- extra.

M·O·S

MUSeum 6667

MAIL ORDER SUPPLY. *The RADIO CENTRE*
Dept. WW, 33, TOTTENHAM COURT ROAD, LONDON, W.1.

Recognised as the Most Reliable Valveholders

Sub-Miniature Valveholders

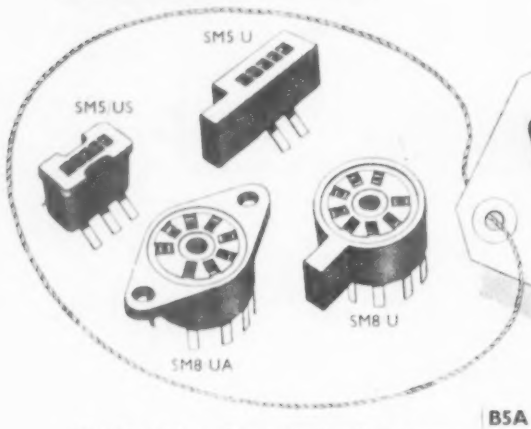

McMURDO Moulded Valveholders

All Moulded in Silica-loaded Polystyrene

B5A TYPES	*SM5 U. Panel Mounting* *SM5 US. Chassis Mounting*
B8D TYPES	*SM8 U. Panel Mounting* *SM8 UA. Chassis Mounting*

Wholesale Enquiries:—CYRIL FRENCH LTD., HIGH STREET, HAMPTON WICK, MIDDLESEX · KIN. 2240
Manufacturers' Enquiries:—THE McMURDO INSTRUMENT CO. LTD., VICTORIA WORKS, ASHTEAD, SURREY ASHTEAD 3401

Your first move . . . **FOR BETTER INSULATION**

CONSULT

Bullers

Makers of Low Loss Ceramics

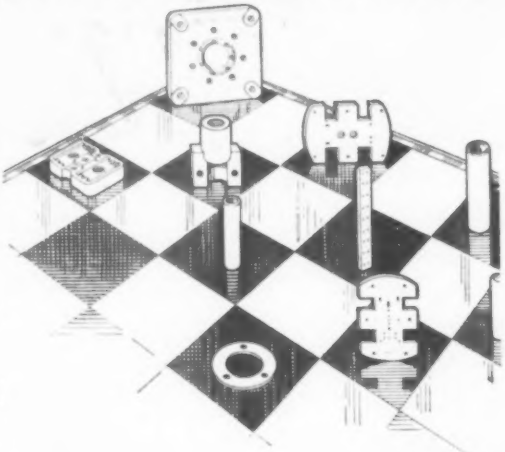

Made in Three Principal Materials—

FREQUELEX An insulating material of Low Dielectric Loss, for Coil Formers, Aerial Insulators, Valve Holders, etc.

PERMALEX A High Permittivity Material. For the construction of Condensers of the smallest possible dimensions.

TEMPLEX A Condenser material of medium permittivity. For the construction of Condensers having a constant capacity at all temperatures.

BULLERS LIMITED

TRADE MARK

6 Laurence Pountney Hill, London, E.C.4. Phone: Mansion House 9971 (3 lines) Grams: "Bullers, Cannon, London"

MORE

- TWO SPEEDS
- THREE MOTOR DRIVE
- FAST REWIND
- A.C. ERASE
- CATHODE-RAY LEVEL INDICATOR
- BUILT-IN SPEAKER
- EXTERNAL SPEAKER OR PHONE JACK
- EASY TO OPERATE
- HANDSOMELY FINISHED
- HIGHLY EFFICIENT
- COMPLETELY SELF-CONTAINED AND PORTABLE

MODEL 2.B
PRICE COMPLETE £60
Including Microphone

but only LESS in price!

"That's the Simphonic Tape Recorder"

Manufactured by
SIMON SOUND SERVICE
Recorder House, 48-50 George Street,
Portman Square · London · W.1.

Telephone: WELbeck 2371 (5 lines) Telegrams: Simsale, Wesdo, London Cables: Simsale, London

If you use solder in any shape or form GET TO KNOW MORE ABOUT THESE PRODUCTS

SUPERSPEED WHITE FLASH
ACTIVATED ROSIN CORED SOLDER to A.I.D. & G.P.O. SPECIFICATION
The high-speed, non-corrosive, quick fluxing, quick melting solder for all types of electrical connexions.

SUPERSPEED *ACTIVATED ROSIN CORED SOLDER WITH RANGE OF* ***COLOURED CORES***
Automatically deposits colour around joint, so making errors easy to check and cutting inspection costs.

SUPERSPEED
INDUSTRIAL SERVICE PACK
Neat, cylindrical insulating dispensers for maintenance engineers, holding 13 or 26 ft. Keeps solder clean up to instant of use.

TELECENE *ACTIVATED ROSIN BASED LIQUID FLUX*
The ideal flux for electrical pre-tinning. All ingredients are dissolved. Leaves no corrosive residue.

TRICENE *SOLDERING FLUID*

Full particulars of the above products will be gladly sent on request.

H. J. **ENTHOVEN** & SONS LTD.
ENTHOVEN HOUSE
89 UPPER THAMES STREET, LONDON, E.C.4.
Telephone: MANsion House 4533
Telegrams: Enthoven, Phone, London.
Works: Croydon, Rotherhithe & Derbyshire.

This MARKS THE SPOT...
FOR AERIAL NEWS AND VIEWS

Laying the Ghost.....

WE can think of nothing more nebulous than a ghost—or, as far as T.V. is concerned, anything more concrete as regards spoiling reception (even if they transmit "Hamlet").

Most large towns have areas where "ghost" images cause trouble. These "ghosts" are due to signals reflected from large buildings, gasholders, etc., which arrive at the aerial later than the direct signal from the transmitter. One cure is to use a highly directional aerial which will receive the best signal (which may be one of the reflected ones) while cutting out the others. Another method is to use an aerial of high front-to-back ratio, positioned so that the "back" faces the unwanted signals. In this case the aerial must have a broad angled forward response to avoid loss of the wanted signal, as the "front" may not be facing towards the transmitter. In both cases positioning and orientation of the aerial is often very tricky; the best arrangement has to be arrived at by trial and error.

Many dealers tell us that they have found the "Antex" ideal for this second and easier method of removing "ghosts." This is to be expected because of its extremely high front-to-back ratio and broad forward response. It has already proved most convenient to handle in making the necessary trials for the best position, owing to its light and compact construction. We are glad to pass on this tip for the benefit of other dealers, particularly those in the Holme Moss area. The "Antex" works equally well with any type of set using standard coaxial or twin feeder cable.

There is a model suitable for every location. Full details in leaflet No. E/50/W sent on request.

ANTIFERENCE *Aerials*
ANTIFERENCE LIMITED 67 BRYANSTON ST LONDON W.1

The Importance of Pulp . . .

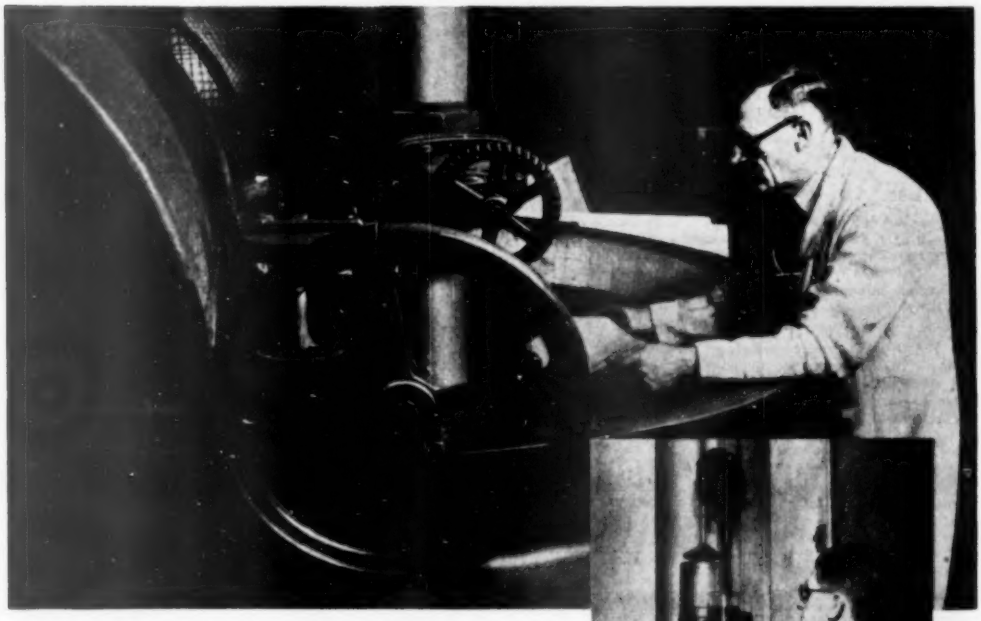

First of a series telling the story of Goodmans Loudspeakers.

Pulp is very important. It is a key stage in the production of a component which forms a vital part of a loudspeaker—the cone. Cone, and hence speaker quality, are dependent on the pulp, and its manufacture is a rigidly controlled process.

The " beaterman " in our illustration is feeding new pulp board into the " beater," where the cellulose fibres are first " brushed out "—stroked and straightened under a precision roller—then " beaten "—cut to an accurately controlled length.

At this stage the pulp is impregnated with neutral dyes (for the cones must be acid-free) and the chemicals which render the cones proof against humid conditions and the attacks of termites and bacteria.

Testing at every stage is the rule at Goodmans. With the Schopper-Reigler apparatus our chemist makes frequent tests for pulp consistency. Length and density of the fibres must be accurately controlled to maintain the quality of the cones.

The pulp is then ready to be formed into " raw " cones or " felts," the second stage of its progress from crude paper mill board to sensitive speaker diaphragm: this second stage will be the subject of the next announcement in this series.

AUDIOM 60

12" 15 watt P.M. Loud-speaker

Limited supplies of this speaker are now available again on the home market. If you cannot obtain supplies, send us your dealer's name.

A TRADITION OF EXCELLENCE

GOODMANS

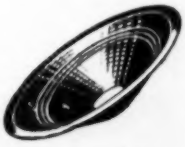

GOODMANS INDUSTRIES LTD Axiom Works, Wembley, Middx. WEM. 1200

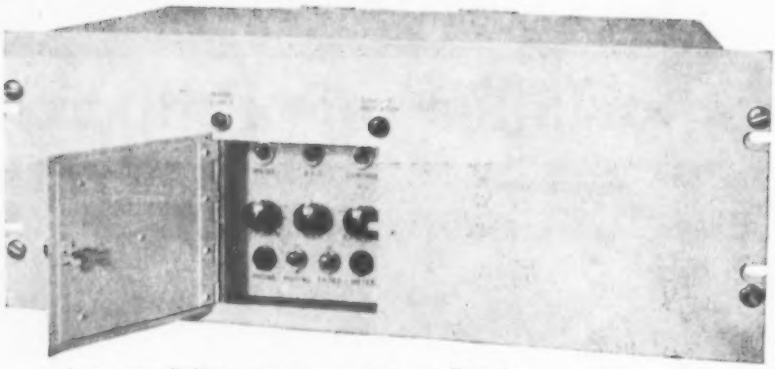

An Important Receiver...

AIRPORT

Redifon Radio

The R.93 is the latest addition to the extensive Redifon range of communications radio. It is a fixed frequency, single channel receiver covering 2 to 20 Mc/s. Its crystal controlled oscillator and other special features make this the ideal unattended receiver for point-to-point and ground-to-air channels and it has full remote control facilities. Specialised applications of the R.93 include monitoring, diversity reception or frequency shift working.

The Redifon range includes MF, HF and VHF transmitters, receivers, radio telephones, navigational aids, AF amplifying systems and other electronic equipment. Enquiries for single units or complete networks including aerials, masts, power supply, land line amplifiers, remote controls and other apparatus are welcome.

Radio Communications Division

The R.93 is designed to the specification of International Aeradio Limited

REDIFON LIMITED, BROOMHILL ROAD, WANDSWORTH, S.W.18

DESIGNERS & MANUFACTURERS OF RADIO COMMUNICATION & INDUSTRIAL ELECTRONIC EQUIPMENT

Phone: VANdyke 7281

The BPL **UNIVERSAL TEST SET** 20,000 Ohms/Volt

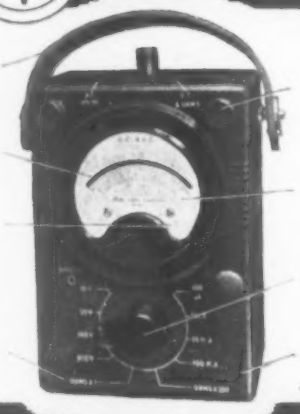

★ Leather carrying handle.

★ Mirror Scale.

★ 20,000 ohms per volt for D.C. and A.C.

★ Two ohms ranges operated from large internal battery. Zero setting holds over long periods.

★ Captive head terminal connectors for all ranges.

★ Easy to read 2 colour dial.

★ Rotary switch selects ranges clearly marked.

★ Solid bakelite moulded case.

FOR ACCURATE LOW RESISTANCE MEASUREMENT

Primarily designed for the easy servicing of all electronic and electrical appliances, radio sets and motor cars. The ranges cover all values normally expected in such work. The electrician and the radio engineer will appreciate the provision of two ohms ranges enabling accurate measurement of low resistance as experienced in testing electric fires, motors, windings of transformers, switches, fuses, electric irons, radio tuning coils, speakers, filaments of valves, etc., and the higher values of resistors.

LIST PRICE

£11.10.0 including test leads. Subject to Trade Discount.

Also supplied:

B.P.L. Super Rangers and D.C. Test Sets.

LONDON STOCKIST:

M.R. SUPPLIES LTD., 68 New Oxford Street, W.C.1.

BRITISH PHYSICAL LABORATORIES

HOUSEBOAT WORKS · RADLETT · HERTS · Telephone: RADlett 5674-5-6

Type T12/44
12" diameter

FERRANTI

flat-faced cathode-ray tubes for television

EXCELLENT PICTURE QUALITY—
THE IDEAL TUBE FOR THE HOME-CONSTRUCTED TELEVISION RECEIVER

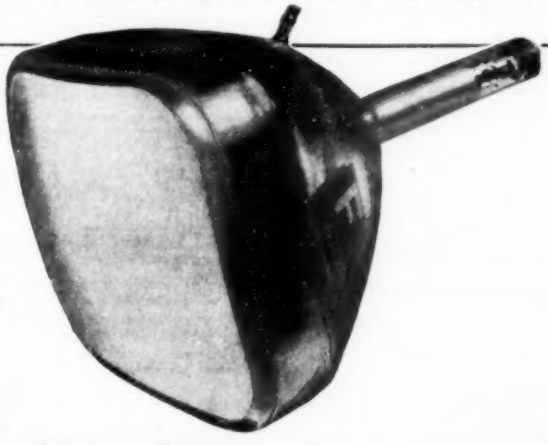

Type TR14/1
14" diagonal
rectangular tube

freedom from ion burns

FERRANTI LTD. MOSTON MANCHESTER 10; 36 KINGSWAY LONDON W.C.2

I take no chances with television! I ALWAYS recommend and instal

TELECRAFT

TV AERIALS

The Famous **FA22** *for Example*

"... because I know they are designed and constructed by a team of engineers with 14 years' practical experience in the design and erection of vision aerials.

That's why my customers are always so very satisfied with their television. ..."

Instal TELECRAFT and see for yourself.

There is a TELECRAFT AERIAL for every contingency—indoors or out.

BETTER THAN ANY—CHEAPER THAN MOST.

Ask your Dealer about TELECRAFT.

Contact your Dealer and insist on TELECRAFT LIMITED *Send for Descriptive Literature*

THORNTON HEATH, SURREY

Tel. THOrnton Heath 1191-2-3.

Depots:—BIRMINGHAM, BRISTOL, MANCHESTER, WORTHING, STOKE-ON-TRENT, GLOUCESTER.

SCOTTISH ENQUIRIES: LOUIS GRACE, 28 Langside Place, Glasgow, S.1. Langside 4433

Only Wolf solderguns have all these time and money-saving advantages—

- OFF-STRAIGHT EASY-GRIP HANDLE
- PERFECT CONTROL
- LOW CURRENT CONSUMPTION
- MODELS FOR EVERY PURPOSE FROM FINE INSTRUMENT TO HEAVY INDUSTRIAL SOLDERING
- QUICKER HEAT-UP
- MAINTAINS CORRECT HEAT
- LOCALISED HEAT

OTHER MODELS TO CHOOSE FROM

TYPE 31
TYPE 41
TYPE 71
TYPE 81

HAVE YOU TRIED AUTOMATIC SOLDERING?

Win new efficiency and economy with Wolf Automatic Soldergun. Its automatic trigger solder-feed action and perfect balance make it indispensable to all modern assembly.

TYPE 51

Also

Wolf *Electric* **SOLDERING IRONS**

TYPE 22

For all who, for special reasons, prefer the conventional straight type handle. Identical as regards elements and bits to Wolf Solderguns but with round hard wooden handle with heat deflecting skirt.

TYPE 32
TYPE 42

It pays to Solder with **Wolf**

ELECTRIC SOLDERGUNS & SOLDERING IRONS

☆ *Obtainable from all high-class stockists and ironmongers*

WOLF ELECTRIC TOOLS LTD.

PIONEER WORKS, HANGER LANE, LONDON, W.5

FREE WITH EVERY CAPACITOR

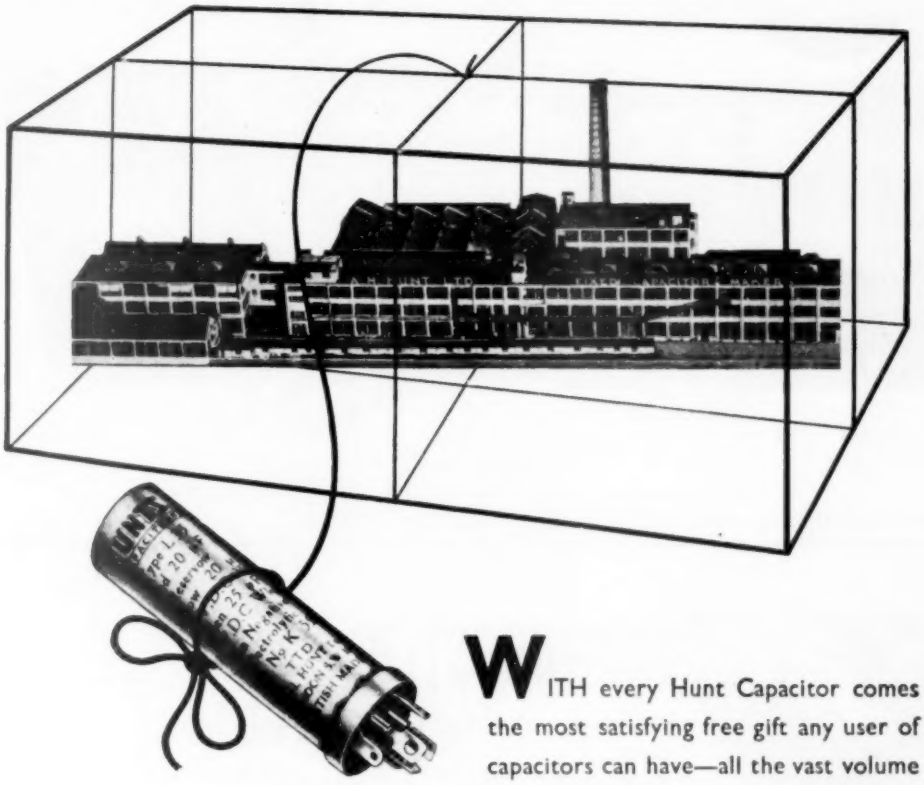

WITH every Hunt Capacitor comes the most satisfying free gift any user of capacitors can have—all the vast volume of knowledge and experience that Hunt's have accumulated over many years of specialisation in nothing but capacitor design and manufacture. And, furthermore, behind every Hunt Capacitor are the resources of the large organisation housed in Hunt's modern factories in England . . . design, research, inspection and production; each unit concentrating on its share of the responsibility of the whole; producing capacitors for every need and application guaranteed for performance, endurance and long life.

DRY ELECTROLYTICS ● MINIATURE & STANDARD
PAPER DIELECTRICS ● MINIATURE METALLISED
PAPERS ● MICA DIELECTRICS ● ETC.

Established 1901

HUNTS CAPACITORS

THE TRADE MARK OF RELIABILITY

A. H. HUNT (Capacitors) LTD. Wandsworth, London, S.W.18. BATtersea 3131. Estd. 1901

SIFAM ENGLAND

Precision **INSTRUMENTS**

Moving Coil

8" Scale

Type M801

The Sifam moving coil Portable 8" scale type M801 instruments are made to B.S.I Specification. Sub-standard accuracy with diagonal lined scale, knife edge pointer. The case is mahogany, wax polish finish with removable hinged lid. The instrument can be supplied as single or multi-range. For D.C. only.

Portable

Pyrometer

A high-grade, 3½" scale moving coil instrument, robust, accurate and speedy in response. Normally supplied with 2 scales, 0-200°C and 0-400°C, with a choice of 3 surface couples. Also supplied with ranges up to 1,600°C for all standard thermo-couples.

Thermo-couples are supplied with 4 ft. compensating leads

● *Write for Catalogue giving full details of the complete SIFAM range.*

SIFAM ELECTRICAL INSTRUMENT CO. LTD., Leigh Court, Torquay. *Telephone : Torquay 4547/8.*

The **BROADCASTER** *Gliding*

SAPPHIRE GRAMOPHONE NEEDLE

Plays for Months without replacement

No. 1

TRAILER for use with heavy magnetic pick-up or ordinary gramophones

No. 2

STRAIGHT for use with standard or crystal pick-up

No. 3

LIGHTWEIGHT for use with miniature pick-up

AS USED FOR BROADCASTING

PRICE 6/6 TAX PAID

OBTAINABLE FROM ALL MUSIC & RADIO DEALERS

or direct from

BROADCASTER RADIO SUPPLIES LTD., 112-114-116 Old Street, London, E.C.1

Telephone: CLErkenwell 2133-7 Telegrams: Plusagram, Cent, London

FOR MAXIMUM EFFICIENCY AND EASE OF MAINTENANCE

THE TYPE V.M.S. MULTI-CHANNEL V.H.F. RADIO SYSTEM

This equipment, designed and manufactured by Automatic Telephone and Electric Co. Ltd., is used to provide radio links where the use of lines is either impracticable or too costly.

Operating on a frequency range of 156-200 Mc's the equipment will give C.C.I.F. transmission standards on up to 36 simultaneous speech channels. By the use of relay stations links may be operated over distances of several hundreds of miles. Each panel comprises a number of sub-units, which are readily replaceable for maintenance purposes, no unsoldering being necessary. All equipment is robust and equally suitable for use in tropical or very cold climates. This is only one of the many types of equipment manufactured by Automatic Telephone & Electric Co. Ltd. for radio telephone links. Write to us for details of equipment for your special needs. Our engineers conduct field surveys throughout the world to ascertain the most suitable equipment for particular purposes.

AUTOMATIC TELEPHONE & ELECTRIC CO. LTD.

(Radio and Transmission Division)

STROWGER HOUSE · ARUNDEL STREET · LONDON · W.C.2

Telephone: TEMple Bar 9262 *Cablegrams: Strowgerex, London*

A1/102.BE07

For EVERY Wireless World Reader!

Sensational New 3-Colour Screen for T/V on MONEY BACK GUARANTEE

Color Vision! REGD.

Now have the grand new thrill of a coloured picture on your T.V set! The "Color-Vision" screen in which three separate colours—blue, magenta and green—are skilfully blended in descending order on to a transparent screen gives you blue skies, pleasantly tinted scenery and green fields. Once fitted an amazing new pleasure from viewing is then YOURS. Color-Vision adds a fascination to Television which you *must* SEE! Don't waste a moment! Have your Color-Vision Screen in time for all the New Year Television programmes. Immediate delivery.

To obtain your "Color-Vision" Screen fill in the coupon below and send it, together with remittance, to us TO-DAY. If at the end of 7 days you are not satisfied, return it to us, when your money will be refunded in full. Prices for all T.V sets up to 12in. screen, 21/-; 15in. screen, 23/6.

TO:—J. & S. NEWMAN LTD.,
100 HAMPSTEAD ROAD, LONDON, N.W.1
(EUS 5176/7)

Color-Vision Screen for

Please send me
9"/10"/12"/15"* television set.
I enclose p.o./cheque money order value
* Strike out sizes that do not apply.

It is understood that my remittance will be refunded in full should I return my "Color-Vision" screen to you within 7 days of receipt.

Name

Address

(BLOCK LETTERS PLEASE)

Here is your area and here is your

Aerialite AERIAL

RANGE

UP TO 15 MILES

MODEL 65 "Aeradoor." Designed for indoor skirting-board mounting. Fitted with one telescopic and one flexible arm. Can be adjusted to any channel. Complete with 5 yards of coaxial lead-in. **PRICE 32/-**

MODEL 65A with 5 yards of Twin feeder. **PRICE 32/-**

Also **MODEL 66**, which has two flexible arms. Complete **PRICE 25/9**

MODEL 66A, with 5 yards twin feeder. **PRICE 25/9**

15 TO 25 MILES

MODEL 74. Has three fully flexible elements. High pickup properties. Trouble-free performance. Centre element has a spring tensioning device and neat connector box. All Channels. **PRICE 13/6**

MODEL 53 (similar to 74). Three rigid metal elements. Installed in variety of positions. All Channels. (Coaxial lead-in extra.) **PRICE 32/6**

25 TO 40 MILES

MODEL 57. Single dipole for chimney stack mounting. Complete with chimney bracket, mast, lashings, etc., ready for installation. Excellent performance. **PRICE 62/6**

MODEL 58. A dipole designed for wall mounting. Cranked stand-off mast similar to Model 57. **PRICE 52/6.** (58A with straight stand-off arm, 47/-.) All Channels.

40 TO 60 MILES

MODEL 55. An H-aerial with dipole and reflector. Forward gain 3.8 dB. Front/back ratio 11.0 dB. Acceptance angle 180 deg. All Channels. Complete with a 10ft. x 2in. dural mast, brackets, lashings, etc. **PRICE £7 19 0.** Various styles of this model available.

60 MILES & OVER

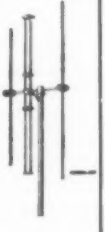

MODEL 63A. For fringe and difficult reception areas. Folded dipole three element aerial. High gain 8.7 dB. Front/back ratio 29 dB. Acceptance angle 90 deg. All Channels. Complete with 10ft. x 2in. dural mast, brackets, lashings, etc. **PRICE £13 5 0**
With 14ft. mast, **£14 2 0.** Various styles of this model available.

A NEW INDOOR AERIAL
MODEL 71. A directional double folded dipole with four fully flexible elements. Easily erected in loft, attic or upper room. Highly directional characteristics. Forward gain 3.75 dB. Excellent reception at considerable distances from transmitters.
Complete ready for erection to any channel specified. **PRICE 25/-**
Send 3d. stamps for FREE Illustrated Catalogue.

AERIALITE LTD., Stalybridge, Ches.

This is the function of a

"FLEXILANT" MOUNTING

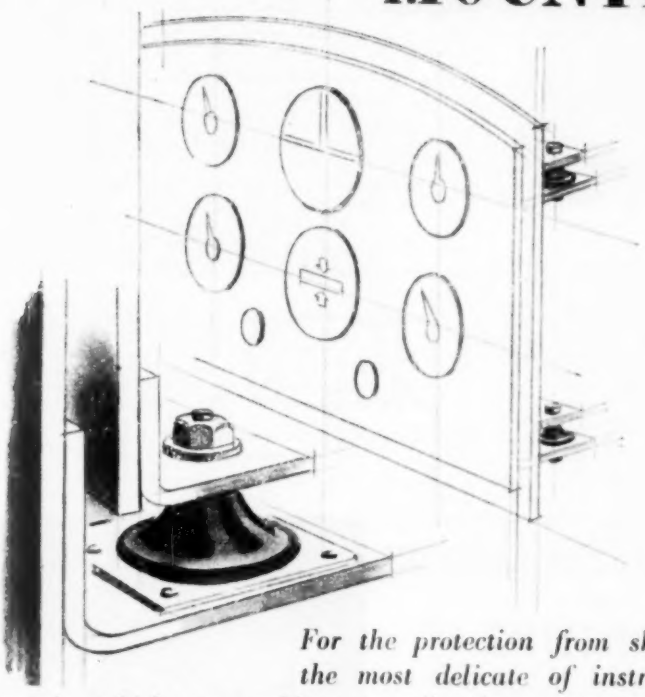

For the protection from shock of the most delicate of instruments and of panels which are subject to vibration, this range of "Flexilant" light mountings is at your service. Have you any problems where we could help?

RUBBER BONDERS LTD

IN ASSOCIATION WITH EMPIRE RUBBER COMPANY

(PROPRIETORS H.G. MILES LTD.)

DUNSTABLE, BEDS.

R.B. 81

FOUNDATIONS OF WIRELESS 5th Edition. *By M. G. Scroggie, B.Sc., M.I.E.E.* Explains the whole basic theory of radio from the most elementary principles. Subjects covered include:- fundamental laws of electricity and radio; theory of valves and transmitters; modern receivers, aerials and power supplies; an introduction to television and radar, etc. 8¼" x 5¼". 328pp.

12s. 6d. net *By Post 13s. 2d.*

Two valuable Radio books

These two books cover their respective subjects in an authoritative, modern style. Already an accepted classic, this new edition of "*Foundations of Wireless*" is a valuable introduction to the principles of radio reception and transmission, whilst the new book "*Advanced Theory of Waveguides*" is a complete treatise on this highly specialised subject.

ASSOCIATED ILIFFE TECHNICAL BOOKS

From all booksellers or direct from:— Dorset House, Stamford St., London, S.E.1

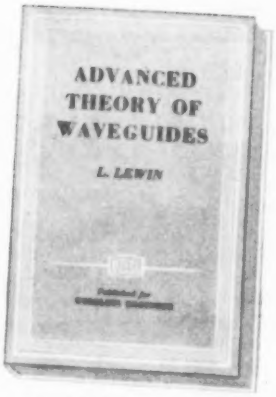

ADVANCED THEORY OF WAVEGUIDES. *By L. Lewin.* Sets out various methods of treating the problems arising in work on the subject. Contents include:— Electromagnetic Theory and its application to waveguides; the tuned post and the tuned window; Waveguide steps; T-junctions and Tapers; Radiation from waveguides, etc. 8¼" x 5¼". 192 pp.

30s. net *By Post 30s. 7d.*

13 MODULATION PATTERNS

with the

PHILIPS

Standard Television Signal Generator

The Philips GM.2657 Standard Television Signal Generator is used for the production of complete video signal and pattern, and modulated high frequency signal.

1. *Can be supplied for any fixed vision frequency between 45 Mc/s to 80 Mc/s.*
2. *Can be supplied for any number of lines between 400 and 700.*
3. *Built in sound modulation at 600 c/s.*
4. *Sound and vision frequencies arbitrary and both crystal controlled.*
5. *Choice of 13 modulation patterns.*
6. *Line and frame sync. obtainable separately if required.*
7. *External sound and vision modulation possible.*
8. *Built-in oscilloscope for checking video wave form.*

★ Owing to the unique nature of this equipment interested Engineers are invited to request an appointment to visit the Philips Application Showroom where facilities for full demonstration are available. ★

PHILIPS ELECTRICAL LTD.

CENTURY HOUSE, SHAFTESBURY AVENUE, LONDON, W.C.2.

Twin-channel airfield racks

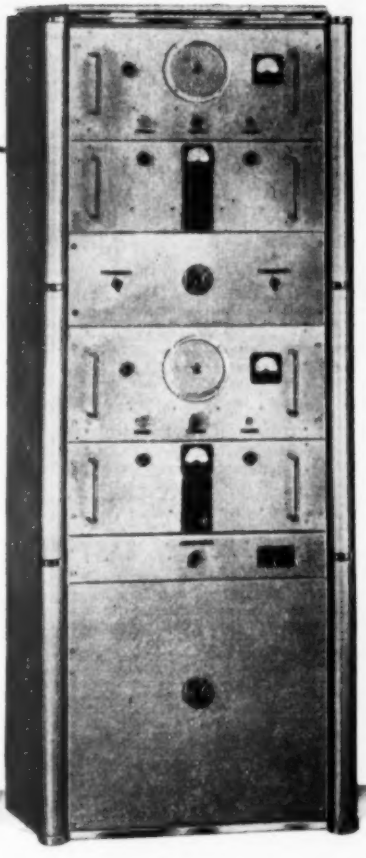

For Ground to Air V.H.F. R/T communication and Ground Radio Links.

Remote control operation over telephone lines is available for distances up to 15 miles.

A two-channel system is illustrated but additional channels may be added as required.

All Pye V.H.F. equipment is fully tropicalised and normally operates in the band 60-184 Mc/s.

Pye V.H.F. equipment is officially approved.

Telecommunications

CAMBRIDGE ENGLAND

Overseas Enquiries to:—

EXPORT DEPARTMENT · PYE LIMITED · CAMBRIDGE · ENGLAND

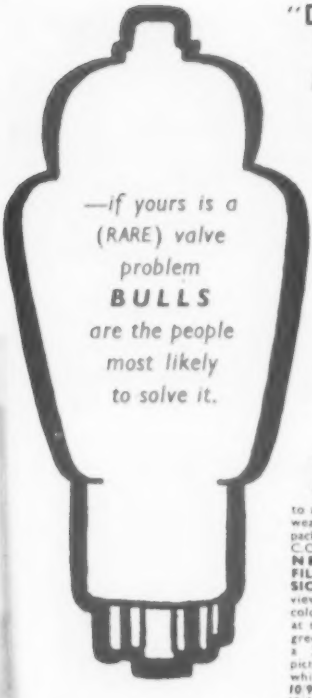

"DEMOBBED VALVES" MANUAL

2/9

Post Free

giving equivalents of British and American Service and Cross Reference of Commercial types, with an appendix of B.V.A. Equivalents and comprehensive Price List. We have still some valves left at PRE-BUDGET rates which are actually sold at the old price.

EXPORT

to all parts of the Commonwealth and beyond—safely packed, fully insured (no C.O.D.) and free of tax.

NEW!—COLOURED FILTERS FOR TELEVISION SCREENS. For viewing in 3 delightful colours graduating from blue at the top, red in centre to green at the bottom. Gives a 3 colour pastel shade picture on any black and white screen. 9in. and 10in. **10/9**; 12in. **12/6**; 15in. **19/6**. Post 1/-.

"ACTIVETTE." Mains unit for Re-activating Dry Batteries. The sensation of Earl's Court Radio Show. Available now **£3/5/-**.

TRIMMER KIT 25/6 post 1/-, which no Amateur or Professional Radio or Television Engineer can afford to be without. Contains: 1 End Trimmer; 1 Screwdriver; 1 Side Trimmer; 1 Set of Feeler Gauges; 1 Yaxley Switch Contact Adjuster; 1 Set of six Box Spanners from 0 to 8 B.A. In durable Black crackle finish metal case.

THE "Q-MAX" CHASSIS PUNCH

¼in., ⅜in.	⅜in.	½in., ⅝in., ¾in., ⅞in.	1⅛in.	2 3/32in.	1in. sq.
10/6	11/6	13/6	16/6	27/6	21/-
Key 9d.		Key 1/-		Key 1/6	Key 1/-

AMERICAN TYPE ELECTRIC SPRAYERS British made. Just plug in and Spray. No vacuum cleaner or compressor needed. Easier than brush and twice as fast. A.C. Model, **£3/15/-**. Post 1/6.

TAYLOR Meters New Range **EASY TERMS**

Up to 10 months, and very nearly Cash Price.

PIFCO ALL-IN-ONE RADIOMETER. A.C. and D.C., tests everything in radio. Complete with test prods, **27/6**, post 1/6.

SERVICE SHEETS: The one you require, if available, enclosed in a dozen assorted, our choice, **10/6**.

CONDENSER TESTERS AND RECTIFIER UNITS: Plugs straight into A.C. mains 200/240 V., and is indispensable for examination of condensers. Very slight and intermittent leakages which cannot be discovered by conventional instruments can be traced by this unit. Complete, **39/6**, post 1/-.

1952 MAILING LIST FREE. W.W.2

COUPON FOR SPECIAL BARGAIN OFFERS.

NAME .....

ADDRESS .....

Please write in BLOCK LETTERS and Post to:

RADIO BULLS VALVES

246 HIGH ST. HARLESDEN NW10

SCP

-towards perfection-

DT/4L

This is the famous Lowther DT/4 tuner especially modified for use with the Leak "Point One" TL/12 amplifier and control unit.

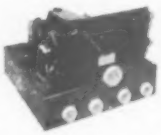

The perfect complement to your record reproducing equipment.

Incorporating a Change-over Switch to conserve H.T. and L.T. consumption when used with a Lowther :- Holme Moss, Sutton Coldfield, London or Wrotham VHF pre-set tuner.

Leaflet with full details please write :—

THE LOWTHER MANUFACTURING CO.

(The Laboratory Production Unit)

Lowther House, St. Mark's Road, Bromley, Kent. RAV. 5225.

FOR GREATEST EFFICIENCY AT THE HIGHER FREQUENCIES

SILVERED JAY CERAMIC

PRECISION CAPACITORS

FOR TELEVISION, F.M., AND ALL U.H.F. APPLICATIONS

Constructors', service replacement, and all kit types.

High precision and laboratory types

(NQUIRIES INVITED)

SPHERE RADIO LIMITED.

HEATH LANE, WEST BROMWICH.

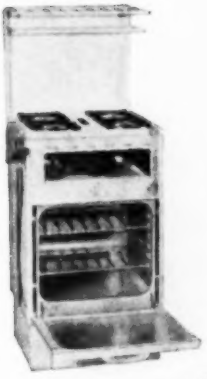

How are YOU fixed?

The makers of the new Main Gas Cooker save labour and material costs on fixings by using 33 Spire Speed Nuts on every cooker. Spire is the name. Speed is the reason. Spire Speed Nuts make faster, easier fastenings — and that means saving. But not saving at the expense of performance. These self-locking fasteners are functionally better than the old methods they replace. Each fastener saves 50/75% on weight of material used.

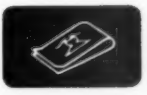

SNU Spire Speed Nuts are used in blind assembly on—back lining protection plate, outer crown to side casing, side casing to front (top), side casing to front, and oven linings, back casing to side, plinth to base and facia to body.

SNO Expansion type Spire Speed Nuts control hob adjusting screws.

SRV Spire Speed spring latches and Ball Studs secure door in closed position. Just a pull — and it opens.

SCA Spire Speed clips secure thermostat control knob and six gas tap knobs to their spindles.

Spire SPEED NUTS *fastest things in fastenings*

Enquiries to:
SIMMONDS AEROCESSORIES LTD., Byron House, 7-8-9 St. James's Street, London, S.W.1.
Head Office and Works: Treforest, Glamorgan. Also Birmingham, Stockholm & Melbourne

CRC255

The Murphy TPG11 is not our only line!

IN the test rooms, research and development laboratories and workshops of almost every Radio, Television and Radar Manufacturer in the country, you will find hundreds of new and renovated electronic instruments supplied by us.

The demand for this side of our work has so far always exceeded our capacity, so we have not hitherto advertised it. Now, we have at last obtained extensive new premises near Archway Tube Station. When alterations are completed, we shall be able to welcome old and new friends to a unique establishment, with comprehensive laboratory facilities and large stocks of new and renovated instruments of all good makes.

OUR POLICY: *Technical accuracy is vital! Advice must be impartial!*

F. LIVINGSTON HOGG

LIVINGSTON LABORATORIES

RETCAR STREET,
DARTMOUTH PARK HILL, LONDON, N.19
Telephone: ARCHWAY 2442

Specialists in Instruments for the Communications Industry

YOUR CAREER and my Personal Guarantee

YOU are probably more clever than you know I can prove this . . .

"I guarantee to provide every one of my students with tuition until he has passed the examination for which he has enrolled." You see I know from experience with men who start with The Bennett College, that they are nearly always more clever than they think they are. I can prove this WITH YOU! If you *want* to succeed there is nothing to stop you. The Bennett College system of *personal* tuition will get you through your exams. You study at home taking your own time. Your books are free. You will realise your capabilities and your ambitions. But first, without any obligation, send me the coupon. I will give you, free, my private advice.

"I WILL TEACH YOU, HELP YOU, UNDERSTAND YOU. YOU WILL LEARN AND BE FOREVER GRATEFUL."

In which of these lies your future?

Aviation Wireless.
Book-keeping.
Civil Service.
All Commercial Subjects.
Draughtsmanship.
Electrical Engineering.
Gen. Cert. of Education.
Languages.
Mechanical Engineering.
Mathematics.
Radio Service Engineering.
Secretarial Exams.
Telecommunications.
Television.
Works Management.
and many others.

TEAR OUT

Please accept this FREE!

To the Governor, Dept. B.41,
THE BENNETT COLLEGE, Sheffield, Eng.
I would like to have (at no cost) your prospectus on .....
..... (subject)

NAME .....

ADDRESS .....

.....

Age (if under 21) .....
Please write in block letters.

The **BENNETT COLLEGE**

ALL the A.C. power you require from your D.C. supply

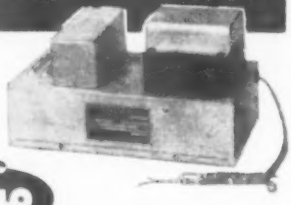

with a

Valradio

D·C·/A·C· CONVERTER

Models for Electric Gramophone from **£8 16 0**

Models for
- Radio-grams and Autochange Radio-grams (inc. 3-speed motors)
- Radios
- Televisions, etc., *from* **£11 16 0**

Input, 6, 12, 24, 32, 50, 110 or 200/250V. D.C.
Output 230V. 50 or 60 c/s.

Valradio *Descriptive literature W.W.12 from the manufacturers:-*
NEW CHAPEL ROAD, HIGH ST., FELTHAM, MIDDX.
Tel.: FELtham 4242

Service Dept.: 57 Fortess Road, London, N.W.5. Tel.: GULliver 5165

Overseas Enquiries to nearest E.M.I. Organisation Depot.

The

ECONOMY of PURPOSEFUL DISK SELECTION

THE great development in the art of direct recording has resulted in the use of disks for a steadily increasing variety of purposes. Some applications call for a disk possessing a quality not demanded by other applications. For example, in the recording of disks as "masters" for processing gramophone records the disk must not only be beyond reproach in performance but also in appearance. On the other hand, there are many occasions, such as auditions, rehearsals etc., when this high standard is not required, and when the extra cost of the finest disks is not justified.

In order to fulfil every possible recording requirement in the most economical way we have arranged that any user can select disks of a quality most suited to the particular recording needs. To this end we have adopted a new and exacting system of classification by which our disk production is divided into four selected groups. Each group has been carefully chosen to cover effectively the class of recording for which we consider the disk most suitable.

THE NEW CLASSIFICATION

WHITE LABEL ("Master")

For processing where a perfect blank is required. Since only one side of a disk can be processed, an easily removable label is affixed to the reverse side.

GREEN LABEL

A disk of excellent quality, recommended for use by Broadcasting Stations, Film Studios and Commercial Recording Studios, where both sides of the disk are required for direct playback.

YELLOW LABEL

A disk of excellent quality, recommended for use by Broadcasting Stations, Film Studios and Commercial Recording Studios, where one side of the disk is required for direct playback. The second side may, or may not, be slightly inferior in appearance, but is capable of being fully recorded for rehearsal or audition.

BLUE LABEL

A high quality double-sided disk which may have one or both sides only slightly inferior to those of the Green and Yellow Label disks. Recommended for use in speech training, speech therapy and for rehearsals.

Since the same high quality M.S.S. lacquer is used for coating the disks in all four groups, the user is assured of the finest possible performance within the price class.

It is opportune to mention here that very large numbers have been selected every year from M.S.S. standard disks for processing by some of the most critical users throughout the world.

M.S.S. disks will in future be available with the labels as shown which indicate their recommended uses.

THE MASTER SOUND SYSTEM

Fullest technical details available on request.

M.S.S. RECORDING CO. LTD. · POYLE CLOSE · COLNBROOK · BUCKS · Telephone: Colnbrook 284.

SALWAY MORGAN & CO LTD
SM
WESTQUAY ROAD, POOLE, DORSET

EXCEPTIONAL OFFER !
(EXPORT ONLY)

UNUSED U.S.A. RADAR EQUIPMENT

TYPE S.Q. All equipment is tropical packed.
TYPE S.G.A. Complete range of Equipment, Stock and
TYPE S.G.I. Tender Spares; large stocks available.

A.M. RADAR EQUIPMENT

TYPE H2S. Reconditioned, with A.I.D. Certificates.

INSTALLATION AND MAINTENANCE SERVICE AVAILABLE

SALWAY MORGAN & CO. LTD.

'PHONE 840, 841, 842.
'GRAMS 'SERVICES, POOLE POOLE DORSET

to-day there is no better television than

AMBASSADOR

ILLUSTRATED LITERATURE FROM
AMBASSADOR RADIO & TELEVISION
BRIGHOUSE YORKSHIRE

M. R. SUPPLIES Ltd

Offer from stock the following brand new (or otherwise perfect) material. All price nett. Immediate despatch.

FRACTIONAL H.P. MOTORS, brand new by B.T.H. 230/250 v. A.C./D.C., 1/20th h.p. Continuously rated. 5,000 r.p.m. Here is a fine F.H.P. Motor which will do a good job of work. Sewing machines, projectors, small lathes, pumps, grindstones, small drills, mixers, agitators, useful to everybody. Approx. size 3in. × 3½in. with shaft projecting approx. 1½in. Real opportunity. 47 6 (despatch 1/6). It is important to note that these are the genuine product of B.T.H. and not conversions.

MAINS GEARED MOTORS. 230/240 v. A.C./D.C. 1/10th H.P. 8in. long, 4½in. dia. Final speed 700 r.p.m. Double-ended final shaft, sturdy construction. New, ex-Admiralty. £4 17 6 (despatch 4/6). **HOOVER SHADED POLE INDUCTION MOTORS**, 200/250 v. A.C. Model SP 202. Body 2¼in. × 2½in. with ¼in. shaft proj. 1½in. 950 r.p.m., very silent. 26 - (des. 1/-).

MINIATURE MOTORS, for models, etc., 12 v. D.C. (up to 20 v. A.C.). Note the small size, 2in. long, 1¼in. dia., fitted removable pulley, with internal adjustable governor, approx. 1,000 r.p.m., good power. 12 6 (des. 9d.).

CAMBRIDGE THERMO-COUPLES (Varmo Junctions). Useful range: 2.5 mA, 5 mA, 10 mA, 20 mA, 25 mA and 50 mA. Full data on each container. Brand new: Unscapped 7 6, capped with 4-pin base. 9 6 (des. 6d.).

TUBULAR HEATERS, 220/240 volts, 240 watts. Length 4ft. Very efficient for the low consumption and ideal for laboratories, workshops, greenhouses, lofts, garages, etc. A good 1 kw. 7½in. barg. at. 27 6 each (des. 3/6 each). Also **PANEL HEATERS**, 220/240 v., 1,250 watts, 24in. × 15in., 35 - (des. 5/6 each).

DAMP-PROOF PLUGS AND SOCKETS, with screw-on 2-pin 5-amp plug and "out of use" cover, ideal for use in open or damp situations. 2 9 (des. 9d.).

VOLTAGE CHANGING TRANSFORMERS, 100/110–200/250 v. 50 c., 1 ph. (and vice versa). Auto-Wound. (A) 500 va. in cylindrical steel housing with conduit entry. £4 10 - (des. 3/6). (B) Loading 1,250 va. in portable housing, with handle. £6 15 - (des. 5/-). (C) Same rating as B but with 10 v. tap selector switch, 200/250 v. and 0-120 v. meter, for accurate step-down from varying mains inputs in portable case with handle. £8 17 6 (des. 6/-).

SANGAMO TIME SWITCHES, synchronous 200/250 v. 50 c. Capacity 20 amps. Min. period between operations 15 mins. Model A provides one on-off sequence per 24 hours and has day-omitting device. Model B is the same style but has three on-off sequences in 24 hours but no day-omitting device. Both in black plastic housing, 5½in. × 4½in. with window. Either £4 12 6 (des. 1/6). Also **SANGAMO SHORT INTERVAL PROCESS TIMERS**. Synchronous 200/250 v. 50 c. Single-pole switch capacity 5 amps. Operation sequence period adjustable for 5, 10, 15, 20, 30 and 60 minutes and timed circuit period continuously adjustable from 5 to 75 seconds for any of the sequence periods. In same style as Models A & B. Very valuable instruments of almost unlimited application. £6 12 6 (des. 1/6).

THERMOSTATS (A.M. frost protection, on at 32 deg. F. off at 40 deg. F., capacity 1.5 amp. (200 v.). 4 6 (des. 4d.). Capillary type, tube 5ft. long, with 8in. phial, range 55/90 deg. F., cap. 5 amps. for air or immersion. 17 6 (des. 1/3). Room type, and for greenhouse, by British Thermostat Co., range 40/80 deg. F., 10 amps. differential 1 deg. 45 - (des. 9d.).

HIGH DUTY RECTIFIER UNITS (S.T.C.). Input 220/240 v. 50 c. 1 ph. D.C. Output 36 v. 50 amps. Rigid spec. ambient 50 deg. C. Metal rectified, fitted switch and fuses and thermostatic control. Size 4ft. 6in. high, 21in. × 18in., weight approx. 3 cwt. £28 (ex England 25/-).

Details on request. Reversible Bridge Meggers, Ohm meters, Lighting Dimmers, Stuart Electric Pumps, Pressure Speaker Units.

M.R. SUPPLIES Ltd., 68 New Oxford Street, London, W.C.1
Telephone: MUSeum 2958

THE POWER AMPLIFIER

—less distortion, greater efficiency

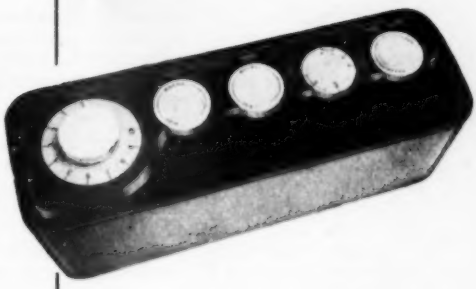

The 'quality' of a power amplifier is directly related to its linearity (without feedback) together with its freedom from phase shift. The power amplifier of the Q.U.A.D. utilises screens dynamically controlled from the anodes in order to obtain the lowest possible distortion within the valves themselves, together with improved efficiency. The following advantages are obtained in the complete design.

(a) In view of the low inherent distortion —0.4 times that of normal triode operation—it follows that overall feedback can be 8db less than would normally be required for any particular distortion rating in the audio range. This leads to the acceptance of some 10db greater signal level outside the feedback range than any other amplifier of comparable rating, a factor of significance in practical applications. Further, there is virtually complete freedom from 'embarrassment' with reactive loads, long leads, etc.

(b) The power conversion is 35% more efficient than any other quality amplifier commercially available—a factor reflected in the size and compactness of design.

The Q.U.A.D. Amplifier . . . .

for the closest approach to the original sound.

£35.

ACOUSTICAL MANUFACTURING CO LTD
HUNTINGDON · HUNTS · TEL: 381

CAPACITANCE STABILITY MEANS

SRC

Our Silvered Mica Capacitors are mass produced to precision standards. Electrical characteristics which have previously been specified for laboratory standards are now a feature of a component which we produce by the million.

Reliability is the key word of our inspection methods which are based on statistical control in addition to the comprehensive application of modern electronic instruments. Quality control of this nature can only be performed by a specialist manufacturer who has carefully collected and analysed the production results of many millions of units over a period of years.

STABILITY RADIO COMPONENTS LTD

COMMERCE ESTATE · WOODFORD AVENUE
LONDON · E.18
TELEPHONE · BUCKHURST 6501/2

GRAM MOTORS for MICROGROOVE & STANDARD RECORDS

PICK-UPS

"K-ray" view of MU-10

B.S.R. MU-10 motors for 33 & 78 r.p.m. Speed change by reversing drive pulley. 10in turntable. 100/250v. £3.15s.

ACOS GP-20 pickups, standard £3.11.5
GP-19 LP microgroove head only £2.3.4

MARCONI Type 14, with matching transformer .. £3.8.4

GOLDRING Type 130 standard lightweight .. £1.15.10
Type 137 De-luxe lightweight £1.19.5
ditto with AUTO-STOP £2.6.7
Type 150 with adjustable counterweight for 33 45 or 78 r.p.m. records. Complete with two sapphires. £3.11.8

DECCA Twin head 'tumorror' £3.19.4

CONNOISSEUR Standard £6.11.8
Super de luxe, with two heads £10.0.0

MU-14

All post free in U.K.!

MU-14 de luxe model with ROTACAM instant speed change for 33 45 & 78 r.p.m. £6. 10s.

GU-4A Three-speed RADIOGRAM UNIT

Now available for the home market, this new combined unit uses the popular MU-14 motor on a unit plate with pickup and AUTO-STOP.

The pickup is of the Acos dual purpose type fitted with a sapphire needle.

Beautifully finished in mottle enamel. £10.

GU-4A

Full list including Auto changers on request!

RADIOCRAFT Ltd
G-PO CHURCH GATE LEICESTER
PHONE 58927

BAKERS 'Selhurst' RADIO

PIONEERS OF MOVING COIL SPEAKERS SINCE 1925

NEW "HIGH FLUX" 1952 MODELS

HIGH FIDELITY SPEAKERS

- The World Famous 12" Triple Cone.
- 12" Single Cone Model.
- 18" "Duplex".

Write for illustrated list and technical details of SPEAKERS, TUNERS AMPLIFIERS & RECORD PLAYERS

BAKERS 'SELHURST' RADIO
Quitable House, Dingwall Road, Croydon
Telephone: CROydon 2271/2

from 10 to 310 mc/s

Within the small compass of 14¼" × 12½" × 7¾", this generator provides facilities as are normally available only in instruments of much greater size and weight—and with an accuracy which suggests something far more costly. Outstanding features include:-Frequency calibration ± 1% ● Max. attenuation error at 300 Mc/s., ± 2db. ● Modulation 30% sine wave at 1,000 c/s. ● Negligible stray field ● Weight 34lb.

Fullest details contained in leaflet S6/W sent on request.

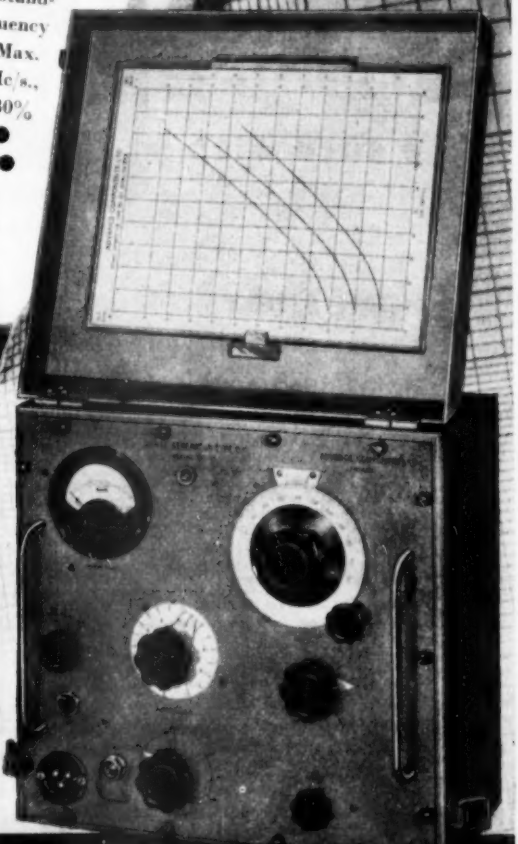

D1

Advance

V.H.F. SIGNAL GENERATOR

ADVANCE COMPONENTS LIMITED

BACK RD., SHERNHALL ST., WALTHAMSTOW. E 17. *Phone*: Larkswood 4366

The Picture can ONLY be as good as the AERIAL - be sure with

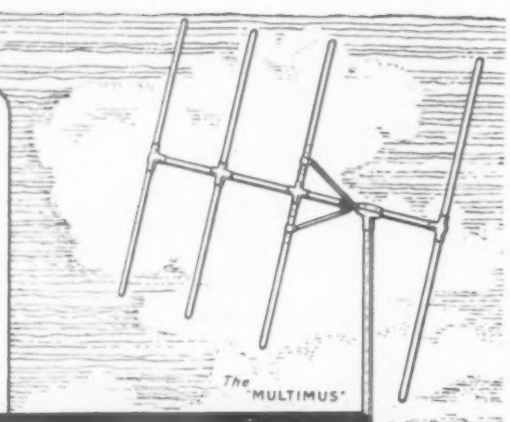

Telerection

specially for Fringe Areas

Antenna Works, St. Paul's

CHELTENHAM Telephone Cheltenham 55960

ICS

HOME STUDY backs radio experience with sound technical knowledge

MANY men who wished to link their radio experience with a sound technological background have received successful instruction by means of an ICS Course. Its value has been proved not only to amateurs but to men who already have a professional interest in radio and television engineering, including those taking qualifying examinations. It is invaluable, also, to students who wish to prepare themselves for a job in this field. Courses of instruction covering radio and, if necessary, television, include the following:

Complete Radio Engineering . Radio Service Engineers . Radio Service and Sales . Advanced Short-Wave Radio . Elementary Electronics. Radar and Radio . Television Technology.

And the following Radio Examinations

British Institution of Radio Engineers . P.M.G. Certificates for Wireless Operators . City and Guilds Telecommunications . Wireless Operators and Wireless Mechanics, R.A.F.

Students intending to sit for the above Examinations should enrol NOW for preparatory Courses.

Using a specially prepared study programme, students study at their own pace, in their spare time and, with time for revision, sit with full confidence of success. (I.C.S. Students are coached until successful)

Moderate fees include ALL books required.

GENEROUS DISCOUNT TO H.M. FORCES.

Write today for our FREE "RADIO" booklet which fully describes the above ICS Courses and the facilities for the complete study of Radio and or Television technology. The ICS Advisory Department will also give free and impartial advice on the need for and the means of instruction.

International CORRESPONDENCE SCHOOLS

Dept. 223A, International Buildings, Kingsway, London, W.C.2

"Cyldon" Variable CAPACITORS

From **MINIATURE TRIMMERS** *to* **HIGH VOLTAGE TRANSMITTER CAPACITORS**

Here are shown just two examples from the comprehensive "Cyldon" range. For precision, stability, and long life, "Cyldon" superiority is recognised by all designers and users of electronic equipment.

No. 26. A new Mica Compression Trimmer

For use in Television circuits. High stability with constant wide capacity swings and long life at high voltage. Blade resilience not affected by continual setting. Low loss Rockite base and best Mica di-electric give very efficient Power Factor. Location method prevents flash-over from blade movement. Capacities up to 1,000 µF at 1,500 or 3,000 v. D.C. test and up to 3,000 µF for 250 v. D.C. vert. 1.725 diam. 1¼in. high.

No. 18/S. Air Di-electric Trimmer

Of high stability and excellent Power Factor. High but smooth operating torque. Metal parts silver plated. First grade ceramic base. Single-hole fixing. Split stator and locking versions also available. Max. capacities from 10-30 µF. Base size 1 x ¼in.

● **Enquiries invited from Equipment Manufacturers and Wholesale Trade only.**

Full details of the complete "Cyldon" range and list of Agents for Home and Overseas available from the manufacturers:

SYDNEY S. BIRD & SONS, LTD.

CAMBRIDGE ARTERIAL ROAD, ENFIELD, MIDDX

Stentorian LOUDSPEAKER CHASSIS

The reasons for the unique quality of reproduction given by W.B. chassis are two — firstly, because the actual designers of the first great W.B. moving coil speaker over 25 years ago are still personally engaged in improving "Stentorians". Secondly, because all operative parts — "Alcomax" magnet, graduated multi-fibre cone, speech coil assembly, transformer are designed and made in the one organisation, under the same knowledgeable supervision.

• A speaker for every need

Type	Cone dia.	Flux Density (Gauss)	Pole dia.	Gap length	Flux face	Total Flux	Speech coil Impedance (Ohms)	Handling Capacity (Watts)	PRICES With Trans. £ s. d.	PRICES Without Trans. £ s. d.
*S.2.57	2½"	7,000	.375"	.033"	.093"	5,285	3	.3	—	18 6
*S.3.57	3½"	7,000	.625"	.035"	.125"	11,500	3	2	—	19 6
S.507	5"	7,000	.75"	.040"	.125"	14,000	3	2.5	1 8 9	1 1 0
*S.607	6"	7,000	.75"	.040"	.125"	20,000	3	3	1 11 9	1 2 6
S.607	6"	7,000	.75"	.040"	.125"	20,000	3	3	1 13 9	1 4 6
S.810	8"	10,000	1"	.043"	.187"	39,500	3	5	2 3 0	1 12 6
S.912	9"	12,000	1"	.043"	.187"	47,400	3	7	2 7 3	1 16 9
S.1012	10"	12,000	1"	.043"	.187"	47,400	3	10	3 3 0	2 4 6
S.12135	12"	13,500	1.5"	.050"	.25"	106,000	15	15	10 0 0	9 0 0

* *All chassis material is of Mazak 3 except those marked with an asterisk which are of Drawn Steel.*

• The ultimate in fine reproduction

Stentorian CONCENTRIC DUPLEX

12" model: series gap magnet Alcomax 3. Total magnetic flux 220,000 lines. Frequency coverage 30-17,000 c.p.s. Power handling capacity 15 watts. Chassis material Mazak 3. Crossover network.

12" Chassis with Crossover Network £17.17.0; 10" Chassis with condenser £6.15.0; Cabinet prices and leaflets on application. Matching transformers available at extra cost.

WHITELEY ELECTRICAL RADIO CO. LTD
MANSFIELD · NOTTS

Murex

ZIRCONIUM

as applied to

THERMIONIC VALVE MANUFACTURE

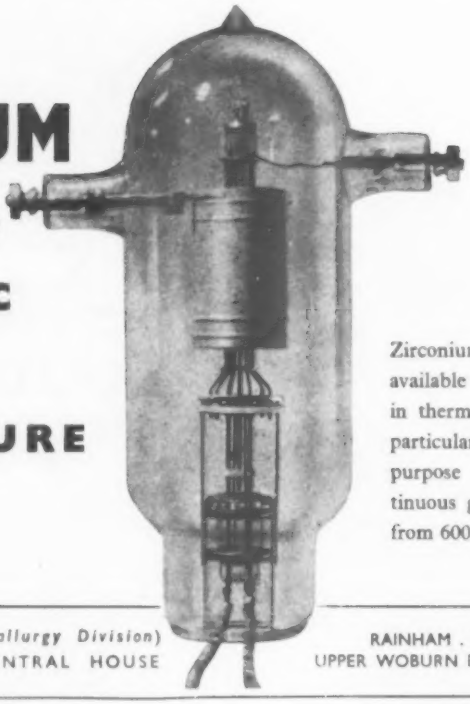

Zirconium sheet is now available for use as a getter in thermionic valves. It is particularly suitable for this purpose since it has continuous gettering properties from 600°C.

MUREX LTD. *(Powder Metallurgy Division)*
LONDON SALES OFFICE: CENTRAL HOUSE

RAINHAM . ESSEX . *Rainham 240*
UPPER WOBURN PL. W.C.1 . *Eus 8265*

SENSITIVE PANEL MOUNTING METERS

SIZE	2½"	3½"	5"
RANGE	25μA to 50A	10μA to 50A	10μA to 50A

(Prices on application.)

S.50 type microammeters are stocked by M.R. Supplies Ltd. at New Oxford Street, W.C.1

All sizes available with MIRROR SCALE 1st Grade Accuracy.

BRITISH PHYSICAL LABORATORIES
HOUSEBOAT WORKS · RADLETT · HERTS
Telephone RADLETT 5674-5-6

CABINETS

Beautifully polished Walnut with Rumanian Birch grille and feet. Lid interior felted. Top plate cut out for gramophone unit. Recessed escutcheon plate fitted in side for volume control. Access trap-door in base. Rubber non-scratch feet. Sub-baffle for 6½in. loudspeaker. External 16 x 14 x 12in. deep. Internal 15 x 13 x 7in. below top plate, 3in. above to lid. Solid and finely built.

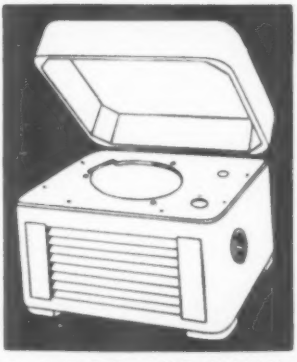

£3. 10. 0.

Each, incl. Purchase Tax Packing & carriage extra

GRAMOPHONE UNITS FOR TOP PLATE AVAILABLE

Send details of your requirements to

N. MIERS
& CO. LTD.

115 Gower Street, London, W.C.1

Phone: EUSton 7815 **Grams: Miersco Westcen**

Valve book of the year!

CHARACTERISTICS OF RECEIVING VALVES

ELECTRONIC DEVICES · CATHODE RAY TUBES

PHOTO CELLS · GERMANIUM CRYSTALS

COMPARATIVE AND REPLACEMENT TABLES

COMPREHENSIVE REFERENCE to G.E.C. television, radio and communication equipment with valve combinations.

TYPICAL VALVE CIRCUITS

PRICE

5/-

Plus 9d. for postage and packing.

Apply to your radio retailer for your copy.

THE GENERAL ELECTRIC CO. LTD., MAGNET HOUSE, KINGSWAY LONDON, W.C.2.

FERROXCUBE

FERROMAGNETIC FERRITE

FOR TELEVISION

THE improvement in television components, with their smaller size and greater efficiency, is largely due to Ferroxcube, the new Mullard magnetic core material.
The uses of Mullard Ferroxcube in the production of TV components fall into these three main groups:

LINE OUTPUT TRANSFORMER CORES

Since the advent of wide-angle television tubes, with the accompanying demand for increased E.H.T. supplies, the need for line output transformers of the highest possible efficiency has been greater than ever. Mullard Ferroxcube, with its low iron losses, completely fulfils this need — also facilitating the assembly of small, compact transformer units by means of solid, non-laminated U-shape cores.

DEFLECTION COIL YOKES

Mullard Ferroxcube cores in ring form are ideal for producing the magnetic circuit around deflection coils. Used in this way, Mullard Ferroxcube makes possible the construction of efficient deflector coils with a high Q factor. In order to simplify assembly problems, these ring cores are supplied either in the form of a complete circle, as two semi-circles, or as castellated yokes.

LINEARITY AND PICTURE WIDTH CONTROLS

Mullard Ferroxcube can very conveniently be extruded into rods and tubes. In this form it is ideal for use in linearity and picture width controls, providing a smooth control in a compact assembly.

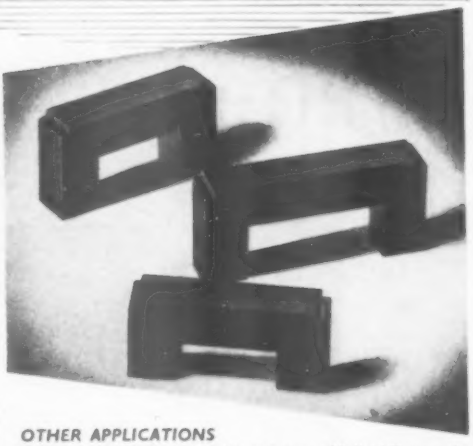

OTHER APPLICATIONS

In addition to its uses in television receivers, Mullard Ferroxcube is also being widely employed in line communications, radar, and other specialised electronic equipments. The purposes for which it is already being most successfully applied in such equipments include filter networks, wide band transformers, magnetic amplifiers, and pulse transformers.

PLEASE WRITE FOR FULL DETAILS

Mullard

Mullard FERROXCUBE

FERROMAGNETIC FERRITE

MULLARD LIMITED CENTURY HOUSE SHAFTESBURY AVENUE LONDON W.C.2.

MF376

BRADMATIC

MAGNETIC TAPE RECORDING EQUIPMENT

Bradmaster Model 5 Tape Desk

- Built to professional standards.
- Two speeds—3¾ and 7½ inches per second.
- Easily adjusted for single or twin track recordings.
- Fast wind and rewind—full reel rewound in 1½ minutes.
- Heavy alloy flywheel. Freedom from "wow" and "flutter."
- Double servo brakes on each hub.
- Push Button control.
- Three heavy duty motors.
- Three shielded Bradmatic heads.
- Size: 13½in. x 15½in. x 6½in. deep.

Price **£41** (fitted with 5 R.P. heads)
or with 6 R.P. heads **£42**

Hi-fidelity magnetic sound heads:	
type 5 R.P. (record/play head)	£3 5 0 each
type 5 E (erase head)	£3 5 0 "
Super fidelity magnetic sound head, type 6 R.P. (record/play head)	£3 15 0 "
Composite screening cans (constructed of steel and mumetal)	4 6 "
Oscillator coils	8 0 "
Oscillator coil type 1.B.	9 0 "
Plate coil type 1.B.	9 0 "
Tape on 7in. reels, 1,200ft.:	
Emitape type 65 Low Coercivity	£1 15 0 "
Emitape type H.60 High Coercivity	£1 15 0 "
G.E.C. Grade "A"	£1 10 0 "
Scotch Boy (Durex) MC1-111	£1 15 0 "

Amplifiers and Microphones supplied.

Trade Supplied. *Send for Lists to the Sole Manufacturers.*

BRADMATIC LIMITED

STATION RD. · ASTON · BIRMINGHAM 6

Phone: EAST 0574. Grams: Bradmatic, Birmingham

All these high-quality features . . . yet it retails at only £5'17'6!

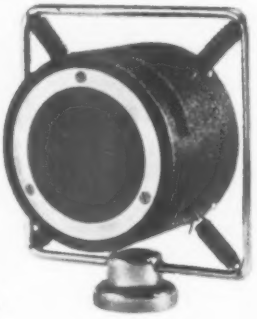

- Non-hygroscopic diaphragm
- Former-less speech-coil
- Good transient response
- Smooth response curve
- High amplifier gain without feed-back
- Stable operation
- Great sensitivity
- High output voltage

Type M.C.R. Moving Coil

GRAMPIAN MICROPHONE

The high flux nickel aluminium magnet and diaphragm assembly is housed in a spring suspended die cast case. Microphone input transformers and three types of stands, folding, table top and heavy-base, to suit this microphone, are also available.

● *Get full details without delay from:*

GRAMPIAN REPRODUCERS LTD

9, HANWORTH TRADING ESTATE, FELTHAM, MIDDX.

Phone: Feltham 2657 *"Grams: Reamp, Feltham*

NEW WINDSOR TESTGEAR

MODEL 66A

SIGNAL GENERATOR
LIST PRICE £22·10

A newly designed A.C. mains operated R.F. Signal Generator of improved performance and reliability. Wide range and accuracy make it an ideal instrument for modern Radio and Television work.

★ **RANGES**
100–320 Kc/s. 3.2–10 Mc/s.
320–1000 Kc/s. 10–30 Mc/s.
1000–3200 Kc/s. 30–80 Mc/s.

★ **ACCURACY**
Frequency calibration accuracy is within ± 1 per cent.

★ **SCREENING**
All unwanted R.F. leakage is eliminated by scientifically designed double screening.

★ **MODULATION**
Internal modulation, of good waveform, is provided at 400 c.p.s. modulating to a depth of approx. 30 per cent.

★ **OUTPUT**
Modulated or unmodulated R.F. output up to 100 millivolts. Terminating unit provides two output levels and incorporates an artificial aerial.

VALVE TESTER
LIST PRICE £24

MODEL 45B

A comprehensive mutual conductance valve tester, suitable for most types of British, American and Continental receiving valves. Supplied with valve chart giving data for testing nearly 3,000 different valves. For use on A.C. mains only.

TESTING FACILITIES

★ **MUTUAL CONDUCTANCE.** Two ranges : 0–3 mA/V and 0–15 mA/V.

★ **CATHODE LEAKAGE.** Tests for Heater/Cathode insulation up to 10 megohms, with heater at operating temperature.

★ **EMISSION.** Rectifiers and Diodes may be tested for emission.

★ **ELEMENT SHORTS.** Short circuits between electrodes are clearly indicated.

★ **GAS TEST.** Press - button test shows abnormal positive or negative grid current.

Please write for further details and information on other WINDSOR and TAYLOR products

TAYLOR ELECTRICAL INSTRUMENTS LTD

419-424 MONTROSE AVENUE, SLOUGH, BUCKS. Phone: SLOUGH 21381

SELECTIVE TRANSMISSION MEASURING SET

B.C.C. introduce another outstanding success in their development of Measuring Instruments.

This instrument is a direct reading, selective, gain and loss measuring set to be used with an external signal generator.

Four terminal networks, active and passive, balanced or unbalanced, can be measured.

Facilities are provided for use as a high impedance Selective Detector Amplifier.

Frequency Coverage : 1—68 Kc/s in 4 ranges.
Range of Measurements : Gain 0-60 db. Loss 0-80 db.
Accuracy : ± 0.5 db.
Impedance range : 75, 150 and 600 ohms., balanced or unbalanced.
Det.-Amp Sensitivity : 10-12 μV.
Power Supplies : 100-150-200-250v. 50 c/s.

Based on Signals Research and Development Establishment design.

Manufactured for Ministry of Supply and G.P.O.

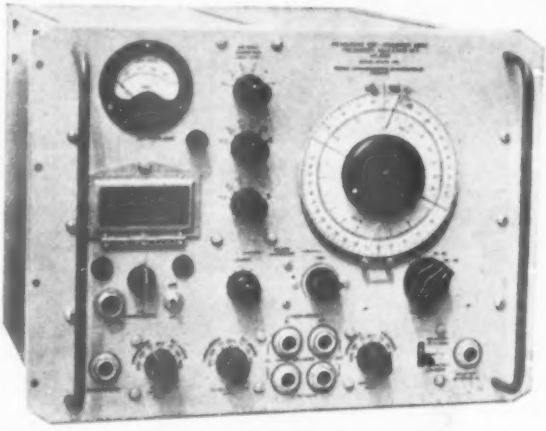

BRITISH COMMUNICATIONS CORPORATION LIMITED
31 GORDON AVENUE, STANMORE, MIDDX. GRIMSDYKE 2266
Cables : BEECEECEE, STANMORE

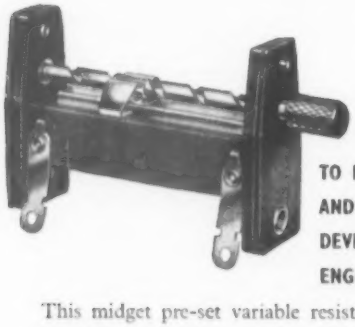

TO RADIO AND T/V DEVELOPMENT ENGINEERS

This midget pre-set variable resistor with new double-slider gives greater stability and makes accurate adjustment easier. Designed for panel or chassis mounting: available in any value from 10 to 25,000 ohms.

EGEN ELECTRIC LTD

Charfleet Industrial Estate, Canvey Island, Essex. Phone: Canvey 691

HANNEY OF BATH

offers the following brand new goods from stock:—

EDDYSTONE 740 RECEIVER, £38 15/-, we pay carriage.

WILLIAMSON AMPLIFIER—mains transformer to specification, 57/6; 10h. 150 mA. choke £1/10/-; 10h. 25 mA. choke, 10/-. Elstone output transformer (3.6 ohm sec.) 90/-; T.C.C. 8 mfd. 600 volt electrolytics, 15/-; KT 66 valves, matched pair, 50/2; EF 37A valves, 25/1. All resistor and condenser kits available as per our Jan. classified advert.

"VIEWMASTER," constructors' envelopes, London, Birmingham or Holme Moss, 5/6, post free. WB100, 18/6; WB101, 5/-; WB102, 18/6; WB103, 37/6; WB104, 15/6; WB105, 32/6; WB103A, 52/6. T.C.C. condenser kit, £7/7/-; Morganite resistors, 35/3; Type Q pots., 5/- each; Westinghouse rectifiers, 30EHT100, 27/10; 14A86, 18/3; WX3 and WX6, 3/6 each. 6 Colvern pots., 22/6. Bulgin kit, 12/6. Wearite coils, London, 22/-, Birmingham and Holme Moss, 30/-. Pre-amp. coils, 5/- pair. Line transformer, 27/-, frame transformer, 21/6, width control, 10/-, boost choke 5/9, focus rings 22/6, tube support, 16/-. Any item sold separately.

CATHODE RAY TUBES. 9in., Mullard MW22-14C, MW22-17, MW22-18, Mazda CRM92, £13/15/7. 12in., Mullard MW31-14C, MW31-17, MW31-18, Mazda CRM 121A, CRM 121B, £18/4/10. Mazda CRM 123, £20/10/4. Brimar C12B, £19/7/4. We pay carriage on all tubes and guarantee safe delivery. (Not sent C.O.D.).

GRAM-MOTORS. Decca 3-speed with turntable 74/4; 3-speed £7/3/4. Collaro RC 500 auto-changer (78 r.p.m.) £12/2/6. Chancery LP attachment, converts 78 to LP, 77/6.

ACOS GP 20 PICK-UPS, standard or LP, £3/11/5, heads only either type 43/4.

SPEAKERS. W.B. Stentorian, 2½in. 18/6, 3½in. 19/6, 5in. 21/-, 6½in. 24/6, 8in. 26/8, 10in. 36/9, 10in. 44/6 (all 2 ohm speech coil). W.B. 10in. concentric duplex speaker, less trans., 135/-. Celestion, 10in. 15 ohm 45/-, 12in. 15 ohm type CT 137 (Rola G12), £8/5/-.

COILS AND COILPACKS. Wearite 'P' coils all types 3/- each. Weymouth 'H' coils all types 3/9 each, Atkins high 'Q' coils 3/6 each, Denco type 'C' TRF coils 8/6 pair, Weymouth TRF coils 10/3 pair, R.M. TRF coils 15/- pair. Wearite type 705 coilpack 53/4, Osmor 'Q' type HO coilpack 52/-/HF stage available at 21/8), Osmor 'Q' battery coilpack 54/2, ETA, 4-station tuning unit 47/4.

SUNDRIES. Valve manuals G.E.C., Brimar and Mullard 5/6 each inc. postage. "Wireless World" reprints, Williamson Amplifier 3/9, Superhet TV Unit 2/9, High Quality Audio Amplifiers 2/9, Radio Valve Data 3/9, all inc. postage. "Sound Reproduction," Briggs, 11/- post free. G.E.C. germanium crystals 4/- each. Brimar metal rectifiers RM1 4/6, RM2 5/-, RM3 6/-, DRM1B 10/-, DRM2B 11/-, DRM3B 13/-. Polystyrene varnish, large bottle 1/10. Solon soldering irons with pencil bit 23/8. Co-axial cable Aerialite, B-Lee, Edlewax 1/3 yard. Nuts, bolts, washers, soldering tags, mounting tags, group boards, ¼lb. reels enamelled copper wire (16 to 40 SWG) etc., etc., etc.

SEND 6d. stamp for our new list which covers all TV designs, Williamson Amplifier and general components. C.W.O. or C.O.D., all goods post free over £1

L. F. HANNEY
77 LOWER BRISTOL ROAD, BATH
Tel. 3811

Constant output – DOWN TO 1·4 C.P.S.

The specially designed resistance capacity circuit of the Ediswan Low Frequency Oscillator type R666 ensures constant output and good waveform even with frequencies as low as 1·4 c.p.s. For testing, calibration, amplifier set-up and in all cases where a dependable low frequency standard is required this instrument is ideal. Supplied in unit form for standard rack mounting. Special stands for bench use (as illustrated) are available.

PRICE

Oscillator . £75 . 0 . 0 Stands (Per Set) . . . £1 . 1 . 0

EDISWAN

THE EDISON SWAN ELECTRIC CO., LTD., 155 Charing Cross Road, London, W.C.2

Member of the A.E.I. Group of Companies

SP58

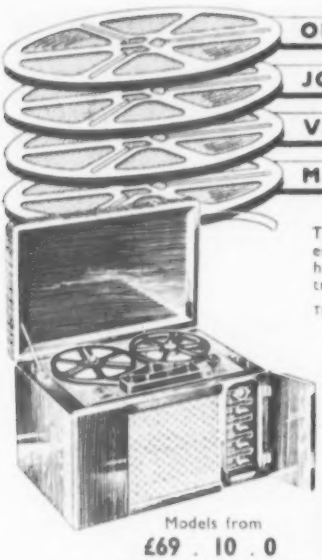

BUILD UP A SOUND LIBRARY

FOR PLAY-BACK WHENEVER YOU WISH

The Soundmirror is an amazing instrument on which you produce your own recorded entertainment. Favourite music or radio items, important events in your family's history—all these can be built up into a library for play-back whenever you wish—treasured sound memories, and unique entertainment for the future.

The Soundmirror has many other applications—it is in daily use in the professions; in teaching and for religious and political activities.

Write for literature or a demonstration by appointment to the manufacturers.

Now available in England—the book "Magnetic Recording" by Dr. S. J. Begun.
A comprehensive treatise. Price 25s. post 9d extra.

Models from
£69 . 10 . 0
exclusive of microphone

THE **Soundmirror**

THERMIONIC PRODUCTS LTD.

(DIV. SM WW), HYTHE, SOUTHAMPTON, *Hythe 3265.* London Showrooms: MORRIS HOUSE, JERMYN ST., S.W.1. *WHi 6422*
Sales and Service Centres: Manchester, Birmingham, Bristol, Leeds, Newcastle, Glasgow, etc.

ARTHURS HAVE IT!

LARGE STOCKS OF NEW VALVES

TEST METERS IN STOCK

"AVO," "TAYLOR" TEST METERS AND SIGNAL GENERATORS

Leak Point One Amplifiers	£28 7 0
Leak Pre-amplifiers	9 9 0
Leak Tuning Unit	36 17 4
Chapman Tuning Units	17 6 8
Crystal and Moving Coil Microphones. Decca Replacement Heads and Pickups.	
Goodman's Axiom 150 Speakers	£10 5 4
Partridge Output Transformers for Williamson Amplifiers	4 12 0
Cossor Double Beam Oscilloscope (1035	85 0 0
Cossor Double Beam Oscilloscope (1049	120 0 0

LATEST VALVE MANUALS

MULLARD, OSRAM & BRIMAR No. 4. 5 - each.
MAZDA 2 - each.

TELEVISION SETS, WIRE AND TAPE RECORDERS ALWAYS IN STOCK.

Goods offered subject to price alterations and being unsold.

Arthurs EST. 1919
PROPS: ARTHUR GRAY, LTD.
first

OUR ONLY ADDRESS: **Gray House,**
150-152 Charing Cross Road, London, W.C.2

TEMple Bar 5833-4 and 4765 WRITE FOR LISTS
TELEGRAMS—"TELEGRAY, WESTCENT, LONDON"
CABLES—"TELEGRAY, LONDON"

Masteradio

'VIBRATORPACK'

EARTH FREE
& Silent as the Stars

FOR
RADIO RECEIVERS
TRANSMITTERS
AMPLIFIERS
PUBLIC ADDRESS SYSTEMS
SCIENTIFIC APPARATUS
EMERGENCY POWER SYSTEMS

Masteradio Vibratorpacks convert low voltage DC to H.T. with minimum loss of power.

Please write for full details:

MASTERADIO LTD.
FITZROY PLACE - - LONDON, N.W.1

Efficient contact between high-speed aircraft depends on instantaneous radio communication. Aircraft radio equipment is used under arduous conditions both in peace and war and must be available instantly throughout the 24 hours of a day.

It is not surprising, therefore, that more and more G.E.C. Quartz Crystal Units are being used, for this is the most critical component and only the best is safe and good enough.

Write for list QC 5012 (R)

SALFORD ELECTRICAL INSTRUMENTS LTD · SALFORD 3 · LANCS

A SUBSIDIARY OF THE GENERAL ELECTRIC CO LTD OF ENGLAND

Three heads are better than one!

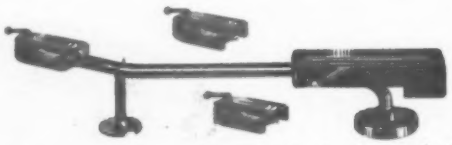

For Standard and Microgroove Recordings

Green Spot with .001" radius sapphire for microgroove recordings.

Red Spot with .0025" radius sapphire for modern standard recordings.

Yellow Spot with .003" radius sapphire for older standard recordings.

These pickup heads are fitted with an easily replaceable armature system complete with a semi-permanent sapphire. Armature mass 20 mg.

Extremely low mass at needle point (4/5 mg. only), allowing for reduction in downward pressure to 10/12 grams for standard recordings and 7/9 grams for microgroove recordings.

Prices: With one head £4 10 0 plus £1 19 0 Purchase Tax. Extra heads each £2 10 0 plus £1 1 8 Purchase Tax. Spare armature system with sapphire 14/8 including tax.

Licensed under Letters Patent No. 586900 and/or 613424.

a **Connoisseur** product

Tel. : HALIFAX 69169.

Manufactured by A. R. SUGDEN & CO. (ENGINEERS) LTD., Well Green Lane, Brighouse, Yorks.

here's your

★ really comprehensive range of **Engraved Control Knobs!**

Adds the 'finishing touch' to your equipment!

These attractive Control Knobs are actually Inscribed In Gold. The range is the most comprehensive available anywhere and caters for the needs of every Radio—Television—Amplifier enthusiast. The following inscriptions are now in universal demand:—

TELEVISION. "Brilliance," "Contrast," "Focus," "Brightness," "Brilliance, On-Off."

RADIO. "Volume," "Tuning," "On-Off," "Radio-Gram," "Tone," "Wavechange," "Vol.-On-Off," "R. M. L. Gram."

AMPLIFIER. "Treble," "Bass," plus any of the above engravings.

Each coated knob is packed separately in a transparent envelope. Available in both Walnut and Ivory 1/6 each.

From your usual dealer or if in difficulty write to

UNCLES, BLISS & CO. LTD.
139, Cherry Orchard Road, East Croydon, Surrey
Telephones: CROydon 3379 & 390

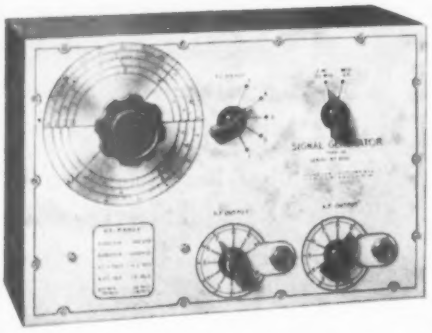

SIGNAL GENERATOR TYPE 10. 100 Kc/s-100 Mc/s

Price £7 . 10 . 0

The accuracy, reliability and comprehensive specification, are some of the reasons why the *TYPE 10* has achieved such outstanding success.

● *100 Kc/s to 100 Mc/s* ● *Modulated or unmodulated carrier* ● *Direct calibration* ● *Adjustable 400 c.p.s., AF signal* ● *Stable RF oscillator* *Large, easily read scale* ● *AC mains operation.*

New instruments now available include the *HOMELAB CHECKTEST* price 37/6d., and a range of accurately calibrated variable condensers, 100pf., 500pf., and 1000pf., price 42/- each.

Obtainable only direct from the manufacturers. Send for full technical details or call at address below

HOMELAB INSTRUMENTS LTD.,
68a, COBDEN ROAD, LONDON, E.11
Telephone: LEY 5651

"Frequentite" is the most suitable insulating material for all high frequency applications. Seventeen years ago we introduced the first British-made low-loss ceramic, and consultation with us before finalising the design of new components is a wise precaution.

STEATITE & PORCELAIN PRODUCTS LTD.

Head Office: Stourport-on-Severn, Worcestershire. Telephone: Stourport 111. Telegrams: Steatain, Stourport

S.P.77

COPPER INSTRUMENT WIRE (ex-stock)

SWG	Inch	ENAMELLED 2 ozs.	ENAMELLED 4 ozs.	TINNED 2 ozs.	TINNED 4 ozs.	COTTON COVERED 2 ozs.	COTTON COVERED 4 ozs.	SILK COVERED 2 ozs.	SILK COVERED 4 ozs.
16	.064	1/3	1/10	1/3	1/10	1/3	1/10	1/3	1/10
17	.056	1/3	1/11	1/3	1/11	1/3	1/11	1/3	1/11
18	.048	1/3	2/-	1/3	2/-	1/3	2/-	1/3	2/-
19	.040	1/3	2/1	—	—	1/4	2/1	1/5	2/3
20	.036	1/4	2/2	1/4	2/2	1/4	2/2	1/6	2/6
21	.032	1/4	2/3	—	—	1/4	2/3	1/7	2/9
22	.028	1/5	2/4	1/5	2/4	1/5	2/4	1/8	2/10
23	.024	1/6	2/5	1/6	2/5	1/6	2/5	1/9	3/-
24	.022	1/6	2/6	1/6	2/6	1/6	2/6	1/9	3/-
25	.020	1/7	2/7	1/7	2/7	1/7	2/7	1/10	3/2
26	.018	1/7	2/8	1/7	2/8	1/8	2/9	1/11	3/4
27	.0164	1/8	2/9	—	—	1/9	2/11	2/-	3/6
28	.0148	1/8	2/10	1/8	2/10	1/9	3/-	2/1	3/8
29	.0136	1/9	2/11	1/9	2/11	1/10	3/2	2/2	3/10
30	.0124	1/9	3/-	1/10	3/3	1/11	3/4	2/3	4/-
31	.0116	1/10	3/1	1/11	3/4	2/-	3/5	2/4	4/2
32	.0108	1/10	3/2	2/-	3/6	2/-	3/6	2/6	4/6
33	.010	1/11	3/3	2/1	3/8	2/2	3/9	2/9	5/-
34	.0092	1/11	3/4	2/2	3/10	2/3	4/-	2/10	5/2
35	.0084	2/-	3/5	2/3	4/-	2/5	4/3	3/-	5/6
36	.0076	2/-	3/6	2/5	4/3	2/6	4/6	3/2	5/10
37	.0068	2/1	3/9	2/6	4/6	—	—	3/4	6/2
38	.006	2/2	3/10	2/8	4/9	3/3	6/-	3/6	6/6
39	.0052	2/3	4/-	2/9	5/-	—	—	3/9	7/-
40	.0048	2/4	4/2	2/11	5/4	4/6	8/-	4/-	7/6
41	.0044	1/6 per oz.		1/9 per oz.				2/3 per oz.	
42	.004	1/9 " "		2/- " "				2/6 " "	
43	.0036	2/3 " "						3/- " "	
44	.0032	3/- " "						4/- " "	
45	.0028	4/- " "						5/6 " "	
46	.0024	5/- " "						7/6 " "	

47 swg Enam. and 47 swg E.S.S.C. wires in stock. State needs.

All above postage extra.

POST ORDERS ONLY PLEASE Send stamp for comprehensive lists. Trade supplied.

EUREKA RESISTANCE WIRES

Prices per ounce

20 swg. D.C.C., 1/6 ; 21 swg. Bare Oxy., 1/6 ; 22 swg. D.C.C., 1/6 ; 23 swg. Enam., 1/6 ; 24 swg. D.C.C., 1/10 ; 26 swg. Enam., 2/- ; 26 swg. D.S.C., 2/3 ; 27½ swg. Bare Oxy., 1/9 ; 29 swg. Bare Oxy., 2/- ; 30 swg. D.S.C., 2/6 ; 32 swg. D.S.C., 2/9 ; 32 swg. Enam., 2/3 ; 34 swg. D.S.C., 3/- ; 35 swg. D.S.C., 3/6 ; 36 swg. Enam., 2/9 ; 38 swg. E.S.S.C., 4/- ; 40 swg. D.S.C., 4/9. Other gauges inc. 44 & 46 swg. available.

LITZ WIRES also available.

Large stocks of B.A. SCREWS, NUTS, WASHERS, SOLDERING TAGS & EYELETS ; Paxolin type TUBING ; Laminated Bakelite and Ebonite PANELS ; TUFNOL and EBONITE TUBES and ROD ; ERIE and DUBILIER RESISTORS ; GERMANIUM and SILICON DIODES

POST RADIO SUPPLIES

33, BOURNE GARDENS, LONDON, E.4.

Widney-DORLEC

REGISTERED TRADE MARKS

CABINETS

We are now able to accept ORDERS for small or large quantities to any specified design

If you do not already know about this unique Cabinet system, write for details to :—

TECHNICAL SALES OFFICE,
59, BROMPTON RD., LONDON, S.W.3

MANUFACTURERS

A Widney PRODUCT

ESTABLISHED 1888

HALLAM SLEIGH & CHESTON LTD
WIDNEY WORKS · BIRMINGHAM 4

New Wharfedale Microgroove Equalizer and L.S. tone control unit

Inserted in a Loudspeaker circuit this new tone control unit gives a falling characteristic of about 3 D.B. per octave at 500 C.P.S. upwards. The unit, a tapped inductance with a six-position switch, is ideal for matching Microgroove recording characteristics or for use as a scratch filter on worn records. It is recommended for speakers of 2-16 ohms impedance up to 30 watts.

Microgroove Equalizer and L.S. Tone Control Unit. Dimensions : 7in. x 4¼in. x 4¼in. Weight : 2lb. 6oz. **Price 55/-**

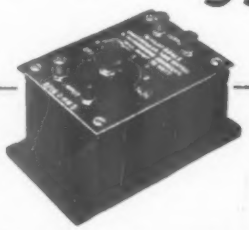

MODEL MG1

WHARFEDALE WIRELESS WORKS

BRADFORD ROAD, IDLE, BRADFORD, YORKS

TEL. IDLE 461

DUBILIER *Miniature* VOLUME CONTROL TYPE Y

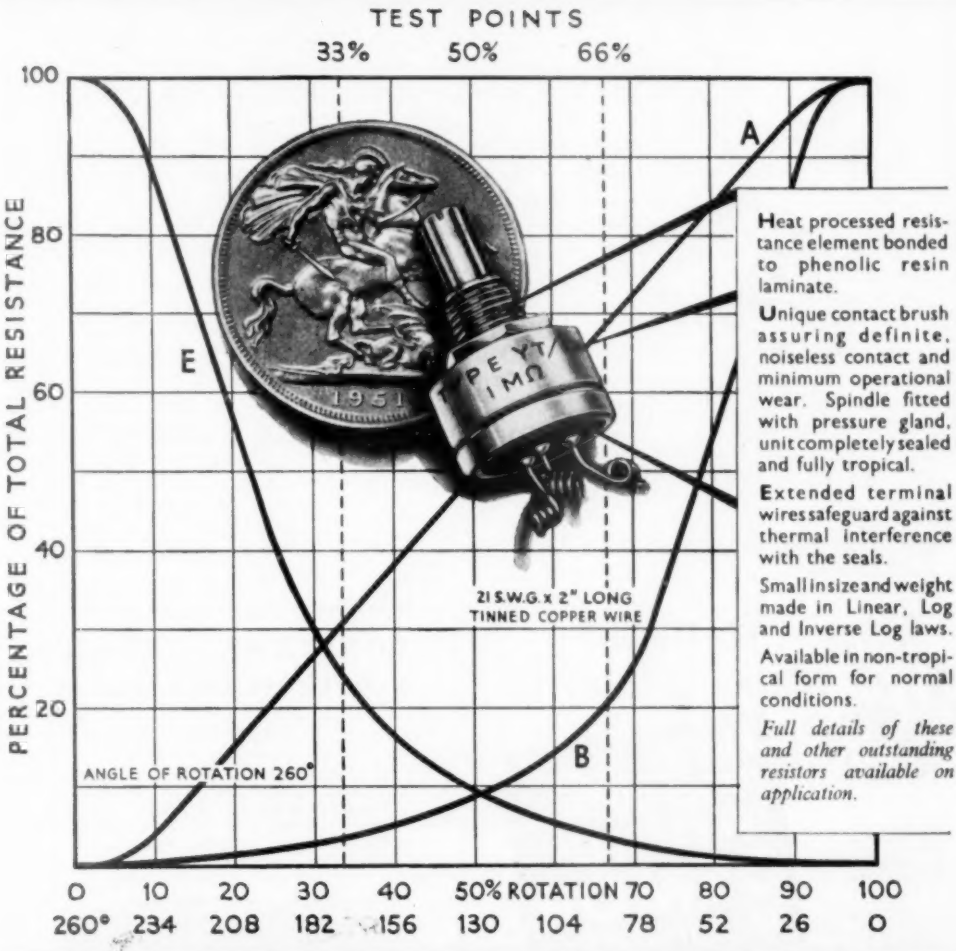

Heat processed resistance element bonded to phenolic resin laminate.

Unique contact brush assuring definite, noiseless contact and minimum operational wear. Spindle fitted with pressure gland, unit completely sealed and fully tropical.

Extended terminal wires safeguard against thermal interference with the seals.

Small in size and weight made in Linear, Log and Inverse Log laws.

Available in non-tropical form for normal conditions.

Full details of these and other outstanding resistors available on application.

A CROWN OF RESISTOR ENGINEERING ACHIEVEMENT

DUBILIER RESISTORS

DUBILIER CONDENSER CO. (1925) LTD., DUCON WORKS, VICTORIA ROAD, NORTH ACTON, W.3.
Telephone : Acorn 2241 (5 lines) Telegrams : Hivoltcon, Westphone, London
Cables : Hivoltcon, London, Marconi International Code.

D61A

SIMON STYLITES* says . . .

Productivity—output per man- and machine-hour—is the urgent need of British industry if our national economic problems are to be solved. Comparisons with American records are constantly thrust before us.

Some British engineering firms have already developed precision mass-production (of loud-speakers for example) up to, and perhaps even beyond, the standards claimed by their U.S. counterparts. When big American companies make that kind of admission, it does a bit of good for the whole industry—and for the old country, too.

★ *Simon Stylites spent much of his life at the top of a pillar, and from this eminence saw very clearly what went on around him.*

ISSUED BY

REPRODUCERS AND AMPLIFIERS LIMITED
WOLVERHAMPTON ENGLAND
Telephone: Wolverhampton 22241 (5 lines). Telegrams: Audio, Wolverhampton.

To avoid radio ailments

EVERY GOOD RADIO DOCTOR PRESCRIBES OSMOR "Q" COILPACKS

As specified for conversion of the Type 25 unit of the TR.1196, Type 18 and Wartime Utility receivers, and others.

Send 1d. (stamp) for free circuits and new illustrated lists of Coils, Coilpacks, and all Radio Components.

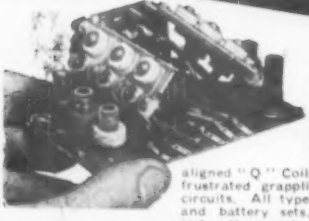

These mighty midget coilpacks will cure your radio troubles and ensure better performance in every way. Easy to assemble, with only five simple connections, the pre-aligned "Q" Coilpack saves hours of frustrated grappling with complicated circuits. All types available for mains and battery sets, complete with full instructions and circuit diagrams.

Avoid inferior imitations! Only ***genuine*** *Osmor Coilpacks are sold under the name "OSMOR"*

OSMOR RADIO PRODUCTS LTD. (Dept. W.27)
BRIDGE VIEW WORKS, BOROUGH HILL, CROYDON, SURREY
Telephone: Croydon 2140 9

CONSTANT VOLTAGE POWER SUPPLY UNITS

MODEL 101-C

Output: 250/400v. 0.250mA max.
Stability: Better than 0.1%.
Output Impedance: Less than 1 ohm.
Output Ripple: Less than 2mV. R.M.S.
Mains Supply: 200/250v. 45-60c/s.
Regulation down to zero load.

DETAILS ON REQUEST.

ALL-POWER TRANSFORMERS LTD.
CHERTSEY ROAD, BYFLEET, SURREY.
Tel: Byfleet 3224/5.

High stability quartz crystals

for frequency measurement and control

CUT from only the finest raw quartz, ***Standard*** high grade crystal units are obtainable to accuracies better than 50 cycles in one megacycle. Artificially aged, gold plated and suspended in vacuo, these crystals greatly reduce drift under working conditions. They will maintain this high degree of accuracy *under conditions of severe vibration* and *sharp changes in climatic conditions* such as are encountered in mobile communication equipment.

Standard **QUARTZ CRYSTALS**

Standard Telephones and Cables Limited

Registered Office: Connaught House, Aldwych, London, W.C.2

TELEPHONE LINE DIVISION North Woolwich, London, E.16 · ALBert Dock 1401

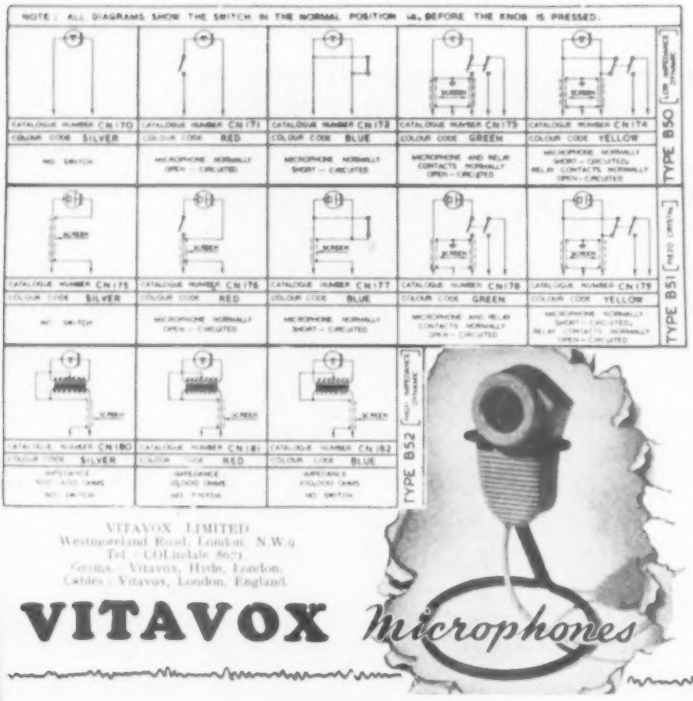

VITAVOX LIMITED
Westmoreland Road, London, N.W.9
Tel: COLindale 8671
Grams: Vitavox, Hyde, London.
Cables: Vitavox, London, England.

VITAVOX *microphones*

Relevant Facts

on B.50 Series Microphones

The VITAVOX B.50 Series is most comprehensive and includes instruments to meet almost every requirement for a hand microphone. The series comprises Type B.50, incorporating a high-grade moving coil element; Type B.51 with crystal insert; and Type B.52, similar to Type B.50 but with a transformer for direct connection to amplifier or medium impedance line. The diagram indicates the wide range of switch circuits available with Types B.50 and B.51, and the different transformer ratios available with Type B.52 which has no switch. Additional versions can be supplied for special purposes when required in quantity.

5585

SHORTAGE OF RADIO & T/V ENGINEERS

The demand of Industry for our trained students is still greater than we can supply —and is likely to remain so for many years.

We offer:

FULL TIME DAY COURSE

1 year course in Principles and Practice of Radio and Television.

Next Course commences 15th April

Write for FREE BROCHURES giving details of the above, of our 3-year course, and of others.

E.M.I. INSTITUTES—the only college which is part of a great industry.

E.M.I. INSTITUTES

(DEPT. 16A), 10, PEMBRIDGE SQUARE, LONDON, W.2. TEL.: BAYSWATER 5131 2

Associated with "H.M.V." MARCONIPHONE COLUMBIA ETC.

URGENTLY REQUIRED

THE FOLLOWING EQUIPMENT IN ANY CONDITION :—

FREQUENCY METERS Type BC.221, BC.221AK, TS.174 U, TS.175, TS.69 AP. Also LR2 (Naval Version) by General Radio Co., and other types.

AMERICAN TEST SETS Type TS.13AP, TS.12AP, TS.34AP, TS.47AP, TS.10, TS.16APN, TS.33, TS.35, TS.36, TS.45, TS.59, TS.110, TS.118, and others.

RECEIVERS Type APR1, APR4, and tuning units.

AR88D spare parts, particularly wave change switches.

ALSO :—IMPEDANCE OR UNIVERSAL BRIDGES, OSCILLOSCOPES, " Q " METERS, VARIACS, OUTPUT METERS, ETC.

Please write, call or phone, giving price, condition, etc.

ELM ELECTRIC CO.,
175, UXBRIDGE RD., HANWELL, W.7
EALing 0779

An Announcement . . .

DUREX ABRASIVES LTD. wish to announce that as from June 14th, 1951, the name of the Company has been changed, and is now the MINNESOTA MINING & MANUFACTURING COMPANY LTD. Identification will be as before, except that the words " Scotch Boy " will be used instead of " Durex " as a prefix to the name of the material, e.g., " Scotch Boy " Magnetic Recording Tape instead of " Durex " Magnetic Recording Tape.

Existing high standards in the quality of the products will be maintained, the change is in name only.

'SCOTCH BOY'
Magnetic Recording
TAPE

ANOTHER 3M COMPANY PRODUCT

Manufactured by:—

MINNESOTA MINING & MANUFACTURING COMPANY LTD

167, STRAND - LONDON - W.C.2 - AND SLOUGH

LONDON, HOLME MOSS, and SUTTON COLDFIELD
We have complete stocks of all "Viewmaster" & "E.E." Components.

BERRY'S
(SHORT WAVE) LTD.
25, HIGH HOLBORN, LONDON, W.C.1
TEL: HOLBORN 6231

THE "WILLIAMSON" AMPLIFIER
All components available including precision resistors and capacitors and Partridge or Vortexion Output and Mains Transformers, Chokes, etc.

MAGNETIC RECORDING MADE EASY!

Today a great number of people own high-fidelity amplifiers capable of reproducing a frequency band far in excess of that required for tape recording. The Berry Magnetic Recording Amplifier Units MRU1 and 2 effectively convert existing amplifiers without internal modification to enable tape recording and playback to be done.
List MTR1 contains full technical details of these units and also information about available accessories for magnetic tape recording. It will be sent on receipt of threepence in stamps.
The circuit diagrams, practical layouts and instructions are also available for a charge of five shillings which will be credited against purchases to the minimum value of Three Pounds.

THE "LINCOLN" OSCILLATOR COIL

Completely enclosed in "Neosid" former ensuring minimum external field. Unusually good waveform with maximum amplitude at 45 kc/s. Numbered tag panel connections and one-hole fixing. Overall size 1¼in. x 1¼in. x 1in. only. PRICE 12.6. Post, packing 6d.

IN STOCK

AMPLIFIERS			
LEAK "Point One"	£28	7	0
RCPA.U. Pre-amplifier	£9	9	0
Tuner Unit	£37	4	6
ACOUSTICAL "QUAD"	£38	0	0
Tuner Unit	£26	0	0
ARMSTRONG CHASSIS			
EXP 73, 7 valves, 3 wave-bands	£25	12	4
EXP 125.3, 14 valves, 5 wave-bands	£53	0	10
CRYSTALS			
Brookes and Q.C.C.	£1	12	6
DENCO			
Chassis mounting coils		3	9
LABGEAR			
Wide Band Couplers	£1	1	0
Transmitting Coils, all frequencies			
MICROPHONES			
ACOS Crystal	£6	6	0
GRAMPIAN Moving Coil	£8	8	0
RESLO Ribbon	£7	10	0
ROTHERMEL D104 Crystal	£5	5	0
TRIX Moving Coil	£8	8	0
VITAVOX Moving Coil	£6	15	0
MOTORS			
CHANCERY Long playing attach.	£3	12	6
COLLARO and Pick-up	£6	10	10
CONNOISSEUR Two-speed	£22	18	8
DECCA 2-speed Record Player	£12	1	6
DECCA MU14 3-speed Motor	£7	3	4
PLESSEY 3-speed 7in., 10in., 12in. Changer	£33	13	0
"Q-MAX"			
84/40 Transmitter	£75	0	0
Chassis Cutters, all sizes.			
Absorption Wavemeter	£1	15	0
"S" Meter	£3	3	0
RAYMART			
Plug-in coils from 11-350 metres.			
Plain and ribbed 4 and 6-pin formers.			
SPEAKERS			
BARKER 148a	£15	15	0
BARKER 150a	£18	18	0
GOODMAN "Axiom 150"	£10	5	6
GOODMAN 15in.	£18	10	0
W.B. Concentric Duplex, 10in.	£6	15	0
WHARFEDALE			
Super 5CS/AL	£4	12	6
Super 8CS/AL	£4	12	6
"Golden" 10in.	£5	2	6
Super 12CS/AL	£15	0	0

"Q-MAX" GD01 GRID-DIP OSCILLATOR

The frequency range is 1.5-300 Mc/s. by plug-in coils. Built-in mains power pack. PRICE 9½ gns. with one coil. (Extra coils 3.6 each.)

These
Richard Allan
Bafflettes

are fitted with
LARGER
Loudspeakers than ANY
similarly priced extension loudspeakers!
The NEW "BONNIE" 39/6
Obtainable from all Good Radio Dealers
Richard Allan Radio Ltd., Bafflette House, Batley, Yorkshire

BRANDENBERG E.H.T. GENERATOR
Type B.G. 6900

Output:—6 to 9 Kv.
Input:—250 to 350 volts H.T., 20 to 25 mA., 6·3 volts L.T.

Totally enclosed in a louvred aluminium case measuring 3¼" by 4½" by 5½" high.
Ideal for new television receivers or as a replacement for E.H.T. transformers, etc.

Price £5 - 15 - 0

BRANDENBERG DESIGNS LTD.
196, DAWES ROAD, S.W.6.
Phone: FULHAM 1534

11—Ia/Va CURVES in 1/50th OF A SECOND!

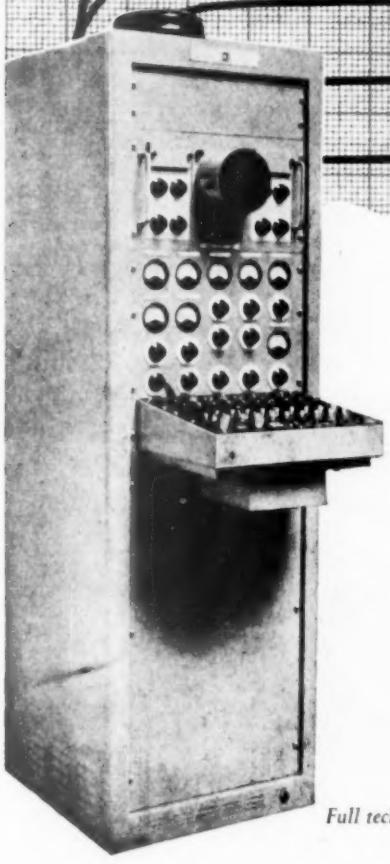

—with the

'CINTEL' UNIVERSAL VALVE TESTER

This instrument will produce a family of eleven Anode Current/Anode Voltage curves on a cathode-ray tube screen and is suitable for testing any receiving type valve. A calibrated graticule enables direct comparison to be made with valve manufacturers' published curves and the optimum operating conditions for a valve in any circuit are easily obtained.

Full technical information is available on application to:—

CINEMA-TELEVISION LIMITED

A Company within the J. Arthur Rank Organisation

WORSLEY BRIDGE ROAD · LONDON · S E 26

Telephone: HITher Green 4600

SALES AND SERVICING AGENTS

F. C. Robinson & Partners Ltd., 287, Deansgate, Manchester, 3 — H. Hawnt & Co., Ltd., 59, Moor St., Birmingham, 4 — Atkins, Robertson & Whiteford Ltd., 100, Torrisdale Street, Glasgow, S.2

CINTEL

REGISTERED TRADE MARK

V.H.F. Bridges

Balanced measurements up to 100 M cs
Unbalanced measurement up to 250 M cs

DURING the last few years a number of techniques have been developed for making V.H.F. impedance measurements with an accuracy of 1% or 2%, so that a V.H.F. Bridge is no longer a novelty. It is still, however, comforting to have a bridge with which parasitic capacities do not cause serious errors in measurement. Wayne Kerr bridges avoid the difficulties arising from parasitic capacities by the use of transformer ratio arms, which give extremely low impedances between the bridge terminals and from the bridge terminals to ground. These V.H.F. bridges are as stable and as simple to use as an audio frequency bridge.

Wayne Kerr

Photo by courtesy Marconi's Wireless Telegraph Co. Ltd.

THE WAYNE KERR LABORATORIES LTD., NEW MALDEN, SURREY *Tel: MALden 2202*

"RD" HIGH FIDELITY EQUIPMENT

"RD" Williamson Model D " amplifier	£29 0 8
"RD" Williamson " pre-amplifier tone-compensation unit	£10 7 6
"RD Junior De Luxe " (KT66) amplifier	£25 10 0
"RD Baby De Luxe " amplifier complete	£17 10 0
"RD3 " Pre-tuned Radio Unit	£17 12 0
"RD 9KC Rejector Unit "	£3 15 0
"RD GP20 Adaptor " Two Models	£1 1 0
"RD Loudspeaker Cross-Over Units " from	£3 0 0
Recommended for use with the above :—	
Barker Model 150 12in. Loudspeaker	£18 18 0
Goodmans Axiom 150 12in. Loudspeaker	£10 5 6
"RD Senior Corner Cabinet "	£35 0 0
"RD Bass Reflex Cabinet " Model B8 A	£16 16 0
"RD Bass Reflex Cabinet " Model G2 8	£17 5 0
Wharfedale W10 CS 10in. Loudspeaker	£8 10 0
"RD Junior Corner Cabinet "	£12 10 0
Connoisseur super lightweight p.u.	£10 0 8
Decca XMS p.u.	£7 0 0
Acos GP20 p.u.	£3 11 5
Connoisseur dual-speed motor	£22 18 8
Decca triple-speed motor	£7 3 4

Full details of the above units are available on request, and demonstrations may be heard daily.

Trade and Export enquiries invited.

● **NEW!** All L.P. Records promptly despatched by post. Orders over £2 post free, under £2 add 1/-.

Complete L.P. Record Catalogue 1/6, post free.

ROGERS DEVELOPMENTS CO.

"Rodevco House", 116, Blackheath Road, GREENWICH, S.E.10

Telephone: TIDeway 1723

ALWAYS SOUND CHOICE

CELESTION

The Foremost Name in Sound Reproduction

Because no radio receiver can give better reproduction than its loudspeaker permits, Celestion has always been the first choice of discriminating buyers. There is a comprehensive range of models with characteristics to suit all requirements. Write today for details.

Wholesale enquiries to:
TRUVOX LTD.,
Exhibition Ground,
Wembley, Middx.
Wembley 1212

ROLA CELESTION LTD.

Phone Emberbrook 3402-6

WORKS · SUNBURY RD · THAMES DITTON · SURREY

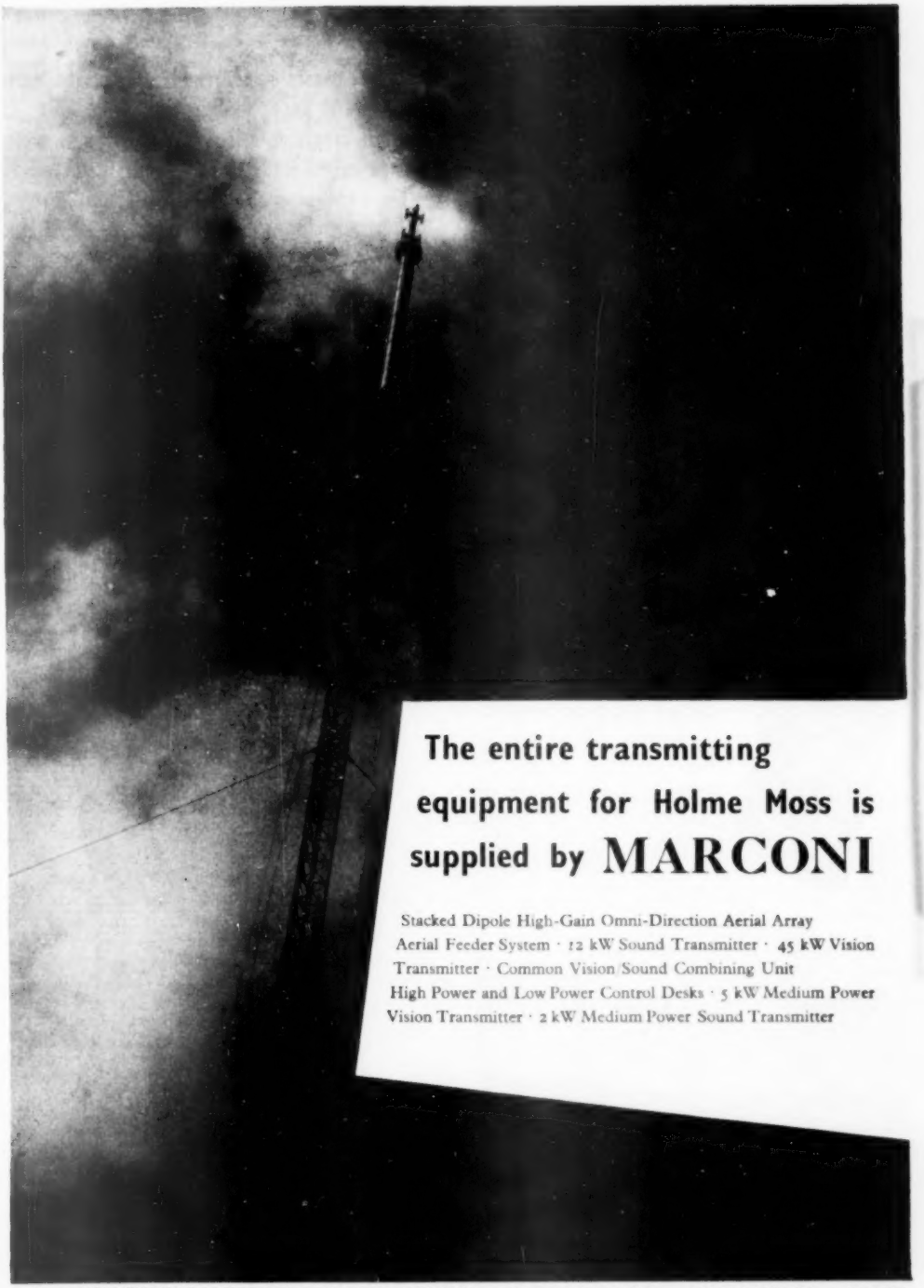
The entire transmitting equipment for Holme Moss is supplied by MARCONI
Stacked Dipole High-Gain Omni-Direction Aerial Array
Aerial Feeder System · 12 kW Sound Transmitter · 45 kW Vision Transmitter · Common Vision/Sound Combining Unit
High Power and Low Power Control Desks · 5 kW Medium Power Vision Transmitter · 2 kW Medium Power Sound Transmitter
MARCONI'S WIRELESS TELEGRAPH COMPANY LTD · MARCONI HOUSE · CHELMSFORD · ESSEX

FIRST AGAIN! ★★★★★★★★★★★★★★★★★★★★★★★★

Here is Your Two-Valve Translator

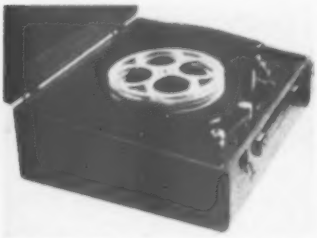

★ 1948 We gave you wire recording utilising a gramophone motor
★ 1949 We gave you talking books for the blind
★ 1950 We gave you tape recording utilising a gramophone motor
★ 1952 We give you now for the FIRST TIME in MAGNETIC RECORDING

A Two-Valve Translator

By clever circuitry we have produced for you a 2-valve translator which supersedes costly amplifiers and saves you needless expense. This unique translator will magnetically record from any microphone or pick-up. This unique translator will playback from any make of recorder. It will (without electrical connection to telephones) record 2-way conversations. It will playback into business intercom systems. It will playback into cinema or wireless relay systems.

You can magnetically record, using your gramophone motor as a drive and the amplifier within your radio as the tape amplifier. Conversion Kit (readily detachable) containing all necessary parts and instructions. £7, includes postage, etc.

The translator has both audio and a radio frequency outlet so that any radio receiver tunable to say 900 metres can boost the output to greater volume if desired. This wonderful new TWO-VALVE TRANSLATOR CHASSIS costs only £12.10.- ready for use on 230 A.C. Other voltages to order.

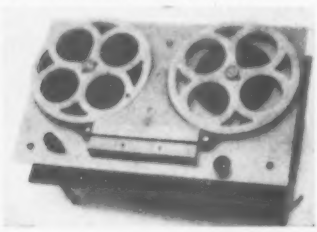

The Diamond Tape Recorder. Two speeds (Diction 2 hours, Music 1 hour). Twin tracks. Fast forward wind and fast rewind. Strongly built for hard work. Can be used with any conventional amplifier or the translator. £25, including choice of tape, Diamond, Scotch Boy, E.M.I., G.E.C.

Recording playback and erase heads for home assembly.
Bandeau Type 7/6 pair. Record/playback and erase. Kit contains all parts and instructions.
Cassette Type 30/-. Contains both record/playback and erase heads in one housing. The heads can be changed about according to tape direction (erase should precede record head). Gaps are adjustable. Cores are stacked mumetal half width for 2-way tracking. Bobbins ready wound Hi or Lo impedance to choice.

Oscillator coils 6/6. For generating 45Kc supersonic bias current and erase current. Primary and secondary windings for Hi or Lo impedance heads.

PARK RADIO OF MANOR PARK

DISTRIBUTORS FOR JUDGE INDUSTRIES
783 ROMFORD ROAD, LONDON, E.12

Phone ILF 2066
for demonstrations by appointment only

A BOOK FOR SOUND ENTHUSIASTS AND MUSIC LOVERS

by G. A. BRIGGS *

192 pp., printed Fine Art paper, size 8½ x 5½, bound full rexine. 102 figures.

"This is a fascinating book, excellently produced and richly illustrated: 192 pages packed with pleasure and profit for all who are interested in the pianoforte and the science of sound."—J. R. Tobin, B.Mus., MUSIC TRADES REVIEW, June, 1951.

"This book is as unusual as the title. It is a comprehensive study of the piano and contains a really fascinating chapter in which half-a-dozen internationally famous pianists answer a searching questionnaire. Mr. Briggs is always understandable, and he brightens the text with many an unexpected witticism."—YORKSHIRE OBSERVER, 4th July, 1951.

*Author of Two Practical Guides to Good Reproduction

DOCUMENTED — AUTHORITATIVE — ILLUSTRATED
LOUDSPEAKERS by G. A. Briggs
The Why and How of Good Reproduction 3rd Edition (5th Impression). A standard reference book, written in the author's attractive style, it answers the numerous questions that arise in connection with the reproduction of sound via the Loudspeaker.
36 illustrations. 88 pages. 7/6 (7/9 post free)
SOUND REPRODUCTION by G. A. Briggs
248 pages, 193 diagrams. Bound full rexine, 10/6.
Our stock of the 2nd Edition is now sold out, but supplies are still available from various dealers and bookshops.

PUBLISHED BY—

Wharfedale WIRELESS WORKS

BRADFORD ROAD, IDLE, BRADFORD, YORKS
Telephone: IDLE 461

made to measure . . .

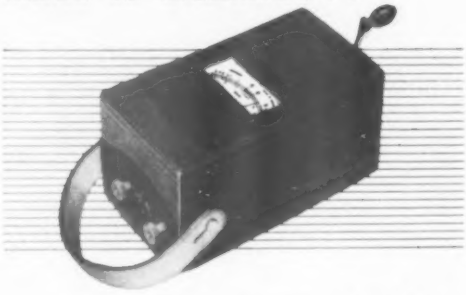

The man who knows exactly the state of his insulation at any time—is wise.

But one who uses a "Record" Insulation Test Set is wisest. It is made to measure—ACCURATELY, by those who were pioneers in this field and who have kept ahead.

RECORD MAKERS OF MANY OTHER FINE INSTRUMENTS

THE RECORD ELECTRICAL CO LTD

BROADHEATH · ALTRINCHAM · CHESHIRE

Phone: Altrincham 3221/2/3 Cables and Grams: "Circscale" Altrincham
London Office: 28 Victoria Street, London, S.W.1. Phone: Abbey 5148 & 2783
Grams: "Circscale" Sowest, London. Cables: "Circscale" London

STRICTLY EXPORT ONLY

HALTRON

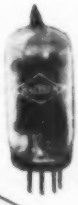

Leading Exporters of all types of Radio Receiving and Transmitting Tubes. Current Production and Ex-Government Surplus Special Purpose Tubes. Over 500 types in large quantities, available Ex-Stock. Suppliers to Foreign Governments, Airlines, etc.

SOME OF THE TYPES CARRIED IN STOCK

1A5GT	6AM6	6SF7	12K8	78	836	BL63	NT63A
1C5GT	6AQ5	6SG7	12K8GT	80	837	CCH35	NU3/U14
1E7G	6AT6	6SH7	12SA7	81	838	CL33	QP21
1G6GT	6AU6	6SH7GT	12SA7GT	82	841	CMG25	OZ4
1G7GT	6A8G	6SJ7Y	12SC7	83	843	CV1501	OZ4A
1LD5	6A8GT	6SK7	12SG7	83V	860	CY32	PEN46
1LN5	6BA6	6SK7GT	12SH7	84	864	D63	PM4DX
1P5GT	6BE6	6SL7GT	12SJ7	89	865	DA60	PM202
1P31	6B7	6SN7GT	12SK7	100TH	866A	DET5	PT15
1R4/1294	6B8	6SQ7	12SK7GT	117L7GT	866JR	DET19	PX4
1R5	6B8G	6SQ7GT	12SL7	210VPT	869B	E1148/CV6	PX25
1S4	6C4	6SS7	12SL7GT	211 (VT4C)	872	E1190	R2
1S5	6C5	6ST7	12SN7GT	220B	872A	E1231	R3
1T4	6C5GT	6U7G	12SQ7	262B	874	E1248	R12
2A3	6C6	6V6	12SQ7GT	304TH	878	E1271	RK28A
2A5	6C8G	6V6G	12SR7	282A	884	E1273	RK34
2A6	6C21	6V6GT	12Y4	304TH	902	E1320	RK59
2C26	6D6	6X4	15E	304T1	923	E1323	RKR73
2C34	6E5	6X5G	25A6G	307A	931A	E1415	RL7
2J21A	6F5	6X5GT	25L6GT	311A	954	E1436	RL37
2X2	6F5G	6Y6G	25Y5	313C	955	E1468	RT20A
2X2A	6F5GT	6Y7G	25Z4G	327A	956	E1516	S27A
3A4	6F6G	6Z5	25Z5	328A/4328A	957	EA50	S130
3AP1	6F7	7A7	25Z6G	357A	958A	EBC33	SO12
3B7/1291	6F8G	7B6	25Z6GT	388A	959	ECH22	SP2
3BP1	6G6G	7B7	28D7	394A	991	EF22	SP4
3D6	6H6	7BP7	30	510A	1299	EF39	SP41
3Q4	6H6G	7C4	32	703A	1613	EF50	SP210
3QSGT	6H6GT	7C5	35L6GT	705A	1616	EK32	SP15297
3S4	6J5	7C6	35T	708A	1619	EL32	STV280/40
3V4	6J5G	7C7	35TG	713A	1622	EL33	STV280/80
4D1	6J5GT	7E5	35W4	715A	1624	GTIC	TT4/NR57
5BP1	6J7	7E6	35Z3	715B	1625	GU20	TZ20
5BP4	6J7G	7E7	35Z4GT	717A	1626	HK54	TZ40
5CP1	6K6G	7L7A	35Z5GT	724A	1629	HP210	U12/U14
5FP7	6K6GT	7N7	36	725A	1633	HP410I	U18
5R4GY	6K7	7Q7	37	726A	1642	HR210	U19
5U4G	6K7G	7R7	38	747	1960	KT24	U23
5V4G	6KB	7S7	39/44	800	2051	KT44	VCU "C"
5X4G	6K8GT	7Y4	40	801	4033A	KT61	VP23
5Y3G	6L5G	8D3	41	801A	4074B	KT66	VR53
5Y3GT	6L6G	9D2	41MXP	802	5763	KTW61	VR90
5Y4G	6L7	10	42	803	7193	KTW62	VR105/30
5Z3	6L7G	10Y	43	805	7475	KTW63	VR150/30
5Z4	6N7	12A6	45	807	8011	KTZ63	VT98
5Z4G	6N7G	12A6GT	45SPEL	808	8012	KTZ73	VT224/RW4
5Z4GT	6N7GT	12AH7	46	810	8013A	L2	VT501
6A6	6P7G-2	12AH7GT	50L6GT	813	9001	LD210	VT505
6A7	6Q7G	12AT6	50Y6GT	814	9002	LS5	VU39A
6AB7	6Q7GT	12AX7	54	815	9003	M1254	VU120A
6AC7	6R7	12AU7	57	826	9004	MH4	VU133A
6AG5	6R7G	12BE6	58	828	9005	ML6	VU508
6AG7	6SA7	12C8	72/RX235	830B	9006	MSP4/NR65	X24
6AK6	6SA7GT	12H6	75	832	AR300	MS/PEN	X63
6AL5	6SC7	12J5GT	76	832A	ATP4	NC13	X65
6AM5	6SF5	12K7GT	77	833/833A	AU5 (VU111)	NGT5	X66

HALTRON **HALL ELECTRIC LTD** HALTRON

89, CHARLOTTE ST., LONDON, W.1. Phones: MUSEUM 9661 (5 lines) Cables: HALLECTRIC LONDON

the new

ADC speaker

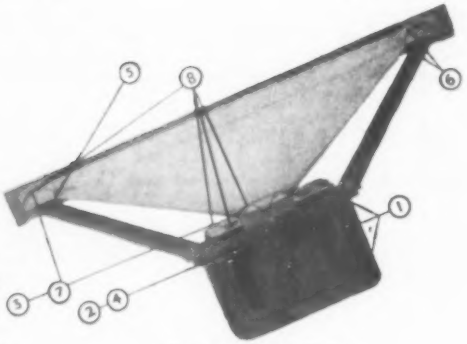

THE A.D.C. SPEAKER DESIGN
Model C

The most revolutionary design in Loudspeakers since the advent of the Moving Coil.

1. Magnet assembly gives 12,000 gauss. 2, 4. Voice coil: both windings operate in undistorted field. 3, 7, 8. The suspension system offers constant frictional resistance to motion. 5. The suspension is such that the terminating periphery of the actual Cone is not a free edge. 6. The Cone and supporting member do not constitute a change of medium at their junctions.

From above follows

A. NO MECHANICAL RESTORING FORCE.
B. THE SYSTEM IS FREE FROM FUNDAMENTAL RESONANT FREQUENCY.
C. THE MOTIONAL DECAY TIME OF THE CONE ASSEMBLY HAS SQUARE WAVE FORM.
D. TRANSIENTS ARE THUS FREE FROM FUNDAMENTAL RESONANT FREQUENCY MODULATION.

A BRITISH INVENTION

PERFECT & NATURAL REPRODUCTION

Technical Details

Resonant Frequency—Nil. Smooth sinusoidal base wave form. No phase change or voltage generated in voice coil. **Decay Time**—Open voice coil circuit, critical non oscillatory. **Cone Damping**—Resistance at all frequencies. **Cone Movement**—Linear at all frequencies. **Air Loading**—Both sides radiating 30 grams. **Motion Modulation**—Electrical, non-mechanical. **Frequency Response**—30 to 16,000 cycles. **Transient Response**—Transients are free of basic resonance and reverse modulation throughout the frequency scale. **High Frequency**—Low ambient noise level, wide angle 70° of axis at 10,000 cycles. **Reproduction**—The tone is without colouration and hardness, therefore the colour-tone of any musical instrument is not altered by the addition of colour-tone from the Speaker.

Write for Illustrated Brochure.

Manufactured by:—

AUDIO-ACOUSTIC DIFFUSEURS LTD.
BROOK HOUSE, PARK LANE, LONDON, W.1
Factory: Tarrant Street, Arundel

The World's first Reproducer of Audio Sound.

The new HYDE
foot operated
WIRE STRIPPER

These two machines will, between them, strip with speed and accuracy practically all types of Insulated Wires and Cables from Small Wires and Flexes up to Cables of 1" diameter. HYDE Stripping Machines are cutting the costs and speeding the production of many world famous manufacturers.
SEND SAMPLES OF WIRES AND CABLES USED, FOR FULL REPORT.

. . . and the
BENCH MODEL

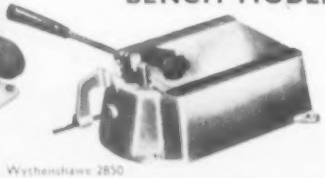

Telephone: Wythenshawe 2850
J. B. HYDE & CO. LTD., Wythenshawe Manchester

S. G. Brown

"F" TYPE HEADPHONES

for LONG LIFE and TROUBLE-FREE SERVICE

This is a featherweight model of exceptionally strong construction and high sensitivity. It appeals equally to both amateur and professional radio engineers. It incorporates powerful cobalt steel magnets with flat Stalloy diaphragms.

D.C. Resistance: 4,000 ohms.
Impedance: 14,000 ohms at 1,000 c/s.

For full details of other models in the wide S. G. Brown range please write for Illustrated Brochure "W."

S. G. Brown Ltd.
SHAKESPEARE ST., WATFORD, HERTS.
Telephone: Watford 7241

THE REPUTATION enjoyed by Marconi Instruments for precision engineering and skilful design is jealously guarded. At all stages of manufacture, and especially in the final testing, the greatest attention is paid to detail. In the future, as in the past, the Company will maintain its policy of producing an unrivalled range of equipment "that is just that little bit better," serving communications and industry, medicine and research, in the precise Marconi manner.

MARCONI instruments

MARCONI INSTRUMENTS LTD · ST. ALBANS · HERTS · Phone: St. Albans 6161/7

Midland Office: 19 The Parade, Leamington Spa. Northern Office: 30 Albion Street, Hull. Export Office: Marconi House, Strand, London, W.C.2.

PULLIN

MULTI-RANGE TEST SET

SERIES 100

The universal testing set for Service Engineers. **Sensitivity — 10,000 ohms per volt.** Strong metal case with carrying handle—complete with leads having detachable bulldog clips and test prods.

RANGES

AC DC Volts ; 10, 25, 100, 250, 500, 1,000.
D.C. Milliamps ; 2.5 10, 25, 100, 500.
AC DC Microamps ; 100 Microamps 10v. range.
Resistance ranges ; 0/1 Meg. (13,000 ohms mid-scale).
0 10,000 ohms 135 ohms mid-scale.

MIP

Measuring Instruments (Pullin) Ltd., Electrin Works, Winchester Street, London, W.3. Phone: ACORN 4651-3 & 4995

A problem of switches
or
a "switch" of a problem !

We can assemble to YOUR specification practically any Oak or A.B. metal switch from parts actually in stock.

Waiting time cut right down !
Keep those production lines running

TELE-RADIO (1943) LTD.
177, EDGWARE ROAD, LONDON, W.2
Phone : PAD. 5626
PAD. 6116
Shop Hours :
Mon.-Sat. 9 a.m.—6 p.m.
Thursday 9 a.m.—1 p.m.

MODERN ELECTRICS LTD.,
164, Charing Cross Road,
London, W.C.2 'phone TEMple Bar 7587
Immediate delivery from stock
Export enquiries welcomed. *Prompt attention to post orders.*

TAPE RECORDERS

SOUNDMIRROR
Table Model..... £69 10 0
Portable Model..... £79 10 0

SIMPHONIC
IA (now booking early delivery)..... £76 0 0

SCOPHONY-BAIRD
Mk. I..... £58 5 6
Mk. II (new model) £68 5 0
"Magnetic Recording" by S. J. Begun. Post free £1 6 0

PICK-UPS AND MOTORS

ACOS G.P.20..... £3 11 5
L.P. and Std. Heads £2 3 4

DECCA Pick-up, Std. £3 15 4
XL. Pick-up, T/O. Head for L.P. and Std. £3 19 2
Mag. XMS. for L.P. and Std. Hds..... £7 0 0

DECCA MOTORS,
33⅓ and 78 spds.... £3 14 4
33⅓, 45 and 78..... £7 3 4

PLESSEY 3-speed Auto-changer unit £23 13 0

RECORDING TAPE

Soundmirror £1 5 0
E.M.I. (Hi-Co)..... £1 15 0
(Med-Co) £1 15 0
Type 57....3250ft..... £6 0 0
600ft. Sin. spool... £1 1 0
Durex (Scotch Boy)... £1 15 0
Philitape £2 0 0
Empty Spools. 4 0 & 6 6

TEST GEAR

AVO
Models 7 and 8..... £19 10 0
D.C. Minor..... £5 5 0
Uniminor £10 10 0
Univ. Bridge £26 0 0
Wide Band Signal Generator £30 0 0
Valve Tester £50 0 0
Electronic Testmeter £40 0 0

PIFCO Radiometer £1 7 6

TAYLOR
ALL THE NEW TAYLOR TEST-GEAR IN STOCK AND AVAILABLE ON H.P. TERMS.
Send S.A.E. for catalogue and terms.

GOVERNMENT SURPLUS

LONDON CENTRAL RADIO STORES

DELIVERY FROM STOCK

PHOTO-ELECTRIC CELLS

Type G816. These cells are the gas-filled type with caesium Cathode. Made by Cintel. Minimum sensitivity 100μA/lumen working volts 100 D.C. or peak A.C. Projected cathode area 16 sq. cm. Suitable for 16 mm. Home Cinema Talkie equipment, Safety Devices, Colour and Photo. Matching, Burglar Alarms, Automatic Counting, Door Opening, etc. Brand new in original cartons. **42/6**

NEW NIFE ACCUMULATORS. 2.5 v. 2½ amp./hours for 8 hours. Size 3×4½×1¾in. (Flat) **6/6.** Post and packing 9d.

SELENIUM FULL-WAVE RECTIFIER. 50 v. 20 amp. Size 11×6×6in. Weight approx. 12 lb. **60/-**

PHOTO-ELECTRIC CELLS

Type CV143

Small infra-red image glass converter, tube 50-100 v. Suitable for all purposes. **14/6**

N.B.—We cannot enter into correspondence regarding these cells.

UNISELECTOR SWITCHES

6-bank, half-wipers, **27/6**

3-bank, full wipers, **19/6.**

Have various applications, including automatic tuning circuit selection, etc. Operates on 25-50 v.

COSSOR DOUBLE-BEAM 'SCOPE

£47.10.0 Carr. Paid.

A Fine Opportunity!

New INERT CELLS

No acid or charging required. Suitable for battery sets, electric bells, etc. 1.5 v., **1/10** each. Post free.

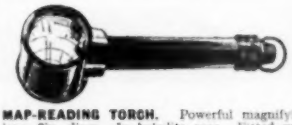

MAP-READING TORCH. Powerful magnifying lens, 3in. diam. In bakelite case. Fitted with dimmer switch. Takes two U cells. With bulb, less batteries. **22/6**

WALKIE-TALKIE Transmitter and Receiver CHASSIS Type 38 Mk. II. Range 7.4-9 Mc/s

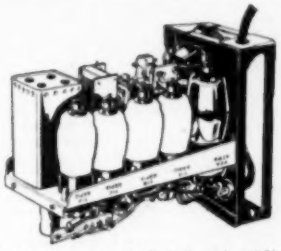

We have just purchased a limited number of Mark II No. 38 Walkie-Talkie sets with one pair of headphones, one pair of throat microphones, an aerial, also junction battery, connection box, all in new condition. **£5.5.0**

ELECTRO-MAGNETIC COUNTERS

FRESH CONSIGNMENT JUST ARRIVED. Ex-G.P.O., every one perfect, electro-magnetic, 500 ohm coil, counting to 9,999, operated from 25 v.–50 v. D.C., many industrial and domestic applications.

ALL EQUAL TO NEW **15/-**

WE URGENTLY REQUIRE FOR CASH
GOOD USED OR NEW EQUIPMENT

MARCONI
De Luxe 8 VALVE

MOTOR TUNING PRESS-BUTTON ALL-WAVE TABLE RADIO SUPERHET

Output 8 watts from 6L6 and High-gain Pick-up input. In use with the latest high-fidelity types. Together with a host of Push-Button Stations this makes a most useful receiver. You can cruise round the dial on the motor tuning. This type of set is not available on the Home market and we are fortunate in being able to offer it to readers.

Complete with makers' Inspection Book. Price

£23.10.0

For callers only.

PHILCO 5-VALVE Reconditioned SETS
— UNIVERSAL MAINS —

These superhet receivers have all been thoroughly overhauled at our works. Ready for immediate use and GUARANTEED. We have sold over 3,000 of these sets all over the country. If in London call and see them for yourself!

184/- ALL-WAVE TABLE MODEL, incorporating two-speed tuning and provision for normal aerial or dipole. Medium or dark walnut cabinet, size 18½×20×9½in. Really excellent performance.

115/- LARGE TABLE MODEL, in light walnut cabinet only, size 19×16×10½in., large dial in metres and frequency. Exceptional high gain using high "Q" IF transformers and special aerial circuit. Normal or dipole aerials may be used.

110/- MEDIUM TABLE MODEL, known as the "Cathedral" Model," receiving all British and European stations with great clarity and freedom from interference. Normal or dipole aerial input. Available in light or dark oak. Cabinet size, 19×14×10in.

Plus **10/6** per set carriage and packing.

VIBRATORS

2-volt, Type R70C. 7-pin self-rectifying. Output 200 v. at 60 m/A. Made by Electronic Laboratories Inc., **7/6.**

Mallory, Type 650, 6-volt 4-pin American base, **7/6.**

Mallory, Type G629C. 12-volt, 4-pin American base, **7/6.**

NEW EX-G.P.O. LOW-VOLTAGE LIGHTING TRANSFORMERS with switch. Power transformer A.C. step down, 200 v. to 250 v. 50 cycles. To 25 v. 25 vA. Size 6½×5×5¼in. Weight 9½lb. Useful for all kinds of other purposes. Price **37/6**

WANTED AR88s · DB 'SCOPES · METERS
ALL KINDS OF TEST GEAR · CONVERTERS, Etc.

SEE ALSO "WIRELESS WORLD," JANUARY ISSUE, CLASSIFIED COLUMNS FOR OTHER GOODS.

Please Note — *All carriage charges relate to Inland Orders only* • *We do not issue lists or catalogues*

LONDON CENTRAL RADIO STORES, 23 LISLE ST. (GERrard 2969) LONDON, W.C.2

Closed Thursday 1 p.m. Open all day Saturday and weekdays 9 a.m. — 6 p.m.

Delay cables

CHARACTERISTICS AND NOMINAL DIMENSIONS

Telcon offers the engineer a series of high impedance delay cables, in which the inner conductor is composed of fine gauge enamelled wire helically wound on an insulating cord. This conductor is provided with a covering of Telcothene* and can be supplied wire-braided and sheathed with Telcovin or finished with a lead sheath, as required.

** Telcothene (Regd.) is polythene processed by Telcon to provide specific characteristics.*

CODE NUMBER	Z.5	Z.3	Z.1	Z.14	Z.6
Approx. overall size, ins.	5/16	5/8	1	1/2	1
Characteristic impedance, ohms.	130	330	550	1000	1900
Capacitance, mmf ft.	55	50	50	80	45
Attenuation, db 100 ft. 1 Mc s.	2.3	1.7	1.4	8	10
10 Mc s.	8	6	5	30	45
100 Mc s.	25	22	23	—	—
Velocity ratio v c	0.14	0.06	0.036	0.014	0.012
Delay microsecs 100 ft.	0.7	1.7	2.8	7.3	8.5

TELCON RF cables

THE TELEGRAPH CONSTRUCTION & MAINTENANCE CO. LTD
Head Office: 22 Old Broad Street, London, E.C.2. *Tel:* LONdon Wall 7104
Enquiries to: Telcon Works, Greenwich, S.E.10. *Tel:* GREenwich 3291

The Finest Needle for your Radiogram

THE GOLDRING ACOUSTIC-FILTERED TYPE S6

- Eliminates Needle Changing
- Gives better reproduction
- Filters out surface noise
- Increases life of records

Goldring Acoustic-filtered Needles suit any Standard Pick-ups.

Look for the Display Card at your Dealers

Goldring Needles cost 10/6, including P. Tax

The Radio Press send you this instruction book to build a Record Player of the highest quality. Price 2/- post free.

ERWIN SCHARF
GOLDRING PRODUCTS
49-51a De Beauvoir Road, London, N.1 Tel.: Clissold 3434/6

The Latest

"CLIFTON" 1952
MAGNETIC TAPE RECORDING MACHINE

Incorporating

- Magic Eye Volume Indicator
- Improved Capstan Drive
- Speeds 15 in.–7½ in.–3¾ in. per sec.
- Playing Time 17–34–68 mins
- Response–50 to 10,000 cycles

PRICE

£55-10-0

EXCLUSIVE OF TAPE OR MICROPHONE

Enquiries: Trade and Retail to:-

Sole Distributors: WILL DAY LTD.
19 LISLE STREET, LONDON, W.C.2
GER. 7105

Manufacturers: BRISTOL MAGNETIC TAPE RECORDERS LTD.
11 ALMA VALE ROAD
BRISTOL 36088

L·R·S

Estd. 1925

For PROMPT and EFFICIENT SERVICE

CASH or EASY TERMS

We have a limited stock of the following quality equipment available for cash or on our Revised Easy Terms.

ARMSTRONG ALL-WAVE CHASSIS

(See Makers Advertisement page 103)

MODEL EXP. 73. Cash £25.12.4 or £6 with order and 11 monthly instalments of 40/-.
MODEL RF. 104. Cash £34.12.10 or £9 with order and 14 monthly instalments of 40/-.
MODEL EXP. 125.3. Cash £53.0.10 or £15 with order and 14 monthly instalments of 60/-.

Passenger carriage 10/- extra payable with deposit.

LOUDSPEAKERS

GOODMAN'S AUDIUM 60. Cash £8.12.6 or £2.5/- with order and 7 monthly instalments of 20/-.
AXIOM 150. Cash £10.5.6 or £3 with order and 8 monthly instalments of 20/-.
WHARFEDALE W.12.CS. Cash £9 or £3 with order and 7 monthly instalments of 20/-.
W.15.CS. Cash £15 or £4.5/- with order and 8 monthly instalments of 30/-.
12in. W.B. CONCENTRIC-DUPLEX. Complete with Transformer and Cross-over Network. Cash £18.18/- or £4.15/- with order and 8 monthly instalments of 40/-.
10in. W.B. CONCENTRIC-DUPLEX. Cash £7.15/- or £2.10/- with order and 6 monthly instalments of 20/-

CONNOISSEUR SUPER L/W PICK-UPS

(See Makers Advertisement page 42)

Complete with one Green Spot and one Red Spot interchangeable Heads for Standard and Microgroove recordings. Cash £10.0.8 or £3 with order and 8 monthly instalments of 20/-.

THE AMAZING NEW

REMINGTON

CONTOUR 6 ELECTRIC SHAVER

will give you the finest possible shave, in the easiest way imaginable.

Available on **TEN DAYS FREE TRIAL** on receipt of **25/-** deposit (returnable if not entirely satisfactory) and 8 monthly instalments of 20/-, A.C. D.C., 200 250v.

Cash Price **£8.19.5**

Other voltages available. Write for Free Brochure.

The L.R. SUPPLY COMPANY Ltd.

(LONDON RADIO SUPPLY CO.)

BALCOMBE - - SUSSEX

Telephone : Balcombe 254

Cold Cathode Triode

CC2R

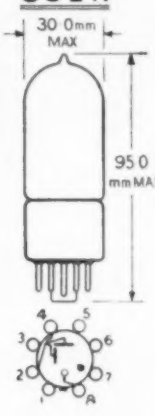

The CC2R is a cold cathode triode on the octal base.

It may be triggered by a power of only a few microwatts and thus provides a means of relay operations from D.C., A.C., or R.F. high impedance sources.

RATINGS

Nominal control gap breakdown	**75 V**
Minimum main gap breakdown	**200 V**
Maximum cathode current (continuous) . .	**10 mA**
Maximum cathode current (Intermittent or pulse)	**30 mA**

HIVAC

THE SCIENTIFIC VALVE

GREENHILL CRESCENT, HARROW-ON-THE-HILL, MIDDLESEX

Telephone : HARrow 2655

They are the most Reliable

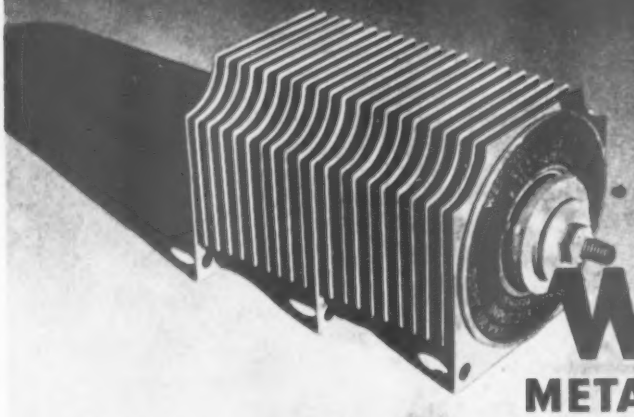

WESTINGHOUSE

WESTALITE METAL RECTIFIERS

WESTINGHOUSE BRAKE & SIGNAL CO., LTD., 82, York Way, King's Cross, London, N.1.

Let the Facts Speak...

Nothing pleases us more than to receive those letters (*) from you stating how satisfied you are with our products! Those extracts from a few of the hundreds received recently convey the facts behind our advertising :—

- "G.B." of Earl Shilton, writes: "*I am very pleased with your 5 valve A.C. superhet just built with your components. It gives beautifully clear reception and I was not expecting as good a performance for my very first attempt at building a wireless set.*"
- "E.W." of Albrighton, writes: "*I have now constructed your 5 valve A.C. receiver and results are excellent. The set worked at full volume without any adjustment whatever. Your Construction Sheets are certainly the goods and your adverts. certainly do tell the truth as the veritable novice could follow them. P.S. Output is really dynamic.*"
- "A.H.G." of Gibraltar, writes: "*Since writing to you last the 6 valve receiver has now been completed and worked from the first switch on and is comparable to A.N.T. commercially built job I have listened to. It is indeed a pleasure to purchase from a firm who turns out its products that do everything that they are claimed to do. More reputable firms like you and "The Old Country" will regain for herself the name that "Made in Britain" used to mean in the days before our struggle. Alas, there are firms who sell "shoddy" goods by high powered sales talk and claims that afterwards leave doubts as to the purchase of anything with that "Made in Britain" legend . . . .*"
- L/Sea. "I.S.H." of H.M. Navy, writes: "*Having recently built one of your superhets I would like to add another testimonial to the quality built of the components and the reproduction of your sets . . the strength of signals is very good indeed—much better than I expected in this area.*"
- "F.W.F." of Southport, writes: "*Your Handbook has proved most useful indeed, but I now require a signal generator, and a ready-made commercial will being beyond my pocket I plan having a go at your design knowing full well from past experience that I can depend upon it.*"

etc., etc., etc.

YOU, too, can get similar results! Whether novice or expert you cannot do better than INVEST 2/6d. in our NEW 1952 issue of the "HOME CONSTRUCTOR'S HANDBOOK" containing TWELVE full page circuits and full details of EASY-TO-BUILD sets and amplifiers. This Book is obtainable by Mail ONLY from

RODING LABORATORIES (Dept. FWW.)
694, LEA BRIDGE ROAD LONDON, E.10

(* The originals of these unsolicited testimonials may be seen at anytime.)

SHORTAGE OF ELECTRONIC TECHNOLOGISTS

The demand of Industry and the Ministries for our trained students is still far greater than we can supply. For top-grade technologists we offer:

THREE-YEAR COURSE IN TELE-COMMUNICATION ENGINEERING
(including one year's Factory attachment)

Next Course commences 23th August

Write for FREE BROCHURES giving details of the above and other day-time attendance courses

E.M.I. INSTITUTES — the only college which is part of a great industry

E.M.I. INSTITUTES
(DEPT 168), 10 PEMBRIDGE SQUARE, LONDON, W.2. Tel.: BAYSWATER 5131/2.

Associated with "H.M.V." MARCONIPHONE COLUMBIA ETC

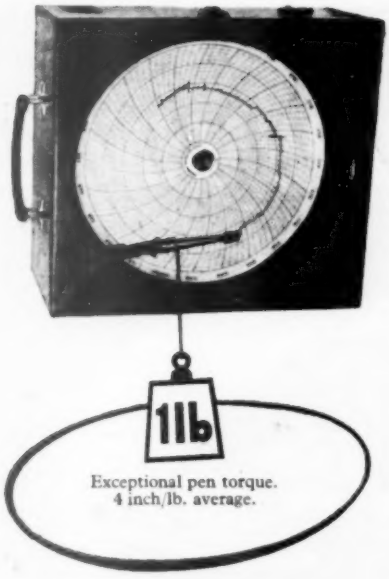

Exceptional pen torque.
4 inch/lb. average.

Fielden SERVOGRAPH

LIGHT CURRENT RECORDER

± 1% accuracy in any position

Pen transit time only 3 seconds

Smallest increments recorded.

The Fielden Servograph is a reasonably priced recording meter of advanced and unique but simple design for industrial and laboratory service. Recording accuracy within plus or minus 1% results from freeing the instrument movement of all recording load. Models for industrial and laboratory use are available to give full scale deflection in ranges of 0 - 50 microamperes and 0 - 15 millivolts upwards.

Fielden INSTRUMENTATION

FIELDEN (ELECTRONICS) LTD., " H " Block, Paston Rd., Wythenshawe, Manchester
FIELDEN ELECTRONICS (Australia) PTY. LTD., 409 Collins Street, Melbourne, Australia

ELAC
MANUFACTURERS OF LOUDSPEAKERS • CHOKES
TRANSFORMERS • TELEVISION FOCUS UNITS • ION TRAPS
ELECTRO ACOUSTIC INDUSTRIES LTD
STAMFORD WORKS BROAD LANE TOTTENHAM N15 TEL: STAmford Hill 5606-8

FOR RECORD PERFORMANCE..

GU4

A beautifully styled three speed gramophone. Complete with ingenious automatic stop and light weight crystal pickup fitted with two permanent sapphire styli.

MU14

A de luxe three speed turntable unit which can be used with the buyer's own choice of crystal or magnetic pickup.

MU10

A high performance two speed turntable unit designed for easy conversion from 78 r.p.m. to 33⅓ r.p.m.

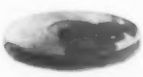

These units set a new high standard of design and quality. They are backed by extensive research and the latest production methods.

BIRMINGHAM SOUND REPRODUCERS LTD

BSR

Old Hill, Staffs. Tel. Cradley Heath 6212/3, Grams: 'Electronic Old Hill, Cradley Heath.'

Wireless World

RADIO, TELEVISION AND ELECTRONICS

41st YEAR OF PUBLICATION

Managing Editor: HUGH S. POCOCK, M.I.E.E.
Editor: H. F. SMITH

FEBRUARY 1952

In This Issue

EDITORIAL COMMENT 41

TELEVISION SET TESTING. By *M. V. Callendar* 42

TELEVISION SOCIETY'S EXHIBITION 45

MECHANISM OF MAGNETIC RECORDING 47

REVIEW OF 460 Mc/s. By *E. G. Hamer* 51

SPEECH REINFORCEMENT IN ST. PAUL'S CATHEDRAL. By *P. H. Parkin and J. H. Taylor* 54

LOUDSPEAKER RESPONSE CURVES 58

LETTERS TO THE EDITOR 59

GENEVA RADIO CONFERENCE 61

WORLD OF WIRELESS 62

EQUALIZATION. By "*Cathode Ray*" 65

IS INFORMATION THEORY OF ANY PRACTICAL USE? 71

STUDYING BRAIN WAVES 72

OXIDE CATHODE LIFE 76

WHY 47? 77

MANUFACTURERS' PRODUCTS 79

RANDOM RADIATIONS. By "*Diallist*" 80

UNBIASED. By "*Free Grid*" 82

PUBLISHED MONTHLY (last Tuesday of preceding month) *at* ILIFFE & SONS LTD., Dorset House, Stamford Street, London, S.E.1. *Telephone:* Waterloo 3333 (60 lines). *Telegrams:* "Ethaworld, Sedist, London." *Annual Subscription:* Home and Overseas, £1 7s. 0d. U.S.A. $4.50 Canada $4.50. BRANCH OFFICES: *Birmingham:* King Edward House, New Street, 2. *Coventry:* 8-10, Corporation Street. *Glasgow:* 26b, Renfield Street, C.2. *Manchester:* 26, Deansgate, 3.

VALVES...and their Applications

INDIRECTLY-HEATED VALVES FOR BROADCAST RECEIVERS

Rectifiers

All the requirements of power rectification in A.C. mains receivers, D.C./A.C. mains receivers and car radio are met by a range of three Mullard rectifiers types EZ40, EZ41 and UY41.

For A.C. mains-operated equipment the EZ40 full-wave rectifier should be used. As in all the rectifiers in this range, the EZ40 has high insulation resistance between heater and cathode. Its heater can therefore be fed, if desired, from the same transformer winding as that supplying the heaters of the other valves in the receiver.

Type EZ41 is also a full-wave rectifier, but has a smaller output rating. It is primarily intended for use in car radio receivers employing non-synchronous vibrator power packs.

The rectifier for D.C./A.C. mains receivers incorporating the 100mA heater range of valves is the half-wave rectifier type UY41.

When using reservoir capacitors of large value it is necessary to limit the surge current through the rectifier by connecting a current-limiting resistance in series with each anode. The minimum permissible values for this resistance for various values of reservoir capacitance are shown in the table on the right.

RECTIFIERS

TYPE EZ40 for A.C. Mains Radio Sets
TYPE EZ41 for Car Radio Sets
TYPE UY41 for D.C./A.C. Mains Radio Sets

		EZ40	EZ41	UY41
Heater				
V_h		6.3	6.3	31 V
I_h		0.6	0.4	0.1 A
Limiting Values				
$V_{a\,(rms)}$	max	2x350	2x250	250 V
I_{out}	max	90	60	100 mA
C	max	50	50	50 μF
$V_{h\,(kpk)}$	max	500	350	550 V
R_{lim}	min	See Table		

Minimum Permissible Values of Limiting Resistance

Rectifier Type	$V_{a\,(rms)}$ (V)	R_{lim} min (per anode) (Ω) for reservoir capacitances of :		
		50μF	32μF	16μF
EZ40	2x350	300	200	100
	2x300	215	140	70
	2x275	175	110	55
	2x250	125	80	40
EZ41	2x250	325	300	250
UY41	250	210	140	100
	220	160	125	90
	127	0	0	0

THE COMPLETE SERIES

	FREQUENCY CHANGER	R.F. or I.F. AMPLIFIER	DET., A.F. AMPLIFR. & A.V.C. DIODE	OUTPUT PENTODES	RECTIFIERS
6.3V Heater	ECH42	EF41	EBC41	EL41; EL42	EZ40; EZ41
0.1 A Heater	UCH42	UF41	UBC41	UL41	UY41

Reprints of this article may be obtained free of charge from the address below.

Mullard MULLARD LTD., Technical Publications Department, Century House, Shaftesbury Avenue, W.C.2

M3VM 889

Wireless World

FEBRUARY 1952 VOL. LVIII. No. 2

Standardizing Television I.F.

THERE is as yet nothing approaching standardization in the frequency of i.f. amplifiers in British television receivers. Some sets work on frequencies that are more susceptible than they need be to interference from the most common sources; to a lesser extent, some of them are apt to radiate oscillator interference affecting other communications. As things are, there is no practicable i.f. value that is completely free of possible interference, but some are far worse than others in this respect.

One of the strongest arguments in favour of adopting a single standardized i.f. band for all domestic television receivers is that the industry would then have a strong case for appealing to the Post Office for "protection" of the chosen band. Indeed, the G.P.O. should obviously come into the picture at an early stage, so that the practicability of giving protection could be discussed before making a final choice.

We believe that a good theoretical case can be made out for setting the i.f. amplifier to cover the band of roughly 34-38 Mc/s, but there still appears to be some lack of agreement as to whether this standard (already adopted in several commercial receivers) will show itself in actual practice to be the best that can be chosen. With well over a million television receivers already in use, we should imagine that the experience on which a quick decision could be made is already available.

Naturally enough, those concerned with all the various branches of radio communication likely to be effected by the choice of i.f. value are anxious that their own particular frequency channels should be taken into account in coming to a decision. So, of course, they should, but it seems to us that the approach to the problem should be at least as much statistical as purely radio-technical.

The transmitting radio amateurs adduce particularly convincing arguments in pleading that television receivers should not embody i.f. amplifiers working within the allotted amateur bands. There are as many amateur stations as all other kinds put together, and many of them are in densely populated areas; most other stations are in open country. Therefore the average viewer stands a greater chance of suffering from an overpoweringly strong "swamp" signal from an amateur station than from any other. The argument appears to be irrefutable. No conscientious amateur transmitter wishes to interfere with the viewer's enjoyment of television, and equally the viewer should be protected from the most probable source of interference. The case for using an intermediate frequency value outside the amateur bands seems to be proved. No i.f. channel can be found that it not already allotted to some other service, but we feel sure the problem can be solved in a spirit of sweet reasonableness on a strictly rational basis.

The Geneva Conference

WE wish that international radio problems could be settled in the same spirit as the simple little internal matter discussed in the preceding paragraphs. When *Wireless World* celebrated its 40th anniversary last year, we promised our readers that the attainment of that age would not be taken as a licence to adopt those attitudes generally associated with middle age. Sighing for the past is traditionally an attribute of the over-forties, but, at the risk of being accused of breaking a promise, we cannot help hankering after the good old days of 1938, when, at the Cairo Convention, frequency allocation problems were amicably settled between the nations on a rational basis by men having predominantly technical interests. Nowadays the scene at such conferences seems to be dominated by what a forthright American contemporary described as "high-power political characters."

However, despite the apparently inevitable East-West cleavage, a considerable measure of success was attained at the recent Geneva conference (reported elsewhere in this issue).

It would appear that saturation point has been reached in many of the bands, and the only possible means of easing the situation seems to lie in the improvement of transmitting techniques. The agreement—signed by sixty-five of the seventy-four participating countries—lays great stress on the need for mutual goodwill and co-operation. Metaphorical iron curtains are not barriers to radio waves.

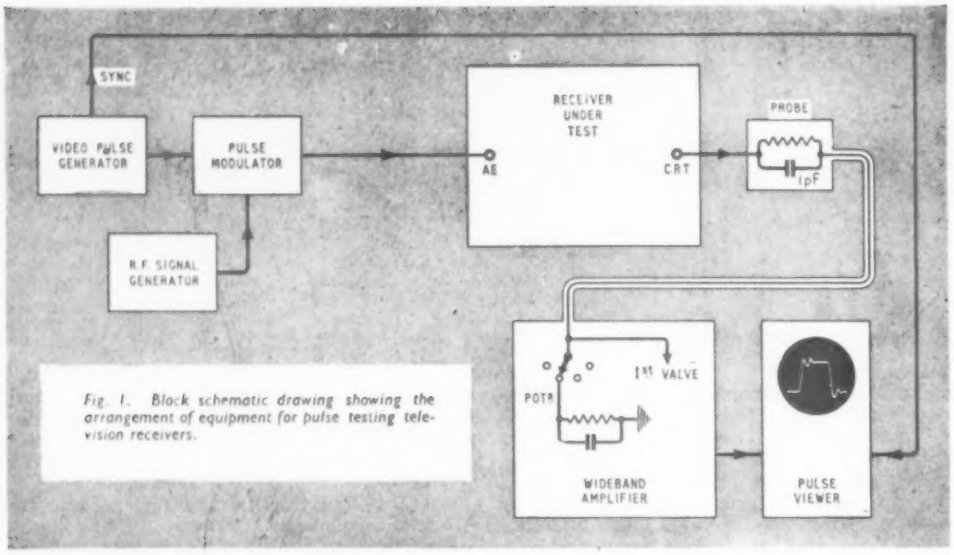

Fig. 1. Block schematic drawing showing the arrangement of equipment for pulse testing television receivers.

TELEVISION SET TESTING

Advantages of Pulse Technique : Type of Equipment Required

By M. V. CALLENDAR,* M.A., A.M.I.E.E.

IT has been normal practice, at any rate until recently, to test television receivers and other television apparatus by continuous wave methods. Thus the usual tests applied to a broadcast television receiver have been: (1) selectivity curve for r.f. and i.f. stages, (2) video frequency characteristic of video stage. These measurements are, of course, supplemented by qualitative observations on the B.B.C. test card C, noting especially the degree of clarity of the 2.5-Mc/s bars, and by looking at picture transmissions. Unfortunately, the transmitted picture quality is still too variable to make this a satisfactory test unless repeated on a number of programmes, and there is even some variation in quality with the test card. To ensure a uniform and continuous transmission, most receiver manufacturers have installed a test pattern transmitter of their own, but it is by no means easy to make this really distortionless.

In some cases, the following additional test has been used: (3) characteristic for modulation frequency versus video voltage at the c.r. tube, obtained by injecting a carrier modulated at video frequency into the aerial terminals.

The use of this test has been restricted by the fact that a special wide-band modulator unit has to be made, the modulation arrangements of a normal signal generator not being suitable. The characteristic for phase-delay against frequency is as important as the amplitude characteristic in determining the response to the impulsive signals of which a television transmission is composed; unfortunately, this characteristic is very difficult to measure and, in consequence, has never been seriously considered as a normal test.

Even supposing that all the above c.w. tests (including that for phase delay) were made, how much further are we with regard to knowing the performance of the set on impulsive signals? In theory, the performance of any network on pulses is completely determined if the amplitude and phase characteristics are known and for many circuits (minimum phase shift type) a knowledge of the amplitude characteristic alone is theoretically sufficient. Unfortunately, the calculation of the pulse response from the c.w. characteristic of a receiver always requires an impracticable amount of labour, and is virtually impossible in many cases.† The best that can be done is to make a rough empirical estimate, based upon experience of previous results of pulse tests upon apparatus of similar c.w. characteristics; this may be supplemented by a knowledge of the calculated pulse response of the simpler individual circuits for which such calculations have been made.

If we compare measured pulse responses of a number of receivers with the corresponding frequency

* E. K. Cole, Ltd.

† W. M. Lloyd, in a valuable paper "Single Sideband Receiver Design" (*Journ. Television Soc.*, Nov., 1950), succeeds in calculating the response for a simple r.f. amplifier, but is compelled to employ drastic approximations in most cases.

characteristics, the fact that stands out is that a comparatively large overshoot, or other form of pulse distortion, may correspond to an almost unnoticeable peak (or other deviation) in the frequency characteristic; for this reason estimates of pulse response from frequency response are never wholly reliable.

Why not, then, use a standard pulse input as the normal method of test, using c.w. methods only in certain cases (e.g., initial alignment of r.f. and oscillator circuits) where they are convenient?

This brings us at once up against the fact that there are no agreed standards, and no really suitable test apparatus readily available; the technique, in fact, of pulse testing is not yet fully developed, and this article is intended to be a contribution to that end.

Since any waveform can be built up from a series of steps, it is clear that a generator producing a step or unit function voltage must form the basis of any such test. We must also have a pulse modulator for tests with r.f. or i.f. units, and a specialised c.r. oscilloscope (termed a "pulse viewer") with a wide-band amplifier to examine the output from the receiver. The best form for the step or pulse, and the most convenient design for the whole equipment, can, however, only be ascertained after considerable practical experience of this type of test. The following considerations have largely determined the design:—

(a) While it is possible to use pulse methods to test the low frequency response of the receiver, this would complicate the equipment; a low frequency check is not usually necessary on conventional receivers, and where necessary (e.g., on multi-stage video amplifiers), it can be made more easily by c.w. methods.

(b) Practical equipment does not necessarily respond in the same way to positive and negative going steps, and both responses are conveniently seen if a short pulse is used for testing; for similar reasons, it is necessary to have both negative going and positive going pulses available. The pulse length should not be less than about 4 μsec, to ensure that the disturbance caused by the start of the pulse does not affect the end; it is useful also to have pulses of 10 μsec and 15 μsec lengths available as well, as respresenting the blanking interval used on the 625 (or 525)-line and the 405-line systems respectively.

(c) To cover all types of television apparatus, a rise time (10 per cent to 90 per cent) of less than 0.02 μsec for the whole test apparatus chain would be the ideal. Practical difficulties multiply rapidly, however, if it is attempted to reduce the rise time for the complete chain of test equipment below 0.05 μsec, since the rise times of amplifiers in cascade may be added quadratically, this allows of testing equipment with rise times of down to 0.07 μsec and is thus just adequate to cover television receivers including the 625-line system (nominal bandwidth 5 Mc/s). Any over or undershoot arising in the test equipment must be kept extremely small (say less than 2 per cent).

(d) The pulse viewer must be equipped with one time scale suitable for viewing the pulse as a whole, and another (say, 2 μsec for the whole scan) for measuring rise times. The time base must be of the triggered type, and a synchronizing pulse with a lead of about 0.25 μsec must be available from the generator to enable the front of the pulse to be observed in cases where the delay in the apparatus under test is small. The front or back of the pulse must be made visible at will on the 2-μsec range by a switch to shift the start of the scan.

(e) The input impedance to the amplifier must be very high (e.g., capacity not more than 3 pF) to avoid disturbance to the conditions at the point of test.

Description of the Apparatus:—The illustration shows three rack-mounted pulse tests units designed for use on the above lines for mass-production testing, and the block diagram, Fig. 1, indicates the usual test set-up for a broadcast television receiver.

The pulse generator employs a multi-vibrator whose frequency is adjustable from about 10 kc/s to 30 kc/s, including a third valve (cathode follower) to ensure quick charging of the timing capacitor. The multi-vibrator feeds a delay line giving the required lag or lead for the sync pulse, which is extracted via a two-stage shaping amplifier. The video output pulse is shaped by a shree-stage corrected amplifier, with output attenuator which can be connected in the anode (for negative pulse) or the cathode (for positive pulse) of the third valve. The pulse modulator is included in the generator and employs two valves in order to balance out the video pulse; even so, a fairly high level of r.f. input to the modulator (at least 0.1 V) is required to make negligible the excitation of the receiver by the residual video voltage existing at the modulator output.

The wide-band amplifier uses 6 stages, with inductive correction. A sufficiently low capacitance input can only be obtained by using a probe which

Test rack on line production of television receivers. A chassis is on test, and the actual output pulse is seen on the tube, with the 10 μsec scan in use

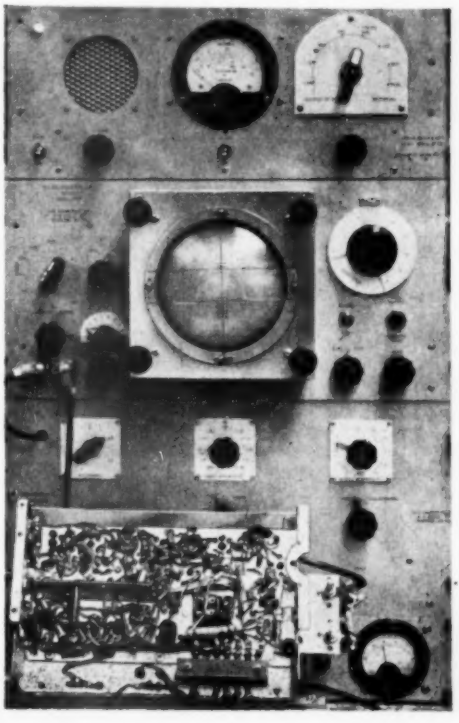

forms part of a capacitance corrected potentiometer; to counteract the loss (about 30 db) in the potentiometer, a rather high gain (total of 60 db) is required from the amplifier. The normal range of pulse amplitudes from about 1 to 100 V is covered with the 2.5-pF probe, and smaller pulses can be examined by an alternative probe provided that a proportionally higher capacitance input can be tolerated. The output stage presents the chief design difficulty; to obtain the required output (up to 50 V) at the bandwidth (8 Mc/s) it is necessary that the pulse be always positive going at the output valve grid (hence switch shown for positive or negative input) and that the valve used should have a high anode current at $V_g = 0$. A wide-band r.f. rectifier circuit is included to enable modulators or transmitters to be tested.

The pulse viewer uses the well-known VCR97 tube, with a simple time base of the type where a capacitor is charged through a resistance from a voltage high enough (relative to the actual scan voltage required) to give a sufficiently linear time scale. An X shift control, with large-diameter scale, enables a time calibration with units of 0.01 μsec to be obtained on the 2-μsec scale, and this can be checked at any time against the built-in marker oscillator operating at 5 Mc/s. Pulse amplitude is readily measurable by a meter on the Y shift. A transparent card, with horizontal lines at 0, 0.1, 0.9 and 1.0 in, is clipped against the face of the tube when measuring rise (10 per cent to 90 per cent) times. A similar card, made matt to take soft pencil marking, is used to delineate the shape of pulses manually without the expense and delay of photographic methods, and as many paper prints as desired can be taken from the transparent card on an ordinary blue print or similar machine.

It should be noted that a qualitative check on the distortion is obtained by viewing the pulse on the actual picture tube.

Results Obtained With Receivers :—Oscillogram (a) in Fig. 2 represents the test pulse, and the words "overshoot," "undershoot," "preshoot" and "step" appended to the other oscillograms represent a suggested nomenclature for the various common forms of distortion of the pulse.

When commercial receivers were first tried out on apparatus of this type the results were somewhat horrifying. Thus oscillogram (b) was obtained from a receiver giving pictures well up to commercial standards, with a noticeable, but not usually very objectionable, overshoot, showing as a white line bordering the right side of black objects (or black line for white objects). On the other hand, oscillogram (c) was obtainable from a receiver which exhibited a rather appreciable lack of definition on some pictures. This oscillogram also shows a spike, best called a "preshoot," which appears before the main transition and shows up on the picture as a line bordering the left side of objects. This often occurs in single sideband receivers and is due to phase shift at frequencies near the carrier.

A "tailing" or "smearing" effect, most often observed on captions, corresponds to an oscillogram of the type shown at (d). If a very long "tail" is seen in the course of a broadcast programme, however, it is fairly safe to attribute it to the transmitter.

It is thus clear that, while a perfect oscillogram will give a perfect picture, some experience is required to assess the degree of deterioration of picture quality corresponding to a given oscillogram. The following limits are put forward as corresponding to a just negligible deterioration in quality on a *good* 405-line transmission.

(i) Short overshoots (less than, say, 0.3μsec duration) and very short undershoots (less than 0.2 μsec) to be less than 6 per cent.

(ii) Longer overshoots and undershoots, including "steps" and "tails," and second overshoots to be less than 3 per cent.

(iii) Rise and fall (10 per cent to 90 per cent) times not to be worse than 0.16μ sec.

A good commercial definition would still be obtained if the percentages given were doubled and the rise time increased by 50 per cent.

It is found in practice that, owing to the fact that a band-pass having a sharp cut-off (say, at 2.5 Mc/s) produces a strong oscillation when pulse excited, a compromise is necessary between the requirements of a short rise time and a low degree of oscillation. The best rise time is obtained when a relatively square-topped band-pass is used, with the response at r.f. carrier frequency 6 db down on that peak, while for minimum overshoot and preshoot, a rounded curve, with carrier about 3 db down only, is best. In the latter case some cathode compensation in the video stage must be added to avoid "tailing."

A further difficulty is that the best compromise varies with the quality of the transmission, the type

Fig. 2. Pulse waveforms (a) before transmission through a television receiver and (b), (c) and (d) after transmission as explained in the text.

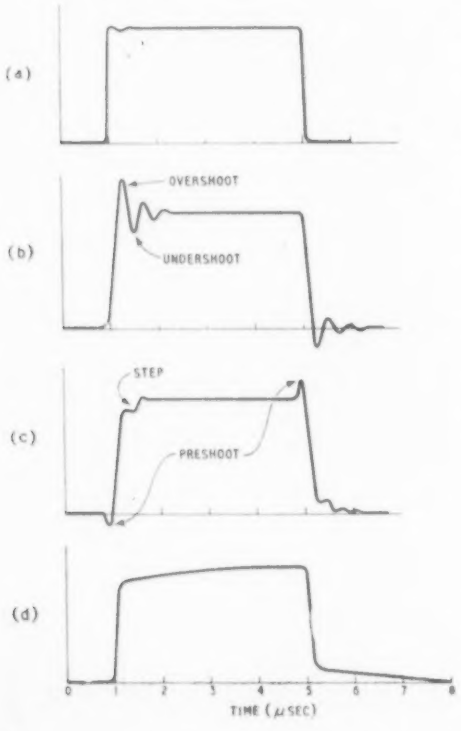

of subject viewed, and with the viewer ; some viewers have been known who felt that a large overshoot gave a three-dimensional quality to the picture. On quite a large percentage of the programmes transmitted, a rise time as bad as 0.4 μsec or a *short* overshoot of 20 per cent (as measured on the fast pulse test) would not be noticeable and on some few transmissions a boosted top response, which would show up as an overshoot on these tests, would actually be desirable.

For viewers in remote areas (vision peak white field strength 100 μV/m or less) a reduced high frequency response is desirable for improving the subjective signal-to-noise ratio. Thus there is as good a case for a picture quality control as there is for the usual tone control fitted to sound receivers.

In spite of the uncertainties outlined in the foregoing description, experience over the last two years has proved the pulse test equipment to be quite indispensable for laboratory design work.

As regards production of broadcast receivers, the greatest weakness in the past has been a relatively large variation in actual performance between individual sets even when trimmed to the closest practicable limits on the usual r.f. curve tracer gear. These variations were sometimes detected on the final test of the receiver on a pattern or B.B.C transmission, but such a test is of a purely qualitative nature, depending critically upon transmission, setting of controls, and observer, and it was not practicable to reject sets on the strength of it unless the lack of fidelity was quite severe. The introduction of a pulse test on all sets has given an unambiguous and quantitative check ; moreover, the test permits of a final adjustment to the video compensation to correct for normal variations in circuit constants (e.g., in stray capacitance at the video output) and in trimming, with the result that the uniformity of the final product is notably improved.

Television Society's Exhibition

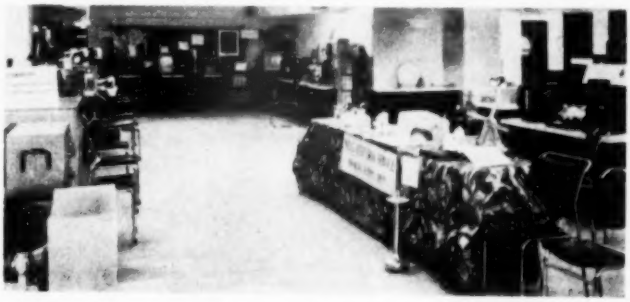

AN exhibition of television and related apparatus was held by the Television Society on 28th and 29th December, 1951 at Century House, Shaftesbury Avenue, London, W.C.2, at which there were some twenty-five exhibitors. The exhibitors were mainly Patron Members of the Society and Members.

The B.B.C. showed a working camera chain in which the camera was trained on visitors and the resulting picture was so placed that the subject could see himself. Pye Radio had a television camera, and some of its associated apparatus, in which remote-control facilities are provided.

On the receiving side, Mullard exhibited a projection receiver with a 25-in picture in addition to 16-in and 14-in direct-viewing sets. They were shown in operation with a test pattern and as an interesting comparison there was a 16-in receiver for 625 lines. Philips also had a projection console model and in a separate room Decca demonstrated front-projection equipment with a picture size of 30 in by 40 in.

A 16-in metal-tube receiver chassis in which the tube is held by a moulded polythene ring for insulation was shown by Ferguson. This set, Model 989T, has a single-valve line-scan circuit, which also provides 14 kV for e.h.t., in which adjustable core saturation is used as a linearity control. The receiver is a superheterodyne tunable over the band 40-70 Mc/s; there is an aerial rejector circuit at 70-100 Mc/s to reduce second-channel interference.

Some interesting test equipment was on view. The most ambitious was undoubtedly the four-rack pattern generator of Bush Radio. Built for factory-production testing, it provides the proper sync waveforms and a

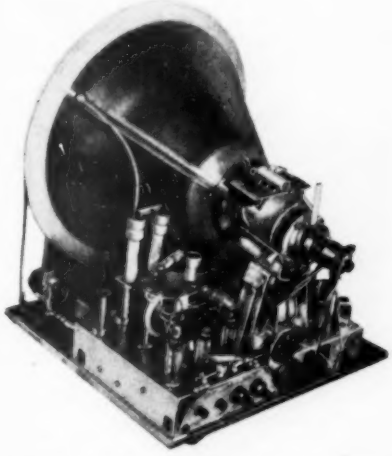

Ferguson Model 989T television receiver with 16-in metal tube.

complex pattern as modulation on all five of the television channels. The pattern includes a pulse which occurs on alternate frames and serves as an interlace indicator.

The Samwell & Hutton wobbulator Type 41 covers all the B.B.C. frequencies and 8-18 Mc/s for i.f. alignment and provides a sweep of 10 Mc/s. There are 5-Mc/s and 1-Mc/s crystal circuits to provide calibration pips on the trace. Other crystals provide marker pips at the sound-channel frequency for each station. The r.f. output is 1 μV to 100 mV at 75 Ω and the oscilloscope input must be 1 V for a trace of 4 cm.

A miniature waveform monitor, type WM3, by E.M.I., measures only 15 in by 7½ in by 14 in and has a 2½-in tube. The vertical-deflection amplifier has two stages, d.c. coupled. The coarse-gain control changes bandwidth as well as gain in three steps and permits pulse rise-times of 0.3, 0.5 and 2 μsec in the low, medium and high gain positions. Provision is made for the measurement of voltage to an accuracy of $+2\frac{1}{2}\%$ over the range of 2 mV to 500 V.

Waveforms Ltd. showed their well-known portable signal and pattern generator and Livingstone Hogg exhibited the Murphy pattern generator. The effect of spot wobble was the subject of a demonstration by Ediswan, using a 15-in receiver and a test pattern. Cinema-Television had a display of test apparatus which included a square-wave generator, and a constant-impedance low-pass filter, a phase-correction unit and a high-speed oscilloscope. Murphy exhibited, in operation, a line-selector which enables any individual line of a television picture to be selected and displayed on an oscilloscope.

Precision oscilloscope tubes, both single and double beam, with flat screens, were shown by 20th Century Electronics, who also exhibited a range of counter tubes.

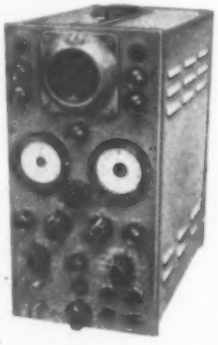

E.M.I. Miniature waveform monitor Type WM3 and (below) Samwell & Hutton television wobbulator Type 41.

Among the private members' exhibits was a new viewing filter shown by C. A. Cove and S. Taylorson of the G.E.C. It comprises a piece of grey fabric with a mesh of 60 threads per inch with a light-transmission efficiency of 60%. It is stretched over the inner face of the clear safety-glass. It is claimed that reflections from the face of the tube are eliminated due to its directional properties.

T. Kilvington, of the Post Office Research Department, showed a timing device for photographing television images. The camera shutter itself gives an exposure of $\frac{1}{4}$th second and operates a mechanism to produce a $\frac{1}{25}$th second brightening pulse which is applied to the c.r. tube. The effective exposure is precisely controlled by this pulse and not by the camera shutter.

An automatic aerial polar-diagram plotter was shown by Belling-Lee; and Acheson Colloids exhibited specimens showing the applications of colloidal graphite which included printed circuits and the screening of television sets by an internal coating to the cabinet.

B.R.E.M.A. demonstrated safety precautions applied to a television receiver in connection with a revision of BS415 (Improvements in Safety of Domestic Receiving Equipment). By pressing buttons it was possible to place defects in various parts of the sets and to demonstrate by lamps the protection afforded by properly placed fuses, cut-out, etc. Tests for the satisfactory isolation of live parts, with a metal finger, a 20-lb straight pull on control knobs, etc., were demonstrated.

RADIO RESEARCH

THE work carried out by the Dept. of Scientific and Industrial Research in 1950, based on the programme of fundamental research drawn up by the Radio Research Board, is summarized in the Report recently issued by D.S.I.R., "Radio Research, 1950."* It opens with a brief review by the chairman of the Board (Sir Stanley Angwin) of the programme of research and of the constitution of the Board. This is followed by a detailed report by the Director of Radio Research (Dr. R. L. Smith-Rose) of the investigations conducted mainly in the Radio Division of the National Physical Laboratory—which includes the Radio Research Station at Slough and its outstations.

Whilst a very large part of the report is concerned with matters relating to the propagation of radio waves —along the ground, through the troposphere, via the ionosphere—and, too, the forecasting of propagation conditions, there are interesting sections dealing with research on materials, valve and circuit noise, atmospheric noise at high frequencies, and decimetre wave-measuring techniques.

The section of the Report dealing with research on materials is concerned largely with semiconductors. It is pointed out that the performance of germanium triodes and diodes, is very dependent upon the concentration and nature of the impurities in the crystal. Arrangements have, therefore, been made with the Chemical Research Laboratory for the investigation of techniques for the analysis and purification of germanium.

* H.M.S.O. price 1s. 9d.

Mechanism of Magnetic Recording

Influence of Asymmetrical Hysteresis on the Recording Characteristics

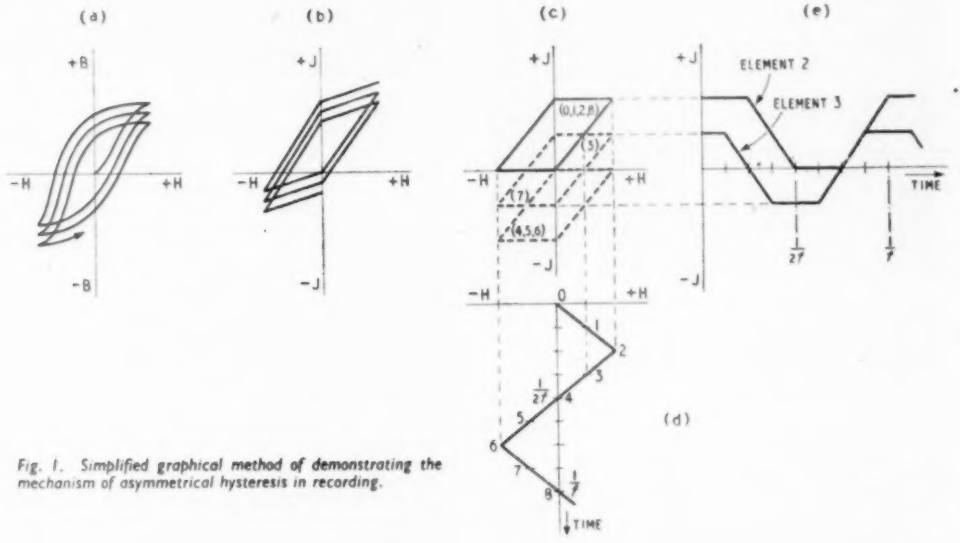

Fig. 1. Simplified graphical method of demonstrating the mechanism of asymmetrical hysteresis in recording.

ALTHOUGH magnetic recording has now established itself as a practicable medium for high-quality sound reproduction, and is widely used in broadcasting and by the record manufacturing companies, no completely satisfactory theory has been advanced to account for all the observed facts.

A recent paper* by P. E. Axon, M.Sc., A.M.I.E.E., of the B.B.C. Research Department, throws new light on the subject and predicts results which are somewhat unexpected. Nevertheless, good correlation between theory and measurement is maintained even when drastic simplifying assumptions are made in order to present the theory in a readily comprehensible form.

The foundation of most attempts which have so far been made to explain magnetic recording has been the stable symmetrical hysteresis loop of the material. Within this framework and with the aid of minor hysteresis loops, recoil paths and the familiar stock in trade of the magnet designer, transfer characteristics have been developed which relate the current in the field coil with the remanent magnetism on the tape. These are satisfactory only to the extent that they show linearization of the characteristic with the addition of high-frequency "bias." A single characteristic of this type implies that, as in the case of a valve characteristic, any distortion remaining should be a function of amplitude and not of frequency. It is known that the *reproducing* gap length affects the response of the system which falls to zero at frequencies where the effective gap length equals an integral number of wavelengths, but it is often stated that the recording gap length is uncritical and that the remanent induction left on the tape is determined only by the magnetic state as each element leaves the gap.

This is only partly true and by using long recording gaps, Axon and his colleagues of the B.B.C. Research Department have proved that, in the absence of h.f. bias, there is not only a cyclic variation of recorded level as the ratio of wavelength to gap length is decreased, but that there is also a cyclic variation of distortion. Briefly, if D is the length of the gap and λ the wavelength at a given frequency and tape speed, it is shown that the magnetic intensity is zero when D = $\frac{1}{2}\lambda$, $1\frac{1}{2}\lambda$, $2\frac{1}{2}\lambda$, etc., and that distortion is zero for D = 0, $\frac{1}{4}\lambda$, etc., and reaches a maximum between D = $\frac{1}{3}\lambda$, and $\frac{2}{3}\lambda$ and between $\frac{5}{6}\lambda$ and $\frac{7}{6}\lambda$.

The simplification which Mr. Axon has made to demonstrate graphically the basis of his theory are given in Fig. 1, which, together with the remaining figures, is based on those given in the I.E.E. paper. Fig. 1(a) shows the character of the asymmetry in the B-H curve of a typical magnetic tape material during the first few cycles after the application of an alternating field in which the first quarter cycle is positive-going. It will be noticed that there is a bias of the "centre of gravity" of the loops towards + B. As a first approximation the loops can be drawn with rectilinear

*Read before the Radio Section of the Institution of Electrical Engineers on December 5th, 1951.

sides, Fig. 1(b), and it is also more appropriate to plot H against J, the magnetic intensity ($B = H + 4\pi J$), since J is more nearly related to the magnetic intensity remaining in the tape after it has left the field. Since the tops and bottoms of the loops approach the horizontal, and since it can be shown that they do not progress far towards the symmetrical condition during the time that any element of the tape is in the gap, a single loop of the form shown full-line in Fig. 1(c) may be substituted. If the first quarter cycle had started from zero and been negative-going the equivalent loop would have appeared below the H axis. The position of the loop will be determined by the first maximum value of the magnetizing field to which any element of the tape is subjected after entering the gap, and bearing this in mind we can trace out the magnetic intensity developed in separate elements of the tape when they enter the gap at various phase intervals of an applied alternating field. It will be convenient to use the triangular waveform of Fig. 1(d) and to consider intervals of $\frac{1}{8}$ cycle. It is assumed that each unmagnetized element will instantly acquire a magnetic intensity proportional to the field prevailing at the time of entry into the gap, and the subsequent waveform of the induction can be traced by following the contour of the appropriate loop.

On this basis the history of two typical elements entering at the instants numbered 2 and 3 in (d) are traced in Fig. 1(e). Element 2 enters at the positive field maximum which it retains during the next quarter cycle, while travelling along the top of the loop from right to left, until it meets the J axis, when it falls to zero, follows the H axis from left to right, then rises again. Element 3 jumps to half positive maximum on entering the gap, but although the field intensity is falling, the induction remains constant, travelling along the top of the middle loop in Fig. 1(c) until it reaches the J axis after $\frac{1}{8}$ cycle and then falling down the left-hand side of the loop to an equal and opposite value before following the bottom of the loop from left to right and then rising up the right-hand side. The numbers inside the loops of Fig. 1(c) indicate the elements with which each is associated.

A complete cycle of intensity curves at $\frac{1}{8}$-cycle increments of time of entry into tha gap is shown in Fig. 2. To find the effect of the recording gap width on the amplitude and waveform of the remanent magnetic intensity on leaving the gap, vertical intercepts are drawn at $\frac{1}{8}\lambda$ intervals, and the values at each intercept are replotted as in Fig. 3.

Inspection shows that output is zero at $D = \frac{3}{4}\lambda$. If one regards zero output as rather bad distortion it is not surprising to find this curve flanked by badly distorted versions of the original triangular wave. A similar if less severe focus of distortion occurs at $D = \frac{1}{4}\lambda$. The original waveform comes through unchanged at $D = \lambda$, $\frac{1}{2}\lambda$, and 0, though the latter is obviously a theoretical abstraction since nothing would in fact be recorded under this condition.

To test the validity of the asymmetrical hysteresis hypothesis the B.B.C. Research Department have carried out accurate measurements of distortion using a fixed recording gap of 350μ length, and a fixed

Fig. 2. Magnetic intensity variation with time of elements entering the gap at phase intervals indicated by the numbers in Fig. 1(d).

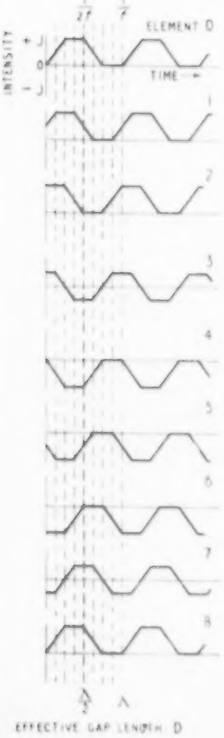

Fig. 3. Waveforms developed by recording gaps of different length, and plotted from amplitudes indicated by vertical intercepts in Fig. 2.

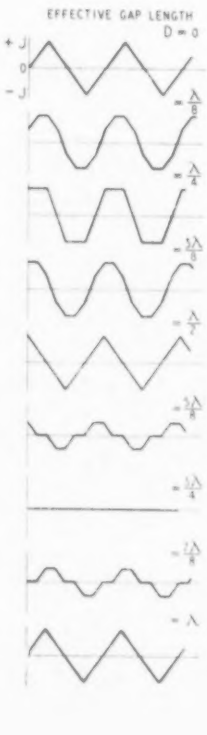

Fig. 4. Experimental verification of dependence of distortion on gap length. As h.f. bias is increased the distortion related to the gap length decreases.

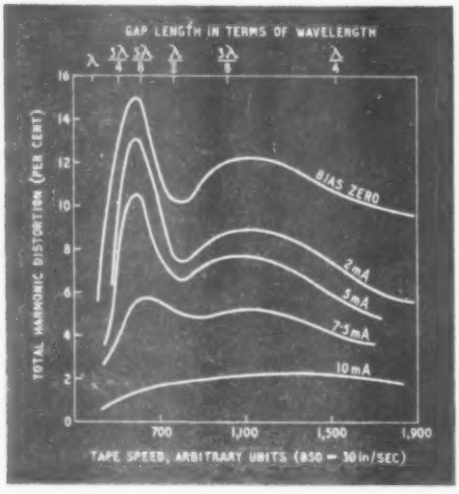

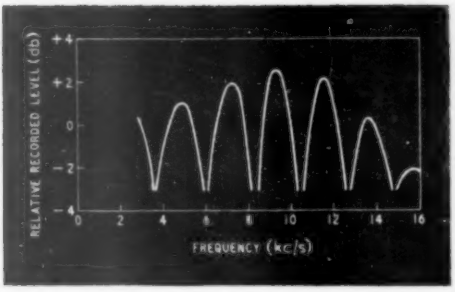

Fig. 5. Overall frequency response with 550-μ recording and 20-μ reproducing head. Tape speed 47.25 in sec. Zero bias.

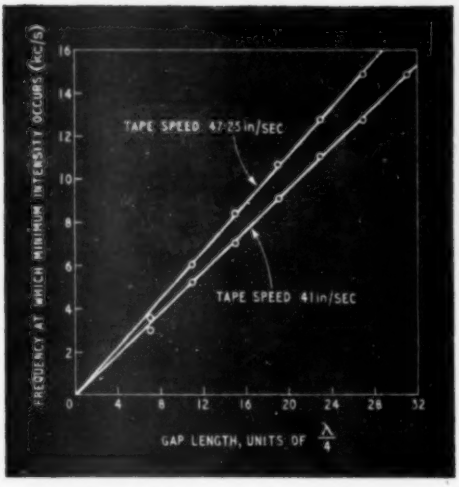

Fig. 6. Relationship between gap length and frequency at which minima occur.

Fig. 7. Elementary graphical presentation of recording with h.f. bias by the same method as Fig. 1 and 2. Signal amplitude 10 units, bias amplitude 15 units. Frequency ratio 1 : 10.

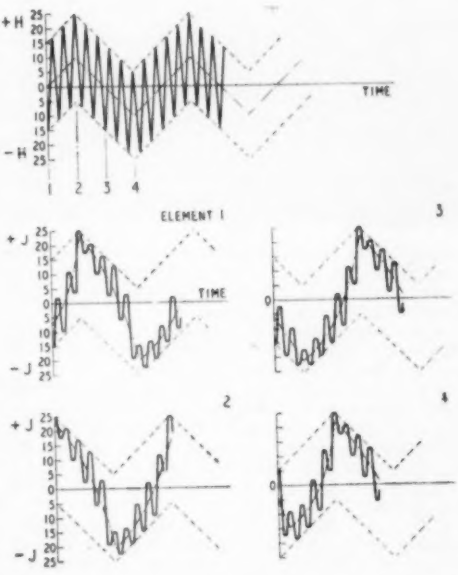

frequency of 1 kc/s to enable a single high-pass filter to be used to separate the distortion products. The ratio of gap length to wavelength was varied by altering the tape speed.

The results of these measurements are shown in Fig. 4 and the predicted minima of distortion at $D = \lambda$ and $\frac{1}{2}\lambda$ are clearly evident; maxima appear between $D = \frac{1}{2}\lambda$ and $\frac{3}{4}\lambda$ and $D = \frac{3}{4}\lambda$ and $\frac{1}{4}\lambda$.

The effect of recording gap length on the recorded level was investigated by using a fixed gap of 550μ (physical) and constant tape speed (47.15 in/sec). The ratio D/λ was varied by changing the recorded frequency and the results are shown in Figs. 5 and 6. The latter represents a plot of frequency against gap length on the assumption that minima occur at $D = \frac{1}{2}\lambda$, $7/4\lambda$, $11/4\lambda$, etc.; in other words the slope of the lines have a slope of $f/4n + 3$. The points obtained from Fig. 5 and a similar plot at another tape speed show a remarkably good fit. The playback head used in these measurements incidentally, was a normal ring type with a 20-μ gap.

From Fig. 5 it will be seen that minima are still occurring at frequencies above 16 kc/s. At 17 kc/s with a 550-μ gap each element of the tape must experience about 8 complete cycles of magnetization, from which it is reasonable to conclude that symmetry has not been reached even after 8 cycles. Under practical recording conditions with a gap of 40μ, a tape speed of 30in/sec and a bias frequency of as high as 100 kc/s, less than 8 cycles of bias will be impressed on any given element while it is traversing the gap.

It follows that the principle of asymmetrical hysteresis can be applied equally well to the case of recording with high-frequency bias. Fig. 7 shows how a graphical analysis, on the lines of Figs. 1 and 2 may be carried out, though far more graphs than are shown there would be necessary for quantitative calculation. After a few cycles (see for example Element 4 in Fig. 7) the pattern settles down to the same steady state, irrespective of the phase at which the element enters the gap, and, unlike the unbiased curves of Fig. 2, the peak intensities are always symmetrical about the horizontal axis. Consequently with adequate bias there can be no cyclical variation of distortion or output, depending on the ratio of gap length to wavelength; and there will be an increase of output when the a.f. component is extracted from the mean of the h.f. intensity fluctuations. The hysteresis asymmetry of the tape material will be impressed on the h.f. intensity variation of each element, and will not affect the a.f. component in the same manner as in the unbiased condition.

That is not to say that distortion no longer exists. The symmetry is not established until a specific minimum amplitude of bias is exceeded. Further

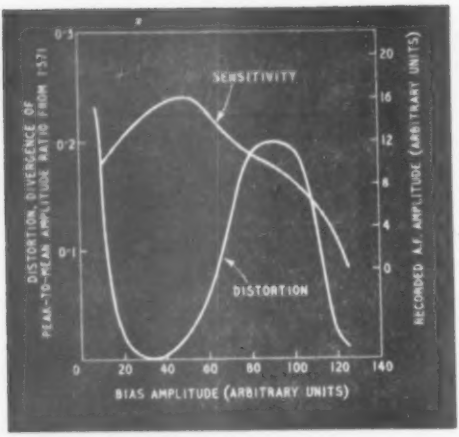

Fig. 8. Calculated variation of sensitivity and distortion with bias amplitude.

Fig. 9. Measured variation of sensitivity and distortion with bias for one particular head and tape speed.

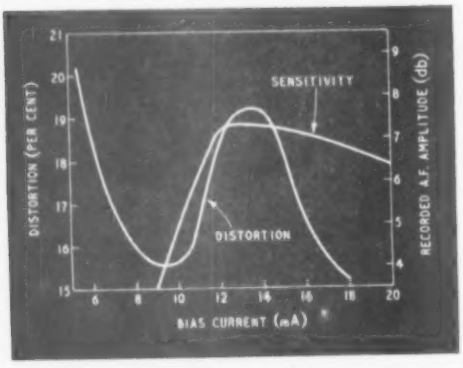

increase of bias amplitude relative to the a.f. amplitude involves the risk of saturation of the tape material on peaks. There is an optimum range of bias values over which distortion is a minimum.

This aspect has been investigated statistically, using calculated peak intensity tables for sinusoidal bias and a.f. components of different amplitudes. The curves of Fig. 8 are based on this analysis and show a strong family likeness to the experimental curves of Fig. 9. The approximate method (peak mean ratio) used in calculating the distortion, losses in the head at the bias frequency and differences in the scales of the curves would account for much of the detailed discrepancy.

The paper deals with many other factors contributing to the recording process, e.g., the relation between the physical and effective length of the recording gap, the influence of the "remanence constant" of the hysteresis loop and of "magnetic viscosity" on the recording characteristics.

As one contributor to the discussion remarked, the original paper is rather like a quarry; it calls for hard work, but has many rich veins.

HOT STYLUS TECHNIQUE

IF a sharp-edged stylus of the type normally used for cutting a wax master is used for direct recording on a cellulose lacquer disc, the background noise is high and for direct recording it is usual to bevel the cutting edges to form what are termed "burnishing facets." Although this reduces surface noise it also results in some loss of high-frequency response.

It is thought that the production of heat at the burnishing facets is an essential factor in the production of a polished groove surface and the reduction of "horns" thrown up at the edges of the groove. The difference in the power required to cut a disc with a modified stylus of this type supports this hypothesis. It is argued that if heat could be applied independently of the cutting process, a sharp-edged cutter, or one with the merest suggestion of a burnishing facet, could be used, and a high-frequency response comparable with wax recording obtained.

There are two schools of thought on how the heat should be applied. C. E. Watts, in this country, favours general heating of the record surface by radiant heat from a suitable lamp, while in America the general practice is to heat the cutting stylus itself by a subsidiary coil wound round the shank.

Some experiences with the latter technique formed the subject of the opening lecture by M. C. Philip at the British Sound Recording Association's "members night" on 21st December last. Mr. Philip showed a series of curves giving the measured relationship between surface noise and recording diameter with and without applied heat. These indicated that whereas the cold stylus gave increasing noise as the groove diameter fell, the noise with hot stylus *decreased*. In the discussion which followed it was suggested that this might be due to increased temperature at the cutter edges as the rate of removal of heat was reduced, but it was agreed that this point could not be settled unless some method could be devised for measuring local temperature at the cutting edge.

It was emphasized by Mr. Philip that the swarf travels further up the back of the cutter with a hot stylus and that reliable swarf control, by pneumatic or rotary collectors, was essential in view of the fire risk. He had found 44 s.w.g. enamelled copper wire suitable and preferable to nickel-chrome for the heater coil, which should be placed fairly high up the shank. Direct-current heating from an accumulator was ideal, but rectified and smoothed a.c. has proved satisfactory.

NEW BOOK

"Microphones."—Although much has been written on the design and use of microphones the material is widely diffused in the literature, and the space devoted to the subject in general textbooks of acoustics is seldom adequate. Not only does this new book collect all the relevant information in one place, but it presents it in lucid and well-ordered manner against a background of simple physical principles.

Written by the staff of the Engineering Training Department of the British Broadcasting Corporation primarily as a manual for B.B.C. engineers, it will prove equally useful to sound recording and public address technicians; in fact, to all with an interest in sound reproduction.

Published for *Wireless World* by arrangement with the B.B.C., this book is obtainable from our Publishers, price 15s 6d (postage 5d). There are 114 pages and 78 illustrations.

ready now!

BRIMAR

The

BRIMAR

radio valve and teletube manual

No. 4

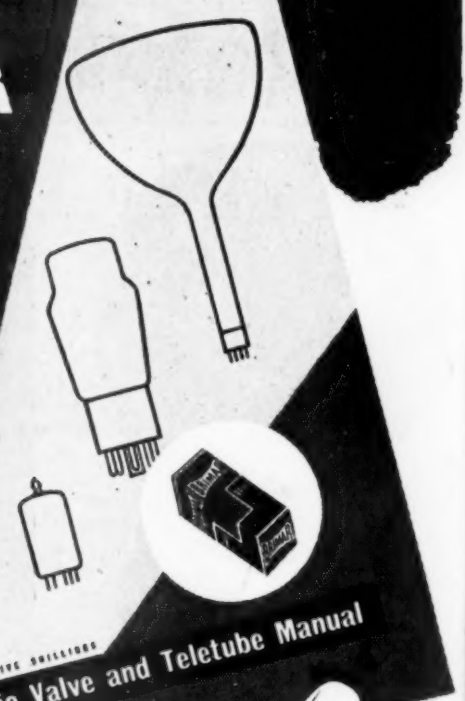

Bigger . . . more comprehensive than ever, this indispensable 224-page Manual has been brought right up to date. In addition to comprehensive data on the whole range of current valve types, including the Trustworthy series, the Manual offers valuable material for Service Engineer and competent amateur.

CONTENTS

- Valve Ratings
- Classified List of Current Equipment Types
- Valve Types (inc. 'Trustworthy' Range)
- Cathode Ray Tubes
- Metal Rectifiers
- Brimistors
- Brimarizing
- Substitution List
- Formulæ
- Output Transformer Ratios
- ABAC
- Conversion Table
- Colour Codes
- Circuits
- Equivalents
- Price List

From your usual Wholesaler

PRICE **5/-**

Standard Telephones and Cables Limited

RADIO RECEIVER VALVE DIVISION

FOOTSCRAY, SIDCUP, KENT FOOtscray 3333

NOW is the time to BRIMARIZE!

acos

high fidelity MICROPHONES

FOR PUBLIC ADDRESS : RECORDING : AMATEUR RADIO

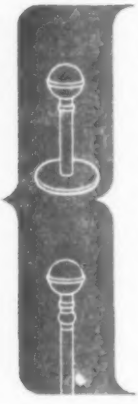

TYPE MIC 22

This model incorporates the famous **Acos** "Filtercel" insert giving extreme sensitivity and high fidelity. Response is substantially flat from 40-6,000 cps. The microphone is vibration and shock proof and is not affected by low frequency wind noises. Two alternative mountings are available for the MIC 22 head :

MIC 22-2 is supplied as a complete unit incorporating an attractive desk stand with cable side entry.

MIC 22-1 is for fitting to any British or American type standard floor stand and can also be used as a hand microphone.

PRICE £6 . 6 (*Either Model*)

TYPE MIC 16

incorporates the **Acos** Floating Crystal Sound Cell giving a response substantially flat from 30-10,000 cps. Performance is unaffected by vibration or shock and low frequency wind noises. As in the case of the MIC 22, two alternative mountings for the MIC 16 head are available :

MIC 16-2 is a complete desk stand unit with side cable entry

MIC 16-1 is ready for fixing to either British or American type floor stands by means of a knurled ring.

PRICE £12 . 12 (*Either Model*)

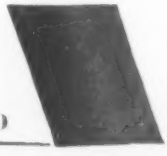

COSMOCORD LIMITED ENFIELD, MIDDX.

P.S. *As you probably know, we make good pick-ups too, in large numbers. But even larger numbers of people want them. Although, therefore we expect to be producing still more and still better pick-ups soon, just now we don't advertise pick-ups at all.*

REVIEW OF 460 MC/S

Can Decimetre Waves Relieve Congestion on the Metre Band?

By E. G. HAMER, B.Sc. (Eng.) (Hons.), A.M.I.E.E.*

THE ever-increasing use of radio for mobile and fixed services has led to serious congestion on the frequency bands at present in widespread use. Therefore, the obvious tendency is for the available channels to be allocated to priority services, less serious users being ultimately forced towards the higher frequencies. But these higher frequencies are still regarded as somewhat unattractive, due to decreased technical performance and higher cost, brought about by the need for special valves and circuits.

This has been true in the past of the "business radio" band (460-470 Mc/s) and other frequencies in the same region, but new technical developments, particularly in valves, make the economics of such frequencies more attractive. As to performance, they can, in fact, closely approach that of the lower frequencies, as a loss in one part of the system can be counterbalanced by a gain in another. The aerial is an important factor in this line of attack; for a given physical size the higher the frequency the better the performance can be made. Smaller aerials also have an attraction where "walkie-talkies" are concerned.

It has been shown that frequencies in the band 460-470 Mc/s can give a very satisfactory mobile service, only slightly inferior to that in the lower bands.[1, 2] One of the main reasons for this is that in mobile systems working at the extreme limit of receiver sensitivity the limiting factor is thermal and man-made noise. It has been proved experimentally that in urban areas the total amount of noise in a given bandwidth decreases as the frequency is increased, and up to about 500 Mc/s the decrease of atmospheric noise more than counterbalances the degradation in performance of the receiver. Above 500 Mc/s the noise factor of the receiver is more rapidly degraded and outweighs any improvement due to the decrease of atmospheric noise.

Taking into account these two factors only leads to the conclusion that the optimum performance of a practical receiver in an urban area will be at a frequency of about 350-450 Mc/s. This, of course, takes no account of the increasing propagation losses at the higher frequencies.

Simple mobile services for "business radio" use would normally be confined to the less serious domestic user. Low transmitter power, simple receivers and free running oscillators would probably be used and it would appear desirable that these types of transmission should be restricted to a band of their own to avoid interfering with priority users. One of the dominating factors in the design of this type of equipment is low cost, and this calls for a relaxation on the usual demands for frequency stability. Such simple equipment can give useful ranges of up to one mile in the open and from 60 to 100 yd when used inside a building, but normally it would not be suitable as part of an existing mobile system.

One of the main deterrents in the past to the design of the transmitting equipment has been the lack of suitable cheap valves. In the past the available valves have been of the disc seal or "lighthouse" type, which are capable of operation at much higher frequencies, and hence are really wasted at these frequencies. These types of valve require elaborate and expensive circuits as they have not normal bases. This position was realized and a disc seal valve assembly mounted in a glass envelope on a B7G base (the Osram type

TABLE 1

Performance of Valves as Oscillators

Valve type	Make	Approx. max. freq.	Approx. power output at 450 Mc/s.
EAC91	Mullard	500 Mc/s	0.1 watt
ECC91 (6J6) ..	Mullard	50 Mc/s	0.3 watt
EC5	Mullard	500 Mc/s	0.15 watt
EC70	Mullard	500 Mc/s	0.25 watt
12AT7		500 Mc/s	0.5 watt
A1714	Osram	1,000 Mc/s	0.6 watt
Det22	Osram	3,000 Mc/s	1–2 watts

The illustration below shows a slab-line oscillator for 460 Mc/s.

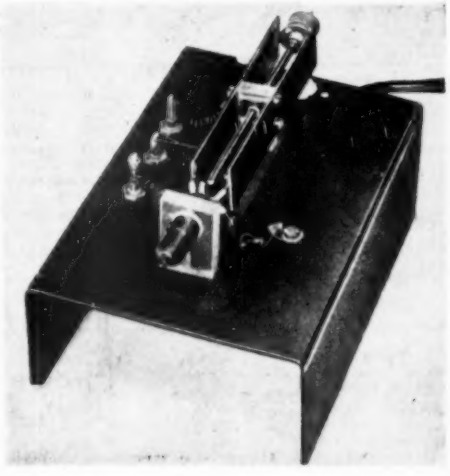

* G.E.C. Research Laboratories, Wembley.

[1, 2] References to be found at end of article.

A1714) was developed and led to a considerable simplification of circuit design.

In recent years further valves capable of operating at 460 Mc/s have been added to the various manufacturers' ranges, and Table 1 lists the approximate measured performance of several different types when used as oscillators. The power output to a large extent depends upon the efficiency of the circuit and how much of the power is directly radiated. It has been found that one of the most efficient simple line circuits is that of the "slab" line; this consists of a central conductor with a flat plate along each side. The photograph shows a half-wave "slab-line" with an EC70 valve on one end and a tuning condenser at the other. Where larger powers are required radio frequency amplifiers may be used, or the last valve may be a multiplier. Disc seal valves connected in earthed grid circuits are often used as amplifiers, and Table 2 gives the performance of some types of valve functioning as amplifiers at 450 Mc/s. Table 3 gives the measured performances of certain valves when used as frequency triplers with an output at 450 Mc/s.

In the design of simple equipment the major difficulty is the reduction of heater power to a minimum; one of the few directly heated valves capable of oscillating at 460 Mc/s is the type 958 acorn. The output in this case is extremely low, and where more power is required a valve such as the EC70 would have to be used although it has a 6.3-volt, 150-mA filament.

Amplitude or frequency modulation may be used with the systems concerned, and in the case of the walkie-talkie Fig. 1 shows the circuit diagram of a simple transmitter using a germanium crystal to produce frequency modulation of the oscillator. The crystal is loop-coupled to the oscillatory circuit and the amount of coupled resistance and reactance is varied by passing the speech currents through the crystal.

For a simple receiver the type 958 valve would make a good detector, or possibly a silicon crystal could be used. Where a more elaborate receiver is envisaged triode valves, such as the 12AT7, Mullard EC91, or Osram A1714, can be used as earthed grid radio-frequency amplifiers and mixers. The measured noise factor of such receivers with a single r.f. stage is 6 to 10 db[1]. An alternative method is to use a silicon crystal mixer followed by a low noise factor i.f. amplifier, and this is capable of giving an overall noise factor better than 10 db. The advantage of r.f. valve amplifiers is that more selectivity may be added without lowering the performance of the receiver. After the mixer circuit the remainder of the equipment could be designed using present techniques, although special designs might be necessary for the wide-band circuits required for multi-channel links. One of the best circuits to use for the early stages of a wide-band low-noise factor i.f. stage is a neutralized earthed cathode circuit followed by an earthed grid circuit, and although the voltage gain will be reduced there is a considerable power gain which makes the noise contribution of following circuits negligible. Table 4 gives the measured overall noise factor at 40 Mc/s of the above-mentioned circuit when using different types of valve.

Many kinds of aerials may be used and at a frequency of 460 Mc/s even the more complex types are attractive by virtue of their small physical size. A corner reflector giving a gain of 10 db would be approximately a 4ft cube, and a helical antenna, or an array of helical antennæ, would be nearly the same volume.[1] For mobile systems an array of vertically stacked dipoles could be used, and two half-wave dipoles with a total stack length of one and a half wavelengths should give a gain of 3 db over a single dipole. Such types of aerial are even feasible for the mobile station as when designed as a whip aerial the total length above the roof of a vehicle need not be more than two feet. The fixed station aerial could, of course, be more elaborate and an omni-directional gain of 6 to 8 db over a simple dipole can be obtained in a reasonable physical size.

At a distance of 30 miles over smooth earth the transmission loss at 460 Mc/s would be some 8 to 10 db greater than at 100 Mc/s, and for fixed-station working this could be overcome by the increased aerial gain possible. For mobile services, where a considerable amount of reflection and refraction is taking place, the level of signal to be anticipated is not so readily calculated. In certain cases measured and calculated values have agreed very well, particularly in urban areas. In towns where the signal strength varies rapidly in a fluctuating manner over a distance of a few feet correlation is more difficult, but practical tests have shown the value of mobile systems operating on 460 Mc/s.[1, 2]

As the nulls of the standing wave patterns at the higher frequencies are much closer than at the lower, careful receiver design is necessary to reduce the effects of "flutter" as the mobile station moves through the resultant radiation field. Even in densely built-up areas communication is possible in streets, etc., considerably out of line-of-sight of the transmitter. In certain cases, however, such as railway tunnels, communication is possible only on the higher frequencies.[2] The mechanism of this is as yet not fully understood, but it is believed to be due to the additional "grazing" losses at the lower frequencies, as satisfactory communication can be established at frequencies even higher than 460 Mc/s.

When investigating the theoretical propagation loss

TABLE 2

Performance of Valves as Amplifiers at 450 Mc/s

Valve type	Make	Approx. power output
Det22	Osram	1–2 watts
Det24	Osram	5 watts
ACT22	Osram	40 watts

TABLE 3

Performance of Valves as Triplers to 450 Mc/s

Valve type	Make	Approx. power output
Det22	Osram	0.5 watt
12AT7		0.25 watt
12AT7 (pair) ..		0.5 watt
QQV06-40	Mullard	5–8 watt

TABLE 4

Valve type	Make	Overall noise factor in db
EC91	Mullard	4.0
12AT7		5.5
ECC91	Mullard	5.5
Z77 (as a triode) ..	Osram	4.0

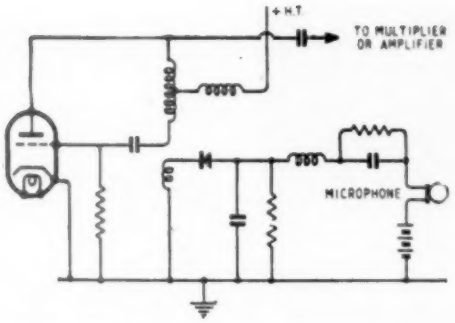

Fig. 1. Circuit diagram of a simple transmitter employing a germanium crystal to produce frequency modulation of the oscillator.

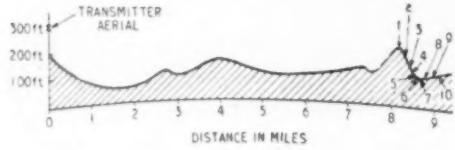

SITE NUMBER	1	2	3	4	5	6	7	8	9	10
THEORETICAL FIELD STRENGTH	3·2	7·2	3·5	3·6	4·1	4·5	4·5	5·2	5·2	5·7
MEASURED FIELD STRENGTH	5·6	12·4	7·2	5·6	7·2	5·6	5·6	7·2	5·6	7·4

Fig. 2. Ground contour to typical sites and comparison of theoretical and measured field strength in μV in half-wave dipole.

the nomograms derived by Bullington have been used,[7] and in many cases have given results very similar to the measured results. Fig. 2 shows a typical contour to a number of sites tested and also the comparison between the measured and theoretical results. The method used was to calculate the free space propagation loss to the site, and then allow for the "grazing" loss due to the first ridge of hills, and the shadow loss relative to free space due to the second ridge of hills. In this instance some 30 measurements were made with the transmitting aerial some 300ft above sea level and over country terrain, with good agreement between theoretical and measured values. Similar tests were made with the identical equipment in a built-up area, with the transmitting aerial approximately 30ft above the level of the roof of the building used and the adjacent buildings. Although consistent results were obtained from some dozen readings, in all cases the measured field strength was some 10 db less than that predicted theoretically, and this is probably due to the fact that the adjacent buildings give additional grazing losses as the height of the aerial is such that first "Fresnel" zone clearance is not obtained for a distance of approximately 0.1 mile from the transmitting aerial. Such a loss is, of course, a function of the height of the aerial above the general roof level rather than its actual height above ground level. Small increases of aerial height above the general roof level would probably give much larger signals and vice versa. In general, a satisfactory service is obtained in built-up areas with good continuous signals even in narrow canyon-like streets, and with little difference between adjacent streets which are radial and circumferential to the fixed station.

In conclusion, it would seem that equipment operating on frequencies of the order of 460 Mc/s is both a technical and economic possibility, in the most adverse case, i.e., mobile systems, there might be some slight degradation of performance from similar equipments operating in the lower frequency bands. American manufacturers have already marketed equipment suitable for these frequencies and such a mobile system is in operation in Chicago.[7]

REFERENCES

[1] E. G. Hamer, "Communication on 460 Mc/s," *Wireless World*, Vol. 56, pp 412-414, Nov., 1950.
[2] A. J. Aikens and L. Y. Lacy, "Tests of 450 Mc/s Transmission to a Mobile Receiver," *Proc. I.R.E.*, 38, No. 11, pp 1317-1319, Nov., 1950.
[3] E. G. Hamer and L. J. Herbst, "Receivers for use at 450 Mc/s," *Communication No.* 454.
[4] J. D. Kraus, "The Helical Beam Antenna," *Proc. I.R.E.*, 37, No. 3, pp 233-272, March, 1949.
[5] J. B. Lovell Foot, "Transmission Through Tunnels," *Wireless World, Vol.* 56, pp 456-458, Dec., 1950.
[6] K. Bullington, "Radio Propagation at 450 Mc/s," *Proc. I.R.E.*, 35, pp 1122-1136, Oct., 1947.
[7] "450 Mc/s Mobile Equipment," *FM-TV Radio Communication*, 11, No. 5, pp 17 *et seq.*, May, 1951.

MEASURING TELEVISION INTERFERENCE

A REPORT describing a prototype test set for measuring the interference produced by motor car ignition systems at television frequencies has been issued by The Electrical Research Association. The basis of the equipment is a five-stage t.r.f. amplifier centred on 45 Mc/s and taken from a war surplus Type 153 receiving unit having a band width of ±2.5 Mc/s. It is coupled by an attenuator and an 80-ohm line to a dipole aerial.

A special rectifying system is employed, which in conjunction with a peak valve-voltmeter gives readings substantially constant over the range of repetition rates encountered in car ignition systems.

Measurements show that the interference from any individual car is reasonably constant over the frequency range 40-70 Mc/s, so that tests made at any one spot frequency within this range will be representative of the interference throughout the whole television band.

A commercially made measuring set based on this report has been produced and its description in a revised Code of Practice (CP1001) is under consideration by the British Standards Institution.

Limited supplies of this report, M/T102, are obtainable from The Electrical Research Association, Throncroft Manor, Dorking Road, Leatherhead, Surrey, the price being 3s 3d by post.

PICKUP CONSTRUCTION

A KIT of parts and full constructional details for making a lightweight moving-coil pickup has recently been issued by A. M. Pollock, 31, Brooklawn Drive, Manchester, 20. The miniature moving-coil armature is supplied ready made in two types for either sapphire or fibre needles, and the kit includes a special Alcomax magnet to give high sensitivity. Construction can be completed with ordinary hand tools. Prices are as follows: drawings and instructions, 5s; kit of parts, 25s; sapphire styli (0.001 or 0.0025in radius), 7s 6d. each.

Vertical loudspeaker column for the dome area mounted to the right of the pulpit.

Speech Reinforcement in St. Paul's Cathedral

By P. H. PARKIN,* B.Sc., A.M.I.E.E. and J. H. TAYLOR,† A.M.I.E.E.

Experimental System Using Line-source Loudspeakers and Time Delays

THOUGH the 17th-century architect, Sir Christopher Wren, showed some interest in acoustics and sound insulation, St. Paul's Cathedral (Fig. 1) must be one of the most difficult buildings for speech in existence. Its large size (the volume is about five million cubic feet) and the lack of sound absorptive materials result when empty in a reverberation time at mid-frequencies of about 11 seconds (Fig. 2); even when full the reverberation time is still about 6 seconds. In addition there are several concave surfaces which produce strong echoes; the most obvious of these is the dome and its drum which is 111ft in diameter at the base and which rises to 216ft above floor level. The unaided voice cannot be expected to be intelligible over the whole congregation area. Various speech reinforcement systems have been tried, but none with complete success. The system in use before the one to be described here succeeded in making speech intelligible, but only at a considerable sacrifice in quality.

This article describes a system, developed by the Building Research Station in collaboration with Pamphonic Reproducers Limited, which has been recommended to the Dean and Chapter as being the most suitable for the Cathedral. The description is in terms general enough to be of help in the design of systems for other reverberant auditoria.

Frequency Response.—The smaller the frequency range used the simpler are the lesser design problems, but at the same time naturalness must be maintained. Beranek, Radford, Kessler and Wiesner have recently described experiments[1] with speech reinforcement systems in reverberant auditoria in which they found that the naturalness of the reinforced speech was not affected if the frequencies below 400 c/s were attenuated. They also found that, contrary to their original expectations, the intelligibility was not improved by attenuating these lower frequencies. These results are not quite the same as those found by one of the present authors (Parkin, unpublished). In Harringay Arena, when full, the low-level system in use there was switched alternately throughout a performance of a musical comedy from the normal full-frequency range to a restricted range of 300 to 4,000 c/s. Of 40 listeners distributed throughout the arena, 28 said the restricted range was more natural compared with 9 who said the full frequency range was more natural; 24 said that the restricted range was more easily intelligible compared with 12 who voted for the full range. Thus in this auditorium, where the reverberation time (full) at mid-frequencies was about 5 seconds (Fig. 2), there was a definite result in favour of the restricted range.

In the Royal Festival Hall a similar test was made with about 100 listeners, and here, where the reverberation time (empty) at mid-frequencies was about 2.2 seconds (Fig. 2), there was no measurable difference in either naturalness or intelligibility between the full and restricted ranges. In the empty Coliseum Theatre, London, where the reverberation time at mid-frequencies was estimated to be about 1.2 seconds, it was obvious to the four people engaged in the tests

* Building Research Station, Department of Scientific and Industrial Research.
† Pamphonic Reproducers Ltd.

[1] Beranek, L. L., Radford, W. H., Kessler, J. A. and Wiesner, J. B.; "Speech Reinforcement System Evaluation." *Proc.I.R.E.*, 39, (11) Nov. 1951, pp. 1401-8.

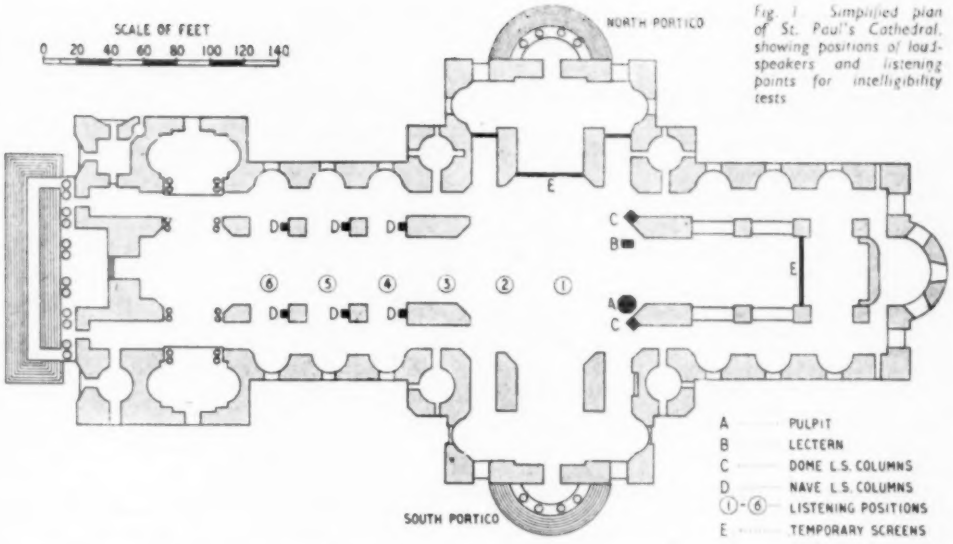

Fig. 1. Simplified plan of St. Paul's Cathedral, showing positions of loudspeakers and listening points for intelligibility tests

that the restricted frequency range was the less natural.

We see, then, that in the most reverberant auditorium the restricted range was better, in the middle auditorium there was no difference between the ranges and in the least reverberant auditorium the full range was better. For St. Paul's Cathedral it could be assumed that the restricted range would probably be better and would certainly not be worse. The range of 250 to 4,000 c/s was decided on for design purposes ; this was very close to the range used in the above tests in auditoria and was exactly four octaves.

Direct and Reverberant Sound.—The intelligibility of speech under reverberant conditions depends, in general, on the intensity of the direct sound, whether from the voice or the loudspeaker, being at a greater intensity than the reverberant sound. With a point source of sound, the energy density, in ergs per cubic centimetre, of the direct sound at a given point is given by

$$E_D = \frac{P}{4\pi r^2 c} \quad .. \quad .. \quad (1)$$

where P is the power of the source in ergs per second, r is the distance in centimetres from the source, and c is the velocity of sound in cm/sec. The energy density of the reverberant sound is given by

$$E_R = \frac{4P}{Ac} \quad .. \quad .. \quad (2)$$

where A is the absorption in the room.

If directional sound source is used directed towards the congregation, the direct sound energy is given by

$$E_D = \frac{\alpha P}{\beta 4\pi r^2 c} \quad .. \quad .. \quad (3)$$

where α is the fraction of the energy directed towards the congregation and β is the fraction of the solid angle 4π into which the energy αP is concentrated. The reverberant sound energy is given by

$$E_R = \frac{4P}{Ac}(1-\alpha a_c) \quad .. \quad .. \quad .. \quad .. \quad (4)$$

where a_c is the absorption coefficient of the congregation. Thus the greater α is and the smaller β is, the higher will be the intensity of the direct sound in relation to the intensity of the reverberant sound.

If we consider the distance from the source at which the direct and reverberant energy densities become equal, in the case of the point source we get

$$r_1 = \sqrt{\frac{A}{16\pi}} \quad .. \quad .. \quad .. \quad .. \quad .. \quad (5)$$

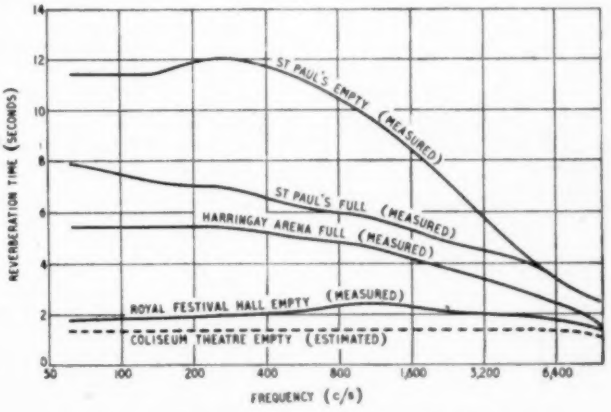

Fig. 2. Reverberation times of some representative large auditoria.

In the case of the directional source we get

$$r_2 = \sqrt{\frac{\alpha A}{\beta 16\pi (1 - \alpha a_c)}} \qquad \ldots \quad (6)$$

Let us assume that we have a directional source in which $\alpha = 0.9$ and $\beta = 0.03$. Then

$$\frac{r_2}{r_1} = \sqrt{\frac{\alpha}{\beta (1 - \alpha a_c)}} \qquad \ldots \quad (7)$$

which, when $a_c = 0.7$, gives $r_2/r_1 = 9$. Thus a directional source with these assumed values of α and β can be expected to cover nine times the distance that a non-directional source would cover before the reverberant sound intensity is as much as the direct sound intensity.

(It should be noted in passing that intelligibility is in practice maintained up to greater distances than those given by the absolute values r_1 or r_2 when $E_D = E_R$. This is because of the ability of the ear to distinguish between wanted and unwanted sound, and because the above calculations are concerned with steady-state conditions, whereas speech is transient. Nevertheless, the *ratio* of r_2 to r_1 does apply to actual conditions.)

Line-source Loudspeakers.—Directional sound sources can be divided into three main types: shaped reflectors, e.g., a parabolic surface with a source at the focus; shaped loudspeakers, e.g., mono-planar horns; and loudspeaker arrays, that is several individual loudspeakers arranged in a pattern to give directionality. Now in St. Paul's Cathedral, and in most cases, we need a beam of sound which is narrow in the vertical plane, so that it can be directed towards the congregation and not towards the reverberant volume above, and which is broad in the horizontal plane so that it will cover the required area. While it would be possible to design sound sources with the required directionality of either of the first two types, the third type—the directional array—is the obvious choice. It is simple to design and can be made from standard loudspeakers with great flexibility. A review of directional arrays is given by Olson[2] and the one that most simply meets the requirements is the straight line source.

The theory of line sources has been known for a long time; Wolff and Malter[3] in 1930 gave a summary of their behaviour, together with the results of measurements, and it is surprising that such sources have not been used more frequently. One of the authors (Taylor) installed two such sources at White City in 1932 which are still in use, but there does not appear to be any reference to their use in this country or in the U.S.A., although they have been developed in Germany recently[4] and are now coming into fairly common use on the Continent.

The directional characteristic of a source consisting of a number, n, of equal point sources radiating in phase, located on a straight line and separated by equal distances, d, is given by

$$R_\theta = \frac{\sin\left(\frac{n\pi d}{\lambda} \sin\theta\right)}{n \sin\left(\frac{\pi d}{\lambda} \sin\theta\right)} \qquad \ldots \quad (8)$$

where, at a large fixed distance from the source, R_θ is the ratio of the pressure at an angle θ to the pressure for an angle $\theta = 0$ (the direction $\theta = 0$ is at right angles (normal) to the line), and where λ is the wavelength. In the limiting case where n approaches infinity and d approaches zero so that $nd = l$ = the length of the line, we have the ideal straight line source. Equation (8) then becomes

$$R_\theta = \frac{\sin\left(\frac{\pi l}{\lambda} \sin\theta\right)}{\frac{\pi l}{\lambda} \sin\theta} \qquad \ldots \quad (9)$$

In the practical cases where the source is made up of a number of loudspeakers mounted close together, formula (9) can be used with sufficient accuracy provided that the distance between the loudspeakers is small compared with the wavelength. Thus with a vertical line source we have a directionality in the vertical plane which increases with increasing frequency; in the horizontal plane this arrangement does not cause any directionality. The polar diagram (up to 30 degrees either side of the axis) in the vertical plane of a vertical line source 11ft long at 1,000 c/s is shown in Fig. 3. It is seen that there are secondary lobes which, although the greatest of them is 13 db below the main lobe, might be troublesome in practice. If the line source is "tapered" in strength so that the sound from each element varies linearly from a maximum at the centre to zero at either end, the directionality is given by

$$R_\theta = \frac{\sin^2\left(\frac{\pi l}{2\lambda} \sin\theta\right)}{\left(\frac{\pi l}{2\lambda} \sin\theta\right)^2} \qquad \ldots \quad (10)$$

Fig 3 shows the directionality at 1,000 c/s of an 11-ft tapered source, and it is seen that the main lobe is slightly broader while the first of the secondary

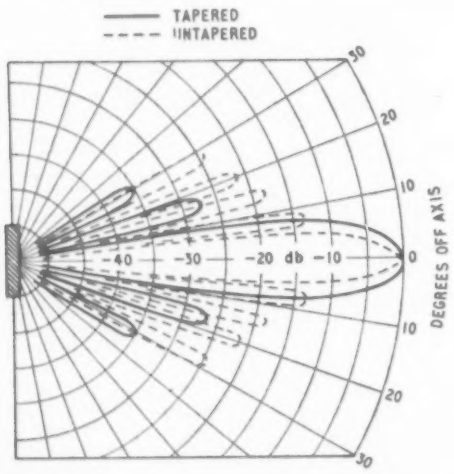

Fig. 3. Directional characteristic at a large fixed distance in the vertical plane of an 11-ft line source at 1,000 c/s.

[2] Olson, H. F., "Elements of Acoustical Engineering," pp. 26-49 D. Van Nostrand, New York, 1947.
[3] Wolff, I. and Malter, L., *Journal of the Acoustical Society of America*, 1930, 2, (2), pp. 201-241.
[4] Meyer, E., Building Research Congress Report, 1951, Division 3, Part 1, pp. 43-48.

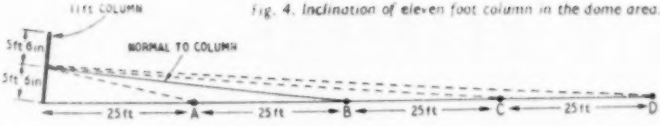

Fig. 4. Inclination of eleven foot column in the dome area.

lobes is reduced to 27 decibels below the main lobe.

We are now in a position to consider the design of loudspeaker line sources (which will be referred to simply as columns) for St. Paul's Cathedral—in the first instance those for the dome area. The two main speech positions were the pulpit and the lectern (Fig. 1) and an obvious decision was to use one column close to each, to be used separately. The horizontal distance to be covered was about 100ft, and the first attempt to cover this area was made using a column mounted about 20ft above ear height and directed down towards the congregation. The expected advantage was that the sound would be nearly all directed into the congregation so that α in equation (3) would be large. It was found, however, that when the dome area was only partly occupied, a condition that the loudspeaker system must contend with, reflections off the stone floor were giving rise to serious echoes. To avoid this, the column was then tried with its bottom at ear height and inclined forward slightly so that the centre of its beam was directed towards the centre of the dome area. The expected disadvantages of this arrangement were that α was smaller and that the sound was at grazing incidence with a corresponding attenuation. In practice, however, these disadvantages were found to be not serious.

This arrangement was, therefore, adopted and it became necessary to determine the length of the column required. It will be remembered that the frequency range to be covered was 250 to 4,000 c/s, and that the directionality of a line source increases with increasing frequency. Without going into detail here, it can be said that in the St. Paul's case a column which was long enough to give sufficient directionality at 250c/s would be too directional at 4,000c/s. Actually, a 6-ft long column for the whole frequency range was tried at one time, but when adjusted so that the listener's ears were at the beam centre when seated, the high frequencies were so sharply beamed that speech became nearly unintelligible when the listener stood up.

It would be possible theoretically to maintain the same directionality over the whole frequency range by cutting off the outer loudspeakers successively with increasing frequency by suitable electrical circuits, but this is rather complicated and has three other disadvantages at high frequencies, at any rate when 10-in loudspeakers are used. The first is that the number of loudspeakers left in circuit is small and cannot then be considered as a continuous line source ; the second is that the speakers left in circuit are not tapered properly ; the third is that in the horizontal plane the speakers are directional, due to their size being comparable with the wavelength.

In St. Paul's, it was necessary to cover a horizontal angle of about 120 degrees, and Olson[5] shows that, for example, a 16-in loudspeaker at 2,500 c/s is about 10 db down at 60 degrees off the axis. On the whole, the best solution appeared to be to use a cross-over arrangement, and the obvious cross-over frequency to choose was 1,000 c/s which divided the total frequency range into two ranges, each two octaves wide.

Considering the low-frequency part of the column, the highest frequency it had to emit was 1,000 c/s and thus the beam width at this frequency had to be adequate to cover the dome area ; it had, however, to be kept as narrow as possible since at lower frequencies the beam would be wider. Any arrangement must be a compromise, since the narrower the beam width the longer the length of the column ; the centre of the column is correspondingly higher above the listening plane and thus calls for a wider beam. A consideration of the geometry (Fig. 4) suggested that an 11-ft column would be suitable : this gave a beam width at 1,000c/s of 6 db down at 5 degrees on either side of the axis. In equation (10), R_θ is unchanged if l/λ is kept constant, so that to obtain the same directionality from the high-frequency section of the column at 4,000 c/s, its length had to be one quarter of the low-frequency section, i.e., 2ft 9in.

If we take listener position B (Fig. 4) as our reference point (0 db) then at position A the intensity at all frequencies will be 6 db higher since it is at half the distance from the source ; but the intensities at A, C and D, which are off the centre of the beam, will vary with frequency. The actual values will be :

Position	Relative Intensities (db)			
	L.F. Section		H.F. Section	
	250 c/s	1,000 c/s	1,000 c/s	4,000 c/s
A	+5.5	0	+5.5	0
B	0	0	0	0
C	−3.5	−4	−3.5	−4
D	−6	−7.5	−6	−7.5

Thus at 25ft from the source, the frequency response is slightly irregular, but comparatively few people are as close as this since the column is covering a fan-shaped area. At greater distances the response is practically uniform.

(To be concluded.)

[5] Olson, H. F., *loc. cit.* p. 132.

SOME 1951 ADVANCES

IN a review of their activities during 1951, The British Thomson-Houston Company mention some interesting new developments in the electronics field. One is a very-high-speed photo-electric counter which will count at rates up to 25,000 per minute. Another is a new type of voltage regulator using magnetic amplification—the use of saturable core reactors in conjunction with contact rectifiers has been well known for many years, but recent improvements in magnetic steels and circuit arrangements have greatly extended the scope of this kind of amplification. In the radar field the most important B.T-H. work has been on a magnetic modulator which is designed to eliminate trigger valves of the thyraton or trigatron types and so increase the reliability of the equipment.

LOUDSPEAKER RESPONSE CURVES

Presentation Showing Distortion as Well as Total Output

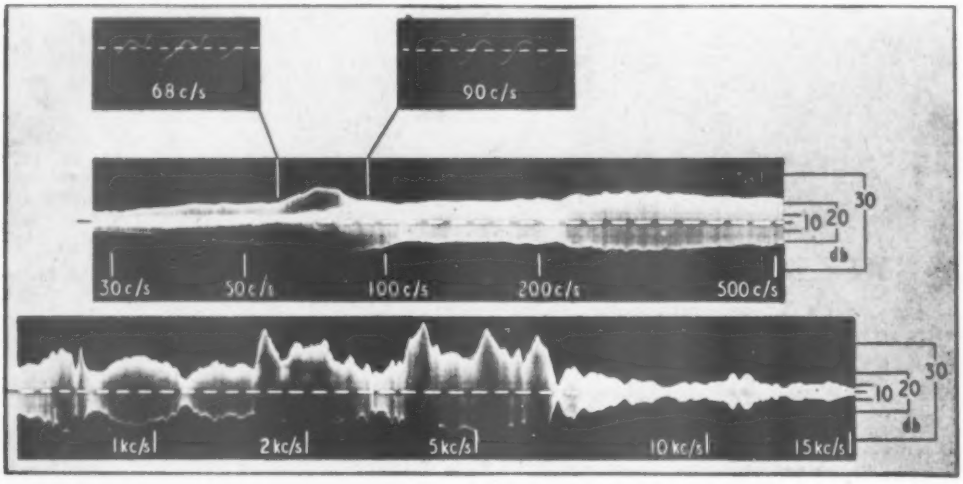

Fig. 1. Oscillographic record of a 10-in loudspeaker, with corresponding waveforms at 68 and 90 c/s.

Fig. 2. Detail of trace with double edge due to the generation of a sub-harmonic (1,100 c/s) in the region of 2,200 c/s.

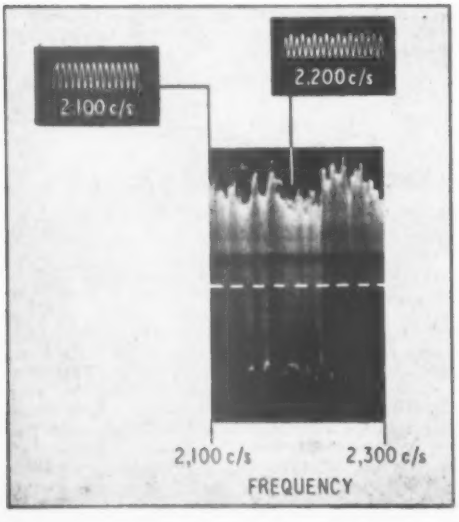

FOR many years the "frequency response curve" giving the relationship between sound pressure output and the frequency of the applied constant electrical input has been accepted as a basis for comparing objectively the relative merits of different loudspeakers. The information which it conveys, though useful, is limited, and unless the conditions of measurement are known it can be misleading. Too often a well-sustained output in the bass is produced by a whole collection of frequencies with very little of the fundamental so optimistically indicated by the figures on the scale below the curve. True, this error can be eliminated, as it is in N.P.L. tests, by the use of filters to ensure that nothing but the fundamental reaches the recorder, but even then the curve does not convey visually the kind of noise which one might expect under working conditions.

Much more information is conveyed by an oscillographic form of presentation of the response curve recently developed by G. A. Briggs of Wharfedale Wireless Works. In this the output waveform is applied to the vertical deflection of a cathode-ray tube while a camera with open lens and slowly moving film expands a record of the trace horizontally.

The virtue of this method is that in addition to the magnitude of the output some indication of the shape of the waveform is impressed on the record. Since the density of the photographic trace is a function of the speed of "writing" of the oscillograph spot, one would expect the trace of a sine wave to be lightest at the centre, where the speed is highest, and progressively heavier towards the edges where the spot is, in fact, momentarily stationary before beginning its return journey. A square wave would give two parallel thick lines with faint uniform shading (if any) between. On the other hand a "chopped" or "limited" sine wave with flattened peaks might be more difficult to distinguish, since there would be

some degree of shading. Harmonics, when they are in favourable phase relationship to the fundamental, often show as bright bands where the speed of the trace has been arrested momentarily by a kink or kinks in the waveform. In other phase relationships the harmonics may give a smooth waveform difficult to distinguish from a sine wave without direct comparison by superposition. There will then be no striations on the trace to reveal their presence. Fortunately such waves are often asymmetrical and give themselves away if the relative amplitudes on each side of the datum line through the centre of the trace are compared. Such waveforms are typical of bass response of loudspeakers with asymmetrical compliance in the centring devices associated with the cone.

Fig. 1, which is a curve taken by Mr. Briggs of a typical 10-inch commercial loudspeaker, shows these effects well. The bright band in the frequency range 30-80 c/s is produced by the major kink in the waveform appended at 68 c/s. Above the cone resonance the waveform appears to be much better, but there is considerable flattening of the upper peaks and a slight suggestion of saw-tooth tilting in the record taken at 90 c/s. The flattening is at once apparent in the asymmetry of the trace at 90 c/s.

Many loudspeakers, particularly 8in types fitted with what are known in the trade as "loud" cones, are prone to sub-harmonics at spot frequencies or narrow bands in the frequency range 1,000-5,000 c/s. This fault is also revealed by Mr. Briggs's method of recording, and a good example is shown by the double edge in the middle of the trace detail of Fig. 2. The corresponding waveform with alternate top peaks of increased amplitude is shown above, together with the undistorted waveform at an adjacent frequency.

Though the new form of presentation may not give the whole picture—transient performance, for instance, is excluded—it is an important advance on conventional curve tracing methods, and sufficient examples have been given to show that it provides ample material for skilful interpretation. The curves shown were all made with sine-wave inputs; possibly a series with pulsed inputs of different waveforms could be devised to present an even more detailed picture of a loudspeaker's performance.

Mr. Briggs has already applied the method to the examination of amplifiers and a.f. oscillators, and has suggested that, with a suitably speeded-up gliding tone record, it could be used for showing non-linearity as well as resonances in gramophone pickups.

LETTERS TO THE EDITOR

The Editor does not necessarily endorse the opinions expressed by his correspondents.

I.F. Interference

IN the January issue of your journal there was a description of an a.m./f.m. receiver for comparing the two v.h.f. systems radiated by the experimental transmitter at Wrotham.

This is stated to have a three-stage i.f. amplifier on 14.1 Mc/s, and I wonder if those responsible for this choice of i.f. are aware that there is an amateur band from 14.0 to 14.4 Mc/s. Any amateur working on this band in the vicinity of a receiver with such an i.f. is almost certain to cause interference, entirely due to the choice of i.f.

It can be argued, of course, that it is very difficult to find a frequency on which to set an i.f. amplifier and be sure that there will not be a transmitter of some kind breaking through, but it is also very certain that the possibility of a commercial station being in the vicinity of the receiver is very small but the possibility of an amateur living close by is quite large.

We amateur transmitters already have our troubles with broadcast interference and television interference; can we beg that designers will take what simple steps they can to avoid adding v.h.f. interference to the list? Make the i.f. 13.1 or 15.1, but don't put it in the middle of our most consistent long-distance band.

Brighton. RICHARD J. DONALD, G3DJD.

Safer A.C./D.C. Sets

REFERRING to C. E. Thorn's letter in your January issue, I am doubtful if his suggestion of using an earthed chassis with one insulated return point per stage would be satisfactory in practice. Although the use of a single point for each stage is usually considered to be ideal, my own experience is that it is usually much better to return everything directly to the nearest point on the chassis.

In this connection I recall reading in an American journal that Mr. Thorn's suggested method had been tried and found unsatisfactory because of the individual return points. The scheme there recommended was an earthed chassis covered on its inside by a layer of insulating material to which was clamped a thin sheet of metal to form the "live" return sheet for all connections. Because of the high capacitance to the chassis proper the sheet formed a satisfactory "earth." If soldered connections are made directly to the sheet, it is obviously necessary to choose an insulating material that will withstand soldering temperatures.

I suggest that the scheme is one worth further investigation. W. TUSTING.

London, N.

Phonetic Alphabets

I AM grateful to you for publishing in your December issue the note on phonetic alphabets, but find its contents most disturbing.

During my service career I wholeheartedly accepted the new "Able Baker Charlie" alphabet as more effective than the older G.P.O. system. But the newest alphabet as introduced by I.C.A.O. appears to have been compiled by and accepted by those without the slightest idea of the requirements of speed and efficiency. What is worse, it ignores the capabilities of modern radio-telephony equipment. For example, take the letter "F" denoted by "Fox" in the Services alphabet, which now becomes "Foxtrot"—much longer. The Services alphabet has a total of 40 syllables against 55 for the I.C.A.O. version. L. E. MOORAT.

Glasgow.

[Many will share our correspondent's dislike of the new I.C.A.O. phonetic alphabet, but in condemning it we must not be too insular. Most of the words chosen have a wide international currency, and so will be widely recognized by those whose mother-tongue is not English. To take the example given, we imagine there is no country into which "Foxtrot" has not penetrated.—ED.]

Jointing Aluminium

WITH reference to A. E. Crawford's letter (your December issue) I do not ask for space for a protracted correspondence on soldering methods, but am

compelled to challenge his statements concerning abrasion tinning. He is obviously completely misinformed in considering that a sound mechanical and electrical joint is not required for cable sheaths. A wiped joint on an aluminium sheathed cable is normally expected to, and does, withstand heavy mechanical stresses, conditions of vibration and high internal pressures. Low electrical resistivity in the joint is a *sine qua non*.

The jointing of cables on site is one of the more obvious examples where ultrasonic methods are inapplicable, but as I stated in my previous letter "both (methods) have their own particular application." I also have one comment on the method of test Mr. Crawford recommended for examination of a tinned surface, namely, wiping the hot surface with a cloth. This test is quoted in my firm's leaflet of instructions to jointers and recommended for the examination of abrasion tinned surfaces.

Johnson and Phillips, Ltd., P. A. RAINE.
London, S.E.7.

Radio's Responsibilities

IS it not time that the radio technologist, among others, showed some sense of his moral obligations to the rest of society? Like the atomic scientist, he possesses knowledge and ability which can be used either for the benefit or the destruction of his fellow human beings, yet he does not seem to be aware of the responsible position this places him in.

The usual argument is, of course, "I'm only doing my job—it's not my business to enquire into the rights and wrongs of it." This point of view may be an estimable one in the bee-hive or the ants-nest, but coming from a human being who uses intelligence and creative inspiration in his work and does so wittingly, with his eyes open, it is something worse than degrading. Unfortunately, it is perhaps more prevalent in the radio engineering profession than in any other, for the development of radio has been extremely rapid and the technologist has been pushing ahead with such enthusiasm that he has had no time to consider the implications of what he is doing. He has had no time to evolve a tradition, like that of the doctor, which frowns on the use of professional knowledge for the destruction of human life. What is worse, he does not realize that he is rapidly becoming a mere tool in the hands of administrators who regard him only as a kind of soulless thinking machine for putting their Napoleonic schemes into practice.

Of course, the technologist is really very human. He says to himself "My duty to my wife and family comes first and this armament contract happens to pay better than domestic receivers." If the individual technologist has sufficient moral courage he can, of course, make his own decisions. But that is not enough. The radio engineering fraternity as a whole should, through its profesional institutions, at least show some recognition of the fact that it has these responsibilities, and, if possible, come to some agreement on a code of ethics. Until it does so, it will never achieve an honourable position in the eyes of a world which already has good reason to regard technological "progress," and those responsible for it, with fear and distrust. JAMES FRANKLIN.

London, S.W.4.

DIELECTRIC AMPLIFIERS

Power Gains Up to a Million per Stage with High Input Impedance

CERAMIC materials of the barium titanate type have high dielectric constant (permittivity) which is dependent on temperature and also on the strains resulting from the application of an electric field. The relationship between permittivity and the applied field follows, under certain condition, a hysteresis loop similar in form to that of an iron core and these dielectrics are said to exhibit "ferroelectric" properties.

Such dielectrics can be used as a control medium for power amplification, much in the same way as magnetic alloys are used in the magnetic amplifier; the alternating current in a circuit which includes a capacitor incorporating the special dielectric can be varied by the application of a "d.c." control field. The chief advantage of the dielectric amplifier is that it is a voltage rather than a current-operated device and its input impedance can be made relatively high by using a high-frequency power supply and a small capacitance.

Circuits are usually of the balanced push-pull type and a survey of representative arrangements is given in a paper by A. M. Vincent in the December, 1951 issue of *Electronics*. This paper also gives details of the operating characteristics of a range of materials compounded from barium and strontium titanate and barium and lead zirconate.

The titanate mixtures exhibit clearly defined maxima of permittivity (Curie points) in the temperature range -20 to 120 deg. C and a working point giving high gain is attended by sensitivity to temperature changes. The zirconates are less susceptible to temparture, but have a lower possible gain.

By the choice of suitable dielectrics and circuits, temperature compensation is possible, and the principle is quite practicable for use in regulators, servomechanisms, and in r.f. circuits at up to 10 Mc/s if lower gains are accepted. The dielectric amplifier is small, and if desired can be used in a wide range of shapes. The cost is low and it is claimed that titanate-dielectric capacitors are cheaper to make than mica or even paper types.

CLUB NEWS

Brighton.—At the meeting of the Brighton and District Radio Club on February 12th, A. Slater (G3FXB) will talk on "DX operating and working." The club meets on Tuesdays at 7.30 at the Eagle Inn, Gloucester Road, Brighton. Sec.: R. T. Parsons, 14, Carlyle Avenue, Brighton, 7.

Cleckheaton.—At the February 27th meeting of the Spen Valley Radio and Television Society, W. G. Merriman will speak on "Electronics in Wartime." The club meets on alternate Wednesdays at 7.30 at the Temperance Hall, Cleckheaton. Sec.: N. Pride, 100, Raikes Lane, Birstall, Nr. Leeds.

Coventry.—"Mathematics Made Easy" is the title of a lecture by T. R. Theakston, B.Sc., to be given to members of the Coventry Amateur Radio Society on February 18th. This meeting is open to the public; tickets are obtainable from the secretary. Meetings are held on alternate Mondays at 7.30 at the Y.W.C.A., Queen's Road, Coventry. Sec.: K. G. Lines, 142, Shorncliffe Road, Coventry.

Birmingham.—Slade Radio Society, which meets on alternate Fridays at 7.45 in the Parochial Hall, Broomfield Road, Erdington, has arranged the following programme for February. On the 15th A. G. McGregor of the Midland Electricity Board will speak on "The generation of electric power" and on the 29th J. Y. Freeman (Birmingham University) will deal with "Selected topics from Nuclear Physics." Sec.: C. N. Smart, 110, Woolmore Road, Erdington, Birmingham, 23.

THE "BELLING-LEE" PAGE

Providing technical information, service and advice in relation to our products and the suppression of electrical interference

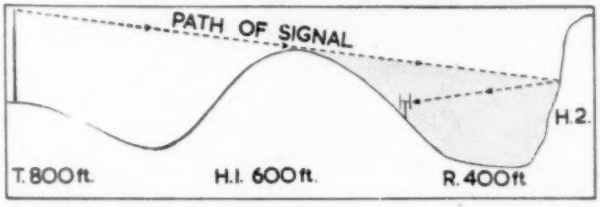

Diagram showing transmitter (T), 800ft. up, and receiver (R), 400 ft. up. Receiver is in shadow of 600ft. hill (H1), thereby obtaining a very weak direct signal, if any, and a strong reflected signal from hill (H2), situated, say, 2 miles away; R would be fortunate if receiving only one "ghost." Recorded field strength on non-directional aerial would be reflected signal plus direct signal, which might show a good reading but might be useless.

Returning to Holme Moss Ghosts

To say that the Holme Moss district is haunted is to put it mildly, but from very careful enquiries the situation doesn't seem to be as serious as was at first thought. (No, we are NOT giving up the Ghost, we hope to lay it.) We do know that the publicity given to this multiple path reception emanates from a noisy minority, but if we had bought a T.V. receiver and couldn't get satisfactory reception, we would want our money back or else; and if we were dealers, faced with the return of one or more receivers because of "ghosts," we would quickly add to the noisy minority.

We are not the only authority working on this problem. At least one very prominent Receiver Manufacturer has carried out an independent investigation, and we know that at least one independent body is starting off. We are all satisfied that at present, there is no known make or design of aerial that is revolutionary. Let it be said now, that these are no last words on a difficult problem. It is as far as we, or anybody else, have got.

Of the centres of population, parts of Sheffield seem to be the worst served district, the strength of the direct signal being very poor indeed. The town is definitely in a "shadow" area, a shadow caused by the high hills to the north-west of the town, and in general the signal is much weaker than reflections.

It is possible that a field strength survey of Sheffield would show a good strong signal, but this would be the sum of the very weak direct signal, plus all the strong echoes. It will be seen just how misleading such a survey could be. There are places like Hebden Bridge with a much smaller population but where conditions are even worse.

At one time it was thought that the thing to do was to orient the aerial on the strongest reflection and bring up the signal, but observation of many such cases shows that the resultant picture is unsatisfactory, as the reflection is rarely a "clean" reflection, therefore the picture looks out of focus. At this point it may be worth mentioning that the Swiss have a technique for beaming a H.F. telephone signal over a mountain. They erect a dipole or stack of dipoles on the summit and beam a signal on to this. The hill top aerial is parasitic, cut to resonate at the transmitter frequency; it does so, and acts as a perfectly clean reflector passing on or re-radiating a strong reflected signal. No doubt the "powers that be" have thought on these things (and many others). A low power transmitter is not likely, as this would have to be run at a different frequency, and there isn't sufficient room on the ether. Moreover, it would necessitate the modification of a very large number of receivers.

Sorry we cannot be more helpful at present, but we did promise to keep our readers informed of progress.

It has been established that a reflection from high ground within three miles and behind the receiving aerial, i.e., further away from the transmitter, is more troublesome than one between the transmitter and the receiver. With this information, we feel we are in a position to say by examination of a contour map, just what districts are likely to be troublesome. In hilly or mountainous districts a certain amount of caution should be exercised before embarking upon the purchase of a T.V. receiver. Generalising (which is always dangerous), steep hills and valleys are likely to be more troublesome than "rolling" country.

By the time this is published, Scottish readers will be very interested in Kirk o'Shotts. We would anticipate difficulties in the valley of the River Forth west of Stirling, and we would be exceedingly cautious before spending much money in Peebles, Innerleithen, or other towns on the River Tweed before it leaves the hills.

Conversion Kits: Holme Moss to Kirk o'Shotts frequencies

Scottish readers and those living near the border, will be interested to learn that we have decided to produce a small range of five television aerial conversion kits for the purpose of converting Holme Moss installations over to Kirk o'Shotts frequencies. Prices of these will be kept as low as possible, and will be announced later.

These kits will be made available for a period of three months only, i.e., from a date one month prior to the official opening of the new transmitter to a date two months following the opening. This period will, in our view, give dealers sufficient time to make decisions and place orders.

The need for conversion kits should be confined to an area north of a line through Penrith and Morpeth. Experience may show that the nature of the ground favours reception from one station more than the other from either side of this line, or that the signal strength from Holme Moss is sufficient to make a charge over impracticable.

Again, in framing our policy we have borne in mind that:—

(*a*) In many cases it will be less expensive to install a completely new inexpensive aerial in a different position.

(*b*) The end cost of the change-over should be kept as low as possible by the *avoidance of changed cable runs*

(*c*) The converted installation should have a new lease of life and be virtually as good as new.

Written 3rd January, 1952.

BELLING & LEE LTD
CAMBRIDGE ARTERIAL RD., ENFIELD, MIDDX., ENGLAND

In the overcast — The advent of jet propelled aircraft on the world's air routes has emphasised the vital necessity of the precision approach.
The new Marconi VHF direction finder, with its local or remote instantaneous presentation of sensed bearings on an 8" diameter meter, provides a unique contribution to the solution of this airport control problem.

MARCONI VHF D/F

MARCONI'S WIRELESS TELEGRAPH COMPANY LTD · CHELMSFORD · ESSEX

Geneva Radio Conference

Review of Results of Three Months' Work

AT Atlantic City in 1947 it was agreed that the world's radio services capable of causing harmful interference and operating on frequencies below 27.5 Mc/s, should in future operate in accordance with detailed frequency assignment plans which were to include projected as well as working services. These plans were to be drawn up by a number of bodies set up by the Conference.

Unfortunately, owing partly to the inherent difficulties of the problem and partly to the loss of that spirit of give and take which marked the Atlantic City Radio Conference, the frequency planning bodies met with indifferent success. It is true, of course, that a plan for European long- and medium-wave broadcasting stations was agreed at Copenhagen in 1948 and put into effect in March, 1950. In addition plans were prepared for medium-wave broadcasting in the North American Region, for the medium frequency services generally in the Eastern Hemisphere and for all maritime and aeronautical mobile h.f. services. At Mexico City in 1948 a basic plan was produced for h.f. broadcasting for one phase of the sun-spot cycle, but this was not acceptable to a number of important countries, and the subsequent conferences at Florence and Rapallo did not produce plans for the other phases of the cycle. Moreover the planning body concerned with the point-to-point services, which occupy a very substantial proportion of the high-frequency spectrum, was unable to produce generally acceptable plans. It was with this somewhat discouraging background that an Extraordinary Administrative Radio Conference was convened by the International Telecommunication Union at Geneva in August last year.

On 3rd December, after three and a half months' work, an agreement was signed by the representatives of 65 countries—that is all delegations present except those of the Soviet Union and of the eight Eastern European countries which supported her throughout the Conference. The effective date of the agreement is 1st March, 1952. The Conference completed and approved plans for most radio services using frequencies from 14 kc/s to 3,950 kc/s (4,000 kc/s in the Americas) and in most cases set dates on which they will come into effect. Plans were also approved for the high-frequency radiotelegraphy and radiotelephony maritime service and the aeronautical mobile service. For the plans between 2,000 and 4,000 kc/s in the Americas, and between 2,850 and 3,950 kc/s in the rest of the world, and for the h.f. maritime and aeronautical mobile plans, the Agreement provides for piecemeal implementation.

The most difficult and most important problem facing the Conference was to devise a means of bringing into force the high-frequency part of the allocation table (3,950-27,500 kc/s). The solutions proposed differed widely. Many delegations advocated further attempts to prepare complete assignment plans incorporating all projected requirements, although those who held this view were not unanimous on the basis upon which this planning should take place. Other countries considered that the only practicable course would be for each Administration gradually to adjust its operations by appropriate exchanges between working frequencies and by the bringing into use by normal methods of new frequencies where necessary.

The Conference, however, agreed on a compromise which provides that this gradual adjustment process shall apply on a voluntary basis throughout the high-frequency part of the spectrum but that in addition the International Frequency Registration Board (a permanent organ of the I.T.U.) shall prepare plans for high-frequency broadcasting. The I.F.R.B. is to co-ordinate proposed frequency changes.

Special safeguards have been provided for the safety-of-life aeronautical and maritime mobile high-frequency services. In particular a broad programme of frequency changes has been drawn up for the maritime mobile frequency bands to ensure continuity of the service, to minimize interference and to allow for the fact that ships' frequencies in the different bands are harmonically related.

Further Review in 1955

No date has been set for the termination of the period of adjustment but the International Frequency Registration Board will provide periodic progress reports and the Administrative Council of the I.T.U. has been invited to review progress in 1955 with a view to recommending to all countries a date for the beginning of a final adjustment period. During this comparatively short period final adjustments in accordance with the allocation table will be compulsory and the High-Frequency Broadcasting Plan, if drawn up and approved by then, will be brought into effect. The Conference also agreed that before implementation of the allocation table, the International Frequency Registration Board should at the end of the final adjustment period re-examine the position and prepare a draft International Frequency List for point-to-point services. This would take into account the current use of frequencies together with requirements remaining unsatisfied at that time. This List will be considered by a further international conference.

In view of the complexities of the problem and the extent to which the interests of the more developed countries, in the radio sense, inevitably conflict with the others, it is particularly satisfactory that so wide a measure of agreement should have been achieved—albeit with some reservations. In the high-frequency field, of course, the Agreement is very largely permissive and a great deal therefore depends on goodwill and also on the improvement of transmission techniques. By promising to restore order in the spectrum and, in particular, to enable the aeronautical and maritime mobile services to operate in their new exclusive bands in accordance with agreed plans, the Agreement is of great importance in the future development of high-frequency radio services.

WORLD OF WIRELESS

Planning Metre-Wave Broadcasting • Instruments Exhibition • Record Exports • Scottish Research

Continental V.H.F.

WITH the recent reorganization of the broadcasting service in Italy, two of the three programmes are now radiated by f.m. transmitters, of which there are now twelve. Similarly, it is learned from the European Broadcasting Union's *Bulletin* that at the beginning of September there were forty-six v.h.f. transmitters operating in Germany.

With this continued growth in the use of v.h.f. for sound and television broadcasting in Europe, it has been decided by the International Telecommunication Union to hold a conference in Stockholm, Sweden, from May 28th, to which all member countries of the I.T.U. in the European area have been invited. The main purpose is to discuss the allocation of frequencies—either to countries or individual stations—for sound and television broadcasting within the three bands (41-68, 87.5-100 and 174-216 Mc/s) allocated to broadcasting at Atlantic City.

The detailed agenda is not known but the questions of propagation and technical standards are bound to come before the meeting.

Physical Society's Show

THE thirty-sixth annual exhibition of scientific instruments and apparatus, organized by the Physical Society and supported by 141 exhibitors, will be held from April 3rd to 8th (excluding Sunday, 6th). As in 1951 it will be set up in both the Royal College of Science, Imperial Institute Road, and the Huxley Building, Exhibition Road, South Kensington.

Tickets will again be valid for specified days or morning (10.0-1.0) or evening (6.0-9.0) sessions, and are available from the Society, 1, Lowther Gardens, Prince Consort Road, London, S.W.7. There will be a break (from 1-2) between the morning and afternoon sessions. On the first, second and fourth days the exhibition will close at 9.0 and on the other two days at 5.0. The exhibition will be open to members of the Society and the Press only on the first day up to 6.0.

Radio Exports

NOVEMBER'S exports of British radio equipment of all kinds (£2,235,367, which is as much as in a year before the war) brought the total for 11 months of 1951 to £20,446,795, compared with £17,750,000 for the whole of 1950. According to the Radio Industry Council, the exports of broadcast receivers, which declined after the post-war peak period, increased in value in 1951 to about £5,000,000, the highest figure yet.

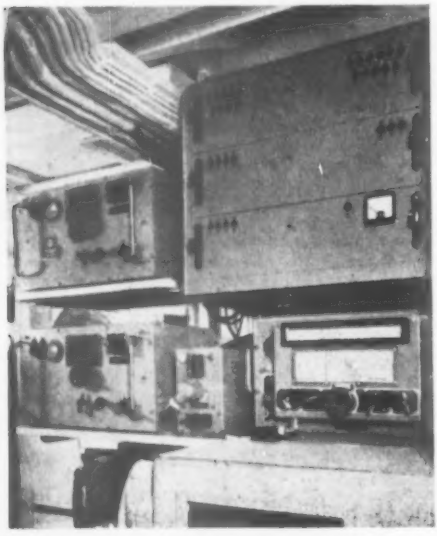

RADIO INSTALLATION in the liner "Gothic" has been supplemented for the Commonwealth tour of T.R.H. the Princess Elizabeth and the Duke of Edinburgh by the addition of high-power radio - telephone and high-speed radio-telegraph equipment to cope with State and Naval traffic and to meet the needs of the B.B.C. and the Press. The Marconi 7-kW SWB11X transmitter is the first of its kind to be fitted on board ship. Above the three receivers of the ship's sound reproducing equipment shown here is the aerial splitter equipment enabling any, or all, of the ship's receivers to be operated from the main receiving aerial.

Transatlantic Veteran

MARCHESE Luigi Solari, referred to in our December issue as the sole survivor of Marconi's original band of associates, is also almost certainly the only surviving participant in the transatlantic transmissions of 1901. His book "Storia della Radio," a copy of which he has just sent to us, throws many interesting sidelights on this historic event, during which he was at the Poldhu station. Details are given of the Solari type of self-restoring coherer, used by Marconi for reception. On the vexed—but perhaps not highly important—question as to why, contrary to usual practice, the letter "S" was chosen for the tests, the book adds some information. Apart from being thought to be easily distinguishable from atmospherics, the three dots were easily sent by unskilled telegraphists and also imposed less strain on the condensers than would a test signal like the conventional "V" which includes a dash.

Electronics in Scotland

AS part of its general policy of industrial development, the Scottish Council is going ahead with a scheme for building up an electronics industry in Scotland. The Government having placed a fair share of research and production contracts with Scottish firms the Council hopes to build up technical facilities which can subsequently be applied commercially. The research and development teams of most of these firms, however, are too small for the kind of work the Government is offering, so it has been necessary to form a co-operative group with one large firm (Ferranti of Edinburgh) acting as a "parent" contractor. It will accept large contracts for subdivision amongst the members of the group and will give technical advice and provide training facilities for new staff. The Government has also built a new laboratory block adjacent to Ferranti's which will serve as a base for the work of the group.

PERSONALITIES

Dr. E. C. S. Megaw, O.B.E., formerly Superintendent of Research at the Admiralty Signal and Radar Establishment, Haslemere, and now Director of Physical Research at the Admiralty, has been promoted to the rank of Chief Scientific Officer in the R.N. Scientific Service. Prior to joining the Admiralty in 1946, he was for sixteen years in the Research Laboratories of the G.E.C., where he specialized in the

study of transit-time oscillators. Dr. Megaw, who received the degree of D.Sc. from Queen's University, Belfast, in 1946, has contributed a number of articles to our sister journal *Wireless Engineer*.

Anthony W. Martin, M.B.E., Assoc. I.E.E., is among three new directors appointed by E. K. Cole, Ltd. He joined the company as research engineer in 1928 and was appointed chief of research in 1942 and chief engineer in the following year. During the war he was concerned with the development of radar. He will continue to be responsible for the design and technical development of Ekco equipment.

George W. Godfrey, who joined E. K. Cole, Ltd., as radio sales manager in 1945 and three years later became general sales manager (Radio Division), has been appointed an executive director. Mr. Godfrey, who is chairman of the Television Promotion Committee of the British Radio Equipment Manufacturers' Association, held executive positions at H.M.V., E.M.I., Baird and Ultra before joining Ekco.

Walter D. Kemp has left the Planning and Installation Dept. of the B.B.C., where he has been in charge of television recording, and is joining High Definition Films, Ltd., as chief engineer. Before going to the B.B.C. in 1946 he had been with E.M.I. and R.F. Equipment.

Col. W. J. Kent, C.B.E., D.L., chairman of the group of companies controlled by Taylor, Tunnicliff & Co., was created a Knight Bachelor in the New Year Honours.

M. V. Callendar, author of the article "Television Set Testing," was in charge of the research section of Lissen, Ltd., from 1929 to 1933 and with Pye (1933-39) before joining Ekco, where he worked on radar and army walkie-talkie sets Nos. 46, 78 and 88 during the war. He is now engaged mainly on television receiver problems.

E. G. Hamer, author of the article "Review of 460 Mc/s," joined the Admiralty Signal and Radar Establishment in 1940. Towards the end of the war he went to the Middle and Far East, where he was concerned with the establishment of radio maintenance units. In 1947, Mr. Hamer joined the Research Laboratories of the General Electric Company, where he has worked on the development of v.h.f. multi-channel and mobile communications systems.

P. H. Parkin, co-author of the article "Speech Reinforcement in St. Paul's Cathedral," graduated in electrical engineering in 1938 and undertook post-graduate research on dielectric strength of air at high frequencies. In 1940 he joined the Admiralty for work on counter-measures to magnetic, acoustic and pressure mines, and since 1946 has been at the Building Research Station of D.S.I.R., where he is now Principal Scientific Officer in charge of the sound insulation and acoustics section of the Physics Division.

J. H. Taylor, co-author of the article "Speech Reinforcement in St. Paul's Cathedral," was trained at Faraday House. He left Standard Telephones and Cables in 1931 to become one of the co-founders of Pamphonic Reproducers, Ltd., where, except for service as a radar officer in the R.A.F., he has been since then.

IN BRIEF

Licences.—A record monthly increase of 81,950 television licences was recorded by the Post Office at the end of November, bringing the total to 1,113,900. The total number of broadcast receiving licences (including television) in force in the U.K. at that time was 12,525,900.

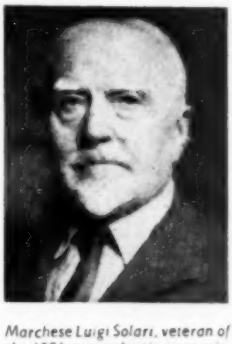

Marchese Luigi Solari, veteran of the 1901 transatlantic transmission tests. (See opposite page)

Isle of Wight Transmitter.—Despite the Government's shelving of the B.B.C.'s plans for the erection of five low-powered television stations to serve the areas not adequately covered by the main stations, the Corporation's engineers are going ahead with site tests. The Isle of Wight County Planning Committee has approved—with certain provisos—the erection of a 750-ft lattice steel mast and transmitter buildings at Rowridge, Carisbrooke.

"Contacts," used in its literal sense, is the title of a convention being organized by the East Midland Centre of the I.E.E. for April 7th-9th, which will be held at Loughborough College. The first part of the convention will be devoted to the subject of "Light-Duty Contacts in Theory and Practice" and the second to "Heavy-Duty Contacts." Further particulars and registration forms can be obtained from R. G. L. Ryan, the Brush Electrical Engineering Co., Ltd., Loughborough. The convention will not be confined to members of the Institution.

Electronic Instruments.—A course of lectures covering electronic instruments and their applications is being held at the South-East London Technical College, Lewisham Way, S.E.4. The first part of the course covers, in eight lectures, the general subject of instruments, part two (six lectures) deals with electronic computing, and part three (four lectures) with cathode-ray oscilloscopes and their applications. The lectures, which will be held on Tuesdays, began on January 8th and will continue until May 13th. The fees are: parts one and three £1 5s inclusive, part two 12s 6d.

"Sensitive T.R.F. Receiver."—Reprints of the article from our November issue describing a sensitive t.r.f. broadcast receiver are now available from our Publishers; price 1s, or by post 1s 1½d. The reprint includes an introductory article (October issue) on the automatic gain control system embodied in the receiver.

N. American Television.—A network of television relay stations linking Buffalo, N.Y., with Toronto and Montreal, via Ottawa, is planned by the Canadian Broadcasting Corporation. The relay stations, which are not expected to be completed until 1953, are being erected by the Bell Telephone Co., and will permit an interchange of Canadian and U.S. programmes. Each of the fifteen relay stations will be equipped with two pairs of 10-ft square horn radiators. The television stations in Montreal and Toronto will not be ready for some time, although the Marconi studio and O.B. equipment for them was shipped some time ago.

Radio Officers' Pensions.—A supplementary non-contributory pension scheme for radio officers in the employ of the company is announced by the Marconi International Marine Communication Co. The scheme is independent of the Merchant Navy Officers' Pension Fund and National Health Insurance pensions, and is open to radio officers who joined the company prior to January 1st, 1937, and will be 65 before 1978.

S.W. Listening Contest.—This year's short-wave listening competitions, organized by the International Short-Wave Club, will be held during the second and third week-ends in February. Full particulars of the competition, which covers the reception of both amateur and short-wave broadcasting stations on the African continent, are obtainable from A. E. Bear, I.S.W.C., 100, Adams Gardens Estate, London, S.E.16.

B.B.C. Reception.—The mobile transmitter brought into use by the B.B.C. on December 23rd—the seventh of the twelve low-power stations to improve reception of the Home Service—is set up in Folkestone and not Eastbourne as stated erroneously last month.

Manchester Television Centre.—With a view to forming a Manchester Centre of the Television Society, a meeting will be held at 3.0 on February 9th in the Milton Hall, 244, Deansgate, Manchester, 3. Following the discussion regarding the formation of the Centre, a talk entitled "The Television Aerial and its uses," will be given by L. D. E. Perkins (Belling-Lee). Particulars are available from R. Lawton, 10, Dalton Avenue, Whitefield, Nr. Manchester.

INDUSTRIAL NEWS

Emitron valves and cathode-ray tubes, made by Electronic Tubes, Ltd., of High Wycombe, Bucks (a subsidiary of E.M.I.), are now available to the public through the normal channels. They have so far been available only to set makers.

Ediswan-Clix Amalgamation.—The Edison Swan Electric Co. announces that it has acquired the share capital of the General Accessories Co. and British Mechanical Productions, Ltd. All G.A.C./Clix products will be marketed through Ediswan distribution channels.

Columbia-Philips Agreement.—Philips Phonographic Industries, Baarn, Holland, has reached agreement with Columbia Records Incorporated, U.S.A., to co-operate on a world-wide basis for the exploitation of their record libraries, with effect from January 1st, 1953.

Mullards have opened a valve and c.r.t. service depot at Berry Lane,

Halifax (Tel.: Halifax 5722), to serve retailers and service technicians in the North of England.

S.T.C.—The London sales office and warehouse of the Rubber & Plastic Cables Division of Standard Telephones & Cables has been transferred to 48, North Row, Mayfair, W.1 (Tel.: Mayfair 4392).

Sobell Service.—New Service depots have been opened by Sobell Industries at Room 15, Regent House, Cannon Street, Manchester, and 135, Renfield Street, Glasgow (Tel.: Douglas 6061). The company's Birmingham depot has been transferred to Emitron House, 117, John Bright Street, Birmingham (Tel.: Midland 2574/5).

Rola Celestion, Ltd., of Thames Ditton, Surrey, announce that the retail distribution of their loudspeakers will in future be handled by the associated company, Truvox, Ltd., Exhibition Grounds, Wembley, Middx. (Tel. Wembley 1212), who will also deal with the repair of speakers.

F. Livingston Hogg has notified us that the Livingston Laboratories are now at Retcar Street, Dartmouth Park Hill, London, N.19 (Tel.: Archway 2442), where all his activities will be concentrated.

Hunts.—So that the registered name of the company includes a reference to its products A. H. Hunt has adopted the name A. H. Hunt (Capacitors), Ltd.

Jay Developments is being formed by Sphere Radio, Ltd., Heath Lane, West Bromwich, to undertake the manufacture of Jay miniature silvered ceramic capacitors. A new factory is in course of erection at Bromford Lane, West Bromwich. Leaflet No. 52 gives data and specifications for these and other types of capacitors.

Du Bois Co.—Shipments of Tri-Sol activated resin cored solded during a recent period of six weeks included 20 tons to the Argentine and 10 tons to Brazil.

Coulphone Radio has now closed down and any communications should be addressed to J. B. Coulborn, Sea View House, St. Bees, Cumberland.

MEETINGS

Institution of Electrical Engineers

Faraday Lecture on "Sound Recording—Home, Professional, Industrial and Scientific Applications," by G. F. Dutton, Ph.D., B.Sc.(Eng.), at 6.30 on February 12th, at the Central Hall, Westminster, London, S.W.1. (Tickets must be obtained from the I.E.E.)

Radio Section.—"Factors Affecting the Design of the Automatic Electron Trajectory Tracer," by K. F. Sander, M.A., Ph.D., C. W. Oatley, M.A., M.Sc., and J. G. Yates, M.A., on February 13th.

Debate on the motion, "In the opinion of this House, the lone worker can no longer make a major contribution to Radio Development" on February 25th. Proposer, Geoffrey Parr; Opposer, M. G. Scroggie, B.Sc.

The above meetings will be held (except where otherwise stated) at 5.30 at the I.E.E., Savoy Place, London, W.C.2.

East Midland Centre.—Junior Members' Night at 6.30 on February 26th at Loughborough College.

Western Centre.—"The Sutton Coldfield Television Broadcasting Station," by P. A. T. Bevan, B.Sc., and H. Page, M.Sc., at 6.0 on February 11th, at the South Wales Institute of Engineers, Park Place, Cardiff.

Scottish Centre.—"The London-Birmingham Television Radio-Relay Link," by R. J. Clayton, M.A., D. C. Espley, O.B.E., D.Eng., G. W. S. Griffiths and J. M. C. Pinkham, M.A., at 7.0 on February 13th, at the Heriot-Watt College, Edinburgh.

North Eastern Radio & Measurements Group.—"An Investigation into the Mechanism of Magnetic Recording," by P. E. Axon, O.B.E., M.Sc., on February 4th.

Address by D. C. Espley, O.B.E., D.Eng., chairman of the Radio Section, on February 18th.

Both meetings will be held at 6.15 at King's College, Newcastle-upon-Tyne.

Cambridge Radio Group.—"Colour Television," by L. C. Jesty, B.Sc., at 6.0 on February 5th, at the Cambridgeshire Technical College.

British Institution of Radio Engineers

London Section.—"Search Radar for Civil Aircraft" by P. L. Stride (Ekco) at 6.30 on February 20th at the London School of Hygiene and Tropical Medicine, Keppel Street, London, W.C.1.

Scottish Section.—"Some Special Oscillograph Techniques" by Prof. F. M. Bruce, M.Sc., Ph.D. (followed by visit to the Electronics Laboratory) at 7.0 on February 7th at the Royal Technical College, Glasgow.

"The Clerk-Maxwell Memorial Lecture" by Prof. G. W. O. Howe, D.Sc., LL.D., at 7.0 on February 14th at the Natural Philosophy Department, The University, Edinburgh.

"V.H.F. Broadcasting" by Paul Adorian, at 7.0 on February 27th, at the Institution of Engineers and Shipbuilders, Glasgow.

North Eastern Section.—A symposium of papers by Student Members at 6.0 on February 13th at Neville Hall, Westgate Road, Newcastle-upon-Tyne.

South Midlands Section.—"Gas Discharge Devices as Switching Elements" by E. A. R. Peddle, B.Sc. (G.E.C. Research Laboratories) at 7.15 on February 13th at Corporation Street Civic Restaurant, Coventry.

West Midlands Section.—"Valve Manufacture," by C. C. Vodden, M.Sc., at 7.15 on February 26th at Wolverhampton and Staffordshire Technical College, Wolverhampton.

Television Society

London Section.—"In Search of the Perfect Raster" by P. J. Edwards (P.O. Eng. Dept.) on February 14th.

"Television Receiver Design" by J. E. Hillyer and A. E. Howard (Plessey) on February 29th.

Both meetings will be held at 7.0 at the Cinematograph Exhibitors' Association, 164, Shaftesbury Avenue, London, W.C.2.

British Sound Recording Association

Portsmouth Centre.—Annual General Meeting. "Development of Tape Recorders" by J. Collinson at 7.30 on February 14th at the Central Library, Guildhall Square, Portsmouth.

Institute of Practical Radio Engineers

Thames Valley Branch.—"Interference on Television Wavebands" by C. W. Cobb and F. Clarke (G.P.O. London Telecommunications) at 8.0 on February 5th at the Wheatsheaf Hotel, Kingston Market Place, Kingston-on-Thames, Surrey.

Institute of Navigation

"Navigation Aids for Military Aircraft" by Sqn. Ldr. D. Bower at 5.0 on February 15th at the Royal Geographical Society, 1, Kensington Gore, London, S.W.7.

Institution of Electronics

North Western Branch.—"Development in Multi-Range Electronic Measuring Instruments" by S. R. Wilkins, M.Brit.I.R.E., Assoc.I.E.E. (Avo) at 7.0 on February 20th at the College of Technology, Manchester.

Electro Physiological Technologists' Association

General Meeting with papers and demonstrations at 10.30 on February 9th at the Maida Vale Hospital, London, W.9.

RECORDINGS being made on an E.M.I. magnetic-tape recorder at the receiver-testing bench at the company's Hayes factory for the B.B.C's overseas programme "A Good Job", which recently featured the radio industry.

VORTEXION

High Quality Reproduction

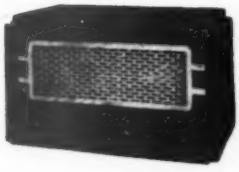

"FIFTY and THIRTY WATT" CINEMA AMPLIFIERS as illustrated for single or double P.E.C. input with separate adjustable bias. Full range of tone controls to suit all needs with built-in Exciter Supply if required.

TYPE C.P. 20A AMPLIFIER For AC Mains and 12 volt working giving 15 watts output, has switch change-over from AC to DC and "Stand-by" positions. Consumes only 5½ amperes from 12 volt battery. Fitted with mu-metal shielded microphone transformer for 15 ohm microphone, provision for crystal or moving iron pick-up with tone control for bass and top. Outputs for 7.5 and 15 ohms. Complete in steel case with valves.

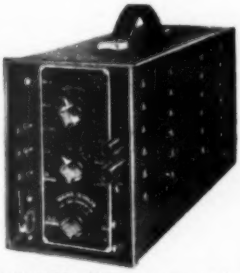

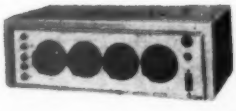

FOUR-WAY ELECTRONIC MIXER This unit has 4 built-in balanced and screened microphone transformers, normally of 7.5–30 ohms impedance. It has 5 valves and selenium rectifier supplied by its own built-in screened power pack consumption 20 watts. Suitable for recording and dubbing, or large P.A. Installations since it will drive up to six of our 50 watts amplifiers whose base dimensions it matches. The standard model has an output impedance of 20,000 ohms or less and any impedance can be supplied to order.

OTHER MODELS IN OUR RANGE OF AMPLIFIERS ARE

"SUPER-FIFTY WATT"
"THIRTY WATT"
"10-15 WATT RECORD REPRODUCER"

These are fitted in well ventilated steel cases with recessed controls, as illustrated.

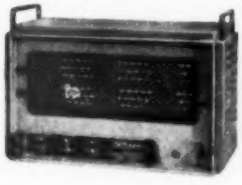

Full details upon request.
Export enquiries invited.

VORTEXION LTD.,

257-261 THE BROADWAY, WIMBLEDON, LONDON, S.W.19

Telephones: Lib 2814 and 6242-3 Telegrams: "Vortexion, Wimble, London."

SenTerCel

rectifiers

for the radio industry

WHEREVER a radio or television diagram shows a rectifier operating at 0.5 Volts or higher, at a frequency below 5 mc/s, *there is almost certain to be a* ***SenTerCel*** *Selenium Rectifier* which will do a better job because it :

1. **Saves space and weight.**
2. **Reduces wiring.**
3. **Withstands an unlimited instantaneous overload.**
4. **Reduces heat dissipation.**
5. **Needs no "warming-up" period.**
6. **Saves the cost of a valveholder.**
7. **Is practically indestructible in service.**
8. **Imposes no limit on the size of the reservoir capacitor.**
9. **Is low in cost.**

Please write for leaflets F/SRL9 9a, 10, 11

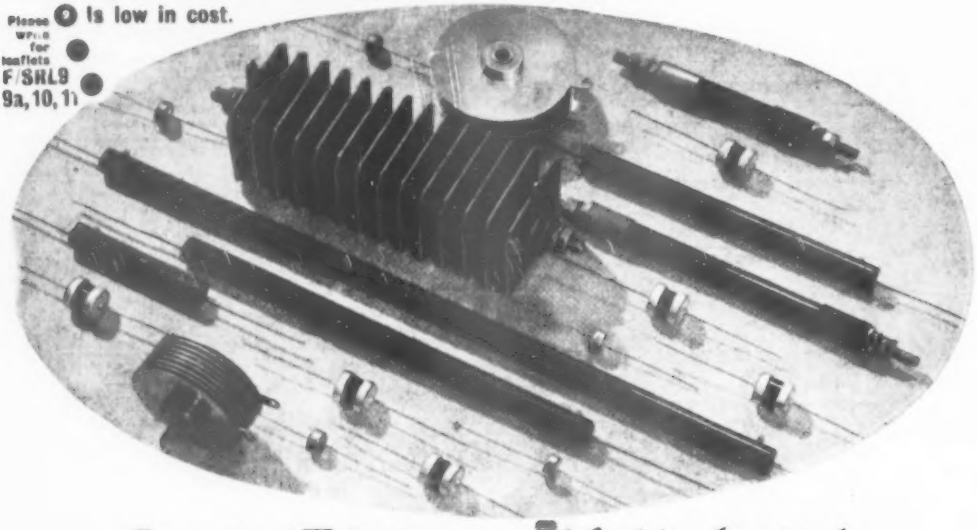

Standard Telephones and Cables Limited

Registered Office : Connaught House, Aldwych, London, W.C.2

RECTIFIER DIVISION : WARWICK ROAD : BOREHAM WOOD : HERTS
Telephone : Elstree 2401 *Telegrams : SenTerCel Borehamwood*

SELENIUM SenTerCel RECTIFIERS

EQUALIZATION

How to Find the Right Values for Tone-correcting Circuits

By "CATHODE RAY"

WHAT are commonly called tone controls and tone correction circuits are known by the professionals as *equalizers*, because they are meant to make the overall gain of an amplifying system equal at all frequencies. For instance, if Fig. 1(a) is the frequency characteristic of, say, a sound recorder, it can be put right by an equalizer with a characteristic like Fig. 1(b). The overall result, seen by adding the two together (c), is flat.

A great deal of information has been issued about this sort of thing. But unless one is exceptionally good at calculations and electrical circuit theory, putting it into practice is hard work, and slow too. Judging by the advertisement pages during the last few months, there must be a good many people beginning to take an interest in sound recording in general and tape recorders in particular. The frequency characteristic of the recording head and tape is so very far from flat that considerable equalization is quite essential. The gramophone enthusiasts have been familiar with the same sort of problem for quite a while. And in the form of pre-emphasis it crops up in frequency modulation. Tone controls are useful in radio receivers and many other kinds of amplifiers. So altogether this subject must concern a largish percentage of *Wireless World* readers. But there seems to be a gap between those who are content to follow cut-and-dried circuits and those who can work everything out for themselves from first principles. Is it possible to find suitable component values for correcting given departures from the flat without spending a lot of time performing intricate calculations?

Well, I have recently been devising an amplifier for a tape deck, and quite frankly I couldn't spare the time to work out the equalizing circuits to a fraction of a decibel in the approved manner. The method I did use can be explained in one article; and having a suitable audio oscillator and output meter I was able to check that the results were quite good enough for practical purposes. The method is applicable, of course, to other systems than tape recorders, and even to r.f. circuits such as detector output filters.

Before we get down to some examples it would

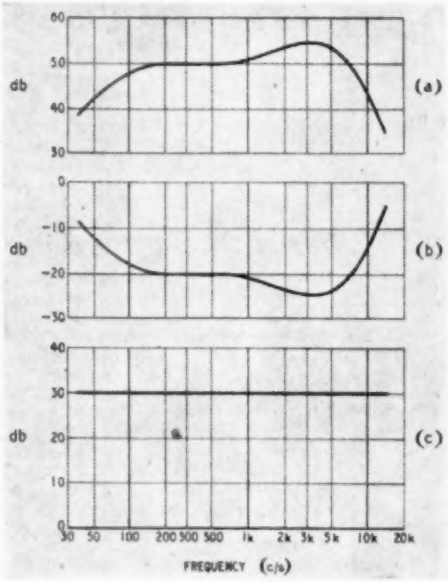

Fig. 1. (a) Example of a hilly frequency characteristic to be equalized; (b) required frequency characteristic of equalizer; and (c) extremely satisfactory result of adding (b) to (a).

(Below left) Fig. 2. 6db rise at the low-frequency end would be unlikely to cause frequency distortion, but it might easily cause non-linearity distortion by overloading the output stage because it is double voltage and fourfold power.

(Below right) Fig. 3. Frequency characteristics obtained by passing a constant current through resistance and the two kinds of reactance. There is no significance in the zero position of the db scale; the only purpose of the scale is to show the slope of the reactance lines—6db per octave.

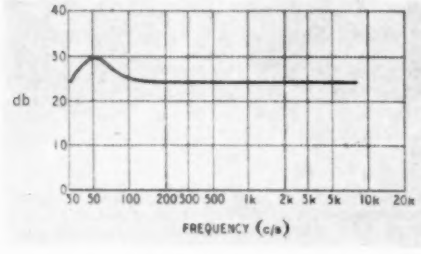

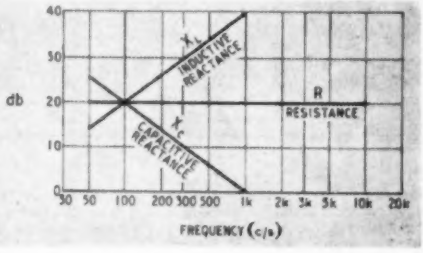

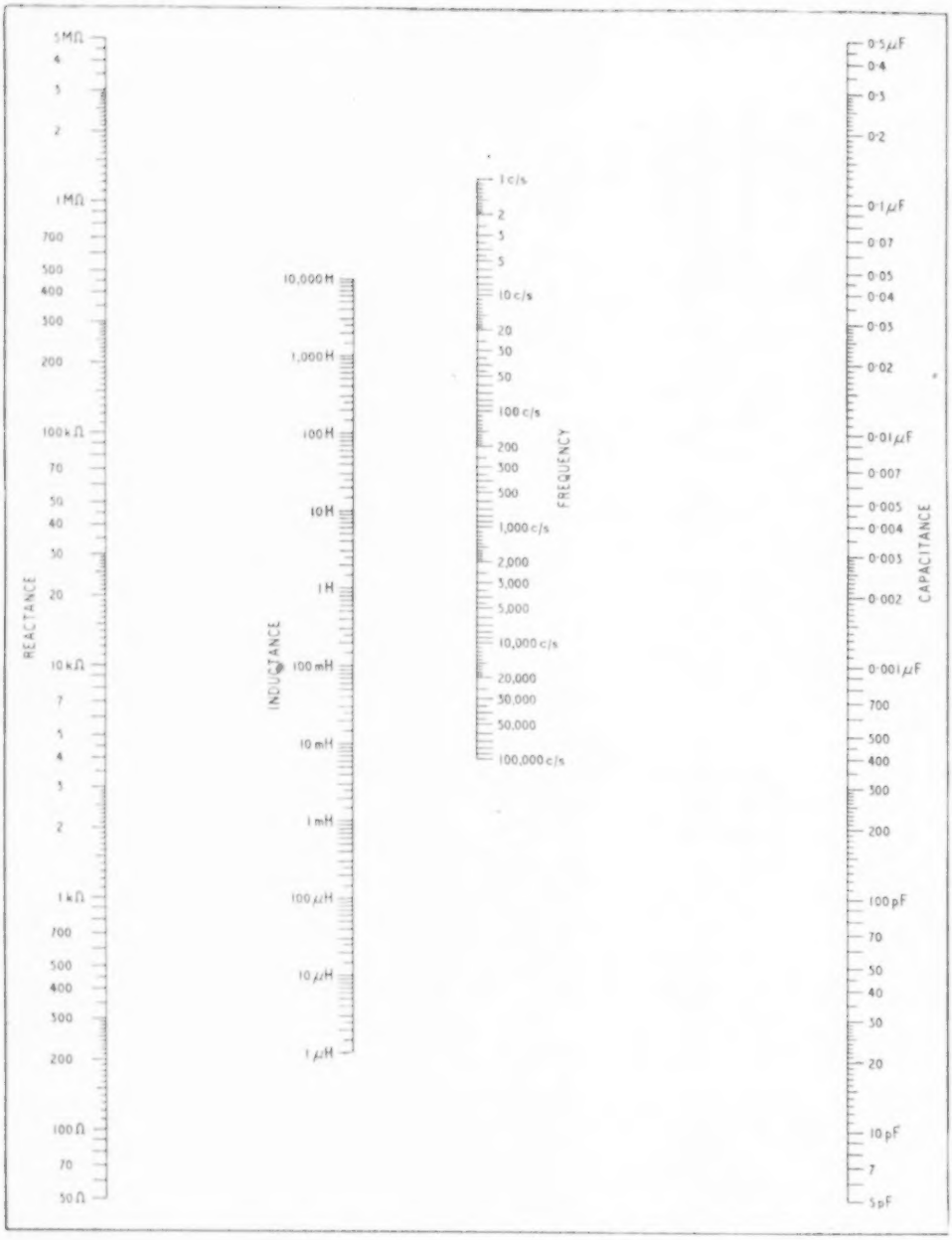

Fig. 4. By using a stretched thread or ruler edge to pass a straight line through any values on two of the scales (such as a capacitance and a frequency) the same line points out the corresponding values on the other scales (such as the reactance of that capacitance at that frequency, and the inductance which would tune that capacitance to that frequency).

probably be a good thing to pick out and remind ourselves of those principles that we are going to employ.

Perhaps we should start by asking why we want a flat frequency characteristic at all. The stock answer is that anything else is what is commonly called frequency distortion, so of course we want flatness. But while one could not deny that that is theoretically correct, it misses the point. To criticize an amplifier whose frequency characteristic shows a bump or hollow of a db or two, on the ground that it would introduce frequency distortion, shows a lack of practical understanding. For it is a kind of distortion that is accepted daily without a thought, being in fact quite inevitable. However perfect the amplifer and other reproducing equipment, and even if they are abolished altogether by bringing the source of sound into the same room as the listener, the reflections from the walls make the overall frequency characteristic look like a panorama of the Alps. So if the amplifier has a slight uneveness here or there in its characteristic it is just about as likely to improve the overall result as to make it worse.

But that is no excuse for going to the other extreme and not bothering at all about the frequency curve. The ideal of flatness is quite right, but the most important reason is not to avoid frequency distortion but *non-linearity* distortion. That may sound strange. But look at Fig. 2, for example. The 6db bump in the extreme bass might well improve the overall frequency characteristic by helping to compensate for the falling off that is typical of most loud speakers below about 80c/s. If so it could hardly be condemned for causing frequency distortion. But consider what will happen in the output stage if one attempts to run it at its full rating. Any very low-frequency full-amplitude sounds, such as one gets in organ music, will apply double the maximum allowable signal voltage to the grid, causing large quantities of the worst kinds of distortion. Alternatively, if one cuts down the volume until the bump comes within the acceptable distortion limit, the power output is reduced to one quarter, so that what should be perhaps a 4-watt output stage is reduced to an effective 1-watt rating (so long as the programme is liable to contain strong low notes).

For this and other reasons it is wise to aim as far as possible at a flat frequency characteristic, not only for the system as a whole but for each part of it separately. A droop of a few db at each end may not matter much in one link of the chain, but it is a common tendency in every one of them, and if tolerated the separate slight droops may add up to so many db that the loss is really serious and the frequency distortion can no longer be disguised by the inevitable irregularities of listening conditions.

But when it is necessary to include something whose nature it is to depart seriously from the straight and level, then one must make the best of it with tone correction. To avoid the overloading or power-limiting trouble it is advisable to do what is necessary at a low-level stage in the system, particularly if the correction is considerable—say 10db or more.

The basis of tone correction is the fact that reactance (unlike ordinary resistance) varies with frequency. Inductive reactance is directly proportional to frequency, and capacitive reactance is inversely proportional. If a certain alternating current is passed through a resistance, the voltage across it is the same at all frequencies. The resistance can be said to have a flat frequency characteristic. But if the current is passed through a reactance, the voltage rises or falls with frequency, depending on whether the reactance is inductive or capacitive. If inductive, doubling the frequency doubles the voltage; if capacitive it halves it. When it is frequency that is doubled (or halved) the usual way of expressing it is to say it is raised (or lowered) an octave. And when it is signal level that is doubled (or halved) the usual way of expressing it is to say it is raised (or lowered) 6db. Therefore if the current through a reactance is kept constant at all frequencies, the voltage across it varies 6db per octave. The basic characteristics of resistance and the two kinds of reactance are compared in Fig. 3. These are the raw materials of tone correction, the art of which consists in blending them to get the desired effects.

Simple Example

A tremendous amount of time and effort is saved in all this sort of work by making use of an abac or nomogram due to the late W. A. Barclay and reproduced (with modifications) as Fig. 4. This, and a similar one connecting voltage, resistance, current and power, together make a comprehensive guide to choice of components. As you see, Fig. 4 has scales of reactance, inductance, frequency, and capacitance; and if the values of any two of these are known the corresponding other two can at once be found simply by laying a straightedge across the scales. A piece of thread will do, but I prefer a strip of Perspex or other transparent material with a fine straight line scratched down the centre. Somewhat similar abacs, covering audio and radio frequencies separately and so having rather clearer scales, are included in "Radio Data Charts, 5th Edition, by J. McG. Sowerby; the audio one is No. 22.

Clearly, if the characteristic to be equalized happens to slope 6db per octave it can be compensated by using the signal voltage developed across a reactance. But it must be remembered that the necessary condition is that the current must remain the same at all frequencies regardless of the variations in reactance. Theoretically this necessitates a signal source of infinite resistance, but in practice it is usually enough to derive it from an r.f. pentode, having an r_a of one or two megohms. It may even be good enough to connect a relatively high resistance in series with the reactance. Of course, this means that only a small fraction of the available signal voltage can actually

Fig. 5. Example of an equalizing circuit consisting of a stage of amplification in which the usual resistance coupling is replaced by inductive reactance. The result is Fig. 6.

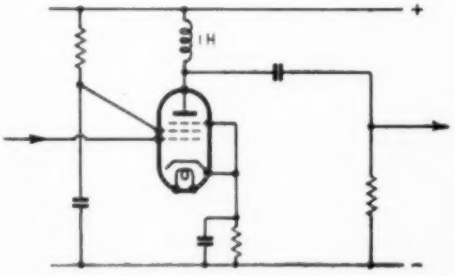

be used. So the amplification of the stage is largely or even wholly thrown away. It may be necessary to have one or possibly more than one stage for tone correction only, over and above those needed for amplification.

To take a simple example, suppose the usual coupling resistor in a typical amplifier stage is replaced by a coil of, say, 1 henry (Fig. 5). The g_m of a suitable high-resistance valve might be 1.5mA/V, and its r_a 2MΩ. So long as the coupling impedance is well below this, a practical approximation for the voltage gain of the stage is obtained by multiplying the impedance (in kΩ) by the g_m (in mA/V). At 1,000c/s, say, the impedance of a reasonably low-resistance coil would be almost entirely reactance, and can be found from $X = 2\pi f$, or by using Fig. 4; and in this case comes to 6.28kΩ. So the voltage gain at this frequency is $6.28 \times 1.5 = 9.4$, or 19.5db. There is no need to work it out for other frequencies, because it rises with frequency at 6db per octave. At least, within limits. When, towards the low-frequency end, the reactance of the coil falls until it is no longer much larger than its resistance, the slope gradually flattens out. And at the high-frequency end a point will be reached when the reactance is no longer much less than the source resistance, r_a, and again the slope will flatten out, as in Fig. 6.

If the characteristic to be equalized flattens out somewhere, the aim must obviously be to proportion reactance to resistance so as to make the equalizer fit. That may be the point at which some people fear they are getting out of their depth. If so, good! Because I hope to be able to show that it is really quite easy.

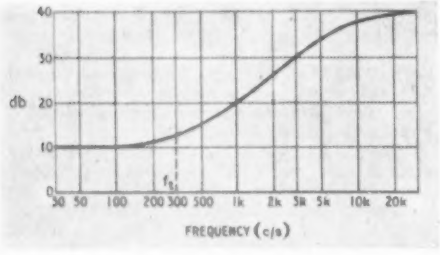

Fig. 6. Type of frequency characteristic obtained by Fig. 5.

Fig. 7. Enlarged view of the bend in Fig. 6. This shape of bend is standard for all non-interacting circuits having resistance and one kind of reactance.

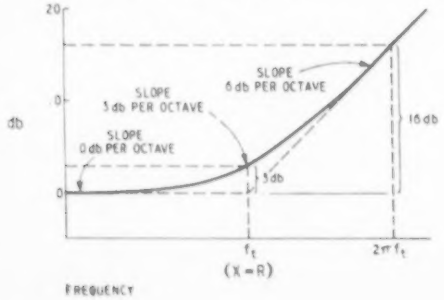

Looking at Fig. 6 again, we see that at the extreme left the curve is flat, due to the fact that the reactance of the coil is so small that it is negligible compared with its resistance. In effect, then, one has a resistance coupling of low gain. At the middle frequencies the reactance swamps the resistance and provides the standard slope of 6db per octave. Around the frequency marked f_t the curve is neither one thing nor the other; the two parts gradually merge. Now this is the key to the whole situation: *f_t stands for what I call the turning frequency, because the slope is halfway—3db per octave—and it is the frequency at which the resistance and reactance are equal.* It is also 3db above the point at which the level and sloping parts would meet if produced, so it is fair to think of f_t as the frequency at which the effect of the reactance is beginning to be noticeable. All this can be seen more clearly in Fig. 7, which is a magnified view of the bend. No calculation of any kind is needed, for f_t can be read off from Fig. 4, given the resistance and inductance (or capacitance); and all the particulars of the situation are delightfully easy to remember.

Designing a Bass Lifter

What is usually wanted, of course, is the value of inductance or capacitance needed to put f_t in the right place, and that is just as easily found. A good example to work out is a bass lifter to compensate for the loss which occurs in the making of disk records and which usually amounts to 15db at 50c/s, sloping off at 6db per octave. What happens below 50c/s is rarely of more than academic interest, because few reproducing equipments are capable of handling full level there even if it were provided. So we shall assume that the slope can be allowed to flatten out when it reaches 15db above the general level.

We need the opposite kind of slope to Fig. 6, so the coil will have to be replaced by a capacitor. And as that alone is incapable of feeding anode current, some conductive path having a relatively high impedance at all concerned frequencies must be provided in parallel. Fig. 4 shows that a coil to have a reactance of 100kΩ at 50c/s would have to be about 320H, and with so many turns would probably need a Mumetal case for keeping out hum, and altogether would be much bulkier and more expensive than a 100-kΩ resistor. Much more resistance than 100kΩ would not bring anything like a proportionate gain, because it would reduce g_m; and much less would bring unnecessarily little. For remember that even at 50c/s the real coupling element—the capacitor—should have a substantially lower impedance than the feed resistor if the 6db per octave slope is to be maintained up to or nearly up to that frequency. Allowing for the fact that resistances and reactances add up at right angles to one another, 30kΩ should be ample. Fig. 4 shows the nearest stock capacitance is 0.1μF, which is 32kΩ at 50c/s. With a 1.5mA/V valve, the 50-c/s voltage gain (neglecting the small loss due to the 100-kΩ shunt and the grid leak of the following valve) is $32 \times 1.5 = 48$, which is a little over 33db. This falls off at 6db per octave, and after dropping 15db should be level. So for the rest of the frequency scale we want a resistance coupling giving a gain of about 18db, which is a voltage gain of 8. This is g_m times the required resistance, which is therefore 5.3kΩ. Having neglected some items at 50c/s we know this to be an

overestimate and would have no hesitation is rounding it off to 5kΩ. So the required circuit is Fig. 8. Here the coupling has been connected to −h.t. instead of +h.t. so as to avoid making most of the signal currents go through the h.t. source, but it is nevertheless effectively in parallel with the anode feed resistor.

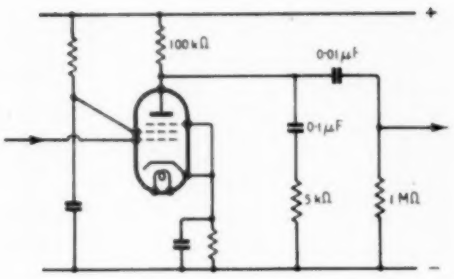

Fig. 8. Circuit designed as described, to compensate for loss of bass in gramophone recording.

Using the Abac

You may think the foregoing procedure is not so very simple, and I agree. I shall now show how I would do it. Anybody who knows enough about recording characteristics to be wanting to do this job at all would know that the bend of the curve is round about 250-300c/s. This is where resistance and reactance should be equal. Pivoting the line about that frequency on Fig. 4, one looks for a standard capacitance value in line with a suitable number of ohms. 0.05μF (which requires 10 or 12 kΩ) might be considered, but its reactance at 50c/s is seen to be 60kΩ, which is getting rather too near 100kΩ for the feed shunting to be neglected. So 0.1μF (generally an easier value to buy) and 5 or 6kΩ is an obvious choice. With Fig. 4 the whole process takes perhaps half a minute. And the result, Fig. 9, is quite good enough.

Of course, one has to make sure that the 50-c/s boost is not being lost because of inadequate blocking capacitance in relation to the grid leak resistance. This resistance would probably be at least 0.5MΩ so as not to shunt the anode feed resistance too much. Say 1MΩ. The blocking capacitance, being in series, tends to cut off the very low frequencies. But the loss at 50c/s will be negligible if the turning frequency is, say, 20c/s. Fig. 4 shows that the capacitance which equals 1MΩ at 20c/s is 0.008μF, so the next larger stock value—0.01μF—would do nicely.

And what about the very high frequencies? The output capacitance of one valve, plus the input capacitance of the next valve, plus the stray capacitances of valve holders, resistors, capacitors, and wiring, might be estimated at 30pF (it need not be more if the wiring is reasonably intelligent). It comes in parallel with, say, 5kΩ at the high-frequency end. Fig. 4 shows the corresponding turning frequency (where the loss due to strays would be 3db) is above 100kc/s. So it is hardly enough to worry about at audio frequencies, even of the "hi-fi" order! But if one were attempting high gain in a straight amplifying stage, with 250kΩ coupling resistance feeding into a triode, whose Miller effect brought the effective stray capacitance up to 150pF, the turning frequency would be about 4kc/s, which is quite another matter.

Fig. 9. Freqency characteristic of Fig. 8., including effects of 100-kΩ feed resistor, 1-MΩ grid leak, and 0.01-μF blocking capacitor.

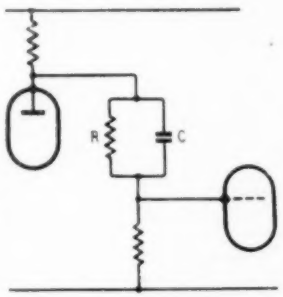

Fig. 10. Another example of tone-correcting circuit, in which the reactance is in series with the source. This is a common method of boosting the top frequencies.

Pre- and De-emphasis

Armed with Fig. 4 (or its equivalent) and the f_t idea, one has only a few minutes work to find suitable component values for amplifier circuits, putting in deliberate frequency distortion where it is required and avoiding it where it is not. Even if the values are only required as a basis for experiment, it saves an awful lot of time to have them nearly right from the start. Of course, one needs some practice to tackle the more complicated requirements with confident speed. So far we have been conveniently assuming that the slope to be corrected is 6db per octave. Often, as in f.m., that slope (pre-emphasis) is due to a tone circuit of the kind we have been considering, so will not only have the right gradient but also a bend shape that can be exactly fitted by the equalizer. As I explained some while ago* it is the custom among f.m. types to reckon emphasis (pre- and de-) in microseconds. There is something to be said for this, because the number of microseconds is equal to L/R (in microhenries and ohms) in the pre-emphasis circuit and CR (in microfarads and ohms) in the de-emphasis circuit. For instance, to correct the usual 50 microseconds of pre-emphasis one needs 50 microfarad-ohms in the receiver; so if 1MΩ is a suitable resistance the capacitance to go with it must be 50pF. *If you divide one million by the number of microseconds you have the frequency at which the rise or fall amounts to*

* "Pre-emphasis and De-emphasis," May, 1947.

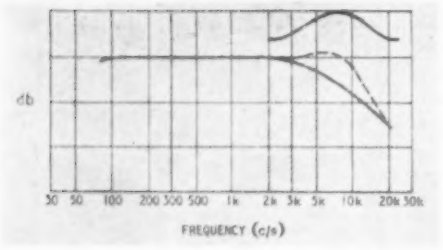

Fig. 11. A blunt resonance curve, added to a frequency characteristic with a droop, is useful for building out a shoulder, as shown dotted.

16db—so in this case it would be 20,000 c/s. And this 16db frequency links up with our f_t scheme because it happens to be $2\pi f_t$. So the turning frequency for a 50-microsecond circuit is 20,000 divided by 2π (roughly 6), or 3,200c/s. But note that what I have just said in italics applies only to the sorts of circuit that come into effect with increasing frequency, such as L and R in series for pre-emphasis, or C and R in parallel for de-emphasis. For those that work with falling frequency—such as Fig. 8—the 16db frequency is not $2\pi f_t$ but $f_t/2\pi$. There is no catch like this with my f_t 3db clue, which applies to all kinds of resistance/reactance tone circuits, including some I have not mentioned, such as Fig. 10, where the tone circuit CR is on the "source" side, and boosts the signal at the upper frequencies. The simple turning-frequency fact is not only easier to remember and (with Fig. 4) to use, but is safer.

But the slope to be corrected does not always chance to be 6db per octave. If it is 12, the solution is obviously to have two correcting stages. And if it is not exactly a multiple of 6 but is fairly close, a little over- or under-correction will probably not be noticed by ear. Remember, too, that the slope flattens out again where the infinite-source-impedance condition begins to break down, as in Fig. 9, and with a little jugglery a double-bend curve which is 6db per octave at its steepest can be made to compensate reasonably well for, say, a 4db slope.

If no combination of simple resistance/reactance pairs yields the desired result it may be necessary to use both kinds of reactance at once to form a tuned circuit. This is particularly useful when one wants to prolong a flat characteristic at one end and then let it cut off sharply, as in Fig. 11. An advantage of Fig. 4 over the kind of abac in "Radio Data Charts" is that at one stroke it shows both capacitance and inductance needed to tune to a given frequency, and also their reactance (which, of course, is equal at that frequency). This reactance value gives some guidance to the amount of resistance the circuit should have, for it should not be much less than the reactance, otherwise the circuit will resonate sharply; and while this may be useful for producing a steep slope in one stage it is generally unwise because of the transient distortion it causes.

Still another device is negative feedback with reactance in the feedback circuit. But we are getting right beyond *simple* tone correction. So let me summarize my recommended procedure, which can be made to cope with most of the situations one actually comes across:—

(1) Examine the frequency characteristic to be equalized, and see if it can be analysed into horizontal and 6 (or 12, or 18) db per octave sections. If so, note the turning frequencies.

(2) Sketch out circuits with reactances to give slopes in the opposite directions.

(3) Use Fig. 4 with the straightedge pivoted at the turning frequency, to find the reactance to go with a resistance that gives the right level for the adjoining flat section.

ADHESIVE RESISTORS

A NEW type of resistor has been developed by the American Bureau of Standards for use on printed circuit units. It consists of a strip of asbestos paper sprayed with a mixture of graphite or carbon black and silicone resin. This composition is slightly adhesive and is protected, prior to the actual use of the resistor, by a thin film of polyethylene.

Strips cut to the required size are stuck on to the printed plates and then subjected to a heat treatment involving temperature of the order of 300 deg C, which not only hardens the graphite-resin mixture but also causes it to adhere firmly to the silvering on the printed circuit plate. Resistance values can be varied over wide limits by changing the graphite or carbon content of the mixture.

Owing to the high processing temperature these resistors are only suitable for use on ceramic or other heat-resisting base plates. Investigation is well under way with lower temperature processes and it is expected that it will soon be possible to produce adhesive strip resistor suitable for the more commonly used types of plastic materials.

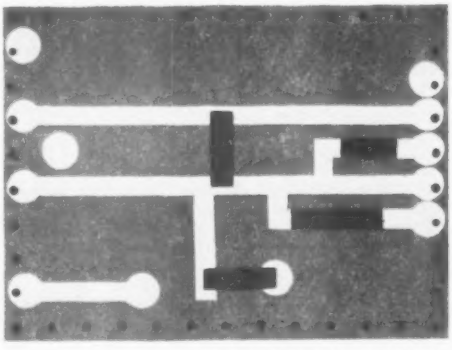

Courtesy Nat. Bureau of Standards, U.S.A.

Typical printed circuit showing adhesive tape resistors bridging gaps in the "wiring." Reproduced from "National Bureau of Standards, Technical News Bulletin."

MARCONI

serves

mankind

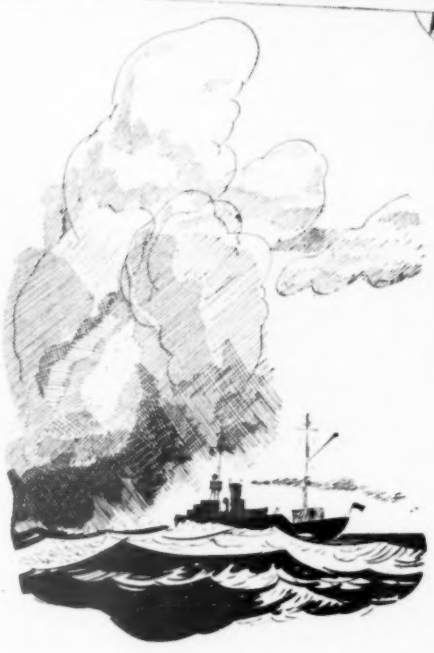

When Marconi died, one tribute said of him "What other men had been content to prove impossible, he accomplished". From simple beginnings his inventions in wireless have been extended to hundreds of activities. Every weather-ship report, every wireless-bearing taken from a flying-boat and every radio programme broadcast traces back to the pioneer who put his genius at the service of mankind.

MARCONI'S WIRELESS TELEGRAPH COMPANY LTD · CHELMSFORD · ESSEX

THE GREATEST ADVANCE TOWARDS PERFECT REPRODUCTION

AM ING

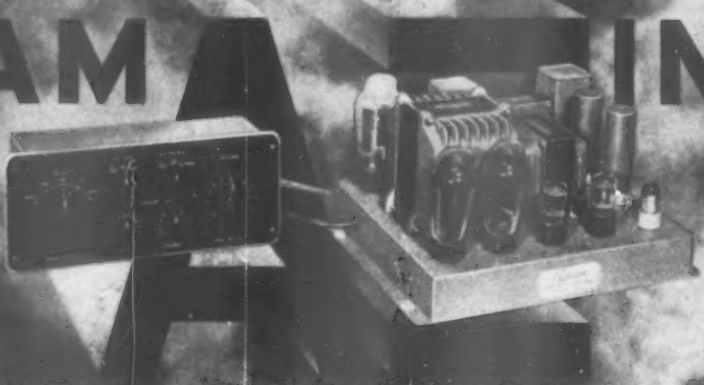

THE NEW TONE COLOUR UNIT PLUS THE AZ TYPE AMPLIFIER £32.10.0

SOUND SALES LIMITED
DEMONSTRATIONS at our London Showroom:
LLOYDS BANK CHAMBERS, 125 OXFORD STREET, W.1 (Entrance in Wardour Street)
Telephone: GERrard 8782
(Works: West Street, Farnham, Surrey. Telephone: Farnham 6461)

N.P.L. CERTIFIED PERFORMANCE

WESTON *Test Sets*

High sensitivity, wide range coverage, robust construction and simplicity in operation have established "Weston" as the pre-eminent instruments for the testing and servicing of radio and television equipment and also for laboratory and research work. Full details will gladly be supplied on request.

ABOVE *Weston Model S.75. 53 ranges for measuring A.C. and D.C. current and voltage, resistance and insulation.*

RIGHT *Weston Model E.772 Analyser. Sensitivity as on Model S.75—namely 20,000 ohms per volt on all D.C. ranges and 1,000 ohms per volt on A.C.*

SANGAMO WESTON LIMITED
ENFIELD, MIDDLESEX
Tel: Enfield 3434 (6 lines) & 1242 (4 lines) Grams: Sanwest, Enfield
Branches: Glasgow, Manchester, Newcastle-on-Tyne, Leeds, Liverpool, Wolverhampton, Nottingham, Bristol, Southampton, Brighton.

Is *Information Theory* of any Practical Use?

ALTHOUGH modern Information Theory owes its existence mainly to the efforts of communication engineers, it is now being applied to many other branches of science in which transmission of information is a vital function. Physiologists, computing and radar engineers, statisticians, mathematicians, neurologists, physicists, psychologists, phoneticians and economists are all discovering that it has something for them. As a result, this strange child of the older Communication Theory (Hartley Law and all that) has now grown out of all recognition and communication engineers are beginning to look at it with the perplexed eye of a father who wonders whether he really was responsible. In fact, they are beginning to ask themselves whether this block off the old chip is now of any real practical use to them.

Information Theory is not in any way concerned with the meaning, value or truth of messages. It regards information merely as a commodity, and defines it simply as a change in what is already known —whether that change is in the sequence of symbols of a code message or in the structure of a waveform carrying speech, music or television images. Thus the amount of information received is proportional to the "amount of change" it has caused, and since this change can be measured the information is put on a quantitative basis.

One type of unit in which information is measured is the *logon*—the smallest possible change that has any effect on what is already known. Another one is the *bit* or *binary digit*. This comes from the notion that any message transmitted down a channel has been selected from a finite number of possibilities by a series of simple yes-no choices, as in the binary code.

This selection idea is very important in Information Theory. Modulation, for instance, is regarded as the encoding of symbols selected from a finite "alphabet" into signals suitable for the channel. The symbols forming this "alphabet" (which can be, say, amplitude levels of a television waveform) are known also at the receiving end, and demodulation is a matter of selecting them according to the code signals which come in and so reconstituting the "message." If something is known about the statistical structure of the "alphabet" (probabilities of the symbols occurring) at the receiving end, a certain amount of "guessing" is possible in reconstituting the message, and this facility is known as redundancy. Elimination of redundancy would save quite a lot of bandwidth in our communication channels but it would also destroy this facility for "guessing," which allows us to bridge the gaps in a message broken by noise or imperfect transmission. So redundancy, in spite of its name, is quite a good thing to have.

There is no doubt that Information Theory has some value as an aid to the understanding of communication techniques which are already established. But then, of course, it is very easy to be wise after the event. What engineers would really like to know is whether the Theory can be used in a more active way, for improving techniques and devising new ones. This was the main theme of a recent informal discussion at the I.E.E. following an introductory lecture by E. C. Cherry; the title was "What Practical Benefits can Communication Engineers Expect from Modern Information Theory?" Some of the speakers thought that the Theory might help to concentrate effort on profitable lines of development by indicating clearly the limits of what was possible. For example, C. E. Shannon had evolved a formula which represented an upper limit of the capacity of a particular channel for conveying information; this might provide a yardstick against which various modulation methods and codes could be assessed.

The lecturer stressed that one useful concept provided by the Theory was that the significance of an item of information went in proportion to its unexpectedness. More information, for example, was conveyed in the steep portions of a waveform than in the relatively flat portions and this fact suggested the desirability of expanding the more significant or "steep" parts of a "message" and contracting the remainder, in order to improve the utilization coefficient of the channel.

The idea of redundancy was also thought to be fundamental and suggestive. (This had been brought out earlier by a gramophone record of speech in which the waveform has been clipped top and bottom and so reduced to a series of identical pulses having only significant spacing—it was nevertheless intelligible.) The Vocoder had already shown that if such redundancy in speech could be reduced a great compression of telephony bandwidths would be possible. Information Theory, however, suggested that a good deal more compression might be achieved by alteration of the statistical structure of the signal—and the same applied to television.

In general, speakers felt that Information Theory opened up the possibility of greater economy in communication systems in future by the planning of the system of coding to suit both the channel and the message.

HEARING-AID BATTERIES

L.T. as well as h.t. hearing-aid batteries are now covered by the revised edition of the British Standard BS966, originally published in 1949. "Dimensions and Nominal Voltages of Batteries for Valve-Type Hearing Aids," as it is called, specifies the designation, nominal voltages, dimensions and methods of connection. The test to be employed to determine the contact resistance of battery socket contacts is also given.

Copies of BS966:1951 may be obtained from the British Standards Institution, 24, Victoria Street, London, S.W.1, price 2s, post free.

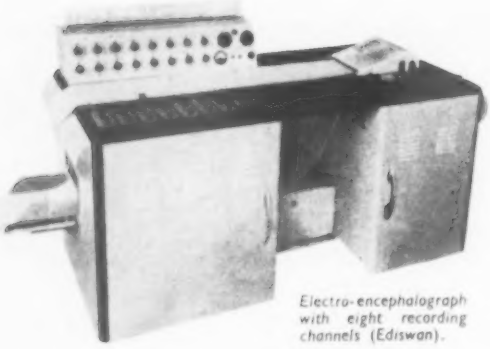

Electro-encephalograph with eight recording channels (Ediswan).

STUDYING BRAIN WAVES

Electronic Techniques in Electro-encephalography

IN the human brain there are something like ten thousand million cells, interconnected by a vast, complex network of nerve fibres. Each cell can be imagined as a tiny accumulator, taking in and putting out electricity to the accompaniment of chemical changes—only its capacity is so small that charge and discharge currents amount to no more than electrical impulses in the external circuit. Such impulses are the signals of the brain's communication system.

Under certain conditions whole masses of the cells act in synchronism, and then the impulses add together in a periodic fashion to form a continuous waveform strong enough to be detected. Fig. 1 shows the kind of thing. Records such as this are the everyday language of electro-encephalography. As well as contributing towards our general understanding of the mechanism of the brain, they are widely used in the diagnosis of brain disorders and even have some value in psychological tests. A person's electro-encephalogram is as individual as his fingerprints, and so far no two have been found alike.

If the electro-encephalographer is able to get at the brain itself during an operation, he has potentials of up to about one millivolt to work with, but otherwise he must be content with what gets through to the surface of the scalp, after something like twenty-fold attenuation in the skull. At first, the mirror galvanometer was used for recording, but nowadays, of course, the brain waveform can be amplified until it will drive quite a robust instrument, and without imposing too much of a load on the human generators. The electro-encephalograph, then, is basically a high-gain amplifier (10^7 to 10^9) coupled to a recording instrument, although in practice it usually contains six or eight channels to permit simultaneous recording from various parts of the brain. Pen recorders are generally used for routine work as the EEG* is immediately available and the recording medium, paper, is cheap (each patient requires about 40 yards).

The low periodicity of the EEG waveform (1-30c/s) presents something of a problem in amplifier design. Direct-coupled stages would be ideal, but they are difficult to keep stable at such high gains. On the other hand, RC-coupled stages with sufficiently long time-constants tend to "block" with momentary overloads. The usual way out is a compromise, with RC coupling in the early high-gain voltage-amplifying stages and direct coupling in the later power-amplifying stages.

Interference is another problem. To avoid extraneous pick-up, most EEG amplifiers use balanced push-pull stages throughout—interference signals will generally be in the same phase at both grids and so will balance out at the anodes. In particular the input stage is designed to have a very high discrimination against these "in-phase" signals. The early stages are also vulnerable to 50-c/s mains hum from the power supplies, so it is common practice to build them as a pre-amplifier and run this from batteries. There are, however, different ideas on the subject. The Ediswan electro-encephalograph, for instance, has a pre-amplifier with batteries for h.t. and grid bias and mains-derived stabilized d.c. for the heaters, while the Marconi instrument is run entirely from the mains.

Apart from reducing interference, another reason for having a balanced input to the EEG amplifier is to permit a number of channels to be connected to the scalp without "cross-talk." The electrodes are usually arranged in lines as shown in Fig. 2. This method of working from a pattern of electrodes on the head is very useful in locating particular sources of activity, such as tumours. (A tumour in the brain generally produces a low-frequency rhythm of 1-3c/s.) The electrodes are connected to the amplifiers in such a way that the signals from those on either side of the source give deflections in an opposite sense, and so the "focus" can be found.

Perhaps the strongest form of electrical activity in most people is the "alpha rhythm," arising at the

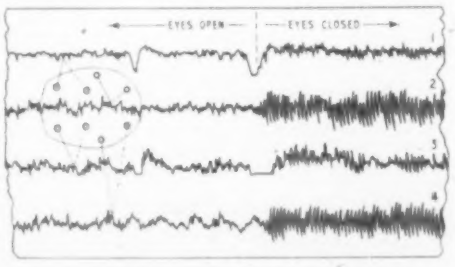

Fig. 1. Section of an EEG record showing the pairs of electrodes on the patient's head from which the four traces were obtained. These are "alpha rhythms" and it can be seen that they are strongest from the back of the head (channels 2 and 4).

* EEG is a general abbreviation used for the science, the instrument, the waveform, the record, and so on.

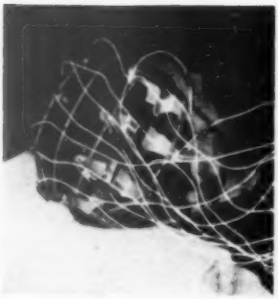

Left: Fig. 2. Showing the "helmet" used with the Marconi electro-encephalograph for holding electrodes in contact with the head.

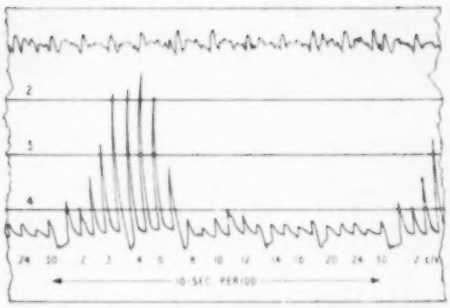

Right: Fig. 3. Section of an EEG record carrying an automatic frequency analysis of the waveform in channel 1.

back of the head. It is most pronounced when the brain is at rest, and seems to have a lot to do with the mechanism of vision for there is a very marked drop in amplitude when the eyes are opened—especially if they occupy themselves with any kind of pattern—and a rise again when they are closed (see Fig. 1). The effect may be useful in character tests, for people who tend to think in visual images have small alpha rhythms while those who think in abstract terms have large ones, and in both types the rhythms are unaffected by opening or closing of the eyes. People who use both kinds of thinking show the "responsive" type of alpha rhythm in Fig. 1. A popular theory just now is that the alpha rhythm is part of a scanning system for converting the spatial electrical images on the "screen" of the visual cortex (projected there by the eyes) into ordinary time-sequential brain signals.

The frequency of the alpha rhythm is about 10c/s but there is generally a periodic rise and fall in amplitude which suggests the beating together of several frequencies, and when the rhythm is analyzed it shows a number of components between 8 and 13c/s. Most EEG records do, in fact, contain periodicities which are not obvious to the eye but all the same have a definite significance in the study of the brain. To sort them out, electro-encephalographers often resort to the waveform analyzer. A rather interesting one has been developed by Ediswan from an original design by Dr. W. Grey Walter. Used in conjunction with an electro-encephalograph, this will do a frequency analysis every 10 seconds and automatically write it on the part of the EEG record to which it refers. The record looks something like Fig. 3. Each period of 10 seconds along the time scale represents a complete frequency spectrum. The spikes stand for particular frequencies and the height of each one indicates the integrated amount of that frequency component present in the waveform over the 10 seconds. How is it done? The simplified block diagram in Fig. 4 will give some idea.

After amplification, the EEG waveform goes to a bank of 24 frequency selectors which separate the components, and the output from each selector serves to control the amount of charge received by a capacitor through a pentode. The 24 capacitors, with charges proportional to the frequency components, are then scanned by a motor-driven rotary switch and the resulting voltages go to a recording pen to give the "kicks" shown in Fig. 3. (This pen, incidentally, is displaced along the EEG record so that it writes out the analysis at the correct place.) To give a continuous analysis, two sets of 24 capacitors are provided, C_{1A}-C_{24A}, and C_{1B}-C_{24B}, and the rotary switch is arranged to work the switch S so that one set is being charged while the other is being scanned and recorded. The frequency selectors are actually two-stage amplifiers with frequency-selective feedback—in fact RC-oscillator circuits—and they have resonant characteristics similar to ordinary tuned circuits. These are used because the conventional tuned circuit is not very satisfactory at the low EEG frequencies.

A somewhat simpler method of analysing the waveform is by use of the human ear, which is in itself an extremely sensitive harmonic analyzer. It has been found, too, that if the EEG is being observed on a c.r.o., an audible pulse locked to the sweep is a help in detecting some consistent disturbance when the signal/noise ratio is very high.

While the type of EEG record in Fig. 3 will give a great deal of information to anyone who can be bothered to look for it, as a method of presentation it is not particularly happy. The main trouble is that it does not give a *geometrical* picture of the brain's electrical activity. However, the problem has been taken up and various attempts have been made to display the brain pictorially. One of the early systems used a cathode ray tube to represent it; the pattern of electrodes on the head was "scanned" by a high-speed rotary switch while the beam of the tube was deflected across the screen in a corresponding pattern, the

Fig. 4. Simplified block diagram of automatic frequency analyser designed for electro-encephalography.

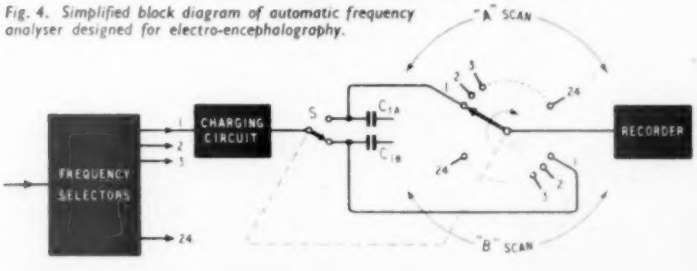

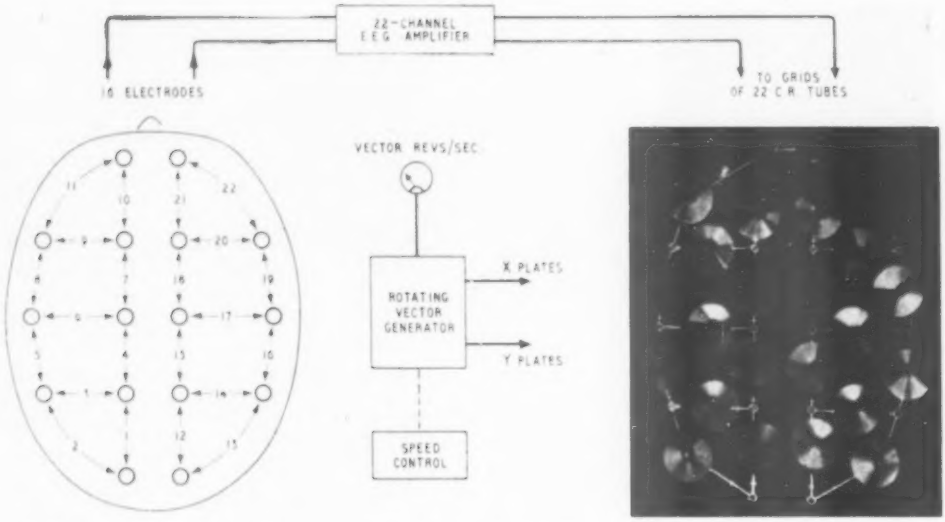

Fig. 5. Essentials of Grey Walter's "toposcope" for giving a pictorial presentation of the electrical activity of the brain. 22 small cathode ray tubes are mounted in a transparent plastic screen (right) which represents the arrangement of electrodes on the patient's head (left).

Display console of the "toposcope" installed at the Burden Neurological Institute. The camera in the foreground is for making permanent records and is remotely controlled by an operator who is in a position to observe both the display and the patient.

brain potentials being used to modulate the beam intensity.

This method, of course, only gave an indication of the relative amplitudes of the electrical sources, with their positions. A more recent apparatus, devised by Grey Walter and Shipton, shows frequency and phase relations as well. But it does not work on the scanning principle and instead of a single tube to represent the brain it uses a number of small one—in fact, one for each EEG channel. Sixteen electrodes are arranged on the head as in Fig. 5 to provide a total of 22 channels. Each channel, then, takes an EEG from a particular part of the brain, amplifies it and presents it on a c.r. tube at a corresponding position on the display.

The amplitude of the EEG is apparent from the brightness of the tube. Its frequency, however, is indicated in a rather unusual way. Each tube is like a p.p.i. radar display, with a radial vector rotating about the centre of the screen. If a signal of the same frequency as the rotational speed is applied to the tube, a section of the screen will be brightened and the remainder darkened. So to find the fundamental frequency of an EEG it is only necessary to alter the speed of the vector till a stationary sector appears. Two bright sectors would mean a frequency of twice the vector speed of course. Phase relations are easily indicated as the vectors on all the tubes come from the same generator and rotate in synchronism. If the same signal was applied to all the tubes they would all be brightened at the same instant and the sectors would point in the same direction—indicating the same phase. Thus with different signals on the tubes the phases are given by the relative "bearings" of the sectors.

The rotating vector is generated in much the same way as in radar. An oscillator produces the necessary deflection waveform and this is fed through a magslip to the X and Y plates of the tubes to give the rotating effect. The motor driving the magslip has a speed control and an indicator to show the revs/sec of the vector.

While plenty of information about the brain can be

obtained simply by measuring its "standing" voltages under "quiescent" conditions, a great deal more can be discovered under "operating" conditions. So electro-encephalographers often make the patient do things or give him drugs or apply stimuli while observing the EEG. Repetitive stimulation from a pulse generator is particularly useful as it can be controlled and related to the EEG record with great precision. It is often used to evoke special brain rhythms which are not spontaneously generated by the patient under passive conditions—in much the same way as radar pulses will evoke responses from a transmitting aerial which cannot be found by ordinary d.f. because it is not radiating. The stimulation can be applied to the brain through various channels but the eyes are used most as it is easy to impulse them with a flashing light, and they produce good electrical signals.

One difficulty in dealing with these special brain rhythms is that they usually require a certain critical frequency and phase of stimulation to keep them going. Without this, the action of successive stimulating impulses would not be cumulative and the rhythm would fade out. Consequently, a great deal of trial-and-error searching is necessary to find the right frequency and phase. To avoid the tedium and uncertainty of this process H. W. Shipton has devised a system in which the brain generates its own stimuli at the correct repetition frequency. This is done by using the brain rhythm as the frequency-selective element in a positive-feedback loop, as shown in Fig. 6. After going through a conventional EEG amplifier the brain wave actuates a trigger circuit which, in turn, fires a gas discharge lamp. The flashes of light from this stimulate the eye, which sends impulses back to the brain via the optic nerve. By adjusting the variable time delay—provided by a CR time constant in the trigger circuit—the lamp can be made to fire at the correct point on the brain rhythm to keep it going. If the required rhythm is obscured by other rhythms in the EEG and so fails to actuate the trigger it can be picked out by switching in the filter—this is actually a resonant amplifier of the "RC-oscillator" type.

Incidentally, this method of stimulus has been particularly useful in diagnosing doubtful cases of epilepsy. The brain of an epileptic person is characterized by having certain groups of cells which are very easily excited and a fit is caused by these going into oscillation; a large-amplitude low-frequency waveform is generated, and this spreads until the whole brain is behaving something like a "motor-boating" amplifier—with, of course, violent results in the nervous system. Since the oscillation is caused by positive feedback in the brain, a similar effect can be induced artificially by the external positive feedback loop in Fig. 6. Examination of the resulting EEG record then shows up any epileptic tendencies.

Another interesting example of the brain being used in a feedback loop—negative this time—is provided by an apparatus devised by Bickford for automatically maintaining anæsthesia at a constant level. It works on the alpha brain rhythm, which has the property of decreasing in amplitude as the patient falls asleep, so giving an electrical indication of the degree of unconsciousness. After amplification the alpha rhythm serves to control the plunger of a syringe which applies liquid anæsthetic to the patient. Thus a servo system is formed. If the patient tends to regain consciousness his alpha rhythm increases and so applies more anæsthetic; if he goes under too deeply the flow of

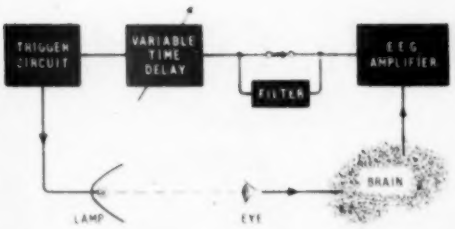

Fig. 6. The brain generates its own stimuli at the required repetition frequency in this feedback arrangement.

anæsthetic is decreased. The actual level of unconsciousness at which the servo finally balances itself—shown by the amplitude of the alpha rhythm—can be controlled by altering the gain of the amplifier. During the last war a similar system was devised for maintaining a constant degree of wakefulness in pilots and drivers who tended to doze off without knowing it, but here, of course, a stimulator was used instead of the anæsthetic syringe.

Short-wave Conditions

Predictions for February

THE full-line curves given here indicate the highest frequencies likely to be usable at any time of the day or night for reliable communications over four long-distance paths from this country during February.

Broken-line curves give the highest frequencies that will sustain a partial service throughout the same period.

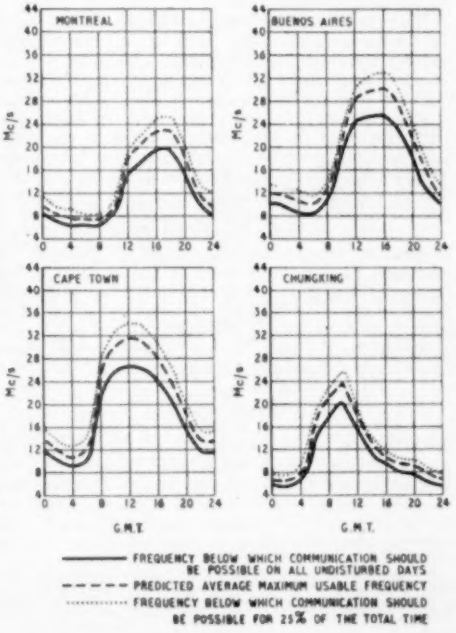
MONTREAL
BUENOS AIRES
CAPE TOWN
CHUNGKING
Mc/s
G.M.T.
FREQUENCY BELOW WHICH COMMUNICATION SHOULD BE POSSIBLE ON ALL UNDISTURBED DAYS
PREDICTED AVERAGE MAXIMUM USABLE FREQUENCY
FREQUENCY BELOW WHICH COMMUNICATION SHOULD BE POSSIBLE FOR 25% OF THE TOTAL TIME

Oxide Cathode Life

Investigations into the Causes of Loss of Emission

A PAPER* read recently at the Institution of Electrical Engineers described the results of work by the Electronics Division of the Post Office Research Station (with its associated small valve factory) on the development of long-lived valves. The Post Office is interested in such valves mainly because of the need for them in submarine repeaters and other inaccessible apparatus; but their development is of considerable moment to others as well.

Apart from structural failures, with which the paper was not concerned, the life of a valve depends mainly upon the rate at which the emitting qualities of its cathode deteriorate with use. Loss of emission is the disease; if its causes are completely understood, we are more than half-way on the road towards finding a cure. There are two main accepted causes of oxide cathode deterioration: poisoning by attacks from residual gases, and the development and growth of interface resistance; on both of these the paper throws much new light.

Interface resistance was the subject of a recent article in *Wireless World*.† The authors of the paper agree with Eaglesfield in accepting Eisenstein's view that interface resistance is due to the growth of a film between the cathode body and the oxide matrix, and that its production is due to deliberately introduced impurities, chiefly silicon.

They find, though, that the film does not increase in thickness as the valve ages. It appears to build rapidly up to its maximum thickness, after which a steady change in its nature sets in; it is to this change that the increase in resistance is due. They consider that it is caused, in part at any rate, by deactivation of the interface by gas poisoning, much as the matrix itself is deactivated; hence the complete elimination of residual gas would be likely to check the growth of interface resistance, in addition to ensuring longer life for the emitting surface of the cathode.

A method has been developed of making a triode or pentode measure its own residual gas pressure. As electrons flow from cathode to anode some collide with gas molecules. The positive ions, so formed, travel to the negatively biased control-grid and set up reverse grid current I_{rg}, from which the residual pressure can be derived. It has, however, been found more convenient to use a "vacuum factor":

$$k = \frac{I_{rg}\ (\mu\mu A)}{I_a\ (mA)}$$

Investigation of the behaviour of the residual gas under working conditions showed that when k was plotted against time there was always a sharp initial rise, followed by a slow, roughly exponential fall until a value k_0 (the "residual vacuum factor") was reached; the value of k_0 is constant. The area enclosed by the $k=f(t)$ and k_0 curves is a measure of the residual gas driven into the cathode and has been named the "gas integral." It was found that valves with a high gas-integral were short-lived and that a low gas integral was an indication that long life might be expected.

Here, then, was one method of forecasting valve life after a test of comparatively brief duration; reliable tests of this kind are clearly needed for dealing with valves whose working lives may range up to 60,000 hours—say seven years of continuous running! Another of great value that has been evolved is the low-temperature total-emission test. Under working conditions emission is limited by the space charge; to measure the total emission there must be no such limiting factor. It is also desirable that the cathode temperature should be low enough for ionic equilibrium to be maintained within it. The method developed is to use the control grid as collector, making its potential +5V and earthing the other electrodes; for 6.3-V valves the heater is at about 2.6V.

In practice, valves are taken from the life-test rack, where they are running under working condition, and put through the total-emission test. The total emission, after a given number of working hours, can thus be plotted as a percentage of its original value.

The authors have no doubt that the amount of barium used for gettering the average valve is amply sufficient to absorb all residual gas *if* (and that is one of the big problems) physical association of gas and getter can be established. They have given much attention to the preparation of electrodes and supports and to pumping, gettering and ageing valves. It has been found that when residual gas is reduced (by methods suited so far to the laboratory rather than to the mass-production factory) to amounts far smaller than those in commercial valves, no deterioration in the emission occurs after thousands of hours of use. The authors' estimates are always conservative; they see no reason why valves, with assured lives of 40,000 hours or more, should not be produced.

Poisoning of the cathode by occluded gases released from metal parts produces non-emitting patches on the surface of the cathode, which may be small and evenly distributed, or large and irregular. The authors in their investigations have found a new and unexpected source of cathode-poisoning gas. "A gas derived either directly or indirectly from the heated glass envelope," they state, "is more destructive in action than any of the normal gas so far examined." This gas is believed to be water vapour, which has been shown to have dire effects on a cathode at 1,000° K.

A second possibility is that the water vapour reacts with metallic carbides in the valve to produce unsaturated hydrocarbons of the acetylene type, which dissociate to form non-emitting carbon patches on the cathode.

R. W. H.

* "The Life of Oxide Cathodes in Modern Receiving Valves." G. H. Metson, S. Wagener, M. F. Holmes and M. R. Child.

† "Valve Cathode Life." C. C. Eaglesfield. *Wireless World*, December, 1951.

designed . . . .

with YOUR needs in mind

Designed by electronic engineers who are intimately concerned with the problems which technicians have to face, the Cossor Oscillograph with unique Double Beam Tube has the advantage of enabling the traces of two related phenomena to be examined simultaneously. The 4" dia. flat-faced Tube is operated at 2kV. and signals are normally fed through the Amplifiers, the calibrated Y-Shift controls providing a measurement of the applied voltages. The Time Base operates repetitively, or by external trigger (for single stroke operation), whilst the calibrated X-Shift control provides for the measurement of Time. Fully detailed specification will be gladly supplied on application.

Model 1428
CAMERA

Specially developed for use with Cossor Oscillographs and equipped with a fixed-focus lens of F3.5 and shutter, this camera will photograph stationary waveforms, and in conjunction with a motor drive will also record slow transients. Standard 35mm. perforated stock is used and the cassettes will accommodate 25 ft. lengths, the exposed portion being cut off by a self-contained guillotine.

COSSOR

Double Beam OSCILLOGRAPH

Please address enquiries :
A. C. COSSOR LTD., INSTRUMENT DIVISION (DEPT. 1), HIGHBURY, LONDON, N.5
Telephone : CANonbury 1234 (30 lines)
C128

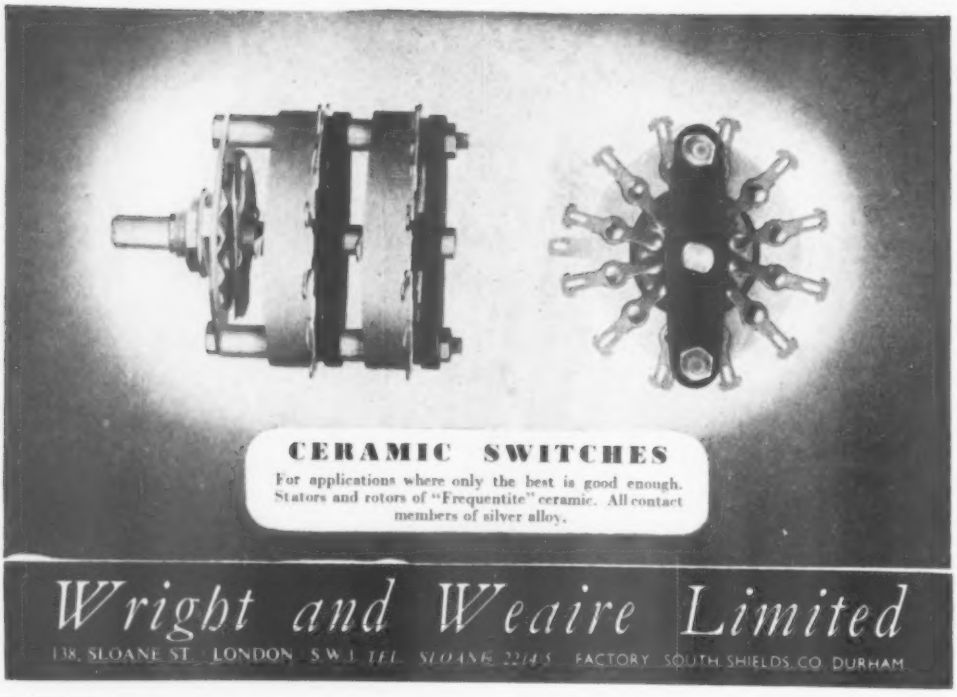

CERAMIC SWITCHES

For applications where only the best is good enough. Stators and rotors of "Frequentite" ceramic. All contact members of silver alloy.

Wright and Weaire Limited

138, SLOANE ST. LONDON S.W.1 TEL. SLOANE 2214/5 FACTORY SOUTH SHIELDS, CO. DURHAM

SUCCESS?

START HERE

In Radio, Television, and Electronics there are many more top jobs than engineers qualified to fill them. Because we are part of the great E.M.I. Group we have first-hand knowledge of the needs of employers, thus our Home Study courses are authoritative and based upon modern industrial needs. Alternatively, our courses will prove equally valuable to you in furthering your hobby.

POST THIS COUPON NOW

E.M.I. INSTITUTES, Postal Division, Dept. 15, 43, GROVE PARK ROAD, CHISWICK, LONDON, W.4.
Please send, without obligation, your FREE BROCHURE.
I have marked the subjects which interest me.

☐ Mechanical Eng. ☐ Electrical Eng. ☐ Draughtsmanship.
☐ Radio. ☐ Television. ☐ Production Eng. ☐ Automobile Eng. ☐ Aeronautical Eng. ☐ General Cert. of Education (Matric.). ☐ Civil Service.
Also Courses for A.M.I.Mech.E., A.M.I.C.E., A.M.Brit.I.R.E., A.F.R.Ae.S., CITY and GUILDS EXAMS. in Mech. Eng., Elect. Eng., Telecommunications, etc.

Other Subjects .....

NAME .....

ADDRESS .....

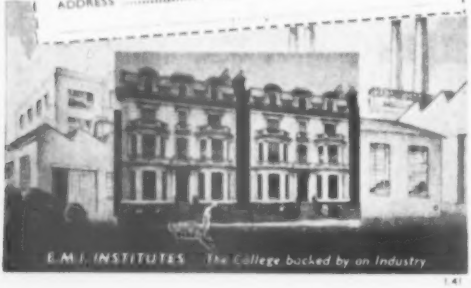

E.M.I. INSTITUTES The College backed by an Industry

1.41

MODERN PRACTICAL RADIO AND TELEVISION

This work covers every phase of Radio and Television Engineering from many viewpoints and meets a great demand. The author, C. A. Quarrington, A.M.Brit.I.R.E., with a long and wide experience of Radio Engineering, has been responsible for training a large proportion of the Radio and Television Service Engineers in this country, and is also well known as a lecturer on Radio and Cathode-ray subjects to Universities, Radio Societies, Trade Associations and other interested bodies throughout the country.

It is impossible to detail even briefly in this small space the exhaustive ground covered by this comprehensive work, but the pamphlet we can send you will show you that these few remarks are no exaggeration.

THE ILLUSTRATIONS

"Modern Practical Radio and Television" is profusely illustrated. It contains 16 full-page plates, over 400 diagrams in the text and 7 large folding insets. Each illustration has been specially selected for its practical utility.

SEND FOR FREE PARTICULARS

To THE CAXTON PUBLISHING CO. LTD. 42, Morley Hall, St. George St., Hanover Sq., London, W.1.
Please send me, free of charge, particulars of "Modern Practical Radio and Television," together with your terms of easy payment.

Name .....
(*Send this form in unsealed envelope*) (1½*d.* stamp)

Address .....

R.T.9. .....

WHY 47?

The Reason for the Oddness of Preferred Values

"DIALLIST" recently disposed of the impression that when a resistor is marked 47,000 ohms it is necessarily something quite different from a 50,000-ohm resistor. As he pointed out, a usual tolerance is ±10%, so the "47-kΩ" resistor would be within its rights if its actual resistance were anything between 42.3 and 51.7 kΩ. For most purposes, then, 47 and 50 are interchangeable.

That being so, why "prefer" 47 to 50? Or 22 to 20, or 68 to 70, or any of the other new-fangled numbers to the easily remembered 10, 25 and 50?

It all arises from the fact that it is impossible to manufacture anything *exactly* to a given value. There must always be some tolerance, however small. And the cost goes up very steeply as the tolerance is reduced. So it is wasteful to specify a closer tolerance than is really necessary. In ordinary receiver circuits there is rarely anything substantial to be gained by keeping the values of components, except those required for tuning, within closer limits than ±10%. In fact, many of them can be allowed a ±20% tolerance, which means that one marked 50 may be anything from 40 to 60.

In the old days, the main standard values were 10, 25 and 50, with their multiples of ten. Assuming a ±20% tolerance, the allowable spread of each value is shown here in the right-hand column of Table I:

TABLE I

Nominal value	Acceptable values for ±20% tolerance
10	8–12
25	20–30
50	40–60
100	80–120

All is well so far, but what intermediate values would you choose? Even with such a wide tolerance as 20%, there is a large gap between nominal 10 and 25. A likely value would be 15, which would spread from 12 to 18, and so would begin where the nominal 10 left off. But there would still be a gap from 18 to 20. If a standard value of 20 were added, this would spread from 16 to 24, so components that measured between 16 and 18 would be in rather an ambiguous position, since they could be sold as either 15 or 20! Similarly for those between 20 and 24.

So our tidy, sensible round-number scheme is already beginning to look a little less tidy and sensible. It was this that led to the idea of choosing nominal values such that the usual tolerances would include all possible values without any gaps or overlapping. The problem was to divide the whole scale from 10 to 100, so that each division would represent the same tolerance spread from a nominal value. Obviously, if this were done from 10 to 100 the same plan would work for 1 to 10 and 100 to 1,000, and so on, covering every possible value.

Musical readers will see that this is the same kind of problem as what they call equal temperament—the dividing-up of the octave into a number of equal intervals corresponding as nearly as possible to the existing musical scales. But, as they know, it is impossible to make equal divisions correspond *exactly* with the simple ratios required for perfect tuning, and the equal temperament whole tone—corresponding to tolerance in our problem—cannot be exactly the 9:8 ratio that makes a true whole tone. Another similar problem, a little nearer our subject, is the dividing-up of the 1:10 ratio, or decade, into the ten equal-ratio parts we call decibels.

Starting off with the widest standard tolerance, ±20%, we see from the above table that the top-limit value is in every case 1½ times the bottom limit. We want to make the first standard value 10, and, as we have seen, the corresponding limit values are 8 and 12. Multiplying 12 by 1½ brings us to 18, which is the top limit for 15. The top limit for the next preferred value would be 1½ times 18, which is 27, and the number that 27 is 20% more than is 22.5. That is already beginning to look a little odd. Proceeding in the same way to the next preferred value, we find it to be 33.75, which is worse. But that is not the worst of the matter because it turns out that we do not arrive, as we had wanted, at 100. It falls between two of the preferred values found in this way. After all, it is rather too much to expect that a sequence based on a previously chosen tolerance would end up exactly on 100. One could, of course, abandon the idea of trying to fit the series exactly into a decade scale, but that would sacrifice the immense advantage of having the same numbers repeating as multiples of ten in both directions without limit.

So it is necessary to begin afresh. The kind of scale on which a given ratio is represented everywhere by the same length is the logarithmic scale, with which slide rules are marked. If we try to divide the 1:10 slide-rule scale into equal lengths representing 1:1½ we see, as we have already found by calculation, that it does not go exactly. The nearest whole number is six times, and the ratio represented by one-sixth of the whole scale is about 1:1.468, instead of the 1:1.5 we wanted. The corresponding ± tolerance is just under 19%.

Now, if 47±20% is considered rather odd, what would people say about 46.4195 etc. ±18.96 etc.%, which is the sort of thing a mathematically perfect preferred-value system would give! This was considered rather too much to swallow even in the interests of science, so it was decided to accept slight overlapping of some of the divisions in order to retain the standard tolerance

figures and also to allow the "perfect" nominal values to be rounded off to not more than two significant figures. The sequence so obtained is 10, 15, 22, 33, 47, and 68; and it starts all over again with 100, as shown in the diagram:

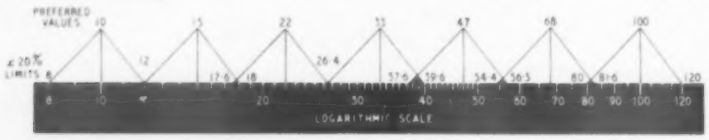

So we see that if, for example, we had a vast stock of resistors of every possible value between 8 and 80, we could sort them out into six piles labelled 10, 15, 22, 33, 47, and 68, without any of them being more than 20% high or low. And 36 piles would provide for every value between 8 ohms and 8 megohms.

Half the tolerance, ±10%, or a 9:11 ratio, is represented by half the distance on the logarithmic scale; so twice as many piles are needed, the new ones being centred on the limit values for the 20% classification. There is no difficulty in deciding on 12 as the first of these additional preferred values, because that is exactly 10+20% and 15−20%, but there might be a difference of opinion about some of the others. As a matter of fact, the correct approach is to begin with the smallest standard tolerance, ±5%, and divide the decade into 24 sections. The exact tolerance with no overlapping would then be about ±4.8%, but this allows no margin for any rounding off of the nominal centre values. When they have been rounded off to the two-figure numbers that give the smoothest sequence, the ±5% values are 11, 12, 13, 15, 16, 18, 20, 22, 24, 27, 30, 33, 36, 39, 43, 47, 51, 56, 62, 68, 75, 82, and 91. Crossing out every alternate one leaves the ±10% values, 12, 15, 18, 22, 27, 33, 39, 47, 56, 68, and 82; and repeating the process leaves the ±20% values, 15, 22, 33, 47, and 68, as before.

So the whole list of preferred values can be set out as shown in Table II.

TABLE II

20%	10%	5%
10	10	10
—	—	11
—	12	12
—	—	13
15	15	15
—	—	16
—	18	18
—	—	20
22	22	22
—	—	24
—	27	27
—	—	30
33	33	33
—	—	36
—	39	39
—	—	43
47	47	47
—	—	51
—	56	56
—	—	62
68	68	68
—	—	75
—	82	82
—	—	91

There is no attempt to divide the values any finer for the higher-grade components having standard tolerances of ±2% or ±1%; so if you wanted, say, 80Ω ±2%, it would either have to be ordered as a non-preferred value, which might not be readily obtainable, or searched for out of an 82-Ω wider-tolerance batch.

Incidentally, resistors with silver or gold bands in addition to the usual 3-band colour code are not, as might be supposed by the uninitiated, of a particularly select kind; their tolerances are 10% and 5% respectively. The more choice 2% and 1% components are distinguished respectively by an uninteresting red or brown. If there is no tolerance colour at all, ±20% must be assumed.

"CATHODE RAY."

MANUFACTURERS' LITERATURE

Industrial Electronic Equipment; a well-illustrated booklet showing various applications, from Philips Electrical Ltd., Century House, Shaftesbury Avenue, London, W.C.2.

Counter Tubes, halogen quenched and ethyl formate quenched; technical details in leaflets from E. K. Cole Ltd., Southend-on-Sea, Essex. Also a booklet describing the Ekco **Airborne Search Radar** equipment.

Moving-coil Microphone, type 4035A; specification in a leaflet from Standard Telephones and Cables Ltd., Connaught House, Aldwych, London, W.C.2.

Television Cables (downlead); a technical data leaflet from British Insulated Callender's Cables Ltd., Norfolk House, Norfolk Street, London, W.C.2.

Instrument Cases and Racks in a catalogue from Alfred Imhof Ltd., 112-116, New Oxford Street, London, W.C.1.

Capacitors for industrial applications; technical details in leaflets from A. H. Hunt Ltd., Garratt Lane, London, S.W.18.

Coaxial Connectors catalogued in a leaflet from Transradio Ltd., 138A, Cromwell Road, London, S.W.7.

Test and Measurement; a catalogue of equipment (2nd edition) made by Taylor Electrical Instruments Ltd., Montrose Avenue, Slough, Bucks.

Manufacturers' Products

New Equipment and Accessories for Radio and Electronics

Vibration Generator

THE industrial vibration generator made by Goodmans Industries, Ltd., Axiom Works, Wembley, Middlesex, is for testing radio and other equipment for ability to withstand mechanical vibration.

Goodmans industrial vibration generator set up for testing miniature valves.

It consists of a large permanent magnet having an armature actuated by a moving coil. A sturdy connecting rod transmits the movement to a carrier or table according to the nature of the equipment being tested. In the illustration a small table is carrying three different types of valve undergoing tests for microphony and general ability to withstand vibration.

The moving coil can be driven either by a fixed or variable frequency oscillator or by a 50 c/s a.c. mains supply. Without assisted cooling it will handle up to 40 watts but with forced air cooling this can be raised to 120 watts. The magnet pot is 6½ in in diameter, weighs 26 lb and the impedance varies from 7 to 16 ohms according to the method of operation. The price is £65 which includes a felt-lined instrument carrying case.

Magnetic Coating Compound

MAGNETIC recording is effected by the use of coated tape or film. For special requirements such as for high-speed computors, however, the magnetic medium may be disposed on the surface of a drum, and the Minnesota Mining & Manufacturing Company, 167 Strand, London, W.C.1, has produced a magnetic dispersion intended for application to rigid surfaces by spraying or dipping. It will adhere to the rigid surface of a variety of metals and plastics—in some cases after the application of a primer—but not to a flexible material such as a thin tape. It is known as Dispersion B25S and is supplied in quart tins with an instruction leaflet.

Miniature Coils

RECENTLY introduced by Osmor Radio Products, Ltd., Bridge View Works, Borough Hill, Croydon, Surrey, is a range of miniature coils measuring 1 in high only and fitted with adjustable dust cores. There are over 30 types in all covering the requirements of aerial, r.f. and oscillator circuits for a tuning range of 13 to 2,000 metres.

Polystyrene formers are employed and a good design feature is that the soldering tags are carried by a disc of bakelized material and not by the polystyrene, which is rather heat sensitive.

The superhet coils are designed for an i.f. of between 450 and 480 kc/s and there is an i.f. filter and an all-wave choke; the series also includes a spiral-wound frame aerial small enough for use in "personal" portables. The coils cost 4s each (frame aerial 2s 6d).

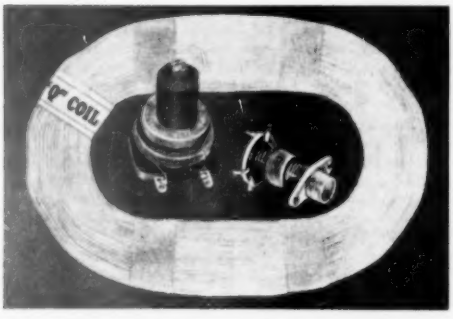

Specimens of Osmor miniature coils and spiral-wound frame aerial.

TRIX
Quality
SOUND EQUIPMENT

HIGH FIDELITY MICROPHONE

Model G7808, moving coil type. New design, neat and unobtrusive, with die-cast alloy grille. Fitted with switch and plug and socket connection.

ENCLOSED RACK EQUIPMENT

For medium powered installations, incorporating 20 or 30 watt amplifier unit, radio receiver with monitor speaker, and gramophone unit if required. Provision for microphone input and multiple speaker matching.

Send for latest catalogue and price lists of the Trix range of Sound Equipment.

THE TRIX ELECTRICAL CO. LTD.
1-5 Maple Place, Tottenham Court Road, London, W.1. 'Phone: MUSeum 5817
'Grams & Cables: "Trixadio, Wesdo, London"

AMPLIFIERS · MICROPHONES · LOUDSPEAKERS

RANDOM RADIATIONS

By "DIALLIST"

Electrogremlins

YOU HAVE, no doubt, observed the queer proneness of wireless and other electrical gear to break down at times when it is impossible to get replacements. Early closing days, for instance, and week-ends. And Christmas, with the appropriate shops closed for anything up to five days was a wonderful opportunity for the electrogremlins to get busy with their pranks. Fate was, however, kind to me, for I detected and nipped in the bud an incipient fault in the wireless set on December 22, when it was still possible to buy what was needed. She did me a second good turn, too; for whilst I was in the shop I was inspired with the idea that it might be a good thing to replenish my stock of 60-watt and 75-watt lamps. It was lucky that I did, for when I got home I found that there had been no spares of either kind left; and I was able to smile when a 75-watt lamp expired with a sharp "pink" on Christmas Day and a 60-watter did likewise on Boxing Day. Not quite so fortunate was a dear old lady, whose home is not far from mine.

First Aid

Calling to see her on Christmas morning, I found her almost in tears. Her wireless set refused to work, she did so want to hear the King speak and doctor's orders prevented her from going to someone else's house to do so. I said I would see what I could do. It was a smallish set, so I carred it off to my workshop, hoping for the best. One of the handiest ways I know of making a quick examination of a sick set is to use a pair of prods connected to the resistance-measuring section of a multi-range meter. It worked like a charm in this case, for in a very short time indeed I had found a radio-frequency choke which showed infinite resistance between its terminals. A rummage through the junk box unearthed something that would do and it duly took the place of the choke with the "dis." The set was no longer silent; but it was not working properly. It might be all right for a minute or two, but then symptoms of motor boating developed. The prods disclosed that a grid resistor, colour-coded as being of one megohm, had an actual resistance many times greater. That was easily replaced. Things were then a whole lot better, but reception was noisy and the volume level was poor and wobbly.

Unwanted Ohms

If one resistor had been faulty, might not there be others whose values had suffered changes? There were! I found two anode decouplers which had managed to wander from their original orange spot class well up into the yellows. When they had been replaced the set worked well enough for speech to be intelligible and music not too awful. That, anyhow, was all I had time to do. But I had found half a dozen other resistors that were, so to speak, sailing under false colours; and when I took the set back to the old lady I impressed upon her that she must ring up a wireless shop as soon as it reopened and have the whole thing properly serviced. What worries me is that there seem to be rather too many untrustworthy resistors about nowadays. Or have I just been unlucky with resistors? I don't know. What I do know is that when a fault develops one of the first questions I have come to ask myself is: Could it be due to a dud resistor? And too often it is. What are your experiences?

Poor Fish!

A LEICESTER READER sends me an account of a puzzling effect observed by a friend of his, together with an explanation which I do not find entirely satisfactory. The said friend had a home-built a.c. receiver, working from a 3-pin wall socket. Having acquired an aquarium, he rigged up a 15-watt lamp to illuminate it, connecting the leads to phase wire and neutral at the input to the mains transformer of the set. The idea was that when the set was switched on the fish, snails and whatnot could be watched, bathed in gentle light. On switching off, peace should have been restored to both listener and whatnots; but it didn't work out like that. Turning over the switch duly silenced the set; but it left the lamp glowing, what is described as, cherry red. Two electrical crimes become immediately apparent: in the first place, it is clear that the set had only a single-pole switch; secondly, the plug must have been wired wrongly, with the result that the switch was in the neutral "leg." That much emerged at once when the "effect" was investigated. The set had a mains filter, consisting, it is stated, of a 0.1-μF capacitor from each mains lead to earth. My reader's explanation that one of these provided the return path won't do, for at 50 c/s the reactance of a 0.1-μF capacitor would be over 30,000Ω and not enough current could have passed to produce the dimmest glimmer from the lamp. Either there was a leak to earth from the neutral contact of the lampholder *via* water and filling pipe, or (as I think more probable) the capacitor was of 1 μF. Anyhow, the moral is that one should always be careful to wire up a 3-pin plug properly and that the on-off switch of a receiver should be of the double-pole variety.

The Seeing Eye

DID YOU, I wonder, see the Oxford and Cambridge rugger match on your television receiver? If so, you can hardly have helped being struck by the remarkable light-sensitiveness of the tubes used in the television cameras. Sometime before the end of the game the commentator began to complain of poor visibility; play was largely on the side of the field remote from his box and he kept on saying "The ball's gone into touch, but the light is so bad that I don't know how it happened . . . Can't see whose ball it is." Meantime, there was no sign on the television screen of the gloom of which he so often spoke. Viewers saw clearly not only the players and all parts of the ground, but even the spectators in the stand on the opposite side. The screen left one in no doubt about whose ball it was, for there was the touch judge as plain as a pikestaff, with his flag raised and his disengaged hand pointing in the appropriate direction. The television camera is far more sensitive than the human eye and I suggest in all seriousness that commentators on outdoor events in winter should be provided, as a matter of course, with this means of supplementing the shortcomings of human eyesight.

It's A Gift

HAVE YOU EVER NOTICED what an uncanny knack some people, with very little theoretical knowledge,

have of tracking down faults in wireless gear with speed and certainty? And, on the other hand, some men who know the last thing about the way in which each bit and piece functions are often hopelessly at sea when it comes to diagnosing the cause of a breakdown. Give them time and they will find out what is the matter; but the fellow fortunate enough to be endowed with the trouble-spotting instinct will be far quicker than they in putting an unerring finger on the faulty lead, valve, or component, even though he possesses but a tiny part of their knowledge of how things work. It's a gift and I only wish I had it. One of the best radar mechanics I had during the war was a Scottish crofter who, in civil life, had never handled any electrical apparatus more complex than a flashlamp. Put that man on to the job of locating a mysterious fault in a radar receiver containing the best part of a hundred valves, and nine times out of ten he would have got the answer and put things right before your hard thinking had been able to reduce the possible causes of the trouble to less than about a dozen. Combine the gift of fault locating with sound knowledge of theory and you have the perfect serviceman, worth his weight in gold.

Purchase Tax and All That

THE PRESENT unconscionably high rate of purchase tax is not exactly helping the progress of wireless. I am not thinking only of its effects on the sales of broadcast and television receivers, but of the way in which it cramps the style of the amateur experimenter—and there is no need to remind you of the good work which has been done, and still could be done, by such. I know of one young fellow who will make his mark one day if he has a proper chance of developing the bright ideas that crowd into his brain; but it is no small handicap to him, with his present salary, to find that purchase tax raises the cost of three valves that he needs to try out one promising device from £1 18s to £2 14s 7d. If you are fond of figures, you may find it interesting to work out just how much a broadcast listener, paying income tax at 8s 6d in the pound on all earnings beyond those needed to provide bare necessities, must earn if he wants to buy a receiver costing £28; and what percentage of the total is mopped up by income tax and purchase tax. Try it. You'll be surprised!

NEW

BULGIN MULTI-POLE CHASSIS PLUG & SOCKET

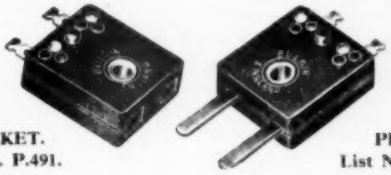

SOCKET.
List No. P.491.

PLUG.
List No. P.490.

BULGIN "DOMINA" TWO-POLE UNIT PLUGS & SOCKETS FOR INTER-CHASSIS & INTER-STRUCTURE CONNECTIONS

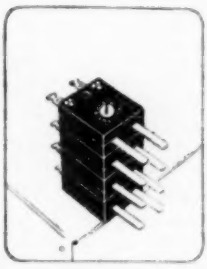

SUGGESTED STACKING OF PLUG MEMBER

THESE new connectors, moulded in high grade phenolic thermo-setting plastic, are intended for interconnection of chassis and structures (e.g., chassis / rack connections) in reliable and unfailing manner, and can be grouped and used to provide non-reversible or polarised connections.

Suitable for up to 500V. between adjacent poles and to chassis, and for up to 10A. When used as separable under load, 250W. max. loading is suggested.

Fixing is by single screw or rivet, a keying spigot being provided for chassis or base, with counter-hole(s) for key(s) from further unit(s) when stacking, as shown. Also provided with colour-key-"sinks," but supplied un-coded.

Normal colour of mouldings, BLACK.

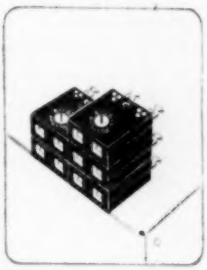

SUGGESTED STACKING OF SOCKET MEMBER

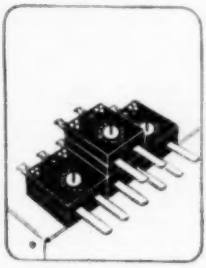

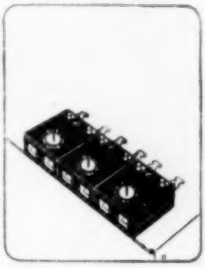

SEND FOR CATALOGUE No. 190 WW PRICE 1 - POST FREE

"The Choice of Critics"
regd. trade mark

MANUFACTURERS OF RADIO AND ELECTRONIC COMPONENTS

BULGIN Components

A.F. BULGIN & CO. LTD
BYE-PASS ROAD BARKING
TELEPHONE [illegible]

UNBIASED

By FREE GRID

Hospital Wireless

AT this damp and dismal time of the year when our spirits are drooping, our temperatures and tempers rising and our noses running, it is fitting that I should write about hospitals. In pre-broadcasting days hospitals were cheerless places with nothing to pass the weary hours. I well recollect an occasion when I was myself incarcerated in one; the only literature available was an old railway timetable which enabled me to plot in imagination slow-tempo journeys from Gravesend to Bury St. Edmunds and other sepulchrally suggestive places.

The coming of broadcasting changed all that. Wards were wired up for headphones fed by a master set, and, since there were no official funds available for this purpose, it was done voluntarily by local radio societies, wireless-set manufacturers and others who undertook not only to install but to maintain the apparatus. But all that was in the days of long ago, and, although I do not doubt that there are a large number of hospitals where wireless programmes are still available at every bedside, I know also from personal experience in recent months, as a visitor at several metropolitan hospitals, that in many cases there is to-day a far different tale to tell. Headphones with broken leads, soundless sockets, weak signals and atrocious quality are only a part of the sorry story.

The trouble is one which could be so easily remedied, but it appears to be nobody's job to see to it.

Another gripe I have is against the wretchedly uncomfortable, old-fashioned and thoroughly unsuitable type of headphones available. Is not the hearing-aid type more suitable for a bedridden patient who dislikes having his few remaining hairs torn out by the roots? Cannot something be done also to provide patients with simple talking-book units—preferably tape recordings—similar to the disc type which benefit blind folk? In at least one hospital the photographic industry has beaten us to it by providing microfilm-book units where the patient "turns the page" by means of a simple bell-push type switch. But for patients with defective eyesight sound recordings would be better, and, in any case, most people prefer being read to. But all these things are at present just luxury "extras." The first task is to get at least two radio programmes to every hospital bed in the country; but whose responsibility is it to provide the funds?

Temperature and temper rising.

This was an admitted stumbling block in pre-nationalization days, but even now the problem is as great, for apparently the radio installation was not nationalized with the hospital. Although everything from the X-ray apparatus to the electric light and plumbing is looked after by proper maintenance engineers, it seems to be nobody's business to see to the radio gear which falls into rags and tatters like Cinderella—or should I say Radioella—while the step-motherly State looks grimly on. Won't some M.P. act the part of Prince Charming and ask a question about the matter in the House?

Seen in the Crystal

WHEN broadcasting began many people saw in it the doom of the gramophone, instead of which it has provided a tremendous boost to the sales of records which have now reached a figure far in excess of what would have otherwise been attained. Now this is partly due to the fact that the hearing of a piece of music which takes your fancy, naturally makes you want to buy a permanent record of it. But, despite this, I don't think so many records would have been sold if listeners had been compelled to crank up a separate gramophone of the so-called "acoustic" type every time they had wanted to hear a record. It is, I think, only because records can be played with a minimum of effort through the ordinary amplifier and loudspeaker of the domestic wireless set that they have become so popular.

The question which arises in my mind is whether television will perform a similar office for the home ciné as sound broadcasting did for the gramophone. On the face of it the question looks rather absurd because you certainly can't buy a ciné film of anything which takes your fancy on television. Even if you could do so, the home ciné—except to its own particular devotees—is a bit of a nuisance to drag out complete with screen, etc., every time you want to show a film. It is in much the same position as the "acoustic" gramophone which I have already mentioned.

But the time is coming when you *will* be able to buy a film of anything which takes your fancy on television and you will be able to view it on the screen of your television set. The film will, however, not be a ciné film; in fact, the "film" is more likely to be a disc which you will "play" through special P.U. terminals on the set. Baird recorded

Vision of 1961.

television on a disc long years ago and in a few years the idea will, in my opinion, be developed commercially. It will be possible to use an automatic record-changer as for gramophone records. Of course, the recordings could equally well be made on film or on magnetic tape. This "radiogramoscope," as it is likely to be called, will probably appear about the time of *Wireless World's* jubilee in April, 1961.

B.B.C. Headache

I HEAR it rumoured that Scottish nationalists are asking for the artificial "bars" radiated from the Kirk O'Shotts television station (now undergoing tests) to be arranged as a St. Andrew's cross instead of a St. George's cross as is the present practice of the B.B.C.

This would give the B.B.C. engineers a bit of a headache, for these bars are, of course, produced electronically by the use of two pulse generators. The diagonal cross would certainly be much more difficult to generate.

If, however, the powers that be agree to pander to this nationalism, then what will happen should there be a similar request from the Welsh at the opening of the Wenvoe station? It would be extremely difficult, if not altogether impossible, to generate a leek electronically. The only suggestion I can make is that a worm's-eye view of the Welsh national emblem should be shown, i.e., a circle. This, I understand, would not be an easy matter to produce but it would certainly provide a stringent test for receivers. But, after all, as those of you well versed in heraldry and hagiology know, the problem should not arise, for the St. David's cross has the same crucial form as St. George's.

Is your amplifier good enough for use

by the B.B.C. and many Commonwealth and foreign broadcasting Corporations in Monitor systems and as a driver amplifier in the speech modulator chain of broadcast transmitters ?

by famous record manufacturers for disc recording ?

Professional audio engineers have chosen the TL/12 amplifier for the above applications to help bring to you the music on which you rely for your pleasure.

This is a unique distinction for an amplifier available to the general public.

Used with the RC/PA/U pre-amplifier and the best available complementary equipment the TL/12 power amplifier gives to the music-lover a quality of reproduction unsurpassed by any equipment at any price.

These amplifiers are built to a tropical specification and they are distributed throughout the world. During 1951 to date orders totalling over 2,000 have been received from the U.S.A. for RC/PA/U and TL/12 amplifiers for high quality radio/gramophone reproducers for the home.

This illustration shows the RC/PA/U pre-amplifier mounted in a console cabinet designed for armchair operation. The TL/12 amplifier is mounted in the base of the cabinet. The Leak Dynamic pick-up and Leak radio unit are also incorporated. This console was presented to Harold Rawlinson, Esq., conductor of the Insurance Orchestral Society, on the occasion of the Society's Silver Jubilee.

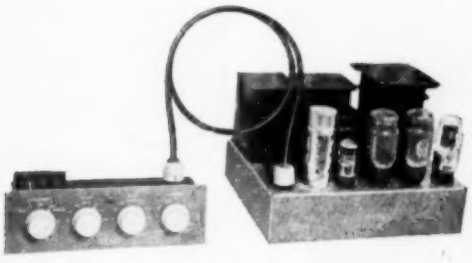

RC/PA/U
REMOTE CONTROL
PRE-AMPLIFIER
PRICE 9 GUINEAS

" POINT ONE " TL/12
TRIPLE LOOP FEEDBACK
12 WATT AMPLIFIER
PRICE 27 GUINEAS

Craftsmanship is apparent on inspection. Performance is certified by the N.P.L.

★ A 28-page illustrated booklet describing these amplifiers and containing much information of interest to music lovers seeking the highest standard of reproduction is available free on request. ★

H. J. LEAK & CO. LTD. (Established 1934)

BRUNEL ROAD, WESTWAY FACTORY ESTATE, ACTON, W.3

Phone : SHEpherds Bush 1173 Telegrams : Sinusoidal, Ealux, London Foreign : Sinusoidal, London

ELPREQ PAGES

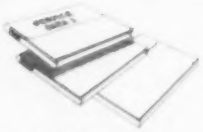

SERVICE DATA

100 service sheets, covering British receivers which have been sold in big quantities, and which every service engineer is ultimately bound to meet. The following makers are included: Aerodyne, Alba, Bush, Cossor, Ekco, Ever-Ready, Ferguson, Ferranti, G.E.C., H.M.V., Kolster Brandes, Lissen, McMichael, Marconi, Mullard, Murphy, Philco, Philips, Pye, Ultra. Undoubtedly a mine of information invaluable to all who earn their living from radio servicing. Price £1 for the complete folder.

Out folder No. 2 consists of 100 data sheets covering most of the popular American T.R.F. and superhet receivers "all dry" etc., which have been imported into this Country. Names include Sparton, Emmerson, Admiral, Crossley, R.C.A. Victor, etc. Each sheet gives circuit diagrams and component values, alignment procedure, etc., etc. Price for the folder of 100 sheets is £1. Post free.

MISCELLANEOUS BOOKLETS

These give circuit diagrams and details of Ex-Government receivers and equipment. In practically all cases the information has been extracted from official publications. Separate booklets for each piece of equipment. Booklets available covering the following:—R1155, R208, R109, TR1196, TR18, BC348, BC312, R1116, R107, R103, BC221, BC342, Pre-Amp. from RF27, Pre-Amp. from Unit 208A, T.V. Receiver from 1½-metre superhet for London or Birmingham, T.V. receiver from 3170, etc. T.V. receiver from 194 strip. Dual band T.V. receiver. Price of any of these booklets is 1/6 each—all post free.

EXTENSION SPEAKER IN METAL CABINET

This has a 6½in. P.M. Goodman's Speaker, heavy magnet type, complete with an output transformer. It is fitted in grey steel case with perforated front and back, ideal for P.A. work in canteens, clubs, etc., 27/6 each.

TWO-VOLT ACCUMULATORS

Made for the Forces by one of the most famous firms in the world. 15 amp.-hour size approx. 6in. × 1¾in. square in ebonite case, pre-charged, only need filling with acid, 5/9 each, plus 1/3 post and insurance. Six or more post free.

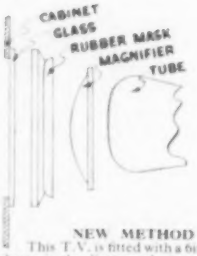

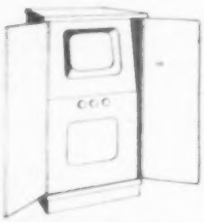

NEW METHOD IMPROVES APPEARANCE

This T.V. is fitted with a 6in. (VCR97) tube, but by using the method shown in the diagram, the impression of a much larger tube is created. We have available magnifier, mask and armoured glass in the parcel, price 29/6 the set, plus 2/6 post. Please note that the magnifier is tinted to offset the green effect. Mask and armoured glass only 7/6 the two, plus 2/6 post.

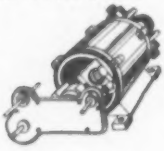

MULTI-SPEED MOTORS

You can adjust this motor to almost any speed you want, it will work directly off A.C. mains, or if you require greater power or greater speed work it through a metal rectifier. This motor is fitted with a gear box enabling speeds down as low as 1 r.p.m. to be obtained. Price 14/6, postage and packing 1/6 extra.

VALVEHOLDERS

Type	Paxolin	Amphenol	Ceramic
	s d	s d	s d
British 4-pin	6	—	9
British 5-pin	6	—	9
British 7-pin	6	—	9
British 9-pin	9	—	—
UX 4-pin	6	—	1 6
UX 5-pin	6	—	9
UX 6-pin	7	—	—
UX 7-pin	8	—	—
Large UX7	—	—	1 0
Diode B3G	6	8	—
B7G	6	8	10
B8G Loctal	9	—	—
B8A	1 3	1 6	—
B9A (Noval)	1 3	—	—
B9G	1 0	1 0	—
B12A (Duodecel)	1 3	—	—
Int. Octal	6	9	1 6
Mazda Octal	6	9	—
8-pin side Contact	—	2 6	—
Jumbo 4-pin	—	—	3 6
4-pin Hivac	9	—	—
5-pin Hivac	9	—	—
5-contact Acorn	—	—	1 6

VALVE SCREENING CANS

	s d
Suitable for standard size valves consists of three parts, bottom plate, main body and spring top	1 3
B7G fixing base and top screen with spring	1 6
Screen for octal G.T. Valves	6

VALVE RETAINERS

Spring type for EF50	3
Threaded type for EF50	3
General type for all valves, consists of a silk cord and two springs	3

VALVE TOP CONNECTORS

Type	Plain	Scr'ned	Insulated
	s d	s d	s d
British ¼in. top	1½	9	1 6
American ¼in. type	1½	9	1 6
Screw to clip adaptor (for modern equivalents)			6

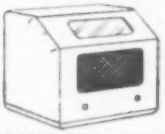

BARGAIN FOR CALLERS ONLY

Cabinet size 12in. × 10in. × 7in. deep, nicely finished in pastel shades, suitable for bedroom radio or extension speaker. Only 7/6 each. (We regret we cannot dispatch these.)

TUNING ASSEMBLY

Comprises 2 gang condenser, 6 iron cored coils, dial, wave-change switch and trimmer assembly for superhet covering 13-500 metres. Price 27/6.

COIL PACK

Covering same range as above, aligned for 465 kc/s I.F. Price 25/-.

SPADE TERMINALS

Heavy duty, fit ex Government car batteries, 9d. each. Bin C20A.

Q-MAX CHASSIS CUTTER

For electricians and radio engineers. Will cut steel, aluminium, etc. Will save its cost over and over again. ⅜in. (button base), 9/6 each, key 9d. extra. ½in. (D8A base), 9/6 each, key 9d. extra. 1in. (jacks, etc.), 12/6 each, key 1/- extra. 1¼in. (octal base), 12/6 each, key 1/- extra. 1½in. (English bases), 12/6 each, key 1/- extra. 1¾in. (EF50 base), 12/6 each, key 1/- extra. 2⅛in. (meter), 25/- each, key 1/6 extra.

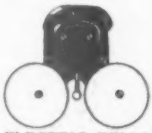

ELECTRIC BELLS

Loud ringing with double gong, operate off hand magneto or A.C. mains. Price 25/-.

Ex-equipment small round type, e.g., all the works under the dome for operation from dry batteries. Price 3/6 each.

Similar ditto, but for use on A.C. mains or magneto. Price 3/6.

PYREX AERIAL INSULATORS

Ideal for aerial connections through cabin walls or through panels. Consists of glass dome with threaded rod and terminal ends, and metal fixing flange. Price 2/- each.

FLEXIBLE COUPLINGS

These are sometimes known as bellows couplings because they will extend as well as bend. They are ideal for joining shafts which are out of alignment and for slug tuning controls, where the core has to come in and out. Price 1/9 each.

TRANSFORMER BARGAINS

All by famous makers.

200 mA., 340-0-340 v. 6.3 v. at 4 amps., 5 v. at 4 amps., 4 v. at 3 amps., unshrouded but fully impregnated, a really first-class transformer. Price 25/-.

150 mA., 425-0-425 v. 6.3 v. at 6 amps., 6.3 v. at 6 amps., 5 v. at 3 amps., 4 v. at 2 amps., 4 v. at 1 amp. Price 65/-.

150 mA., 350-0-350 v. 6.3 v. at 4 amps., 5 v. at 3 amps., upright mounting. Price 32/6.

80 mA., 300-0-300 v. 6.3 v. at 4 amps., 4 v. at 3 amps., half shrouded drop through. Price 18/6.

80 mA., 320-0-320 v. 6.3 v. at 4 amps., 5 v. at 3 amps., half shrouded drop through. Price 19/6.

70 mA., 230-0-230 v. 6.3 v. at 3 amps., 5 v. at 2 amps, fully shrouded upright mounting. Price 22/6.

60 mA. 260-0-260 v. 6.3 v. at 3 amps., 4 v. at 2 amps., half shrouded drop through. Price 16/6.

60 mA., 260-0-260 v. 4 v. at 4 amps., 4 v. at 2 amps. Price 16/6.

T.V. TRANSFORMERS

TYPE 1.—Fixed Primary H.T. Secondary 425-0-425 v. at 250 mA. 4 v. at 6 to 8 amp., 4 v. at 5 to 6 amp., 5 v. at 2.5 amp, 2 v. at 1 amp. Dimensions are 4¼in. × 4in. × 4¼in. Price 27/6, plus 2/6 packing and postage.

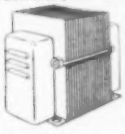

TYPE 2.—Primary as Type 1. H.T. Secondary 300-0-300 v. at 150 mA. L.T. 7.5-0-7.5 v. at 3 amps. and 4 v. at 3 to 4 amps. Dimensions are 4¼in. high × 4in. × 3¼in. Price 17/6, plus 2/- postage and packing.

AUTO TRANSFORMERS

For operating 100 v. apparatus off 230 v. mains or vice versa.

Totally enclosed 50-75 watts 20/-
Totally enclosed 100-150 watts 32/6
Open Type, 100-150 watts 25/-

FILAMENT TRANSFORMERS

6.3 v. at 1 to 1.5 amps., standard type for receivers. Price 6/6.

6.3 v. at 1.5 to 2 amps., standard type. Price 8/3.

2 v. at 2.5 amps., highly insulated for television. Price 7/6.

STOP PRESS OFFER

3-speed Gram. Motor

£4/15/-.

Limited quantity — act quickly.

GUESS WHAT FOR £5

This month it is ingenuity which is required to win our Competition. The chassis illustrated alongside is our IF/AF Amplifier for which we think there is a big future. It is fully described overleaf.

The IF's are standard 465 kc. type which are tuneable over a fairly wide range. Some obvious uses are: —

(a) As a Signal Tracer.
(b) As a standard Amplifier.
(c) As a radio set when a tuning condenser and coil pack are added.
(d) As a device for checking and calibrating coil packs during manufacture.

These are uses which have already been suggested, we believe there are many more and we invite your suggestions. Our prizes to the value of **£5, £3,** or **£2** will be awarded to the most ingenious.

Final day for entry February 29th.

DEMOBBED VALVES

Gives the commercial equivalents of many thousands of Service valves, and conversely gives service equivalents of commercial types, an invaluable publication recently revised. Price 2/3.

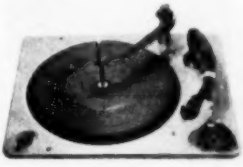

AUTO-CHANGE GRAM UNITS

Single speed and 3-speed models available from stock. The one illustrated is the Collaro 3-speed model with dual-purpose pick-up. Price **£15/11/9**, carriage paid.

OFFICE INTERCOM OUTFIT

Consists of Master station and 3 sub-stations. The master can contact any of the sub-stations, all of which can call the master. In new, unused and good working order and including 3 speakers. Limited quantity

Price **£14/10/-**.

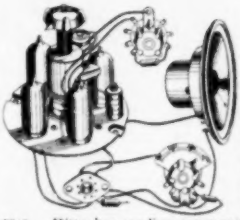

BATTERY PERSONAL CHASSIS

This 4-valve all-dry battery-operated receiver is of such small dimensions that it will fit into a cabinet only about 6in. × 4in. × 3in. and still leave ample room for batteries. The chassis is all wired and complete with speaker, volume control, wave-change switch, etc., and only first-grade components have been used. Prices are: Chassis complete less valves (three type 1T4 and one type 3V4)—to operate on long and medium wave-bands, **59/6**. Ditto but medium wave only, **49/6**. Add 2/6 to cover postage and insurance.

Orders by post are dealt with by our Ruislip depot. To avoid delay address to Electronic Precision Equipment, Ltd., Dept. 2, Windmill Hill, Ruislip, Middlesex.

THERMAL DELAY SWITCH

Hermetically sealed with 4-pin base, the operating voltage is 6 v. with a delay of 1 minute. Price **12/6**.

TUNGAR VALVE RECTIFIERS

Replacement for many home and industrial chargers:

1 amp. type 6B502. Price **9/6**.

3½ amp. type 6B507. Price **12/6**.

MERCURY VAPOUR RECTIFIERS

CV2946 max current, 1.8 max. 1,000 v. Price **6/6**.

VU29 max current 2.5 amps., max. 2,000 v. Price **9/6**.

BD10, max. current 2.5 amps max. 1,000 v. Price **£6/10/-**.

TUNING UNITS

American made units, available are TU5B, TU6B, TU9B, TU10B, TU13A, TU17A, TU25A, TU47, TU48, TU49, TU51, TU52, TU54, TU60. All **19/6** each, plus 3/6 carriage.

ALL MAINS CHASSIS

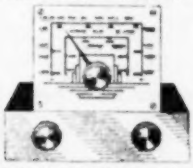

This is the equivalent of a 4-valve receiver for it uses three valves and metal rectifier. It is all wired up ready to work off A.C. mains, complete with modern valves, ganged tuning, high precision dust-cored coil, first grade condensers and resistors, all on metal chassis. Tunes long and medium wave-bands. Large clear dial. Receives Home services; Light programme; Luxemburg, etc. Chassis size approximately 9in. × 4in. × 5in. Complete with valves, but less speaker, **69/6**. Suitable speaker with matching transformer, **16/6**—nothing else needed. Postage and packing 2/6 extra.

TELEPHONE JACK PLUGS

As illustrated **7d.** each, sockets to suit, **10d.** each.

Orders under £2 add 2/6, under £1 add 1/9. Postable items can be sent C.O.D., additional charge approx. 2/6. List 6d.
Early Closing days: Wednesday, Ruislip; Saturday, City.

ELECTRONIC PRECISION EQUIPMENT

WINDMILL HILL, RUISLIP, MDX. Phone: RUISLIP 5780

152-153 FLEET STREET, E.C.4. Phone: CENTRAL 2833

ELPREQ PAGES

HIGH - VOLTAGE BLOCK CONDENSERS 4 mfd. 3,000 v., new and perfect, a real bargain at 15/-. Many other sizes in stock, please state your requirements.

BASEBOARD MOUNTING VALVE-HOLDERS For Octal Valves 2/3 each.

ADJUSTABLE THERMOSTAT

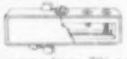

These have, silver contacts rated at 1 amp. 250 v. and can be adjusted to operate from 70° to 90° F. These are suitable for directly controlling aquarium heaters, electric blankets, etc. They can also be used to control heating installations if the thermostat is used to operate a larger relay or contactor. Price 3/6.

FUSE BOARD In metal case with conduit knockouts, 12/6.

T.V. BUILDERS

"Practical Television," October and November, showed how the 14-valve Government surplus unit type RDF1 could be made into a very useful Televisor. We have a quantity of these units, the price is 49/6, plus 5/- carriage. A reprint of the article is also available free with the unit or separately 1/6 (refunded if you purchase later).

SLIDER RESISTORS

Heavy-duty type size.
Size 7in. × 1¼in., 1.2 ohms 15 amps. Price 15/-.
Size 9in. × 1¼in., 3 ohms 10 amps. Price 15/-.
Size 13¼in. × 1¼in., 11 ohms 4.5 amps. Price 22/-.

OCTOPUS CLIPS

An ideal clip for fixing anything to a rod or pole, this is self adjusting from 1¼in. to 4¼in. Price 1/- each.

12-CELL ACCUMULATOR

This accumulator can be coupled up to give 24 v. with all cells connected in series or 12, 6 or 2 volts by series parallel arrangements. They were originally made for the Admiralty by a leading manufacturer, have never been filled, and are in excellent condition. Each is contained in a wooden crate as illustrated. Price 27/6 each. Postage and insurance 5/-.

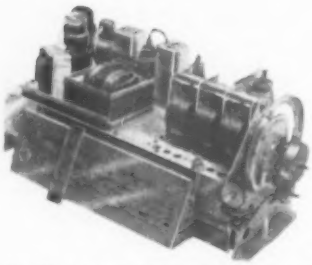

7 VALVE, 5 WAVE-BAND RADIO CHASSIS

A famous set by a famous manufacturer. Undoubtedly a serious listener's receiver. Among many special features are a H.F. stage and tuning indicator. Tunes up to 11-metre band. Price new with all valves, but less speaker, **£14 19/6**, carriage and packing 15/-, partly returnable. A.C. mains and car-battery models are available.

PROFESSIONAL RADIOS YOU CAN MAKE

You will find that the building of our all-mains radio receivers is simplicity itself, and the more you make the less time each takes, everything down to the last nut and bolt is supplied, and everything fits together in a professional manner. When finished the receiver looks and plays as well as those being offered in radio shops at anything between £10 and £14.

The one illustrated above we call "The Occasional" in a choice of colours, Ivory, Walnut or Green, and the T.R.F. costs just less than £6 to make, while the superhet costs approximately £9.

The other radio illustrated we call the "White Lady" this is an extra fine cabinet of pure white. The complete T.R.F. receiver costs about £6 5/- to build, and the superhet receiver costs about £9 5/- to build. Constructional data for either set is available at 1/6 post free.

5-VALVE IF AF AMPLIFIER
(For AC/DC working.)

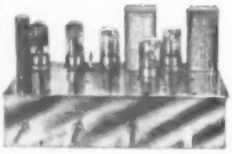

The subject of this month's "Guess What" Competition. This is on an aluminium chassis, size 11¼in. × 7in. × 3in. deep. The layout is neat and simple and provision is made and in fact holes are drilled so that tuning condenser and coil pack may be easily fitted if same are required. Alternatively this vacant space can be used for mounting a control panel to which various points of the circuit can be brought to plugs, this making faults tracing by circuit substitution a very simple job. It uses one of the latest valve line-ups as follows: 14S7 Triode Hexode, 7B7, IF Amplifier, 7C6 D.D.T. 35A5 output, 35Z3 Rectifier. The IFs are preset at 465 Kc/s, but are variable over a fairly wide range. Price £6 10/-.

THIS MONTH'S SNIP

This month we offer you a really lovely loudspeaker fabric "Somweave" at approximately a third of today's cost. It is 42in. wide and our price is 12/- per yard or panels 12in. × 12in., 1/9 each. This is also very suitable for covering plain wooden cases, for portable radiograms, amplifiers, etc.

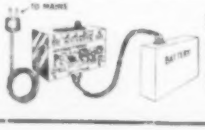

RECHARGE DRY-BATTERIES New device which will save its cost within a very short while for with it the life of batteries, either H.T. or L.T. can be extended six or more times. Price £3/5/-.

ELECTROLYTIC CONDENSERS

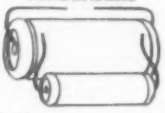

1 mfd. 150 v.	1/-
1 mfd. 250 v.	1/-
1 mfd. 450 v.	1/3
2 mfd. 350 v.	1/3
2 mfd. 450 v.	1/6
4 mfd. 350 v.	1/8
4 mfd. 450 v.	1/10
8 mfd. 150 v.	1/6
8 mfd. 350 v.	2/-
8 mfd. 450 v.	2/6
8 mfd. 500 v.	3/3
8 mfd. 500 v. centre-screw fixing	1/6
8 mfd. 600 v. centre-screw fixing	1/9
16 mfd. 350 v.	2/9
16 mfd. 450 v.	3/6
16 mfd. 500 v.	4/9
32 mfd. 150 v.	2/3
32 mfd. 250 v.	2/3
32 mfd. 350 v.	2/9
8 mfd. × 8 mfd. 350 v.	3/-
8 mfd. × 8 mfd. 450 v.	3/9
8 mfd. × 8 mfd. 500 v.	3/9
8 mfd. × 16 mfd. 450 v.	4/9
8 mfd. × 16 mfd. 500 v.	6/-
16 mfd. × 16 mfd. 450 v.	6/-
16 mfd. × 16 mfd. 500 v.	7/-
20 mfd. × 20 mfd. 200 v.	4/-
24 mfd. × 24 mfd. 200 v.	4/6
25 mfd. × 25 mfd. 200 v.	4/9
32 mfd. × 32 mfd. 150 v.	4/9
32 mfd. × 32 mfd. 450 v.	6/9
100 mfd. × 100 mfd. 150 v.	5/6
10 mfd. 25 v.	1/-
12 mfd. 50 v.	1/4
20 mfd. 50 v.	1/6
25 mfd. 25 v.	1/6
25 mfd. 50 v.	2/-
50 mfd. 12 v.	9d.
50 mfd. 50 v.	2/3
250 mfd. 12 v.	2/3
8 mfd. × 8 mfd. × 8 mfd. 450 v.	3/9

"SNIPERSCOPE"

Famous wartime "cats eye" used in conjunction with a lens system and h.t. for seeing in the dark. This is an infra-red image converter cell with a silver caesium screen which lights up (like a cathode ray tube) when the electrons released by the infra-red strike it. It follows that as light from an ordinary lamp is rich in infra-red these cells will work: burglar alarms, counting circuits, smoke detectors and the hundred and one other devices as will the simpler type of photo cell. Here then is a golden opportunity for some interesting experiments price 9/6 each, or six for 52/6. Data will be supplied with cells if requested.

RADIO CHEMICALS CLEAR CEMENT. Almost instantaneous drying for coil winding and all repairs, 1/6 per tube.

"ENAMACLEAN." For safely removing the enamel off the finest wires, 2/- per tube.

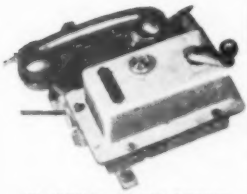

EX-ROYAL NAVY SOUND POWERED TELEPHONE

These require no batteries, and will go for long periods without attention. Complete with generator and sounder which gives a high pitched note, easily heard above any other noise. Also fitted with an indicator lamp which in quiet situations can be used instead of the sounder, or where several 'phones are used together will indicate which one is being called. Size 7¼in. × 9in. × 7¼in., wall mounting, designed for ships' use, but equally suitable for home, office, warehouse, factory, garage, etc. Price 37/6 each, plus 3/6 carriage.

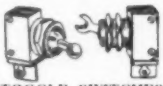

TOGGLE SWITCHES

Metal body standard size, made by a leading maker. Available with round dolly or with special V cut dolly. State which type when ordering. Price while stocks last only 1/6 each.

EX-GOVT. CATHODE RAY TUBES

Note :—All these tubes have green fluorescence.

VCR97. Brand new and unused, these are not the "cut-off" type. Gives full picture. Price 42/6, carriage and insurance 5/- extra.

5CP1. 5in. electrostatic, American manufacture—medium persistence, suitable for T.V. or 'scope, in original cartons, 19/6, carriage and insurance 2/6.

VCR517. 6in. electrostatic, medium persistence, suitable for T.V. or 'scope work — unused, ex-new equipment, 22/6, carriage and insurance 5/-.

VCR516. 9in. magnetic tube, long persistence which makes it rather unsuitable for T.V. Price £2/10/-, postage and insurance 10/-.

CV3776. 5in. electrostatic medium persistence suitable for experimental T.V. or 'scope work—unused 22/6, plus 5/- carriage, etc.

VCR138. 3½in. electrostatic short persistence, suitable for T.V. and ideal for 'scope work, 27/6, plus 3/6 carriage, etc.

VCR112. 5in. electrostatic, persistence not known, 22/6 each, plus 5/- carriage, etc.

CV966. 6in. electrostatic, persistence not known, 22/6 each, plus 5/- carriage, etc.

RADIOGRAM CABINETS

Full size console type cabinets with highly polished walnut finish. Designed to take standard type auto change gram unit. You can have these at £12/10/- each, which means a really nice radiogram for less than £30, for we can supply a 5-valve 3-waveband chassis at £10/10/-. (Minor alterations to the radio chassis will, of course, be necessary.)

Special offer. Gram unit ordinary from £5/5/-, auto from £11/15/-. Cabinet complete with auto change gram. unit and pick-up £22/10/-. Please note delivery charge will depend on distance.

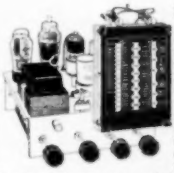

3 WAVE-BAND 5 VALVE SUPERHET CHASSIS

Brand new, tested and ready for immediate operation, full vision scale size 6in. × 8in. covering the long wave 900-2,000 metres, medium wave 185-550 metres, and short wave 16-50 metres. Complete with valves and covered by our six months' guarantee.

First-class parts, Parmeko mains transformer, Erie resistors, Hunts condensers, etc. Special points include (1) Flywheel tuning. (2) Dust cored I.F.'s. (3) Sockets for extension speaker and pick-up. (4) 4 watts output. (5) Coil assembly removable as a unit. Price complete with 8in. speaker £10/10/-, carriage, packing and insurance, 7/6d. extra.

A POWER PACK FOR 15/-

Efficient power supply, O.K. for operating a receiver, amplifier, instrument or other device requiring up to 80 mA. at approx. 250 v. Parcel consists of filament transformer, rectifying valve, smoothing resistor and 16 × 16 mfd. 350 v. Electrolytic condenser. Note the filament transformer will supply enough current to operate 3 or 4 other 6.3 v. valves.

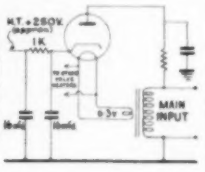

EQUIP YOUR DEN

You often need to measure the capacity of small condensers, so why not make a unit to do this. We can supply circuit diagram and all parts, total cost being only 10/-, battery model; 25/- mains model. Circuit separately 1/6, refunded if you buy the kit.

RADIO STETHOSCOPE.

A novel device aptly called a Radio Stethoscope is described in a recent edition of the "Radio Constructor." This is compact and can be slipped into the pocket rather like a fountain pen. With it in most districts a receiver can be checked from the grid of the first valve right through to the output without a signal generator. The stethoscope will operate in both L.F. and R.F. circuits without alteration. It is a complete fault finder.

The only parts needed to make the simple circuit tracer are a pair of crocodile clips, a germanium crystal, and a paper tubular condenser and we will supply whole outfit for 6/6 post free, and with each outfit we will give re-print of the article as it appeared in the "Radio Constructor."

NOTE.—If you wish to make it up as a pocket unit then you will need a few other odds and ends, solder tags, etc., from your spares box.

Orders by post are dealt with by our Ruislip depot. To avoid delay address to— E.P.E. Ltd., Dept. 2, Windmill Hill, Ruislip, Middx.

MIDGET EXTENSION SPEAKER

3½in. moving coil speaker in bakelite cabinet with metal grill and back fitted with terminals, size 4½in. × 4in. × 2in. Ideal as desk extension or for bedroom, kitchen, etc. Also makes good microphone. Price 18/6, or cabinets only 6/6.

SPEAKERS

P.M. TYPE

2½in.	14/6
3in.	14/6
3½in.	12/6
5in.	13/6
6½in.	13/6
6½in. Truvox Monabolt	18/6
8in.	14/6
12in.	£3

ENERGISED TYPE

6½in. Rola, field resistance 700 ohms, 12/6. 10in., field resistance 1,100 ohms, 20/-, post paid. Add 1/- per speaker for packing and insurance.

REPEATER MOTOR (SELSYN)

Made for the Government, number AP.1730P. Size 1½in. deep, 2½in. diameter.

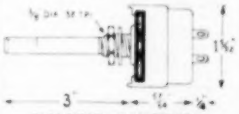

VOLUME CONTROLS

We carry a full range of standard-size volume controls from 2K, to 2 meg. Prices are: less switch, 3/-; Single pole switch, 4/-; double pole switch, 5/-. We can also supply midget-type controls, less switch, 4/-; single pole switch, 5/9; double pole switch, 6/6. Each of these midget controls has a serial number and carries a 12-month guarantee by the makers; they are made on the new moulded track principle and really do perform well.

MINIATURE MICROPHONES

Carbon type measures less than 1¼in. across and only ¼in. thick. 2/6 each.

Orders under £2 add 2/6, under £1 add 1/9. Postable items can be sent C.O.D., additional charge approx. 2/6. List 6d.
Early closing days: Wednesday, Ruislip; Saturday, City. **Telephone: Ruislip 5780**

WINDMILL HILL, RUISLIP, MDX. Phone: RUISLIP 5780

PRECISION EQUIPMENT (2) **152-153 FLEET STREET, E.C.4. Phone: CENTRAL 2833**

CLYDESDALE

Bargains in Ex-Service Radio and Electronic Equipment

ELECTRONIC IGNITION TESTER
Type V.E.D. Patt. 563562, made by English Electric. In Original Maker's Case.

A Cathode Ray tester employing an entirely new technique in ignition testing of internal combustion engines. Enables the electrical performance of the entire ignition system to be observed on the screen of the Cathode Ray tube while the engine is running. Will operate from 6, 12 and 24 volts D.C. or 230 v. A.C. Built into a black crackle case with hinged front and carrying handle. Dim. 15½ × 13½ × 11½in.

CLYDESDALE'S PRICE ONLY **£35 . 0 . 0** CARRIAGE PAID

BATTERY CHARGER
Rectifier type 42A. Ref. 10DB 1630

A compact battery charger, output 4 amps. at 6 or 12 volts D.C. Input 230 v. A.C. 50 c.s., with ammeter, reversible lines control switch for each circuit, input and output points, contained in well ventilated black crackle metal case, for wall or bench mtg.

CLYDESDALE'S PRICE ONLY **£5.19.6 each** CARRIAGE PAID

220 VOLT D.C. CHARGING BOARD

For charging 6 to 60 cells at 5 amps. Made by Bepex, Cricklewood, with 100 ohms resistance, 5 amp. meter, 250 v. cutout fuses and switches, all mounted on metal case 21in. × 12½in. × 4½in. Well ventilated with 4 lugs for wall mtg.

CLYDESDALE'S PRICE ONLY **£2 . 5 . 0** CARRIAGE PAID

EX-U.S.A.A.F. IN ORIGINAL CARTON COMBINED PRESSURE AND VACUUM PUMP

1374-1798 made by G.M.C. (Delco-Remy) 24 v. D.C. 11.2 amp., 0.500 r.p.m., 4 h.p. motor, with vacuum and pressure pumps, whole assembly 19 × 7½ × 9in. Shock mtd. on board 14½ × 9½ × 3½in. Accessories include oscillating and Schrader regulating valve.

CLYDESDALE'S PRICE ONLY **£4 . 4 . 0** CARRIAGE PAID

PUMP DESSICATOR ADM. PATT. 12128 FOR TELESCOPES AND BINOCULARS.

Hand operated complete with intake pet cock and connections. Stroke cap. 180 c.c., fitted bronze/S. gauge, reads 10-100 cm. vacuum gauge 0 to 60 in. In steel transit case 20½ × 9½ × 9½in.

CLYDESDALE'S PRICE ONLY **£5 . 10 . 0** CARRIAGE PAID

COOLANT PUMP BY PACKARD U.S.A.

A turbine type pump, directly driven from semi-ball joint mtd. socket by motor not supplied, clockwise rotation with water jacket, gasket seal, etc.

Dia. of turbine 6in., dia. of pump chamber 8½in. depth 2¾in. Inlet and outlet dia. 1¼in. Over all dim. 11½ × 7½ × 13½in.

CLYDESDALE'S PRICE ONLY **49 6 each** CARRIAGE PAID

FEATHERING PUMP SU 402

Driven by 24 v. D.C. motor type C2001 through 2:1 reduction gear fluid mounted to two 7-inch wheels. Safety valve fitted. Overall dimensions 12½ × 6 × 8in. Pumping rate, lubricating oil 2 gals per min. approx. Air pressure 40lb. per sq. in. Hi pressure, over 1000lb. per sq. in. Inlet and outlet 1in.

CLYDESDALE'S PRICE ONLY **£2 . 10 . 0** CARRIAGE PRICE

HAND GENERATOR 10 WATT MK. II

Designed for W.S.48 and W.S. 18 direct to two handles, complete with operator's seat. Speed should be 50-70 r.p.m.

Smoothed outputs: 100 v. 60 m.a., 24 v. 2 a. and 12 v. (generator 230 v. 2½ × 2½ × 6½in., weight 13lb.

Leg × seat dim. 24 × 9 × 20in., weight 25lb.

Legs 12×12in., 28 × 4in.

CLYDESDALE'S PRICE ONLY **45 -** CARRIAGE PAID

TELEPHONE TYPE TELE.F

A table type Field Telephone in bakelite moulded case, with bell and magneto generator, operated from internal 2-volt "B" or "T" cell battery (not supplied). Suitable for two-way communication up to a mile distance, when speech is easy. Overall dimensions 9½ × 8½ × 5½in. Weight 6lb.

CLYDESDALE'S PRICE ONLY **£3 . 19 . 6** POST PAID

VISUAL SIGNALLING

Signal Lamp Type 2. Ex-R.A.F. ref. 5A/3284. Complete reflector 4½in. dia., 1½in. depth and 12 v. 20 w. prefocus lamp, enclosed, and mounted with two handle grips, triggered for a finger pressure lever. Alignment sights with rubber eye piece fitted, plus 50 ft. of rubber covered flex terminated with 2-pin 2 amp. plug.

In wood transit case 9½ × 8 × 6½in. with handle.

CLYDESDALE'S PRICE ONLY **25 -** POST PAID

Spare Lamps extra, 1 6 each.

NAVIGATION

Pneumatic Hand Compass Type 05-A. Ex-R.A.F. fitted with sighting prism, enabling a viewed object to be sighted and the bearing read simultaneously.

The Cardinal disc, marked in degrees 0-360, can be illuminated for night use, provision for batteries (not supplied) in handle with ON-OFF switch.

Dim. 4½in. dia. length 9in. In padded transit case 10½ × 9½ × 5½in.

CLYDESDALE'S PRICE ONLY **£3 . 15 . 0** POST PAID

CDN. NO. 9 SET MK. I RECEIVER UNIT WITH POWER SUPPLY UNIT

A ten-valve 7/ARP3, 2/12SC7, 12V4, band-pass, superhet receiver, frequency range, 2 to 5 mcls., with built in calibrator, switched H.T. and "S" meter, H.F. and L.F. gain, B.F.O., etc., etc.

Separate Power Unit operation from 12 v. D.C., 115 v. A.C. or 230 v. A.C./Z4 cold cathode rectifier, with spares kit, all valves, aerial, insulators, headphones.

CLYDESDALE'S PRICE ONLY **£10 . 0 . 0** CARRIAGE PAID

W.S.18 RECEIVER SECTION

Superhet chassis, range 6-9 mc/s. (50-33.3 metres) with 4 valves 3/ARP.12, AR8, etc., etc., on 8½ × 5 × 1in. chassis, front panel, 9½ × 4½in.

CLYDESDALE'S PRICE ONLY **25 -** POST PAID

Circuit 2/3.

Also available with partly stripped (M.O.S.) Tx. section, no valves, or meter, in metal carrying case. 19in. 11 × 10 × 17in.

CLYDESDALE'S PRICE ONLY **37 6** CARRIAGE PAID

Circuit for 4/6.

FOR EXPORT ONLY
WIRELESS SET NO. 38 MK. 2. BRAND NEW

A haversack type transceiver-range up to 5 miles. Frequencies 7.7 to 9 mc/s., 5 valves, 4/ARP12, ATP4, operated from dry batteries, H.T. 120 v., L.T. 3 v. (not supplied), complete with headphones, junction box, spares, satchel and instruction card.

4 complete units packed in wood case, 37½ × 14 × 14in.

PRICE ON APPLICATION

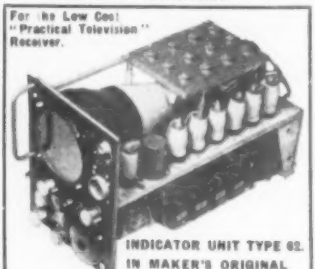

INDICATOR UNIT TYPE 62. IN MAKER'S ORIGINAL CASE.

Containing VCR97 C.R.T. with mu-metal screen, 100k/s. crystal unit 10X/2, 16 VR65's (SP61), 2 VR54's (EB34), 2 VR97's (EA50), plus various pots, switches, H.V., conds., resistors, etc., built on metal chassis to fit box 18 × 8½ × 11½in.

All controls brought to front panel beside viewing screen.

CLYDESDALE'S PRICE ONLY **£5 . 9 . 6** CARRIAGE PAID

Also available in used, Fair condition.

CLYDESDALE'S PRICE ONLY **79 6 each** CARRIAGE PAID

Circuit at 1/3.

MAINS TRANSFORMER (TOP QUALITY)

Pri. tapped 200-250 v. A.C. Sec. 350-0-350 v. 180 m.a., 6.3 v. 3 a., 6.3 v. 6 a., 5 v. 3 a. Price post paid **65** each

E.H.T. TRANSFORMER (TOP QUALITY)

Pri. 4 tapped 230-250 v. A.C. Sec. 2500 v. 3 m.a., 4 v. 1 a., 4 v. 1 a. C.T. Price, post paid **50** each

NEW LIST NO. 8

Bring data's and illustrations of ex-services items and cancelling all previous lists and supplements.

Now Ready—Price 1/6

Price credited on first purchase of 10/- or over.

VIEWMASTER TELEVISION

Built it yourself. Circuits with templates and all data (London "A" 5/-
Sutton Coldfield "B" 5/-
Holme Moss and Kirk-o-Shotts "C" 5/-
All components normally in stock. Subject to manufacturer's production. Coils for all areas including Band III.
Hedge Mounted Kirk-o-Shotts, each 2/-
Set of Coils, Filter and Choke, post paid 30/-

Components for the Constructor Mfg Surplus

RADIO CABINET

A handsome walnut finish wooden cabinet well ventilated with removable back panel. External dim.: ht. 9½in. × 15in. × 8in. approx. External appearance facing cabinet speaker opening right side. Ht. 2½in., 18½in. 4½in. Dial opening, left side, ht. 3½in., 6½in. 5½in. Internal dim.: ht. 8½in. × 7½in. approx.

CLYDESDALE'S PRICE ONLY **25 - each** POST PAID

RADIO CABINET

Smart plastic cabinet, with ornamental speaker grill and dial apertures, top front centre.

Colours: walnut, mahogany, white and black.

External dimensions: ht. 12½in. × 7½in. × 6½in.

Internal dimensions: ht. 11in. × 6½in. × 4½in.

CLYDESDALE'S PRICE ONLY **15 - each** POST PAID

8in. P.M. LOUDSPEAKER

With transformer, standard chassis type. Brand new in original carton.

CLYDESDALE'S PRICE ONLY **17 6 each** POST PAID

2-GANG VARIABLE CONDENSER

Cap. per section 0.00025 mfd. Size 2½ × 2½ × 1¼in. with standard spindle.

CLYDESDALE'S PRICE ONLY **7 6 each** POST 9d.

3-GANG VARIABLE CONDENSER

Cap. per section 0.0005 mfd. Size 4 × 2½ × 2½in. with standard spindle.

CLYDESDALE'S PRICE ONLY **7 6 each** POST 9d.

L. T. CHOKE ADM. AP45069

0.5 henries, 0.1 ohms at 2.5 amps. Made by Parmeko. Dims. 3 × 2½ × 1¼in., 4-hole fxg.

CLYDESDALE'S PRICE ONLY **3 6 each** POST 9d.

MOVING COIL METERS
Ampmeters

E784. Range 0-1 amp., price each **12 6**. 2½in. round flush mtg., drilled flange, post paid.

E785. Range 0-10 amps., price each **12 6**. 2½in. round flush mtg., plug-in. Post paid.

D.C. Voltmeters

E729. Range 0-750 volts, 200 ohms per volt, each **25 -**.

E750. Range 0-1,500 volts, 250 ohms per volt, each **26 -**.

E751. Range 0-3,000 volts, 200 ohms per volt, each **27 6**.

All 2½in. round, flush mtg., drilled flange. Post paid.

VARIAC TRANSFORMER

Type 200 C.U. Ref. ZC70334. Three-hole flange mounting. Input 115 volts A.C. Output 0-135 volts A.C. at 800 watts. 10½in. × 6½in. × 5½in. Wgt. 9lb.

CLYDESDALE'S PRICE ONLY **£3.15.0 each** POST PAID

EX-U.S. NAVY TEST OSCILLATORS

TS24 ARRE. A battery powered unit for alignment of T.R.F. aircraft radio, produces 465 kc. H.F. signal and 540 to 830 kc/s. tunable L.F. signal. Using two 1S5 acorn tubes, a safety time switch with indicator (30 minutes) is fitted.

Finished in black crackle case 9½ × 7½ × 7in.

CLYDESDALE'S PRICE ONLY **£4 . 9 . 6** CARRIAGE PAID

Circuit available at 1/3.

TS24A ARRE. Similar TS24, has additional features, tone modulation, three 1S5 tubes, optional audio signal output, otherwise description and dimensions the same.

CLYDESDALE'S PRICE ONLY **£4 . 19 . 6** CARRIAGE PAID

TRANSMITTER TUNING UNITS

Unused, but externally soiled, cases slightly dented and scratched, dim. 17½ × 7½ × 8in. approx.

T.U.5B, a few only at **35 -**.

T.U.6B, T.U.7B, T.U.8B, T.U.9B, T.U.26B, 1st grade at **22 6** each. 2nd grade at **18 6** each.

AMPLIFIER A1271

A one-valve (VR56=EF36) Amplifier Chassis, with 400 ohm 1M 2B relay, 2 transformers, vol. control, cond. and resistors, mounted on rubber in a black finished metal case 5 × 5 × 4½in.

CLYDESDALE'S PRICE ONLY **10 6** POST PAID

GLASS DOMED INSULATOR 154

Ref. 10B/404, 10B/507. With metal clamping ring. Insulating bush with rubber washer, top dome enables insulator to be waterproof by tightening. Flange dia. 6½in. Dome 2 × 6in.

CLYDESDALE'S PRICE ONLY **7 6 each** POST 1/-

70/80 ohms **CO-AXIAL CABLE**, dia. 5 mm., 7/0076 centre polythene insulation. Ideal for T.V. aerials.

Price **1 3** per yard. Minimum quantity 10 yds. or 100 yards coil at **£5** each.

Large and varied selection of Books on Radio and Television always available. Also Circuits of ex-Service units.

Order direct from —

CLYDESDALE SUPPLY CO. LTD. 2 BRIDGE STREET GLASGOW . C5

Phone: South 2706 9 Branches in Scotland, England and Northern Ireland

LASKY'S RADIO

Tele-vision Renowned for Service & Reliability

TELEVISION CONSOLE CABINETS

DE LUXE BEAUTIFUL WALNUT VENEER

For 12in. cathode ray tubes. Beautiful figured medium walnut finish, with high polish. Fitted with shelf for receiver, glass, speaker baffle and fret, and castors for easy movement. Undrilled, Suitable for use with the Viewmaster. "Practical Television," "Practical Wireless," and "Wireless World" televisors.

LASKY'S PRICE

£8 . 10 . 0

Carriage 12/6 extra.

Outside dimensions of cabinet: 17½in. x 16½in. x 32in.

Why not convert your table receiver to a console?

Adaptor frames for fitting 9in. or 10in. C.R. tubes available if required.

W.B. & PLESSEY T.V. COMPONENTS.

Tube Supports	16/-
Line E.H.T. trans.	27/6
Frame trans.	22/6
Boost choke	5/9
Scanning Coils	29/6
Heater trans. 103	37/6
103A	52/6
Focus ring. Triode	21/6
Tetrode	21/6

Postage extra.

SUPPLEMENT YOUR E.H.T. FROM THE LINE FLYBACK, AND USE A LARGER C.R. TUBE, by using a BOOST E.H.T. KIT. Comprises one selinium rectifier, one 2-meg. resistance and two T.C.C. .001 mfd. 6 kV condensers. For converting 9in. T.V. receivers to 12in.

LASKY'S PRICE 20/- Post Free.

METAL RECTIFIERS FOR TELEVISION.

WX3	3/7
WX6	3/7
14A86	18/3
14D36	11/-
36 EHT 25 1·8 Kv.	13/10
36 EHT 35 2·5 Kv.	18/2
36 EHT 40 2·9 Kv.	20/6
36 EHT 45 3·4 Kv.	22/6
36 EHT 50 3·6 Kv.	24/10
36 EHT 100 7 Kv.	28/-

Postage 6d. per item extra.

FRAME BLOCKING OSCILLATOR TRANSFORMERS. **LASKY'S PRICE 4/6** each. Post 4d. extra.

CO-AXIAL CABLE
Standard impedance.
Single screened, 1/- per yard.
Twin screened, 1/6 per yard.
Twin balanced feeder, 7½d. per yard. Post extra. Any length cut to your requirements. 10% discount on 50 or more yards.

CATHODE RAY TUBES. All types and sizes available from stock. Brand new and fully guaranteed.

12in.	from £18 4 10
15in.	from £22 16 10
16in.	from £24 6 5

CATHODE RAY TUBE SCREEN ENLARGERS. 6in. clear, 25/-; filter 27/6, carriage and ins. 3/6 extra. 9in.-10in. clear 55/-; 12in. clear 75/-, filter 80/- carriage and ins. 7/6 extra.

EVERYBODY IS BUILDING THE VIEWMASTER

The television set you can build at home from standard parts.
Kirk o' Shotts, Holme Moss, Sutton Coldfield and Alexandra Palace operation.
Brilliant high definition black and white picture.
Superb reproduction.
Uses 9in. or 12in. Cathode Ray Tube.
Table or Console Model.
Incorporates all the latest developments.
Television for the home constructor at its finest.
Send to-day for the CONSTRUCTION ENVELOPE, a 32-page booklet crammed with top-rate information and all the necessary data, also 8 full-size working drawings and stage by stage wiring instructions. Model "A" for use in London and Home Counties. Model "B" for use in Sutton Coldfield Area. Model C for Holme Moss. Model D for Kirk o' Shotts.
PRICE 5/- per copy Post free.

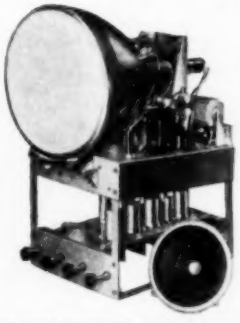

ALL COMPONENTS IN STOCK AND SOLD SEPARATELY

5in. CLOSED FIELD LOUDSPEAKERS. Ideal for television receivers. Less o/trans. 3 ohms. Will not affect your C.R. tube.

LASKY'S PRICE 17/6 Post 1/6 extra.

T.C.C. VISCONOL HIGH VOLTAGE CONDENSERS (Cathode ray).
.001 mfd. 6 kV. Price 4/6 each.
.001 mfd. 12.5 kV. Price 7/6 each.
.1 mfd. 7 kV. Price 15/- each.
.1 mfd. 6 kV. Price 10/- each.
All post extra.

ENGRAVED KNOBS. 1¼in. diameter. ¼in. Spindle. For television, radio and amplifiers. All types. (Brilliance, tone, etc.).
PRICE 1/6 each. Post extra.

WIREWOUND COLVERN POT METERS. Most values.
LASKY'S PRICE 3/6 each.
Post extra.

TELEVISION VALVES. MOSTLY AT PRE-BUDGET PRICES. EL38, EL33, 6P28, 6K25, EY51, 62BT, 7C5, PL38, PZ30, GZ32. Etc. **NO SHORTAGE AT LASKY'S.**

CATHODE RAY TUBE MASKS.

9in., with fitted armour plate glass	10/6
less glass	7/6
10in.	9/6
12in. soiled white	10/-
Brand new white	19/6
Special for flat face tubes	22/-
Grey rubber sorbo. Flock sprayed	7/6

Postage 1/6 each extra.

ARMOUR PLATE SAFETY GLASS. For 9in. tubes 3/-, 12in. 4/- per piece. Post 1/- each.

TINTED SCREEN FILTER PLATES. 9in.-10in., 18/6. 12in., 25/-. Postage 1/- each extra.

A FEW LEFT. VCR140 C.R. TUBES. Ex Government, 12" magnetive focus and deflection. Green screen. Suitable for T.V. New and unused.
LASKY'S PRICE £5/10 Carriage 12/6 extra.

RECEIVER UNIT TYPE 153, (45 Mcs. Pye Strip). BRAND NEW AND UNUSED. Contains 4RF stages, detector, video amplifier and phase splitter. Uses 6 EF50 and 1 EA50. Stripped from brand new equipment. Supplied with all 7 valves. Full circuit and data free with each unit.
LASKY'S PRICE 63/- Post Free.

VCR97 C. R. TUBES. BRAND NEW AND UNUSED. In makers original sprung wood transit case. Supplied with fully insulated and totally enclosed base holder.
LASKY'S PRICE 40/- Carriage 5/- extra.

E.H.T. TRANSFORMER FOR VCR97. Primary 200-250 v., 50 cps. Secondary: 2.5kV. 4 m.a.; 4v. 1.1a.; 4v. (CT) 1.5 a.
LASKY'S PRICE 39/6 Postage 1/6 extra.

LASKY'S RADIO

LASKY'S (Harrow Road) LTD.

370 HARROW ROAD, PADDINGTON, LONDON, W.9

(Opposite Paddington Hospital)

Telephones: CUNningham 1979 and 7214

Hours: Mon. to Sat. 9.30 a.m. to 6 p.m., Thurs. half day 1 p.m. Send 2½d. stamp with your name and address (in block letters please) for a copy of our current stock list giving details of our supplies of new manufacturers' surplus equipment and ex-government radio, radar and valves, etc.

LASKY'S RADIO
World Renowned for Service & Reliability

Enclose 2½d. stamp for full details, circuit diagrams and illustrations.

PRICE SLASH!

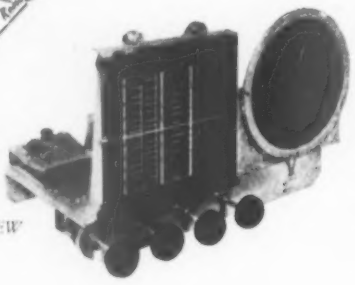

FRONT VIEW

5 VALVE ALL WAVE RADIO CHASSIS

★ Superhet, 465 Kc/s.
★ Brand New.
★ Tested, working.
★ Large edgelit dial, 7½in. square.
★ Fully aligned.
★ Factory Built.
★ Not a kit.
★ 2 Speed tuning, with nylon drive.
★ Sockets for p.u. and extension speaker. ★ A.V.C. ★ 4 Watts output.
★ Variable tone control. ★ Finest components. Not ex-Government.
★ Full size chassis :—15½in. wide, 8in. deep, 2½in. high.

£9·16·6
CARRIAGE PACKING & INSURANCE 10/6 EXTRA
COMPLETE WITH 5 NEW BRIMAR VALVES & 8" SPEAKER

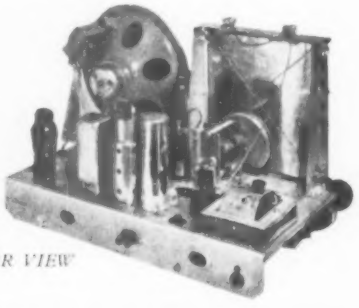

REAR VIEW

DO NOT MISS THIS GREAT MONEY SAVING OPPORTUNITY!

LASKY'S RADIO

Lasky's (Harrow Road) Ltd.,
370 HARROW ROAD, PADDINGTON, LONDON, W.9
(Opposite Paddington Hospital) *Telephones:* CUNningham 1979 and 7214

Hours: Mon. to Sat. 9.30 a.m. to 6 p.m., Thurs. half day 1 p.m. Send a 2½d. stamp with your name and address (in block letters please) for a copy of our current stock list giving details of our supplies of new manufacturers' surplus equipment and ex-Government radio, radar and valves, etc.

WEARITE LF. TRANSFORMERS. Type 550

Permeability tuned. 445-520 K/s. Type 551. Critically coupled with tapped connection. Type 552. Closely coupling for feeding diode circuit. Q=115. Inductance 700 microhenries at 465 K/s.

Band width of each of the above transformers is 7-20 K/s at 3-20 Dbs. Size:—3½in. high, 1½in. square. Supplied with fixing screws and nuts.

LASKY'S PRICE 6 6 each 12 6 per pair

ALL YOUR RADIO VALVE REQUIREMENTS AT LASKY'S

CARBON POT METERS

All with long spindle, ¼, ½ and 1 meg.

LASKY'S PRICE less switch 3 3 each. With switch 4 3 each.

All post extra.

Short Spindle and pre-set. PRICE 1 6 each. Post extra.

SMOOTHING CHOKES

20 M a. 40 H.	3 11
40 M a. 8 H.	3 11
40 M a. 10 H.	4 3
80 M a. 10-20 H.	4 11
120 M a. 10-20 H.	7 6
150 M a. 10-20 H.	10 6
150 M a. 5 H.	3 3
350 M a. 5 H.	10 6

Postage extra.

EXPANDED METAL SPEAKER FRET

Metal, one side finished gold, other side silver. Size: 12in. × 12in.

LASKY'S PRICE 4 3 per piece.

Post 6d. extra.

RADAR INDICATOR UNITS TYPE 162C

BRAND NEW IN MAKER'S ORIGINAL WOOD CASE. Contains 1 cathode ray tube, 6in. VCR517. Also the following valves: three SP61, one 6J5, three EA50, one D1. Dozens of components, coils, resistance, condensers, seven pot. meters, etc. Enclosed in metalcase, size 12in. × 9in. × 13in. Weight, 40 lb.

LASKY'S PRICE Carriage 7 6 extra. 75 -

METAL RECTIFIERS

No. 1. 125 volts at 60 m.a. Price 3 11. Post 4d.
No. 2. 125 volts at 100 m.a. Price 4 3. Post 4d.
Any number can be used together, either in series or parallel

P.M. LOUDSPEAKERS

New and unused. First quality. All less o. trans.

3in.	12 11	8in.	14 5
5in.	12 6	10in.	28 6
6½in.	12 6	12in.	75 -

Postage extra on each speaker.

ALL THE BEST MAKES AT THE BEST PRICES.

COIL PACKS

No. 1. 2 Waveband. 12-25 metres; 30-100 metres. 200-550 metres. ¼in. spindle, 1¼in. long wavechange switch. Completely assembled and wired. Size: 4in. × 4in. × 3in. BRAND NEW.

LASKY'S PRICE 16 - Postage 1 - extra. Circuit available price 1 -.

No. 2. Midget Coil Pack. 3 wavebands. Standard long, medium and short. ¼in. spindle, 2in. long wavechange switch. Completely assembled and wired. Size: 2¼in. × 1¾in. × 2¼in. BRAND NEW.

LASKY'S PRICE 24 6 Postage 1 - extra. Circuit available price 1 -.

ALL OTHER TYPES AND MAKES OF COIL PACKS AVAILABLE

Osmor, Weymouth, Wearite, etc., etc.

LASKY'S RADIO FOR ALL TEST GEAR. AVO, TAYLOR, G.E.C., ETC. Immediate delivery from stock.

EX-GOVERNMENT TEST INSTRUMENTS. PERFECT CONDITION. Evershed and Vignoles, 250 volt bridge megger tester. In leather carrying case.

LASKY'S PRICE £18 18 - Carriage extra.

CIRCUIT TESTING OHMMETER. By Evershed and Vignoles. In leather carrying case.

LASKY'S PRICE £4 19 6 Carriage extra.

CONDENSER CORNER

8 mfd. 500 v.w.	3 -
8 mfd. 450 v.w.	2 6
8 + 8 mfd. 500 v.w.	4 6
12 mfd. 50 v.w.	1 -
16 mfd. 450 v.w.	4 11
16 mfd. 500 v.w.	5 3
16 × 16 mfd. 450 v.w.	5 6
24 mfd. 450 v.w.	6 11
25 mfd. 25 v.w.	1 6
30 × 40 mfd. 350 v.w.	6 11
32 mfd. 450 v.w.	5 11
32 mfd. 500 v.w.	6 6
32 × 32 mfd. 350 v.w.	5 6
50 mfd. 12 v.w.	1 9
50 mfd. 50 v.w.	3 9
50 mfd. 350 v.w.	4 11
50 mfd. 350 v.w. A.C.	17 6
12 × 12 mfd. 350 v.w.	8 11

Postage extra.

EPICYCLIC DRIVES

For ¼in. spindle. Standard reduction.

LASKY'S PRICE 1 6 each.

Post 4d. extra.

A GENUINE MINIATURE 2-GANG TUNING CONDENSER

.0005 mfd. Size: 1¼in. deep, 1¼in. high, 1in. wide. ¼in. spindle. With fixing feet.

LASKY'S PRICE 6 6 each.

Post 6d. extra.

INTER-COM UNIT SCOOP

Manufacturer's surplus. Brand new. For 6 station operation, uses 3 valves, 1 each 2S24, KT32 and 6J7. AC/DC mains.

LASKY'S PRICE. Chassis less valves and indicator bulbs £3 9 6

Carriage 2 6 extra.

Chassis complete with all valves, 3" speaker and all indicator bulbs £5 5 0

Carriage 2 6 extra.

Incomplete chassis £1 15 0

Carriage 2 6 extra.

Chassis Cabinets. Light walnut veneer £1 5 0

Carriage 2 6 extra.

Speaker cabinets. Suitable for use with 3" speaker. Light walnut veneer. Supplied less speaker 12 6

Carriage 2 6 extra.

COLLARO AUTOMATIC RECORD CHANGERS

Model RC.500. Magnetic pick-up £11 15 7
Model RC.500. Xtal pick-up £12 3 0
Model RC.511. 3 speed, with dual purpose pick-up head £15 10 6
Model RC.511. 3 speed, with 2 crystal pick-up heads £18 14 1

DECCA GRAM MOTORS

Single Speed £3 14 4
Three Speed £7 3 4

B.S.R. GRAM UNITS

3 speed unit with pick up and change over crystal head. Supplied with two sapphire styli £9 19 11

J.BA.2. 10-12 WATTS CHASSIS AMPLIFIER

Uses an L63 feeding 2 KT61s in push-pull. Rectifier type U50. Size: 6in. × 12in. on 2in. chassis.

LASKY'S PRICE £7 19 6

Carriage and packing 10 - extra.

Send 3d. stamp for further details of J.BA.2 Amplifiers

OUTPUT TRANSFORMERS

Miniature Pentode (1S4, 3S4)	3 11
Midget Pentode, 60 M a.	4 3
Multi-Ratio Standard	6 11
Push-Pull, 80 M a. Ratios of 40 : 1 and 40 : 1	8 6
Push-Pull for PX4's	12 6
80 M a. heavy duty, multi-ratio	12 6
10 Watt multi-ratio	16 11
30 Watt, 70 M a. Multi-ratio	29 6
Bulgin inter-valve transformers. Ratio: 4 : 1	3 11
5 : 1	5 11
Standard Pentode, 60m/a.	3 11

Postage extra

FILAMENT TRANSFORMERS

All primaries 230 volts 50 c.p.s.

FIL 2. 6.3 v. 1.5 a.	Price	6 11
FIL 3. 6.3 v. 3 a.	Price	9 6
FIL 4. 2 v. 2 a.	Price	4 11
FIL 5. 6.3 v. 4 a.	Price	12 6
FIL 6. 12 v. 3 a.	Price	15 -

Special Transformer. 30 volts at 2 amps. with the following tappings:—3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 20, 24 and 30 volts Price 19 6

All 6½ trans. 1 - extra per item postage.

MAINS TRANSFORMERS

All 200-250 volts 50 c.p.s. primary. Finest quality, fully guaranteed.

MBA 5. 350-0-350 v. 80 M a., 6.3 v. 3 a., 5 v. 2 a. Both filaments tapped at 4 volts. An ideal replacement trans.	Price	18 6
MBA 5. 350-0-350 v. 120 M a., 6.3 v. 4 a., 5 v. 3 a. With mains tapping board	Price	27 6
MBA 6. 350-0-350 v. 100 M a., 6.3 v. 3 a., 5 v. 2 a. With mains tapping board	Price	22 6
MBA 7. 250-0-250 v. 80 M a., 6.3 v. 3 a., 5 v. 2 a. Both filaments tapped at 4 volts	Price	18 6
AT 3. Auto transformer, 0-70-120-200-230-250 volts, 100 watts	Price	19 6
AT 4. Auto transformer, 100 volts and 230 volts. Step up or down. 60 watts	Price	9 6

Postage 1 6 extra per transformer.

ANTENNA ROD SECTIONS

Each section is steel heavily copper plated, 12in. long and ¼in. in diameter. Any number of sections can be fitted together. LASKY'S PRICE 2 6 per doz.; 6 - for 3 doz.; 11 - per half gross; 20 - per gross. Post free.

DUAL WAVE COILS

M. & L. T.R.F. AE. and HF.

LASKY'S PRICE 5 11 Per pair.

Post 6d. extra

EX-A.M. COMMUNICATION RECEIVER TYPE R1155

BRAND NEW IN WOOD TRANSIT CASE. Aerial-tested before despatch. Supplied complete with 10 valves. Circuit: R.F.O., A.V.C., R.F. Amp., two I.F. stages, magic eye, etc. Frequency ranges: 18.5-7.5 Mc/s.; 7.5-3.0 Mc/s.; 1,500-600 kc/s.; 500-200 kc/s.; 200-75 kc/s.

LASKY'S PRICE £12 10 -

Carriage (in wood case) 7 6 extra. Full modification data and circuit details supplied.

CRYSTAL DIODES

Wire ends. Supplied with circuit.

LASKY'S PRICE 3 11 each

Post 3d. extra

VIBRATOR PACKS

12 volt input. Fitted with synchronous vibrator. Brand new and unused.

No. 1. Output 250 v. 100 M a.

LASKY'S PRICE Complete Less vibrator 20 -. 29 6

No. 2. Output 150 v. 50 M a.

LASKY'S PRICE Complete Less Vibrator 17 6. 25 -

Carriage 2 6 per pack extra.

No. 3. For use with P.C.R. Phillips Communication Receiver. Supplied complete with metal rectifiers, and vibrator etc.

LASKY'S PRICE Carriage 5 - extra. 39 6

SETS OF ENGRAVED KNOBS

1 each: Tuning, Volume, L.M.S.G., and Tone.

LASKY'S PRICE 4 - the set. Post extra.

LASKY'S OWN TEST PRODS

Made for safety.

Fused test prods. Fully insulated pencil type with retractable point. Contact is only made when desired by pressing top. Each prod contains a cartridge type fuse and spring

LASKY'S PRICE 4 11 per pair (one red, one black). Post 6d. extra.

CAR BATTERIES

By DELCO-REMY. Ex-American Army. Absolutely perfect, brand new and unused, in maker's original packing. No. 1. 6-volt 140 A.H. approx. Size: 7in. deep, 13in. wide, 8½in. high. In genuine hard rubber case.

LASKY'S PRICE Carriage 7 6 extra. £4 19 6

No. 2. 6-volt 90 A.H. Size: 9in. wide, 7in. deep, 8in. high. In genuine hard rubber case.

LASKY'S PRICE Carriage 7 6 extra. 87 6

MAINS DROPPERS

All types from 2 6 each. 12 assorted, 25 -. Post free.

MIDGET YAXLEY SWITCHES

4 pole 2 way. Long spindle.

LASKY'S PRICE 2/11 Postage 3d. extra.

LARGE STOCKS OF RESISTANCES ALWAYS AVAILABLE

All values. Prices:—1/10th and 1/8th watt, 7½d. each; ¼ and ½ watt, 6d. each; 1 watt, 8d. each. Postage extra.

MONEY BACK GUARANTEE

Everything ordered from Lasky's is guaranteed to be as advertised. If you are not more than satisfied return goods for cash refund.

BUILD A PROFESSIONAL RADIO OR AMPLIFIER AT LESS THAN HALF TODAY'S PRICE

You're SURE to get it at

STERN'S

ESTABLISHED 25 YEARS

ALL KITS INCLUDE "EASY TO FOLLOW" POINT-TO-POINT WIRING DIAGRAMS

A MAINS OR BATTERY PORTABLE KIT

A Midget 4-valve Superhet Portable Set covering medium and long wavebands.
Designed to operate on A.C. mains 200/240 volts, or by an "Alldry" battery. The set is so designed that the mains section is supplied as a separate unit which may be added at any time. The Kit therefore can be supplied as an "Alldry" Battery Superhet Personal Set, which can then be accommodated in the Attache Case as illustrated above (size 9½in. × 4½in. × 12½in.). This is attractively finished in Dark Green or Blue Rexine (3/- extra) or as a Combined Mains/Battery Superhet Portable Receiver, for which a polished Wood Cabinet is available to accommodate both Mains Unit and Batteries together. Circuit incorporates delayed A.V.C. and Pre-selective Audio Feedback. Kit is complete in every detail and includes ready wound frame aerials, fully aligned I.F. Transfs., and drilled chassis, etc. Overall size of assembled chassis 9½in. × 8in. × 6½in.
We can supply the set either as a complete Kit of Parts for **£8 16 9** (incl. P.T.) (plus Cabinet and Mains Unit), or by supplying the components separately. The complete Assembly Instructions, which include full price detail-covering prices of individual components, Circuit and Component Layout, etc., are available for **1 9** (incl. postage).

A T.R.F. BATTERY "PERSONAL" KIT

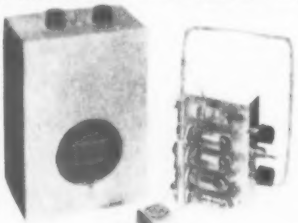

A complete Kit of Parts to build a Midget 4-valve Alldry Battery Portable Set, covering medium waveband.
Consists of Regenerative T.R.F. circuit, employing Flat Tuned Frame Aerial with Trimmer from Dust Cored Coil. Valve line-up: Two 1.T.4's, S.P. Abso. and 1S4, 1S5 and 3S4 output.
Kit is complete in every respect and includes drilled chassis and latest type 8in. P.M. speaker. Overall size of assembled chassis 10in. × 7½in. × 7½in.
We can supply the Complete Kit (less cabinet) for **£6 4 8** (incl. P.T.) or by supplying the components separately. The Complete Assembly Instructions, including individual component prices, Circuit and Component Layout, etc., is available for **1/-**, post paid.

A KIT OF PARTS

Complete in every detail to build a **3-valve Amplifier** for A.C. 50/60 mains 200/250 volts.
Has an output of 3 watts, and incorporates a Tone Control.
Valve line up, 2/6A6, 6Q7, U50.
Our price of **£4 12 6** for complete kit includes a matched 6in. P.M. speaker.
This Amplifier can also be supplied assembled and ready for use for **£5 12 6**.

A MIDGET 4-STATION "PRE-SET" RECEIVER

A complete Kit to build a 4-Station "Pre-Set" Superhet Receiver for A.C. mains operation.
The set is designed for receiving any three stations on medium waveband and one on long waves, each station being received by the turn of a Rotary Switch—No Tuning being necessary.
It is of midget size, being 8½in. × 4½in. × 7in. high, and has the performance of a far more expensive ready-made set, but can be built for half the price.

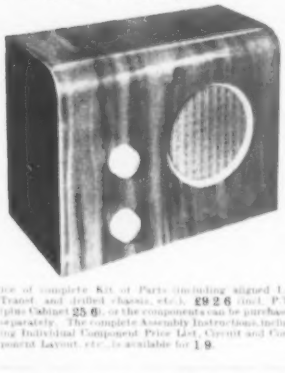

Price of complete Kit of Parts (including aligned I.F. Transf. and drilled chassis, etc.), **£9 2 6** (incl. P.T.) (plus Cabinet **25/6**), or the components can be purchased separately. The complete Assembly Instructions, including Individual Component Price List, Circuit and Component Layout, etc., is available for **1/9**.

STERNS "RADIO TUNER MANUAL," Price 2/6
Plus 3d. Post). Contains complete and detailed assembly instructions showing how to make:
A **1-Valve T.R.F. Tuning Unit**, covering Long and Medium Wavebands.
A **4-Station "Pre-Set" Superhet Tuning Unit**, producing 3 Stations on Medium Waveband and 1 on Long Waves.
A **2-Valve Superhet Tuning Unit**, covering Short, Medium and Long Wavebands.
Each Tuner is for A.C. Mains operation. Circuit Diagrams and Practical Component Layouts are shown, together with complete Component Price Lists.

THE WIRELESS WORLD MIDGET A.C. MAINS 2-VALVE RECEIVER

We can supply all the components to build this set, including Valves and Moving Coil Speaker for **£3 10 -**, including Designer's complete building instructions (these are available separately for **9d.**).

THE "SUMMER ALLDRY" BATTERY PORTABLE

As published in June issue of "Practical Wireless." We can supply, from stock, all the components to build this Midget 3-valve Portable for **£3 2 0** (less valves). This also includes dials, top panel and sky sheet for chassis. The complete article and circuit, including Practical Layout and Price List, is available for **9d.**

PICK-UPS

Cosmocord "G.P.20," for standard records, **£3 11 5**; interchangeable G.P.19 Head for L.P. records, **£2 3 4**.
Decca lightweight "turnover Head" type, for L.P. and standard records, **£3 19 2**.
Marconi, Standard, lightweight Magnetic, **£1 15 10**. Universal Matching Transformer, **7/6**.
Boosting, Standard lightweight Magnetic, **29/6**.

THE WIRELESS WORLD 3-VALVE SET

A Midget 3-valve T.R.F. Receiver for operation on A.C. mains, covering long and medium wavebands.
We are able to supply all of the components to build this set, as designed, and specified in the Feb. 1950 issue, including the drilled chassis, valves and moving coil speaker, etc., at the following prices:—
To construct complete chassis (less dial and drive assembly, **£4 17 9**. Ditto, including dial and drive assembly, **£5 12 9**.
To construct the complete Set, including dial and drive assembly and cabinet, **£6 14 3**.
Overall size of cabinet is 7½in. × 9½in. × 11½in.
A reprint of the designer's article, giving Circuit and Assembly Instructions (this is available separately for **9d.**), together with a Practical Component Layout is included with each of above assemblies.

BATTERY CHARGER KITS

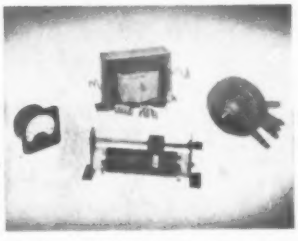

All Kits incorporate Metal Rectifiers, and are for use on A.C. mains 220/250 volts. All Kits include an easily followed Wiring Diagram.
For charging 6 v. battery at 1½ amps., **£1 3 9**.
For charging 6 volt battery at 1½ amps., with Variable Resistor and Meter, **£2 4 3**.
For charging 12-volt battery at 1½ amps., **£1 6 9**.
For charging 12-volt battery at 1½ amps., with Variable Resistor and Meter, **£2 7 6**.
For charging 6 or 12 volt battery at 3 amps., **£1 19 0**.
For charging 6 or 12 volt battery at 3 amps., with Variable Resistor and Meter, **£3 1 6**.

THE WIRELESS WORLD MODERN CRYSTAL SET

Designed for the Pre-selection of THREE STATIONS to suit local conditions, each station being received by the turn of a rotary switch. We are able to supply all components, including drilled chassis to build this new type of Receiver, to the designer's specification, as published in October issue, for **47/4** (including cost of selected coils).
A reprint of the designer's article (available separately for **9d.**), together with a practical component layout, makes the assembly very easy.

★ *Send 6d. P.O. for our STOCK LIST, it shows "hundreds" of Wireless*

When ordering please include

STERN RADIO LTD., 109

Tel. : CENtral

AN A.C. MAINS "ALL-WAVE SUPERHET" CHASSIS

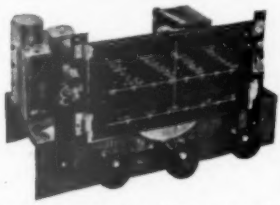

A completely assembled chassis for A.C. mains 200-250 volts, designed for good selective and quality reproduction, and serves as an ideal replacement chassis for that "old radiogram, etc."

It incorporates in addition to the three controls shown above a Tone Control and a Radio-Gram Switch. These two are left on "floating leads" to enable them to be placed in any position in cabinet.

The set employs a modern 5-valve line up, and covers three wavebands, 16-50, 190-550 and 800-2,000 metres. Flywheel tuning is incorporated.

Overall size of assembled chassis, 18½in. × 6in. × 8½in. high. Dial size 9in. × 4½in.; an attractive Dial Escutcheon Plate is supplied.

Price of complete chassis, wired and ready for use, **£14 19 6**.

A QUALITY "PUSH-PULL" AMPLIFIER KIT

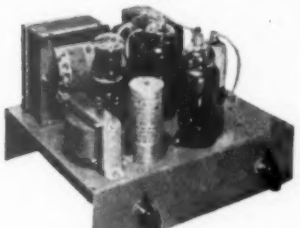

A Kit of Parts to build a 6-8-watt Push-Pull Amplifier for operation on A.C. mains 200-250 volts.

Incorporates a simple arrangement to enable either a magnetic, crystal, or lightweight pick-up to be used.

A 10-watt Output Transformer is designed to match from 2 to 15 ohm speakers. Tone control is incorporated.

The overall size of the assembled chassis is 10in. × 8in. × 7½in. high. Price of kit complete in every detail, including drilled chassis and valves, **£6 5 -**. Component layout is supplied.

Price of assembled chassis, supplied ready for use, **£7 10 -**.

"PERSONAL SET" BATTERY ELIMINATOR

A complete kit of parts to build a Midget "Allstr" Battery Eliminator, giving approx. 60 volts and 1.4 volts.

This Eliminator is for use on A.C. mains and is suitable for any 4-valve Superhet Receiver requiring H.T. and L.T. voltage as above, or approx. to 60 volts.

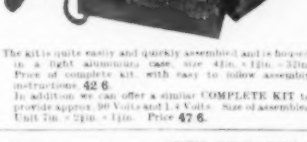

The kit is quite easily and quickly assembled and is housed in a light aluminium case, size 4½in. × 12½in. × 5½in. Price of complete kit, with easy to follow assembly instructions, **42 6**.

In addition we can offer a similar COMPLETE KIT to provide approx. 90 Volts and 1.4 Volts. Size of assembled Unit 7in. × 2½in. × 4½in. Price **47 6**.

You're SURE to get it at

STERN'S

ESTABLISHED 25 YEARS

TWO NEW DENCO ULTRA MIDGET SUPERHET COIL TURRETS

Both having a Rotary Turret Action

(a) The C.T.9 Turret consists of 4 STATION "PRE SET" UNIT, from which any three Stations on Medium Waveband and one on Long Waves can be received by a turn of the Turret Switch.

(b) The C.T.10 Turret, being a 3 Waveband Coil Pack, incorporating a fourth switch position providing for completely switching out Radio when using gram. The complete coverage is: Long Waveband 700 to 2,000 metres; Medium Waves 190 to 570 Metres and Short Waves 16 to 50 Metres.

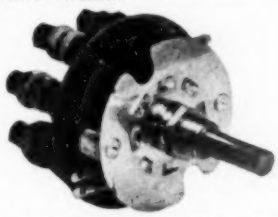

The outstanding advantages these units have over other similar units can be readily seen, the main features being:

(a) Neat and Compact, the overall size being only 2½in. dia. × 1¾in. deep.

(b) Fitting is simplicity itself, each Turret having one hole fixing and requiring only four connections.

(c) The Rotary Turret design switches the actual Coils which incorporate variable iron dust cores, on to positive contacts, thereby reducing stray capacities to the absolute minimum.

(d) They are supplied Factory wired and aligned and have been designed to operate with any conventional circuit arrangement of 465 kc/s, and due to their unique design are extremely sensitive and efficient.

Price: C.T.9 Turret, **39 6**. C.T.10 Turret, **52 -**.

A complete Receiver circuit together with leaflet containing all necessary data is included with each Turret. These can be supplied separately for **6d**.

THE FAMOUS W.B. "STENTORIAN" RANGE OF F.M. SPEAKERS.

Size.	Impedance.	Watts.	Price
2½in.	2-3 ohms	1	**16 6**
3½in.	"	2	**19 6**
5in.	"	2½	**21 -**
6in.	"	3	**24 6**
7in.	"	3½	**23 6**
8in.	"	5	**32 6**
9in.	"	7	**36 9**
10in.	"	10	**44 6**
12in.	"	15	**£9**

New Mfrs. Surplus Speakers. All 2/3 ohms. 2½in. 15/-. 3½in. **14 6**; 5in. **14 6**; 6½in. **16 9**; 8in. **18 -**; 10in. **25 -**. New Type Rola. 3in. **21 -**. 4in. **22 6**.

Output Trans. Midget 60-1 (or 90-1) 1½in. × 1in. × 1½in. **3 9**. 5-watt Multi-ratio, 12 tappings between 24-1 and 114-1 (some C.T.). **8 6**. Wharfedale, 12-watt, push-pull, multi-ratio, **25 -**. P.P. pull, 20-watt, multi-ratio, **7 6**, and many others.

Ext. Speaker Volume Control, **2 6**.

New Electrolytic Condensers. Not Ex-Govt. All 450/500 volts. 8 mfd. (1½in. × 1in. dia.), **3 -**; 8-8 mfd. (1½in. × 1in.), **4 9**; 16-8 mfd. (1½in. × 1in. dia.), **5 6**; 16-16 mfd. (1½in. × 1½in. dia.), **5 9**; 32 mfd. (1½in. × 1½in. dia.), **5 9**; 32-32 mfd. 350 volt, **5 9**; Cardboard Tubular 4 mfd. 500 v., **3 6**; 8 mfd. 500 v., **4 -**; 16 mfd. 500 v., **5 9**. Can Standard size all 500 volts, 4 mfd., **3 6**; 8 mfd., **4 3**; 8-8 mfd., **5 9**; 16 mfd., **5 6**; 16-16 mfd., **7 9**; 32 mfd., **6 9**.

Denco I.F. Liner, for accurately lining 465 K/c. and 1.6 m/c. I.F. channels and associate circuits. Battery operated, small and completely self-contained, **47 6**.

Potentiometers. New, not Ex-Govt. 5K, 5K, 10K, 25K, 50K, 100K, 250K, ½, 1 and 2 meg. Price, less switch, **3 9**. Price with S Pole switch, **5 9**. Price with D Pole switch, **6 6**.

Surplus Pots-Diometers. All standard with extended spindles. 5K, 10K, 15K, 20K, 25K, 50K, 100K, ½, 1 and 1 meg., **2 -** each.

Coils. Denco "Maxi Q," midget size, Litz wound on Polystyrene Formers, with adjustable iron cores. Available for Aerial H.F. and Oscillator 465 K/c. or 1.6 M/c., **3 9** each, or with reaction winding **4 9**. Denco Matched pair T.R.F. Coils for long and medium waves, **6 6** pr. Weymouth matched pairs of coils, for T.R.F. covering long and medium waves, **10 6** pr., or for Superhet covering Long, Medium and Short Waves, **11 6** pr. All types of Wearite "P" coils in stock at **3 -** ea.

Coil Packs. Osmor Midget Coil Pack. Size 3½in. × 2½in. × 1½in., covering S., M. and L. waves. Coils wound on Polystyrene Formers with adjustable iron cores ensure efficient performance. Factory wired and aligned. Price, including full circuits for Superhet 465 K/c. Unit, **52 -** (incl. P.T.). This Osmor Coil Pack is also available for Midget Superhet BATTERY Portable sets, including a matched ready wound Frame Aerial. Price **54 2** incl. P.T.'s. **Weymouth** Midget 3½ × 2½ × 1½in. covering S.M.L. w bands, for 465 K/c., employing Matched Iron Cored Coils on each w band, **51 6**.

Wearite Pack, 4½ × 3½ × 1½in., Type 706, covers two short w bands and medium w band and Type 705 covers short-medium-long waves. Both for 465 K/c. Incorporates gram. position, and employs adjustable cored coils, **53 4**.

All of the above Coil Packs include Switching, Padding and Trimmer Condensers.

L.F. Chokes. Midget 10 henry 250 ohms 40 mA., **4 6**; 20 hy. 250 ohm 60 mA., **6 6**; 20 hy. 300 ohm 100 mA., **12 9**; 5 hy. 50 ohm 250 mA., **28 6**; 20 hy. 250 ohm 120 mA., **15 6**; 9 hy. 350 ohm 120 mA., **8 6**; 18 hy. 200 ohm 250 mA., **26 6**.

I.F. Transformer, 465 K/c. New well-known manufacturer's surplus 1in. × 1in. × 1½in. Iron Core, **9 -** each. Denco Iron Core, 465 K/c. or 1.6 m/c., 1½in. × 1½in. × 3½in., **16 6** pair. Wearite Stand Cap. Tuned 465 K/c., **20 -** pr. New Surplus 465 K/c. Iron Core, 4in. × 1½in. sq., **10 -** pr.

Transformers. (a) Input 230 volt, output 200 volt, 20 m.a., and 6.3 v., 2 amp., **11 -**; (b) Input 230 volts, output 200 volts 30 m.a., and 6.3 volts 1 amp., **13 9**.

E.H.T. Transformer. Prim. 230 v. Sec. 5 Kv. and 4- volt tapped 2 volt, **59 6**. Do. but 4 Kv., **54 -**.

Heater Auto Transformers. (a) tapped 0 v., 4 v. 5 v. and 6.3 volts 2 amp., **9 6**; (b) 4 v. 5 amp. to 5 v. 2 amp. Reversible, **6 6**; (c) 4 v. 3 amp. to 6.3 v. 2 amp. Reversible, **6 6**.

NEW SURPLUS!! FOSTER TRANSFORMERS. Primary 230 volts. Secondary 12 volts 9 amps., **21 -**.

Filament Transformer. Inputs 230 volts, outputs 6.3 v. 1½ amp., **8 3**; 4 v. 1½ amp., **7 6**; Input 200-250 v., output 4 v. (C.T.), 1½ amp., 4 v. 2 amp., 6.3 v. 2 amp., **19 6**. Input 230 v., output 6.3 v. (C.T.) 4 amp., **17 6**.

Metal Chassis substantially made with four sides, 7in. × 4in. × 3in., **3 11**; 9 × 5 × 2½in., **5 3**; 10 × 6 × 2½in., **6 -**; 10 × 7 × 2½in., **6 3**; 12 × 8 × 2½in., **7 9**; 14 × 9 × 2½in., **8 3**; 16 × 8 × 2½in., **9 -**.

Mains Transformers. All New Stock with Pri varies tapped for 200-250 volts. Secondaries (a) 250-0-250 volt, 80 mA., 6.3 v. (tapped 4 v.) 4 amp. and 5 v. (tapped 4 v.) 2 amp., **18 6** also available with 350-0-350 volt at **19 6**. Stern's 350-0-350 volt, 150 mA., 6.3 v. (tapped 4 v.), 4 amp. and 5 v. (tapped 4 v.) 2 amp., **41 6**; (c) 380-0-350 v. 200 mA., 4 volt 5 amp., 4 v. 3 amp., 6.3 v. (tapped 2 v.) 2 amp. and 6.3 v. 6 amp., **84 -**, and many other ratings.

Westinghouse Rectifiers. (a) H.T. 51. Rated 350-0-350 volts 100 mA., **35 -**; (b) H.T.52. Rated 350-0-350 v. 200 mA., **37 6**; (c) H.T.53. Rated 500-0-500 v. 200 mA., **50 -**.

Types. 14DL5G, **11 3**; 16HT2S, **12 6**; 16EHT2S, **17 9**; 36EHT2S, **13 10**; 36EHT3S, **18 2**; 36EHT4O, **20 6**; 36EHT4S, **22 6**; 36EHT5S, **24 10**; 36EHT8O, **25 5**; 36EHT10O, **28 -**; 36EHT13, **7 9**.

F.Wave Bridge Rectifier.

For charging 2, 4 or 6 volt at 1½ amps.	**6 6**
For charging 6 or 12 volt at 1½ amps.	**12 9**
For charging 6 or 12 volts at 3 amps.	**21 9**
For charging 6 or 12 volts at 5 amps.	**31 10**
For charging 12 or 24 volts at 3 amps.	**25 9**

A Variable Resistor for control of Charging Equipment (or Models) up to 3 amps. **15 -**.

Suitable Charger Meter, 0-5 amps., **7 6**.

Meter Rectifiers. Westinghouse 250 micro-amp., **18 9**; 1 mA., **11 9**; 5 mA., **6 9**.

Selenium Rectifiers. H.T. H. wave, 250 v. 50 mA., **5 6**; 250 v. 100 mA., **7 6**; 260 v. 170 mA., **13 9**.

Charger Transformers. Suitable for use with preceding Rectifiers. Each has input of 230 volts. Outputs: (a) 24 volts tapped 15 v., 9 v. and 4 v. at 3 amps., **25/-**; (b) 30 volts tapped 15 v. and 9 v. at 3 amps., **23 3**; (c) 15 volts tapped 9 v. at 3 amps., **19 6**; (d) 12 volts 1½ amps. **12 3**; (e) 15 volts tapped 9 v. at 6 amps., **24 3**; 15 volts tapped 9 v. at 1½ amps., **15 3**; 12 volts 1 amp., **7 6**.

A Battery Charger Wiring Diagram is included with purchase of Charger Transformer and Rectifier.

Adjustable Mains Droppers. 1in. dia. × 2½in. (a) 15 amp. 1,500 ohms, **5 -**; (b) 2 amp. 1,000 ohms, **4 3**; (c) 3 amp. 600 ohms, **5 -**.

Televisors. We keep a very comprehensive range of T/V components. The Viewmaster T-V Assembly Instructions showing Practical Layout and Price List in stock, price **5 6** (incl. post). We can supply all the specified components for the T.V. in stock either by way of individual components or by the published stages.

"G" Max Chassis Cutters. The quickest and most simple method of Chassis cutting consists of a die, punch and 4-hole screw.

To cut 4in. dia. (B7G)	**10 6**
To cut 5in. dia. (B8A)	**10 6**
To cut 1¼in. dia. (Octal)	**13 6**
To cut 1¼in. dia. (Knight)	**13 6**
To cut 1in. dia. (EF50)	**13 6**
Key for any of above	**1/-**

Adjustable **Chassis Cutter** for holes from ½in. to 2½in. dia. (used with hand brace), **7 6**.

The "Handy-Utility" ¼in. Portable Electric Drill for use on A.C. or D.C. mains. A powerful and robust drill that will drill wood, metal and almost anything, can also be used for grinding, buffing and wire brushing, etc. Employs instant release trigger switch. Price **£6 10 -**. Descriptive leaflet is available.

The new **Proskidsderin** iron, with instrument-type bit for use on A.C. or D.C. mains, **22 -**. Spare elements and bits always in stock.

Ex-Govt. complete set of **Moving Coil Headphones** and **Microphone** with headgear, **10 6**.

Components and many KITS OF PARTS for both Sets and Battery Chargers. approx. cost of Post & Packing.

& 115 FLEET STREET, E.C.4

5814 and 2280

GARLAND BROS. LTD

"VIEWMASTER" TELEVISION. Still after two years a best seller. Many thousands have been built and are giving excellent service throughout the land. The instruction envelope with fully illustrated booklet and stage-by-stage full size working drawings make the construction of this set simplicity itself. The components used are standard products of Britain's leading manufacturers. Instruction envelope 5/- each, post free. State whether for London, Birmingham or Holme Moss.

TELEVISION AERIALS. Antiference "Antex." Model X2P. Pole Mounting, $7/-; X2W, 5ft. Mast Mounting, wall fitting, 75/6; X2L, 5ft. mast mounting, chimney lashing, 88/6; X2M, 10ft. mast mounting, chimney lashing, 123/6.

COAXIAL CABLE: ½in. diameter 75 ohm. black co-axial feeder, .0076 flexible centre conductor, 1/3 per yard, £3/5/- per 100 yd. drum.

T.V TWIN FEEDER. 75 ohm, 6d. per yd. Special offer, per 100 yds. in 20-30-yd. lengths, 37/6.

ENGLISH ELECTRIC 16in. METAL CATHODE RAY TUBES. Heater 6.3 v. 6 a.; Tetrode Gun, 14 kV. max. anode voltage; magnetic focusing and deflection; ion trap; giving picture 11in. by 14½in. of high brightness and improved uniformity of focus over the whole picture area. Price £24/6/5, including purchase tax, plus 15/- carriage, packing and insurance. (Full range of B.V.A. C.R. Tubes and Valves also in stock.)

TELEVISION MAGNIFYING LENS. 9in. clear, 55/-; 9in. filter, 60/-; 12in. clear, 75/-; 12in. filter, 80/-. Carriage and packing 5/- each, all types.

EDISWAN 3-SPEED AUTO-CHANGERS.

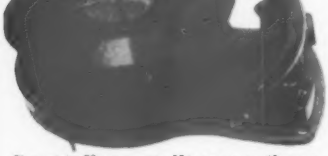

Plays eight 78 r.p.m., ten 33⅓ r.p.m. or 45 r.p.m. records. Replaceable double-pointed sapphire stylus, £23/13/-.

COLLARO 3 RCS11 3-SPEED AUTO-CHANGER. Non-mixing, plays eight 7in., 10in. or 12in. records at 33⅓, 45, or 78 r.p.m. Supplied with two plug-in pick-up heads incorporating sapphire styli, and made by Acos. Price £18/14/1, incl. P.T.

COLLARO RCS11 SINGLE-SPEED AUTO-CHANGER. Non-mixing, plays eight 78 r.p.m. 10in. or 12in. records. Supplied with Acos made plug-in pick-up head incorporating sapphire stylus. Magnetic, price £11/14/11, incl. P.T. Crystal price, £12/3/2, incl. P.T.

COLLARO AC47 SINGLE-SPEED TURN-TABLE AND MOTOR. Centre-drive governor-controlled heavy induction motor, for A.C. 100-130 v. and 200-250 v., with 12in. turntable. Variable speed. Price £6/13/4, incl. P.T.

COLLARO AC 514 RECORD PLAYER. For 78 r.p.m. records. Rim-drive motor, with auto. stop, turntable, pick-up with plug-in magnetic head. Price £6/9/-, incl. P.T.

DECCA THREE-SPEED GRAM MOTORS. For 33⅓, 45 and 78 r.p.m. Instant single-lever speed selection. For A.C. only, 100-250 v. 50 cycle operation. Price (incl. P.T.), £7/3/4.

DECCA TURNOVER PICKUP. A high fidelity crystal pickup with turnover head (two sapphires) for use on the above or other multi-speed motors. Price (incl. P.T.), £3/19/4.

ACOS GP20 HIGH FIDELITY CRYSTAL PICK-UP. Limited supplies of this famous pick-up are again available. Price £3/11/5, incl. P.T.

S.W. TUNING CONDENSERS. 50pF max., 3-hole fixing, spindle diam. ¼in., spindle length 1in., 1/6 each. 160pF (0.00016μF max., upright mtg., with 4 fixing feet, spindle diam. ¼in., spindle length 1¼in., 2/3 each.

TWO-GANG CONDENSERS. .0005μF, with fixing feet. Size 2¼in. x 2¼in. x 1¾in. Spindle diameter ¼in., spindle length 1in., 7/9 each. Midget two-gang condensers .0005μF with trimmers. Size 1¼in. x 1¼in. x 2¼in. Spindle diameter ¼in., spindle length 1in., 8/6 each.

LANE PRECISION BUILT TAPE TABLE

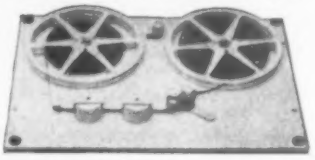

High fidelity high impedance record-playback and erase heads in mumetal shields. Heavy balanced flywheel giving freedom from "wow" and "flutter." Fast rewind. Heads are half-track, giving one hour's playing time with 1,200 foot reel of tape. £16/10/-, plus carriage, etc., 10/-. Demonstrations at Deptford and Lewisham.

TAPE DECK AMPLIFIER EU6. A six-valve record-playback amplifier suitable for use with high impedance heads. Features include variable bass and treble lift, recording level indicator and built-in oscillator supplying h.f. bias and erase sufficient for the highest coercivity tapes. Supplied in kit form, with punched chassis, all valves, components, circuits and full instructions. £10/10/-, plus carriage 5/-.

TAPE DECK AMPLIFIER HNES, a five-valve record-playback amplifier suitable for use with high impedance heads. With built-in oscillator supplying h.f. bias and erase. Supplied in kit form, with punched chassis, all valves and components, circuits and full instructions. £7/10/-, plus 5/- carriage.

MODIFICATION KIT UE2. Enabling the use of any good-quality amplifier for tape recording and playback. For use with high impedance heads, or (with suitable input transformer) for low impedance heads. Incorporating pre-amplifier, oscillator supplying h.f. bias and erase sufficient for the highest coercivity tapes, and recording level indicator. In kit form, with valves, punched chassis, circuits and instructions. (NOTE: H.T. and L.T. supplies required for this unit, viz., 250 v. at 40 mA. D.C. and 6.3 v. 1 a. A.C., can normally be obtained from the main amplifier.) Price £4/4/-, plus 5/- carriage and packing.

MAGNETIC RECORDING TAPE. Emitape, Grade A, 600ft., 21/-; 1,200ft., 35/-. Scotch Boy (Durex), 1,200ft., 35/-. **SPARE TAPE REELS.** 7in. (1,200ft.) plastic, 4/- each.

MAGNETIC RECORDING HEADS. Record-playback half-track high impedance heads, shielded. Mumetal laminations with half-thou. gap of beryllium copper, enabling twin tracks to be accommodated on standard ¼in. tape. Price 39/6. High Impedance Erase Heads to match the above. Radiometal laminations. Price 39/6.

HIGH FIDELITY AMPLIFIER KITS. Our amplifier ACIII is now discontinued, but all orders in hand are being dealt with. In this column next month we shall introduce our new Amplifier ACIV, which we believe will set a new standard in high-quality reproduction at a price within the range of all.

AMPLIFIER ACII. This popular amplifier is still available for those who desire good quality at a low cost. Output is 5 watts, and volume, tone, and variable feedback controls are incorporated. High-grade output transformer. H.T. and L.T. supplies are from mains transformer, thus isolating chassis from mains. Complete kit, including punched chassis, all valves and components, with circuits and instructions, price £5/2/6, plus 5/- carriage. Amplifier wired and tested, £6/2/6, plus 5/- carriage.

LUSTRAPHONE MOVING COIL MICRO-PHONES. Type CS1. Response substantially flat to 8 kc/s. Impedance 20 ohms. Fitted with switch, £5 each. Type CS1.Z. As above, but impedance 200,000 ohms, £5/12/6 each.

CARBON HAND MICROPHONES. Type No. 3. With G.P.O. type carbon insert, press switch in handle, lead and jack plug. New and unused, 5/- each.

SLEEVING. 2 mm. oiled silk, etc., 3/6 per 24 nominal yard lengths, assorted colours, 33/- per two gross ditto.

I.F. TRANSFORMERS. 465 kc. standard size, 3½in. x 1¾in. x 1¾in., 12/6 per pair. Small size, 2½in. x 1¼in. x 1in., 13/6 per pair. Made for us by a leading manufacturer.

TECHNICAL BOOKS: Television Receiving Equipment, by Cocking, 18/6. Radio Data Charts, abacs for receiver design, 8/-. Magnetic Tape Recorder, design and construction, by Cheeseman, 3/9. Cathode Ray Tube Traces, by Moss, 11/-. Electrophysiological Technique, by Dickinson, 13/-. Radio Charts No. 1, a modern superhet for A.C./D.C. mains, 2/9. Radio Charts No. 2, a high fidelity push-pull amplifier for A.C., 2/9. Audio Handbook No. 1, amplifiers, test and servicing, 3/9. The Williamson Amplifier, 3/9. Brimar Valve Manual, 5/3. Ediswan—Mazda Valve Manual, 1/3. Mullard Valve Manual, 5/3. Marconi Osram Valve Manual, 5/3. Television Explained, by Miller, 5/6. Television Servicing Manual, 4/9. A Comprehensive Radio Valve Guide, by May, 5/3. W/W Radio Valve Data, 3/9. The De-Luxe Home Built Televisor and Radiogram, by Flack, 6/9. Radio Circuits, step by step survey of superhet receivers by Miller, 5/6. W/W Guide to Broadcasting Stations, 2/3. Above prices include postage in all cases.

PLUGS AND SOCKETS. Pye angle, 1/-; Pye straight, 1/3; B. & L. 5-pin, 1/6; B. & L. 7-pin, 1/9; B. & L. 10-pin, 2/3; Jones 6-way, 1/6; Jones 8-way, 1/9; E.H.T. Single, 1/-; the above prices include plug and socket in all cases. Pye T-pieces, 9d. Pye connectors, 9d. Pye Angle P. & S. to fit ¼in. cable, 1/3 complete.

BAKELITE-CASED IGNITION SWITCHES: type SC 547. Will switch substantial currents at low voltage; many useful applications. 1/3 each, 13/- per dozen, £6/10/- per gross.

PULLIN MOTORS. Type A 3R. For 24 v. D.C. 3½in. x 2¼in. x 2in., 8/6 each.

MAT RESISTORS. 300 ohm, 250 watt, 2/3 each, 21/- per doz.

ACCUMULATORS. 2 v. 10 A.H. In black moulded bakelite case, unfilled but charged, 4/9 each.

P.O. TYPE JACK SOCKETS: 2 way shorting type Ref. No. 10H/1739, special offer at 1/- each, 9/- per doz.

FLEX CONNECTORS. Ref. Nos. Sc 455 plug, Sc 591 socket. Overall dimensions when joined 2¼in. x ¼in. For joining two lengths of flex or cable. Price complete (plug and socket) 1/3 each, 12/- per doz., £6 per gross.

BRIGHT ZINC PLATED CHASSIS. Two sided with fixing flanges, 13½ x 6 x 2½in., drilled for five-valve superhet, 2/9 each.

BLOWER MOTORS. American make. Nominal input 27 v. D.C. Shunt wound, with field and armature windings brought out separately, so can be put in series for higher voltages. Will also work on A.C., 12/6 each. Tested ex-equipment.

ROTARY SELECTOR SWITCHES. Type 10D/373-374. Sometimes described as impulse relays. 24 v. Solenoid. 52 pulses for one rev. Four position. Single stroke or continuous operation. Platinum contacts. 3/- each, or 15/- per half-dozen.

JUNEERO MULTI-PURPOSE TOOL WITH XACTO SLIDE GAUGE

CUTTING SHEARS FOR ROD
"XAKTO" GAUGE BAR
BENDING DIE FOR STRIP
CUTTING SHEARS FOR STRIP
PROTRACTOR SLIDE PLATE
BENDING JIG FOR ROD
PUNCH FOR STRIP AND METAL
VICE TO HOLD ROD FOR SCREW CUTTING

Some months ago we offered you a free supply of strip and rod to enable you to try the above, which is priced at £1/7/6; we also offered to refund the cost if after one week's trial you did not think it worth the price. We are pleased to be able to state that **not one of the many purchasers asked for a refund.** We now repeat the offer. Among the other Juneero items, of which we carry a complete range, are the Engraving Tool, for A.C. 200-240 v., for engraving on metals, plastics, etc., at 12/6; and the Punching and Riveting Jig, at 7/6.

EXTENSION SPEAKERS

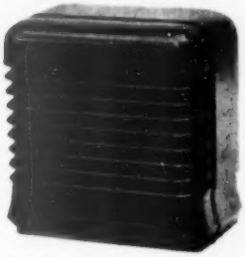

in tasteful brown bakelite louvred cabinet and incorporating an Elac 5in. P.M. speaker (commended editorial columns this journal), and volume control, **£1 7 6.** Cabinet, chassis and back only, suitable for intercom speakers and microphones, 11 - each.

CATHODE RAY TUBES. 5CP1, Electrostatic intensifier-type C.R.T., diameter 5in. max. second anode voltage 2 kv., max. intensifier anode voltage 4 kv., medium persistence screen. Brand new in original crate or carton, **22 6** each.

STABILIVOLT TYPE VS68. Similar to STV280/40. Operating voltages 280, 210, 140, 70 v. Max. electrode current 60 mA. **7 6** each, **78/-** per doz., **£30** per 100.

THYRATRONS. Type NGT1 (CV1141) 4 v. heater, anode volts 350. Anode current, peak 1 a., average 200 mA. Control ratio 40 5-pin British base, with anode top cap. **6 6** each, 72/- per dozen.

HEAVY DUTY OUTPUT PENTODES. Type PT25H. 4 v. filament, British 5 p. base. Have been successfully used strapped as triodes in quality amplifiers. **5/-** each, **48/-** per dozen.

SPECIAL PURPOSE VALVES. CV73, **4 -** ; 9003, **5 -** ; 954, **3 -** ; CV66, **6 6** ; VR136 (EF54), **7 6** ; VU111, **5 -** ; VU132, **3 6** ; CV54, **3 6** ; EI148, **3 6** ; VU33, **3 6** ; CV265, **3 6** ; VU134, **9 6** ; VR64A, **4 6** ; MS/Pen, **6 6.**

MAINS TRANSFORMERS. MT1, 250-0-250 v. 80 mA., 0-4-6.3 v., 4 a., 0-4-5 v., 2 a., **18 6** each. MT2, 350-0-350 v. 80 mA., 0-4-6.3 v. 4 a., 0-4-5 v., 2 a., **18 6** each ; MT3, 0-30 v. tapped to give 13 different voltage outputs at 2 a., **18 6** each ; All above transformers tapped 200-220-240 v. 100 w. auto., 0-10-120-200-230-250 v., **18 6** each.

TRIMMERS. Miniature ceramic air-spaced 3-30pF, **6d.** each. Philips concentric type 3-30pF, **8d.** each. Standard size ceramic air-spaced trimmers, 30pF, **1 -** ; 5pF, **1 -** ; 75pF, **1 3** ; ceramic compression type trimmers, 50pF, **6d.** ; 100 + 100pF, **1 -** ; 200 + 500pF, **1 3** ; 1,000pF, **9d.**

T.R.F. COILS. For long and medium waves. With reaction winding, **6 9** per pair. Without reaction winding, **6 -** per pair.

AMPLION TESTMETER. 10 Ranges A.C. and D.C. Up to 500 v. A.C. and D.C. Resistance up to 200,000 ohms, 1,800 ohms per volt A.C. and D.C. Price **£5.**

METAL RECTIFIERS. Type RM2, 125 v., at 100 mA. Two in series required for mains voltage. Price **4 -** each ; 6 v. 1 a. half-wave (or full wave with C.T. transformer), price **5 -** each ; 12 v. 1 a. bridge, **8 6** each ; 12 v. 4 a. bridge, **22 6** each.

GERMANIUM DIODES. By leading manufacturers. Wire ended, glass enclosed type. Special offer at **4 -** each, or **45 -** per dozen.

MINIATURE TANDEM POTS. 30 k. plus 1.5 k. with S.P. switch. Spindle diameter ¼in., spindle length ⅝in. from end of bush. **2 6** each.

VALVEHOLDERS. Ceramic : UX5 (807, etc.), **1 -** each **10 -** doz. ; UX7 medium (1625, RK34, etc.), **1/-** each, **10/-** doz. ; B9G (EF50, etc.), **9d.** each, **7 6** doz. Amphenol : Int. Octal, **9d.** each, **7 6** doz. ; Br. 7p, **9d.** each, **7 6** doz., Br. 5p, **9d.** each, **7 6** doz. ; UX7 med., **9d.** each, **7 6** doz. ; UX5, **9d.** each, **7 6** doz. Paxolin : Br. 5, Br.7, UX4, UX5, UX6, UX7, **6d.** each.

HEATER TRANSFORMERS. Pri. 220-240 v., Sec. 6.3 v. 1.5 a., **7 6** each. Pri. 220-240 v. Sec 6.3 v. 3 a., **11 6** each. ; Pri. 205-225-245 v., Sec. 6.3 v. 3 a., auto-wound, **8 9** each.

SWITCHES. Rotary : SP3w midget, **1 3** ; 3P3w midget, **2 6** ; 4P2w, midget, **2 -** ; 3P2w, **1 9** ; SP 11w, **2/-**. Rotary Toggle : SP on-off, **2 6.** Toggle switches : SPDT Black Bakelite, **1 9.** DPDT Black Bakelite, **2 6.** Arrow DPDT, **3/-**, Arrow SPDT, **2/3.**

B. & L. TWIN FUSEHOLDERS. Totally enclosed type, in Black Bakelite, for panel mounting, **2/-** each.

EX-GOVT. POTENTIOMETERS

Value	Track	Wattage	Spindle length	Price
50Ω	W.W	5	Preset	2 6
100Ω	W.W	1	Preset	1 9
500Ω	W.W	1	5/16in.	1 9
1kΩ	W.W	3	¼in.	2 6
1kΩ	W.W	5	¼in	2 6
2kΩ	W.W	3	Preset	1 9
2kΩ	W.W	6	¼in.	3/-
3kΩ	W.W	5	Preset	2 6
3kΩ	Carbon Trop.	2	¼in.	1 9
5kΩ	W.W	2	¼in.	2 6
5kΩ	W.W	5	¼in.	3/-
5kΩ	W.W	5	¼in.	3/-
8kΩ	W.W	5	¼in	2 6
10kΩ	W.W	4	¼in	2 6
10kΩ	Carbon Trop.	2	¼in.	2/-
10kΩ	Carbon	1	Preset	1 3
20kΩ	W.W	3	Preset	2/-
20kΩ	W.W	5	¼in.	3/-
20kΩ	Carbon Trop.	2	¼in	1 9
25kΩ	W.W	2	¼in.	3/-
50kΩ	W.W (earthed slider)	3	¼in.	2 6
50kΩ	Carbon Mini.	½	¼in.	1 6
100kΩ	Carbon Mini.	½	¼in.	1 6
200kΩ	Carbon	1	¼in.	1 9
500kΩ	Carbon Trop.	2	¼in.	1 6
500kΩ	Carbon Trop.	2	¼in.	1 9
500kΩ	Carbon Mini.	½	¼in.	1 6
1MΩ	Carbon	½	¼in	2/-

All new and unused. Spindle diameter ¼in. in all cases. Quantity prices on application.

CARBON RESISTORS. Large and comprehensive stocks at following prices : ¼ w., **4d.** ; ½ w., **5d.** ; 1 w., **6d.** ; 2 w., **9d.** ; 4 w., 1/- each. Among the values available at press date are the following :

QuarterWatt : 10, 12, 13, 20, 22, 33, 39, 43, 51, 56, 68, 82, 100, 150, 180, 220, 270, 300, 330, 390, 430, 450, 470, 560, 680, 700 1 k, 1.5 k, 2.2 k, 2.4 k, 2.4 k, 2.7 k, 3.2 k, 3.3 k, 3.9 k, 4 k, 4.7 k, 5.6 k, 6.2 k, 6.8 k, 7.5 k, 8 k, 10 k, 12 k, 15 k, 16 k, 18 k, 20 k, 22 k, 24 k, 25 k, 27 k, 30 k, 33 k, 36 k, 39 k, 40 k, 47 k, 50 k, 56 k, 60 k, 62 k, 68 k, 82 k, 100 k, 120 k, 180 k, 220 k, 270 k, 330 k, 350 k, 390 k, 470 k, 500 k, 600 k, 680 k, 750 k, 820 k, 1 m, 1.5 m, 2 m, 2.2 m, 2.7 m, 3.3 m, 4.7 m, 5 m, 6 m.

Half Watt : 27, 30, 43, 68, 82, 120, 130, 150, 270, 300, 400, 470, 500, 560, 600, 680, 750, 820, 1 k, 1.5 k, 2.2 k, 2.4 k, 3.9 k, 5.1 k, 6.2 k, 8.2 k, 10 k, 12 k, 13 k, 15 k, 18 k, 20 k, 27 k, 39 k, 40 k, 50 k, 60 k, 68 k, 100 k, 500 k, 560 k, 600 k, 680 k, 820 k, 1.5 m, 2 m, 2.2 m, 2.7 m, 4.7 m.

One Watt : 20, 27, 33, 50, 56, 68, 82, 120, 240, 330, 470, 600, 750, 1.2 k, 1.5 k, 1.8 k, 2.2 k, 2.4 k, 3 k, 3.9 k, 4.7 k, 6.8 k, 8.2 k, 18 k, 20 k, 22 k, 24 k, 30 k, 50 k, 55 k, 68 k, 70 k, 80 k, 100 k, 330 k, 470 k, 680 k, 750 k, 1 m, 1.2 m, 1.8 m, 3.3 m.

Two Watt : 47, 220, 270, 470, 600, 1 k, 1.5 k, 3 k, 3.3 k, 4.3 k, 6 k, 8 k, 8.2 k, 10 k, 18 k, 22 k, 27 k, 30 k, 47 k, 50 k, 68 k.

Four Watt : 20, 40 k, 56 k, 68 k, 240 k, 470 k.

HIGH STABILITY RESISTORS. 1% ¼w. : 10 k, 25 k, 100 k, 1/- each. 1% 1 w. : 1 m., **1 3** each. 2% ½ w. : 4 k, 10 k, 13 k, 55 k, 250 k, 1 m, **9d.** each. 5% ½ w. : 39 k, 10 k, 39 k, 75 k, 130 k, 600 k, **8d.** each. 5% 1 w. : 8 k, 510 k, 910 k, 1.8 m, **9d.** each. 5% 2 w. : 10 m, 11 m, 12 m, **1 3** each. We have at press date large stocks of many of these values.

WIRE ENDED WIREWOUND RESISTORS. 4 watt : 50, 90, 1,000, **1 3** each. 6 watt : 14, 25, 15 k, **1 8** each. 10 watt: 90, 170, 350, 950, **1 9** each, 12 watt: 5, 30, 40, 120, 150, 3.5 k, 15 k, **2 -** each. 15 watt : 5, 100, 2.5 k, 3.6 k, 11 k, 30 k, **2 -** each.

CLIP FIXING WIREWOUND RESISTORS. 25 watt : 4, 350, 717, 5 k, 10 k, 75 k, **2 -** each. 45 watt : 14 k tapped 2 k, at **2 3** each. 65 watt : 50 k, at **2 6** each. 200 watt : 430, 10 k, 20 k, 50 k, at **3 -** each. We have large stocks of the heavier wattage resistors ; quantity prices on application.

POTTED TRANSFORMERS. Pri 230v 50 cps Sec. 0-325v 60 mA. 0-6.3 v. 500 mA. Size 3in. x 3in. x 2¼in., upright mounting. **12 6** each. Ex unused equipment.

BAKELITE CABINETS

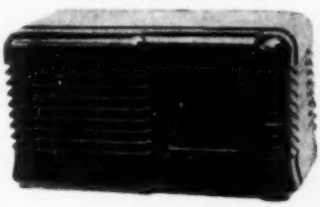

As illustrated, complete with chassis drilled for T.R.F. receiver, back, glass dial, speaker plate, brackets, three knobs. With each cabinet, we give circuits and instructions, with priced parts list for 3 valve T.R.F. receiver, thus enabling you to use the parts you already possess. Each **27 6.**

CLOSE TOLERANCE SILVER MICA CONDENSERS. 10,000pF (0.01μF) plus or minus 2%. Ideal for service bridges, etc., **1 -** each, **9 -** per doz., **£4 10 -** per gross. 1,000pF (0.001μF), ± 1%, **1 3** each. 100pF (0.0001μF) ± 1%, **9d.** each. 400pF (0.0004μF) ± 1%, **9d.** each.

HIGH CAPACITY PRECISION MICA CONDENSERS. We are again able to offer a complete range of these condensers, of which we have now sold over 25,000. Accuracy plus or minus 0.5 (point five) per cent. of stated value. Pure mica and copper foil or silver.

(a) 0.0017970μF	1 3	(b) 0.023570μF	1/3
(b) 0.027400μF	1 6	(c) 0.035020μF	1/6
(d) 0.040710μF	1 6	(dl) 0.048010μF	1/6
(e) 0.055820μF	1 6	(f) 0.065350μF	1/6
(f) 0.082910μF	1 6	(g) 0.087460μF	1/6
(h) 0.108435μF	1 9	(i) 0.123750μF	1/9
(i) 0.147000μF	1 9	(k) 0.205276μF	2/-

Many standard values to better than 1 per cent. can be made up by parallel or other combinations of above, e.g., 4i + 2k = 1μF ; 2k + g + 0.5μF ; c + f = 0.1μF. (A table of over 150 series and parallel combinations of these condensers, invaluable in calculating filter networks, etc., is available on receipt of 2½d. stamp.

CONDENSERS (pFs). 2, 4, 10, 15, 20, 30, 50, 75, 100, 160, 200, **6d.** each, **5 6** doz. 220, 300, 330, 500, 1,000, 2,000, 4,000, 4,500, 4,700, **9d.** each, **7 6** doz.

PAPER CONDENSERS. 1μF 500 v. wkg., 2¼in. x 2in. x ¾in. Inverted mounting, 1/- each, **9 -** per doz., **£3 12 -** per gross. 1μF 600 v. wkg., 2¼in. x 1¾in. x 1in. Upright mounting, **1 6** each, **15 -** per doz, **£7** per gross. 3μF 2,000 v. test, upright mounting Mansbridge type, ex-Govt. **2 9.** 4μF 500 v. wkg., inverted mtg., **2 9.**

HIGH VOLTAGE MICA CONDENSERS. 0.1μF 1,500 v. wkg., by a leading manufacturer. Bakelite cased upright mounting, 3in. x 2¼in. x1¾in. overall. Price **2 -** each, **21/-** per doz. Ceramic feed-through type, 10C/2178, 0.0002μF 5 kv. wkg., **2 6** each.

HIGH VOLTAGE PAPER CONDENSERS : 10C/12541. In black bakelite cylindrical case, single screw fixing. 0.02μF, 5kv. wkg., **1 9** each.

METERS. All 2 in. 0-4 a. D.C., **9 6** ; 0-8 a. D.C., **9 6** ; 0-20 a. D.C., **7 6** ; 0-50 v. D.C., **7 6** ; 0-300 v. D.C., **8 6** ; 0-500 mA. TH.C., **7 6.**

SWITCHBOARD VOLTMETERS. First grade M.I. Meters in robust metal case. 0-5 v. A.C. or D.C. (separate calibration for A.C.). Scale length approx. 6½in. Few only, **37 6** each.

PAXOLIN COIL FORMERS. 1¾in. long by 5/16in. diameter. Also suitable for metal rectifier sleeves. Approx. 50,000 available. **£1** per thousand.

AERIAL RODS. Copper plated steel. Fit into each other to make up any length aerial. Per doz., **2 -** ; per gross, **18 -** ; per thousand, **£4 10 -.**

METAL CUTTING SHEARS. A robust tool, one-inch blades, will cut up to 16 s.w.g. aluminium. Per pair, **2 -** ; per doz. pairs, **21 -** ; per gross pairs, **£11.**

ALL GOODS NEW AND UNUSED OTHERWISE STATED. GOODS SHOWN AS EX-EQUIPMENT HAVE BEEN FULLY TESTED AND ARE IN GOOD WORKING ORDER. **PLEASE ADD POST OR CARRIAGE ON ALL ITEMS. KINDLY PRINT NAME AND ADDRESS.** POST ORDERS TO OUR DEPTFORD ADDRESS. EARLY CLOSING THURSDAY, OPEN ALL DAY SATURDAY

GARLAND BROS. LTD

CHESHAM HOUSE, DEPTFORD BROADWAY, S.E.8
TELEPHONE : TIDEWAY 4412/3

5 OBELISK PARADE, LEWISHAM, S.E.13
TELEPHONE : LEE GREEN 4038

I.F. STRIP TYPE 194. An easily modified I.F. Strip recommended for T.V. constructors who want good results at moderate cost, or for those who have built television sets but are having trouble in the vision or sound receivers. Can also be modified for 2 Channel working as per details in "Practical Television" October issue. This 6-stage strip measures 18in. x 5in. x 5in. and contains 6 valves: VR65, 1 or VR92, and 1 of VR53 or VR56. Mod. data supplied. BRAND NEW. ONLY **45**/- (postage, etc., 2/6).

RDF 1 RECEIVER. A very powerful 14-valve receiver with 4 I.F. stages of 12 m.cs. with 4 mc/s. bandwidth. Will convert into a first-class T.V. receiver for 2 Channel working as described in "Practical Television," October and November issues, a reprint being supplied. Valve line-up: 5 of SP61, 2 of P61, 3 of EA50, and 1 each CV63, EB34, EC52, 5Z4G. ONLY **49 6** (carriage, etc., 5/-).

10-VALVE 11-METRE SUPERHET ZC893I. For long-distance T.V. results. Valve line-up is 6 of VR65, 2 of VR92, and 1 each VR136 and VR137, and the 12 mc/s. 6-stage I.F. Strip gives tremendous amplification with ample bandwidth of 4 mc/s. Easily modified. Full details supplied. ONLY **59 6** (carriage 5/-).

CHASSIS OF RECEIVER 3653. A wonderful "buy" for any constructor, measuring 18 x 11½ x 3in., and although certain items have been removed it contains 17 valve holders, 4 Pye plugs, 85 resistors, 23 tubular condensers, 40 silver mica condensers, trimmers, switches, etc., etc. Has front mounting panel size 11½ x 7½in. and is complete in metal case. In new condition. ONLY **15**/- (carriage, etc., 4/6).

CHOKES. 20 H 80 120 m/a., **9 6**; 5 H 200 300 m/a., **6**/-; 30 H 150 m/a., **12 6** (postage 1/-).

TRANSFORMERS. E.H.T. for VCR97 tube with 4 v. for tube heaters and 4 v. tapped 2 v. for E.H.T. rectifier. ONLY **37 6**. HEAVY DUTY FULLY SHROUDED 350-0-350 v., 160 m/a., 5 v. 3 a., 6.3 v. 6 a., 6.3 v. 3 a., ONLY **42 6**. HEAVY DUTY FULLY SHROUDED 250-0-250 v., 100 m/a., 5 v. 3 a., 6.3 v. 6 a., ONLY **32 6**. UNIVERSAL MOUNTING 350-0-350 v. 80 m/a., 0-4-6.3 v. 4 a., and 0-4-5 v. 2 a., ONLY **18 6**. TRAIN TRANSFORMER giving tapped outputs of 3 v., 4 v., 5 v., 6 v., 8 v., 9 v., 10 v., 12 v., 15 v., 18 v., 20 v., 24 v., 30 v., at 2 a., ONLY **19 6**. TOP SHROUDED DROP THROUGH 260-0-260 v., 70 m/a., 6.3 v. 3 a., 5 v. 2 a., ONLY **16 6**. (POSTAGE 1/6 EACH TRANSFORMER, PLEASE.)

6in. MAGNIFYING LENS FOR VCR97 TUBE. First-grade oil-filled. ONLY **25**/- (postage 1/6).

"PYE" 45 MC/S. I.F. STRIP. Ready made for London Vision Channel. Complete with 6 valves EF50 and an EA50, and details of very slight mods. required. ONLY **37 6** (postage, etc., 1/6).

R.1155 RECEIVER POWER PACK with built-in output stage. A special factory made job designed to plug on to the set and operate it without any internal modification. Will drive any size low impedance P.M. speaker. Housed in attractive black crackle metal cabinet, and complete with valves. ONLY **£5 10**/- (carriage, etc., 5/-).

BALANCED ARMATURE EARPIECES. High-grade ex-Govt. Make excellent midget speaker. ONLY **3 9** (postage 6d.), or **42**/- doz., carr. paid.

100 MICRODAMPS METER. 2½in. Flush mounting. Widely calibrated scale of 15 divisions marked "Yards," which can be re-written to suit requirements. These movements are almost unobtainable to-day, and being BRAND NEW IN MAKER'S CARTONS are a "snip" at ONLY **39 6**.

CAR OR STORAGE BATTERIES by famous American makers. Brand new and unused, these have genuine hard rubber cases. 6 v. 77 a.h. "PHILCO" size 10¼in. long x 7in. wide x 8¼in. high, ONLY **82 6**; 6 v. 90 a.h. "THOR," size 8¼in. long x 6¼in. wide x 7¼in. high, ONLY **87 6** (carriage 5/- each battery).

EX-W.D. TRANSFORMERS. All heavy duty with 230-250 v. primaries. Type A has secondaries of 330-0-330 v. and 4 v. 3 a. ONLY **22 6**. Type B is an EHT transformer with secondaries of 2 v. 1.5 amps., 300 v. 100 m.a., 520 v. 10 m.a., 1,400 v. 2 m.a., ONLY **21**/-. Type C is a Filament Transformer with secondaries of 6.3 v. 7 amps., 4.2 v. 2.5 amps., 4 v. 1 amp., ONLY **19 6** (postage 1/8 each item). ALL ITEMS BRAND NEW AND UNUSED.

PENTODE OUTPUT TRANSFORMER, for 3 ohm speakers, **5 3**.

WHARFEDALE OP3, with ratios of 30, 60, and 90, **6 6** (postage per trans. 4d.).

6.3 v. FILAMENT TRANSFORMER, rated 1½ amps., **7 6** (postage 6d.).

CO-AXIAL CABLE, 75-80 ohms, thin type, **1 3** per yard (post paid 12 yards or more).

VOLUME CONTROLS. New, manufacturer's surplus. Less switch, from 2 k. to 3 megs., **3**/-; with switch from 1 k. to 2 megs. **4 6** (postage 3d.).

HAND MICROPHONE, with carbon granule insert and switch in handle, **3 6** (postage 1/-).

INTERNATIONAL OCTAL PLUG. Fits into I.O. valve-holder, **2**/- (postage 3d.).

VALVE HOLDERS. Amphenol I.O. or M.O., **7d.**, **6**/- per doz. Ceramic Brit. 5-pin, 1/-, **10**/- doz. Diode, **6d.**, **5**/- doz. VCR97 holder, **1 6**, **24**/- doz. (post paid 1 doz. or more).

Cash with order please, and print name and address clearly. Amounts given for carriage refer to inland only

U.E.I. CORPORATION

Radio Corner, 138 Gray's Inn Road, London, W.C.1. *Phone*: TERMINUS 7937.

(Open until 1 o.m. Saturdays. We are 2 mins from High Holborn (Chancery Lane Station) and 5 mins. by bus from King's Cross.)

MAINS TRANSFORMERS

FULLY INTERLEAVED
SCREENED AND IMPREGNATED. ALL GUARANTEED.
ALL PRIMARIES ARE 200/250 v. Half Shrouded.

HSM63. (Midget). Output 250-0-250 v. 60 m/a., 6.3 v. at 3 amps., 5 v. at 2 amps. **18**/-

HS63. Output 250-0-520 v. 60 m/a., 6.3 v. at 3 amps., 5 v. at 2 amps. **18 6**

HS40. Windings as above, 4 v. at 4 amps., 4 v. at 2 amps. Output **18 6**

HS2. 250-0-250 v. 80 m/a. **21**/-

HS3. 350-0-350 v. 80 m/a. **GS30.** 300-0-300 v. 80 m/a. **21**/-

HS2X. 250-0-250 v. 100 m/a. **HS75.** 275-0-275 v. 100 m/a. **23**/-

HS30X. 300-0-300 v. 100 m/a. **HS3X.** 350-0-350 v. 100 m/a. **23**/-

Fully Shrouded

FSM63. (Midget). Output 250-0-250 v. 60 m/a., 6.3 v. at 3 amps., 5 v. at 2 amps. Output **18 6**

FS2. 250-0-250 v. 80 m/a. **23**/-

FS30. 300-0-300 v. 80 m/a. **FS3.** 350-0-350 v. 80 m/a. **23**/-

FS2X. 250-0-250 v. 100 m/a. **FS75.** 275-0-275 v. 100 m/a. **25 9**

FS30X. 300-0-300 v. 100 m/a. **FS3X.** 350-0-350 v. 100 m/a. **25 9**

All the above have 6.3-4-0 v. at 4 amps., 5-4-0 v. at 2 amps.

FS43. Output 425-0-425 v. 200 m/a., 6.3 v. 4 amps., C.T. 6.3 v. 4 amps., C.T. 5 v. 3 amps. Fully shrouded **51**/-

FS50. Output 450-0-450 v. 250 m/a., 6.3 v. 2 amps., C.T., 6.3. v. 4 amps., C.T. 5 v. 3 amps. Fully shrouded **75**/-

F30X. Output, 300-0-300 v. 80 m/a., 6.3 v. 7 amps., 5 v. 2 amps. Framed. Flying leads **31 9**

F35X. Output, 350-0-350 v. 250 m/a., 6.3 v. 6 amps., 4 v. 8 amps., 4 v. 3 amps., 0-2-6.3 v. 2 amps. Fully shrouded **71 6**

FS160X. Output, 350-0-350 v. 160 m/a., 6.3 v. 6 amps., 6.3 v. 3 amps., 5 v. 3 amps. Fully shrouded **47 6**

FS43X. Output, 425-0-425 v. 250 m/a., 6.3 v. 6 amps., 6.3 v. 6 amps., 5 v. 3 amps. Fully shrouded **69**/-

HS6. Output, 250-0-250 v. 100 m/a., 6.3 v. 6 amps., C.T. 5 v. 3 amps. For receiver R1355. Half shrouded **29 3**

HS150. Output, 350-0-350 v. 150 m/a., 6.3 v. 3 amps., C.T. 5 v. 3 amps. Half shrouded **30 9**

F36. Output, 250-0-2 0 v. 100 m/a., 6.3 v. 6 amps., C.T. 5 v. 3 amps. Half shrouded **32 6**

FS120. Output, 350-0-350 v. 120 m/a., 6.3 v. 2 amps., C.T. 6.3 v. 2 amps., C.T. 5 v. 3 amps. Fully shrouded **33**/-

FS256. Output, 250-0-250 v. 80 m/a., 6.3 v. at 6 amps., 5 v. at 3 amps. Fully shrouded **30 9**

PRI 1. Output 230 v. at 30 m/a., 6.3 v. at 1.5/2 amps. **23**/-

FS150. 350-0-350 v. 150 m/a., 6.3 v. 4 amps., 5 v. 3 amps. **34 9**

FS150X. Output, 350-0-350 v. at 150 m/a., 6.3 v. at 2 amps., C.T., 6.3 v. at 2 amps., C.T. 5 v. at 3 amps. Fully shrouded **34 9**

The above have inputs of 200/250 v.

FILAMENT TRANSFORMERS

F4. Output, 4 v. 2 amps., **F6.** Output, 6.3 v. 2 amps. **9**/-

F12X. Output, 12 v. at 1 amp., **9**/-. **F6X.** Output, 6.3 v. 0.3 amps. **6**/-

F12. Output, 12.6 v. tapped 6.3 v. at 3 amps. **18 6**

F24. Output, 24 v. tapped 12 v. at 3 amps. **26**/-

F12 and F24 framed with Flying Leads.

FU6. Output, 0-2-4-5-6.3 v. at 2 amps. **11**/-

F29. Output, 0-2-4-5-6.3 v. at 4 amps. **20 9**

FU6 and F29 Output, framed with Flying Leads.

F5. Output, 6.3 v. at 10 amps. or 5 v. at 10 amps. or 12.6 v. at 5 amps. or 10 v. at 5 amps. **37 9**

F6 4. Output, four at 6.3 v. tapped at 5 v. at 5 amps. per winding giving by suitable series and parallel connections 24 v. at 5 amps., 20 v. at 5 amps., 18 v. at 5 amps., 15 v. at 5 amps., 12.6 v. at 10 amps., 10 v. at 10 amps., 6.3 v. at 20 amps., 5 v. at 20 amps. **57**/-

F5 and F6 4 framed with Flying Leads.

FU12. Output 0-4-6.3 v. 3 amps. **FU24.** Output 0-12-24 v. 1 amp. **19 6**

The above have inputs of 200/250 v.

OUTPUT TRANSFORMERS

MOP1. Ratios, 26, 46, 56, 66, 90, 120-150 m/a. max. current. C.T. for Q.P.P. Class B, etc. Secondary 2/4 ohms. Top panel and clamped, each **6**/-

OP1. Midget Power Pentode, ratios 30, 60, 90-1, 40 m/a. Secondary 2/3 ohms, each **4**/-

OP2. Midget Pentode, ratios 45-1, Secondary 2/3 ohms, 40 m/a., per doz. **39 6**

OP10. 10-15 watts output, 20 ratios on Full and Half primary **19 9**

OP30. 30 watts output, 20 ratios on Full and Half primary **28 6**

Williamson's O.P. Transformer to Author's specification **£4 3 6**

Chokes for Williamson's Amplifier. 30H. at 20 m/a. **15 6**

10H. at 150 m/a. **35 6**

Choke C4. 60 m/a., approx. 8H. 350 ohms **5**/-

Choke C5. 40 m/a., approx. 5 H., 350 ohms **4**/-

Choke C6. 50 m/a., 50 H., 1,500 ohms **22**/-

C8. 360 Micro henries clamped, **5/3. C7.** 90 m/a. 180 ohms, clamped **6 3**

Belling-Lee Co-Axial Plugs. Type 642/P., each **1 3**

Belling-Lee Co-Axial Sockets. Type 604/S, each **1 3**

Quotations, etc.—stamped addressed envelope please.

C.W.O. (add 1/3 in £ for carriage), all orders over £2 carriage paid.

Trade and also Export enquiries invited.

H. ASHWORTH (Dept. WW)

676, Gt. Horton Road, Bradford, Yorks.

MAINS TRANSFORMERS

These transformers are all famous radio manufacturers' surplus and are fully interleaved, impregnated and guaranteed.

Primary 200-250 v. P. & P. on each 1/6 extra.

350-0-350, 100 mA., 4 v. 4 amp., 4 v. 2 amp., upright or drop-through, **16/-**.

300-0-300, 100 mA., 6 volt 3 amp., 5 volt 2 amp., **17/6**.

320-0-320, 120 mA., 6 volt 4 amp., 5 volt 2 amp., **25/-**.

350-0-350, 150 mA., 6 volt 3 amp., 5 volt 2 amp., drop-through or upright mounting, **27/6**.

250-0-250, 100 mA., 6 v. 3 amp., 4 v. 3 amp., 4 v. 3 amp., **17/6**.

250-0-250, 60 mA., 6 v. 4 amp. (to be used on common heater chain with 6/- 5 rectifier), **13/6**.

280-0-280, 80 mA., 6 v. 3 amp., 4 v. 2 amp., drop-through, **14/-**.

Drop thro', 350-0-350 v. 70 mA., 6 v. 2.5 amp., 5 v. 2 amp., **14/6**.

Semi-shrouded, drop-thro' or upright mounting 280-0-280, 80 mA., 4 v. 6 amp., 4 v. 2 amp., **12/6**.

Auto-wound, H.T. 280 volts at 360 mA., 4 v. 3 amp., 2 v. 3 amp., or 6 v. 3 amp. Separate 4 v. 3 amp. rectifier winding (upright or drop-through), **10/6**.

350-0-350, 120 mA., 4 v. 6 amp., 4 v. 3 amp., drop-through, **21/-**.

Auto-transformer, various combinations of voltages including 110 v. 70 watt, and 3/4 volts windings at 1 amp., 2 volt 1 amp., drop-through or upright mounting, **10/6**.

Heater Transformer. Pri. 200-250 v., 6 v. 1½ amp., **6/-**; 13 v. 1½ amp., **6/-**; 2 v. 2½ amp., **5/-**. P. & P. each **9d.**

ELECTROLYTIC CONDENSERS

Ex-Govt. 8 mfd. 500 v. wkg., size 3½" × 1¾in., 2 for **2/6**, post paid.

P.M. SPEAKERS

	with trans.	less trans.
2½in.	—	13/6
3½in.	—	11/6
5in.	15/-	12/6
6½in.	14/6	11/6
8in.	17/-	14/6

10in. M.E. Speaker Field Coil, 1,100 ohms, speech coil 2-3 ohms, 17/6.

P. & P. on each of the above 1/- extra.

Constructor's Parcel, comprising chassis 10½" × 5½" × 2in. with speaker and valve holder cut-outs, 5in. P.M. speaker with transformer, twin gang with trimmers, pair T.R.F. coils long and medium iron cored four valve holders, 20K volume control and wave-change switch. Post paid **21/-**.

Constructor's Parcel, comprising 4-valve T.R.F. chassis, 8½ x 4 x 1¾in., 3 VR65A (using one as an output valve), heater trans. pri. 200-250, choke, O/P trans. 3 valve holders, pair medium-wave coils, 47K. pot, twin gang, and scale, **20/-**, post paid.

Volume Controls, by famous manufacturer. Long spindle less switch, 5 K., 50 K., 500 K., 1 meg. **2/6** each. P. & P. 3d. each.

Frame Blocking Oscillator Transformer, 4/6.

D. COHEN

RADIO & TELEVISION COMPONENTS

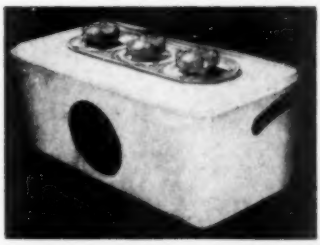

PERSONAL PORTABLE CABINET in cream-coloured plastic; size 7" × 4½" × 3 in. Complete 4-valve chassis. Takes miniature 90 v. and 7½ v. batteries. **13/6** POST PAID.

2½in. P.M. Speaker to fit above, **13/6**. Miniature output transformer **5/-**. Miniature wave-change switch **1/9**. Miniature 1-pole 4-way used as Volume and Off **1/9**. 4 B7G valve holders, **2/-**. Midget twin gang ½in. dia., ¾in. long and pair medium and long-wave TRF coils ¾in. long × ¾in. wide; complete with 4-valve all-dry mains and battery circuit **8/6**. Tuning scale and four knobs **2/6**. Condenser Kit, comprising 11 miniature condensers, **4/6**. Resistor Kit, comprising 12 miniature resistors **3/6**. The above receiver (less valves and batteries) could be built for approximately **55/-**.

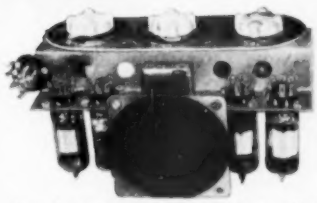

View of chassis as it would look when assembled with valves inserted.

THREE WAVE-BAND COIL PACK, iron-cored coils, 16-50, 180-550, 1,000-2,000 metres. I.F. frequency 465 Kc. Size, 4½" × 1¾in. × 2¾in., **24/-**, post paid. Double-ended perspex trimming tool given free with each pack.

CONSTRUCTOR'S PARCEL comprising 5-valve superhet chassis with transformer I.F. and valve holder cut-outs, size 18" × 5½" × 2¼in., with L.M. & S. scale size 7" × 5in. Back plate, two supporting brackets, drive drum pointer, two-speed spindle, spring, three pulleys and five international Octal valve holders, **11/6**, post paid.

N.B.—To the purchasers of this parcel. Coil pack at the reduced price of **17/6**, post paid.

P.M. FOCUS UNIT. For any 9in. or 12in. tube, except Mazda 12in., state tube, **12/6**.

P.M. FOCUS UNIT. For Mazda 12in., **15/-**.

PENSOLDA 6 VOLT LIGHT-WEIGHT SOLDERING IRON, weight 3½ ounces complete with 1½ yards circular flex, **8/6**. Post & pack, 1/-. Complete with suitable heater transformer Primary 230/250 volts, **10/6**. Post & pack 1/9. Transformer not sold separately.

MAINS or BATTERY SUPERHET PORTABLE COILS. Comprising medium-wave frame aerial and long-wave loading coil, used as aerial coils. Midget iron-cored screened L.M. osc. coils., complete with circuit I.F. frequency 465 Kc., **9/6**.

METAL RECTIFIERS, 250 v. 60 mA., latest midget Selenium type, **6/6** post pd.

OUTPUT TRANSFORMERS. Standard type 5,000 ohms imp., 2 ohms speech coil, **4/9**; Push-Pull 6 v. 6 matching 10-watt 2-ohms speech coil, **6/9**. 42-1 speech coil 2 ohm with extra feed-back winding, **4/3**; Miniature 42-1 2 ohm speech coil **3/3**.

SET OF 3 BROWN KNOBS marked "wave change," "tuning," and "volume," **1/6**.

6-pin 6-volt synchronous vibrator	8/6
6-volt standard 4-pin vibrator	8/6
Vibrator transformer 250-0-250 80 mA. 6 volt P/P.	8/6

EXTENSION SPEAKER CABINET

Polished in a pleasing light and dark shade. Complete with an 8in. P.M. Rubber feet and back. Size 10in. × 10in. × 4¼in., **22/6**, post paid.

TELEVISION MASKS

White Rubber, 9in. with glass, **10/6**. White Rubber, 12in. with glass, **15/-**. 15in. white rubber mask, soiled, **12/6**, plus 1/- P. & P.

All-Dry A.C. Mains Supply Unit, size 3½in. long × 2¼in. wide × 1¼in. deep. We can supply a complete all-dry circuit, using the above Midget Components to incorporate the above Power-Unit, **19/6** post paid with circuit.

Midget Bakelite Cabinet, 7in. × 5¼in. × 5in. c/w 5-valve S.h. chassis, med.-long-wave scale and back (takes std. twin gang condenser and 3½-in. speaker), **15/-**. P. & P. 1/6.

Wave-Change Switches, 6-pole 3-way, 2/-; 4-pole 3-way, **1/9**; 5-pole 2-way, midget, **1/9**; 5-pole 3-way, **1/9**; 3-pole 3-way, **1/9**; 2-pole 1-way, midget, **1/3**; 2-pole 1-way, **1/3**; 9-pole 3-way, **3/6**. P. & P. 3d. each.

Pre-Aligned Midget 465 Kc. Q. 120, **9/-** per pair, post 6d. **Miniature 465 Kc. I.F.s.** Q 120 per pair **10/-**.

465 Kc. Midget I.F.s. Q 120, size 1¼in. long, 1in. wide, ¾in. deep, by very famous manufacturer. Pre-aligned adjustable iron-dust cores, per pair, **12/6**. **465 Kc. Iron-Cored** Q 120 size ¾" × 1in. dia., **7/6**.

Iron-Cored 465 Kc. Whistle Filter, 2/6.

T.V. Chassis. Size 9½" × 9½" × 3¼in., **3/-**.

Standard 465 Kc. I.F.s. Q 120 iron-cored, 3½" × 1½" × 1¼in., per pair **10/6**.

Valve Holders. Paxolin international octal **4d.** each. Moulded international octal, **7d.** each. EF50 ceramic, **7d.** each. Moulded B7G, slightly soiled **6d.** each.

Line Cord 3-way 0.3 amp., 180 ohms per yard, **1/3** per yard. **Ceramic P.F.S.** 3 each of the following, 330, 220 180, and #2 **2/6**.

Trimmers, 5-40 pf., **5d.**; 10-110, 10-250, 10-450 pf., **10d.** Three bank 50 pf **1/3**. Four bank, 50 pf. **1/8**.

Twin-Gang .0005 Tuning Condenser 5/-. With trimmers, 7/6. Post and packing 6d.

Twin-Gang Midget .00037 with perspex dust-cover and trimmers, **8/6**. Post and pkg. 6d.

Mains Droppers 0.3 amp. 460 ohms, tapped 280 and 410 **1/6**; 0.2 amp. 717 ohms, tapped at 100 ohms, vitreous, **1/6**; 0.3 amp. 950 ohms, tapped 700 and 825, **2/6**; 0.2 amp. 1,000 ohm vitreous, tapped, **2/6**. P. & P. on each 3d.

Volume Controls by famous manufacturer. Long spindle and switch ¼, ½, 1 and 2 meg., 4/- each; 20, 25 and 50 K., **3/6** each. Post and packing 3d. each.

THIS MONTH'S OUTSTANDING OFFER

Constructor's 465 kc. I.F. Kit, comprising 4 double pie wound coils on ¾in. Aladdin formers, 4 iron cores, 2 cans 3½" × 1½" × 1¼in., four hundred pf. silver mica 5%, and two paxolin mounting panels **4/6**, post paid.

Terms of business: Cash with order. Dispatch of goods within 3 days from receipt of order. Where post and packing charge is not stated please add 6d. up to 10/-, 1/- up to £1 and 1/6 up to £2. All enquiries and Lists, S.A.E

23 HIGH STREET (Opposite Granada (Cinema), ACTON, W.3

Hours of Business: Saturdays 9—6 p.m. Wednesday 9—1 p.m. Other days 9—4.30 p.m. Telephone: ACOrn 5901

UNIVERSITY RADIO LTD.

Offer Guaranteed Used Equipment at Attractive Prices

Eversheds 500 volt Wee Megger, in leather case £10 10 0
Avo 1948 Signal Generator, as new £12 10 0
Cossor Double-Beam Oscilloscope, model 339, as new £40 0 0
Cossor, as above, model 3339 ..... £36 10 0
Taylor 120A AC/DC Test Meter, as new £6 10 0
Avo Minor, AC/DC, as new £7 10 0
Avo Model 7, as new £14 10 0
Avo Model 40, as new £12 10 0
Eddystone 640, as new £23 10 0
Avo 1949 Capacity and Resistance Bridge, as new £8 10 0

Wharfedale W-10/CS Speaker, 2-3 or 15 ohms, as new £7 0 0
Wharfedale W-12, as new £7 0 0
Wharfedale Twin Speakers, in Wharfedale Corner Cabinet, as new £30 0 0
Decca Record-playing Unit, 78 r.p.m., as new £6 10 0
Ex-W.D. B1 TX RX, in portable case. A.C. and battery power-unit. Coils, phones, key, etc. As new £17 10 0
Avo Electronic Valve-Tester. Latest model, as new £45 0 0
Avo Wide-Range Signal Generator, as new £33 10 0

General Electric (U.S.A.) Tube Checker, in portable case. 110 A.C. as new £11 10 0
Taylor 313C Capacity and Inductance Adaptor, as new £3 17 6
E.D.C. Rotary Convertor, D.C. 220-240, A.C. 220-240, 50 cyl 120 w., in metal silencing case, complete with filter-unit. As new £14 10 0
B.S.R. Disc-Recording Unit, in portable case, as new £65 0 0
Eddystone 258X, with 8 coils, 31 meg. to 100 kc's with A.C. power-pack. As new £22 10 0

WE NEED GOOD USED EQUIPMENT URGENTLY. PLEASE SEND, BRING OR PHONE FOR OFFER. WE NEED AR 88's-BC 221's-348's-342's ALSO COSSOR DB'SCOPES 339A OR 3339 Etc. WE WILL PAY WITHIN £2. 0. 0 OF THE MARKET PRICE.

R.C.A. Volt-Ohmist Junior Valve Voltmeter, as new with manual £16 10 0
Shaftesbury Ribbon Mikes, as new £6 0 0
Voigt Light Twin Speaker Unit, mains energised, complete with mains-energising unit, as new £15 10 0
Voigt Latest Model PM Unit, in Voigt corner cabinet, unpolished. (Not Home Constructor Cabinet) Listed £90, our price, as new £65 0 0

We have in stock several of the latest models of Marconi Signal Generators, etc.
Mullard Oscilloscope, type GM-3152, as new £30 0 0
Cambridge Unipivot Galvanometer, patt. "L," 0-120 millivolts, 6in. scale, as new £8 0 0
B.S.R. Disc-Recording Amplifier, type AR15 in portable metal case. As new £38 10 0

Valradio Convertors, 200-250 D.C. to 200-250 A.C., 50 cycles, 200 watts. As new £10 10 0
Transmitter Type 12, A.C. 200-250 volts, 2.6 to 17.5 Megs., complete with valves and perfect £20 0 0
Thrush Capacity and Resistance Bridge, as new ..... £ 10 0
Weston (U.S.A.) A.C. D.C. Testmeter, model E772, 20,000 o.p.v. in portable case. As new £15 0 0

★ We have a large selection of British and U.S.A. Valve Testers, Test-Meters and Signal Generators, etc. Your enquiries are welcome. S.A.E. please

THESE ITEMS ARE ONLY A SMALL SELECTION FROM OUR STOCK OF EQUIPMENT. YOUR ENQUIRIES FOR ANYTHING THAT YOU MAY NEED WILL BE WELCOME. WE HAVE OTHER EQUIPMENT ARRIVING DAILY!

CASH OR CHEQUE WITH ORDERS. ALL ITEMS ARE CARRIAGE EXTRA.

22 LISLE STREET, LEICESTER SQUARE, LONDON, W.C.2

OUR BRANCH AT 39a (opposite) IS OPEN ALL DAY THURSDAY. *Phone: GERrard 4447, 8582 and 5307. Hours 9 to 6. Thursdays 9 to 1*

TO HAMS & DEALERS

WE WANT TO BUY

AMERICAN SURPLUS EQUIPMENT OF EVERY KIND

FOR RADIO HAM SHACK—
NEW YORK'S LEADING DEALERS

RECEIVERS TRANSMITTERS
TEST SETS SIG GENS
EVERYTHING ELECTRONIC

We are interested in any quantity, from one upwards. 'Phone us immediately transfer charge.

ALTHAM RADIO CO BRAZENNOSE ST
MANCHESTER 2 *Tel: DEAnsgate 5387*

dm AR 15

ALEC Davis SUPPLIES Ltd.

Dept. W.W

18 TOTTENHAM COURT ROAD, LONDON, W.1

Tel.: MUSeum 2453/4539

Shop Hours: Monday-Friday 9—5.30 Saturday 9—1

RELAYS

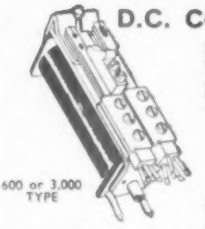

600 or 3,000 TYPE

D.C. COIL RESISTANCE

3,000 TYPES: 1.9Ω to 80,000Ω
600 TYPES: 0.4Ω to 9,200Ω.

ALSO LARGE STOCKS OF DOUBLE & TRIPLEWOUND AND SLUGGED COILS.

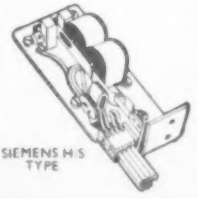

SIEMENS H/S TYPE

CONTACTS

3,000 TYPES: up to 8 sets.
600 TYPES: up to 4 sets.

3,000 TYPES: Make (M), Break (B), in Twin-silver, Twin-platinum, Dome-silver (2 amp.), Tungsten (5 amp.), and Flat-silver (8 amp.). Change-Over (C), in all but Tungsten: Make-Before-Break (K), in Twin-silver and Twin-platinum.

600 TYPES: (M), (B) and (C), in Twin-silver and Twin-platinum.

SPECIAL
High resistance slugged coils (up to 10,000 OHMS with 1" slug) now available.

Henry's
RADIO COMPONENTS
ELECTRONIC & TELEPHONE EQUIPMENT

5 Harrow Road, Paddington, W.2

PADdington 1008 9 and 0401

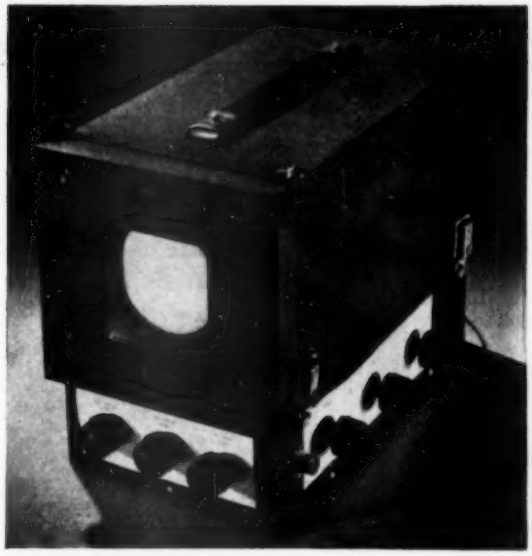

OSCILLOSCOPE TYPE 3BP1

We have pleasure in offering a 'scope designed primarily for simplicity and low cost at the same time giving reliable and consistent results. The Service engineer will find this an invaluable instrument due to its compactness, simplicity and speed of interpreting faults in radio receivers, checking transmitters, modulation, depth, etc.

SPECIFICATIONS

Amplifier : Max. Gain, Peak to Peak = .3 volts per cm. Frequency response 10 c/s—100 k/c. Flat = 100 c/s to 50 k/c. Time Base : frequency range 5 c/s—30 k/c.
Dimensions : 8½ x 6½ x 11½. Weight 17lb. Black crackle finish.
PRICE : Brand New, **£14 14 0**, carr. pd.

Bowthorpe Continuity Meter

Dual scale 0-500 ohms and 100—2X0,000 ohms Moving Coil operated from 4½-volt internal battery. Size 6 x 3 x 4¼in. Original price **£8 10 0**. OUR PRICE, BRAND NEW **£4 4 0**.

RECORD CHANGERS

Collaro RC500 with crystal pick-up	£12 3 3
Collaro RC511 with plug-in pick-up either crystal or hi-Fidelity	£11 16 9
Collaro 3-speed changer	£12 9 9
Plug-in heads for same magnetic	£1 19 6
Plug-in heads for same crystal	£3 2 4
Hi-Fidelity high Impedance	£3 6 0
Hi-Fidelity low Impedance	£1 19 6
MU10 33⅓ r.p.m.	£3 14 4
MU143-speed	£7 3 4
Decca 33⅓ Desk and Pick-up	£9 19 6
Collaro Single Player	£6 10 8
Connoisseur Desk	£22 18 8

MAINS TRANSFORMERS. 250-0-250, 90 m.a., 6.3 v. 3 amp., 5 v. 2 amp., input 110 v.,250 v. **£1**, post 9d.
EX-MANUFACTURERS. 350-0-350, 100 m/a., 6.3 v. 4 amp., 5 v. 2 amp., input 200 250. **25/-**.
REPLACEMENT TYPE. 350-0-350, 90 m.a., 4 v. 6 amps., 4 v. 3 amps., input 200 250. **18/6**.
DUAL PURPOSE TYPE. 350-0-350 80 m.a., 6.3 v. tapped 4 v. at 3 amps., 5 v. tapped at 2 amps., 4 v., **20/-** (post 9d.).

RECEIVER TYPE 25. The receiver portion o the T.R. 1196. Covers 4.3—6.7 Mc/s. and makes an ideal basis for an all-wave receiver as per *Practical Wireless*, August, 1949, issue. Complete with valves type EF36 (2), EF39 (2), EK32 and EBC33. Supplied complete with necessary conversion data for home use. **35/-**. New condition.

GERMANIUM CRYSTAL DIODES, complete with full wiring circuit and diagram, **4/6**.

METAL RECTIFIERS. S.T.C. 200 volts 75 m/a., **6/-**; G.E.C. 6 volts 1 amp., **4/-**; Westinghouse 12 volts 2 amps., **12/6**; Pencil Type E.H.T., 600 v. 1 m/a., **4/7**; Pencil Type E.H.T., 1,000 v. 1 m/a., **6/-**; 12 v. 3½ amps., **17/6**.

S.T.C.R.M.2. 125 v 100 m/a., **4/6**.

R.3515 I.F. STRIP. A complete I.F. Unit, comprising 6 SP61 I.F. Stages, tuned to 13.5 Mc/s., 1 EA50 diode detector, and 1 EF36 or EF39 output or video stage. A few modifications only are required to adapt this unit which will give pictures of extremely good quality. Price complete with valves and foolproof modification instructions, is **45/-**, plus 5/- carriage and packing. Limited quantity only.

RECEIVER R.1355.—As specified for "Inexpensive Television." Complete with 8 valves VR65 and 1 each SU4G, VU120, VR92. Only **55/-**, carriage 7/6.

MOVING COIL METERS. 0—5 m.a. square panel mounting, 2in. scale, **7/6**; 0—50 m/a., square panel mounting, 2in. scale, **7/6**; 0—40 v., square panel mounting, 2in. scale, **7/6**; 0—20 amps., square panel mounting, 2in. scale, **7/6**; 0—300 v., square panel mounting, 2in. scale, **12/6**; 0—40/120 m.a., double reading round scale, **12/6**; 0—1,500 v. Electrostatic 2½in. scale round, **25/-**; 0—100 v. A.C. rectified type, 2½in. round scale, **25/-**.

POWER UNIT. Complete with 5Z4G, VU120, .1 mfd., 2,500 v. wkg. relay and 80 v. input trans., **15/-**, new condition (post 1/6).

RECEIVER UNIT TYPE 159. Containing VR91, VR92, VR65 and 24 v. selector switch. New condition, **15/-** (post 1/6).

CATHODE RAY TUBES. VCR97, brand new, in original crates. Guaranteed for full picture on television, **45/-**, carriage paid. 5CP1, brand new, **25/-**, plus 5/- carriage. 3BP1, complete with base, holder and shield in metal case. Ideal for 'scope. **25/-**, 2/6 carriage.

TUBE ENLARGING LENS for VCR97 or 5CP1. Double your picture area, without distortion. Easy fixing. Really amazing in performance. Only **25/-**.
6in. Masks, standard. For rectangular picture, **7/6**.

E.H.T. TRANSFORMER for VCR97. Input 230 v., output 2,500 v., 4 v. 2-0-2, **39/6**.
E.H.T. TRANSFORMER for 5CP1. Input 230 v., output 3,250 v., 6.3 v. at 0.6 a/m., 2-0-2 v., **39/6**.

"HIGH-VOLT" R.F. OSCILLATOR. 5—7 K.v. at 250 u/a., **£5 10/3**; 12.5 K.v. at 250 u/a., **£10 10/-**.

CONDENSERS. .1 mfd. 2,500 v.w., metal or bakelite, **2/6**. Electrolytics, 8 mfd. 450 v.w., **2/6**. 8 x 8 mfd., **4/-**. 16 mfd. 450 v.w., **3/6**. 16 x 16 mfd. 450 v.w., **5/-**. All midget Tubular Cans, cardboard sleeves. 60 mfd. x 40 mfd. 350 v.w., size 4¼in. "XI," **7/6**. 32 mfd. Bias Condensers, 25 x 25 mfd., 50 x 12, 12 x 50, **1/6**; 50 x 50, **3/-**. All new stocks —NOT surplus.

VR91 (EF50) Red Sylvanian. Brand new, original boxes U.S.A., **10/-**; Silver, brand new, original boxes, British, **8/6**; red or silver ex-units, guaranteed, **6/-**.

CONDENSERS—TUNING. 2-gang .0005 standard ¼ spindle, **5/-**; 2-gang .0005 standard trimmers, **7/6**; 3-gang .0005 with ceramic insulation, ¼ spindle, **7/6**; 4-gang .0005 with ceramic insulation, ¼ spindle, **8/-**. MIDGET TWO-GANG, .000375, with TRIMMERS. Size 2 x 1½ x 1¼in. VANES enclosed in perspex, **7/6**. MIDGET .0005 mfd. 2-GANG TUNING CONDENSER. Size only 2¼ x 1½ x 1¼in., **6/6**; or with built-in trimmers, **7/6**. TWO-GANG MIDGET .0005 with 4-way push-button assembly. Suitable for car radio, etc., **8/6**. 2-gang midget, .0001 ceramic insulation, **5/6**. Single solid dielectric tuning condensers, .0001, 0.0003, and 0.0005 1/8., **3/4**.

RCA 931A PHOTO-ELECTRIC CELL AND MULTIPLIER. For facsimile transmission, flying spot telecine transmission and research involving low light-levels, 9-stage multiplier. Brand new and guaranteed, only **30/-**. Data sheets supplied.

PUSH-PULL OUTPUT TRANSFORMER. U.S.A. potted type primary 10,000Ω sec., 2Ω, 8Ω, 15Ω, 15 watts, **21/-**.

No. 38 "WALKIE-TALKIE" TRANS. RECEIVER. Complete with throat mike, 'phones, junction box and aerial rods in canvas bag. Freq. range 7.4 to 9 mc/s. All units are as new and tested before despatch. As supplied to Overseas Police Forces. **£4 19 6**, carriage 2/6.

WALKIE-TALKIE TYPE 46. Complete with six valves, 2 VP23, HL23/DD, QP25, TP25 and ATP4, 8 aerial rods, I.F. trans., 1.6 Kc/s. In new condition but less transmitting components and coils removed by M.O.S., **45/-**, carr. pd.

WEARITE. 705 Coil Pack, 3-wave band, **37/10**; 4008 Min. I.F.T. 465, **14/-** pair; 501 and 502, 465, **14/-**.

For IMMEDIATE DELIVERY *From* OUR LARGE STOCKS

RESISTORS
HIGH STABILITY, close tolerances ¼, ½, 1 and 2 watt. All values up to 2 meg. also 8, 13 and 30 meg.
CARBON—2 watt and 5 watt.
Standard Car Suppressors 15,000 ohms.

CAPACITORS
Block Paper, Silvered Mica, Mica and Ceramic also 1 MF SUPPRESSORS with Flying Lead.

SWITCHES
OAK, YAXLEY, WAFERS and LOCATORS

VARNISHED COTTON SLEEVING
Various colours ½ m.m. — 20 m.m.

LAMINATIONS
RADIOMETAL 30, 31, 39 and 40
MU-METAL 35. Also other types.

VOLUME CONTROLS
MORGANITE "H" type, "M" type and all other makes

PLUGS AND SOCKETS
PYE PLUGS and SOCKETS
JONES PLUGS and SOCKETS, 4, 6, 8, and 10-way

TRIMMERS
Variable CERAMIC TRIMMERS. Capacities from 5 to 100 pf. Spindle and pre-set types.

Many other lines in stock. All enquiries dealt with individually, but regret no lists are issued.

TRADE COUNTER OPEN 9.30 TO 5.30 MONDAY TO FRIDAY
WHOLESALE, MANUFACTURERS AND EXPORT ENQUIRIES ONLY

RADIO TRADERS LTD
23 WARDOUR ST., LONDON, W.1
Phone: GERrard 3977 8 *Grams: "Radiotrade"*

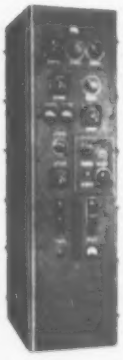

R.C.A. TRANSMITTER ET4336.
Unused and reconditioned. This magnificent transmitter is complete in one totally enclosed rack and includes aerial tuning panel.

TUBE LINE UP: 807 CO-Buffer. Two 813 P.A. Two 805 P.P. Class B modulator. Four 866A rectifiers. Controls: Manual or remote. Power output, 350 watts. Frequency coverage normal. Normal 2-20 Mc's continuous. Frequency control. The transmitter has a detachable front panel for insertion of Wilcox Gay V.F.O. or Crystal Multiplier. 20-page manual and circuit diagram with each equipment. Every instrument is air tested and guaranteed perfect. Also available Wilcox Gay V.F.O., Crystal Multiplier, speech amplifier (British made) with 500 ohm output suitable for use with ET4336. Valves available for ET4336 in large quantities, 813, 805, 866, 807.

ET4336 SPARES: We carry very large stocks of essential maintenance spares and invite enquiries.

RECEIVERS AR88D and L.F. Available with A.I.D. certificate, £75 each.

COMPLETE SETS CRYSTALS AND COILS for BC611 and BC211 handie talkies, SCR640, etc.

TELESCOPIC CAR AERIAL, 7ft. with 10ft. shielded lead coax connector. 15/- each.

EVERSHED AND VIGNOLL BRIDGE MEGGERS, 250 volt £21 each.

BC610 P.A. COILS, in complete sets. 7 Coils bulk quantities only supplied.

McELROY-ADAMS MFG. GROUP LTD.
Sole concessionaires U.K. for Hallicrafter Communication Equipment
46, GREYHOUND ROAD, LONDON, W.6
"Cables: Hallicraft, London" Phone: Fulham 1138 9

VALVES!! TUBES!!

RECEIVING. TRANSMITTING. MAGNETRONS. KLYSTRONS.

CATHODE-RAY TUBES. PHOTOCELLS. ETC.

First Grade Quality - British and American Make - No Dollar Expenditure involved

LARGE QUANTITIES & GREAT VARIETIES
IMMEDIATE DELIVERIES FROM STOCK

Write or 'Phone:-

S. Szymanski

(pronounced SHE-MAN-SKEE)

ELECTRONIC
ENGINEER & STOCKIST

95, STRODES CRESCENT, STAINES, MIDDLESEX

Telephone: STAINES 3971 *Telegrams: "Shemanskee" Staines*

PROBABLY THE LARGEST ACTUAL STOCKIST IN ENGLAND

WHOLESALE & EXPORT ONLY

RADIO SUPPLY CO.

15, WELLINGTON ST., LEEDS. 1. Post Terms C.W.O. or C.O.D. No C.O.D. under £1. Postage 1/3 charged on orders under £3. Open to callers 9 a.m. to 5.30 p.m. Saturdays until 1 p.m.

R.S.C. MAINS TRANSFORMERS

Fully Guaranteed, Interleaved, and Impregnated. Primaries 200-230-250v. 50 c.s. Screened.

TOP SHROUDED, DROP THROUGH

260-0-260 v. 70 ma., 6.3 v. 3 a., 5 v. 2 a. 13/9
260-0-260 v. 80 ma., 6.3 v. 2 a., 5 v. 2 a. 14/11
350-0-350 v. 80 ma., 6.3 v. 2 a., 5 v. 2 a. 16/11
260-0-260 v. 90 ma., 6.3 v. 3 a., 5 v. 2 a. 19/9
350-0-350 v. 90 ma., 6.3 v. 3 a., 5 v. 2 a. 19/9
250-0-250 v. 100 ma., 6.3 v. 4 a., 5 v. 3 a. 21/9
250-0-250 v. 100 ma., 6.3 v. 6 a., 4 v. 3 a., for R.1355 conversion 25/9
350-0-350 v. 100 ma., 6.3 v.-4 v.-4 a. C.T. 0-4-5 v. 3 a. 21/11
350-0-350 v. 120 ma., 6.3 v. 4 a., 5 v. 3 a. 25/9
350-0-350 v. 150 ma., 6.3 v. 4 a., 5 v. 3 a. 27/11

CLAMPED UPRIGHT MOUNTING

250-0-250 v. 100 ma., 6.3 v.-4 v.-4 a. C.T. 0-4-5 v. 3 a. 21/11
250-0-250 v. 100 ma., 6.3 v. 6 a., 5 v. 3 a., for R1355 conversion 21/11
300-0-300 v. 100 ma., 6.3 v.-4 v. 4 a., C.T. 0-4-5 v. 3 a. 21/11
350-0-350 v. 100 ma. 6.3 v. 3 a., 5 v. 3 a. 21/11
350-0-350 v. 150 ma. 6.3 v. 4 a., 5 v. 3 a. 27/9

FULLY SHROUDED, UPRIGHT

250-0-250 v. 60 ma., 6.3 v. 2 a., 5 v. 2 a. Midget type 2½-3-3in. 16/9
350-0-350 v. 70 ma., 6.3 v. 2 a., 5 v. 2 a. 18/9
350-0-350 v. 100 ma., 6.3 v.-4 v. 4 a., 0-4-5 v. 3 a. 24/9
350-0-350 v. 120 ma., 6.3 v. 4 a., 5 v. 3 a. 28/9
350-0-350 v. 150 ma., 6.3 v. 4 a., 5 v. 3 a. 31/-
350-0-350 v. 250 ma., 6.3 v. 6 a., 4 v. 8 a. 0-2-6 v. 2 a., 4 v. 3 a., for Electronic Eng. Televisor 65/-
425-0-425 v. 200 ma., 6.3 v.-4 v. 4 a. C.T. 6.3 v.-4 v. 4 a., C.T., 0-4-5 v. 3 a. suitable Williamson Amplifier 48/9
325-0-325 v. 20 ma., 6.3 v. 0-5 a., 4.3 v. 1.5 a. for Williamson Preamplifier 17/6

FILAMENT TRANSFORMERS

All with 200-250 v. 50 c/s., primaries: 6.3 v. 2 a., 7/6; 0-4-6.3 v. 2 a., 7/9; 12 v. 1 a., 7/11; 6.3 v. 3 a., 10/11; 6.3 v. 6 a., 16/9; 0-2-4-5-6.3 v. 4 a., 16/9; 12 v. 3 a., or 24 v. 1.5 a. 16/9

CHARGER TRANSFORMERS

All with 200-230-250 v. 50 c/s. Primaries:
0-9-15 v. 1.5 a., 12/9; 0-0-15 v. 3 a., 15/9;
0-9-15 v. 6 a., 21/9; 0-4-9-15-24 v. 3 a., 21/9;
0-9-15-30 v. 3 a. 22/9

SMOOTHING CHOKES

200 ma. 5 h. 100 ohms 7/6
100 ma. 10 h. 100 ohms 7/6
90 ma. 10 h. 100 ohms 5/9
80 ma. 10 h. 350 ohms 5/6
50 ma. 50 h. 1,500 ohms (Williamson Amp.) 8/9

AUTO TRANSFORMERS

100 watts 110-200-230-250 v. 19/9

ELIMINATOR TRANSFORMERS

Primaries 200-250 v. 50 c/cs. 120 v. 40 ma. 7/11
120-0-120 v. 30 ma., 4 v. 1 a. 12/9

OUTPUT TRANSFORMERS

Midget Battery, Pentode 66: 1 for 354, etc. 3/6
Small Pentode, 5,000 ohms to 3 ohms 3/9
Standard Pentode 8,000 ohms to 3 ohms 4/9
Multi ratio 40 ma., 30: 1, 45: 1, 60: 1, 90: 1 Class B Push-Pull 5/3
Push-pull 8 watts 6V6 to 3 ohms 8/9
Push-pull 10-12 watts 6V6 to 3 or 15 ohms 15/11
Push-pull 10-12 watt to match 6L6, PX4, 6V6, etc., to 3-5-8 or 15 ohms speaker 15/11
Push-pull 15-18 watts to match 6L6, etc., to 3 or 15 ohm Speaker 21/9

P.M. SPEAKERS. All 2-3 ohms: 5in. 11/9; 6in. 14/11; 8in. 14/11.

M.E. SPEAKERS: 8in. 3 ohms, field 600 ohms, 12/9.

SPECIAL OFFERS.

Fil. trans. (small), 220-240 v. input, 6.3 v. 1.5 a. output 5/9
Auto Trans. 0-200-230-320 v. 70 ma., with separate L.T. 6.3 v. 3 a. 7/6
Standard Output Trans. 5,000 ohms to 3 ohms 3/9
25 mfd. plus 25 mfd. 25 v. Electrolytics 1/9
2,000 mfd. 15 v. Can Electrolytics 7/6
Accumulators, dry charged, 2 v. 10 a. H. 4/9
.0005 mfd. 2-gang variables (ex. E.M.I.) 5/9

RECEIVER CHASSIS, 16 s.w.g., aluminium undrilled) 10-5¼-2in., 3/6; 11-6-2¼in., 3/11; 12-8-2¼in., 4/11; 16-8-2¼in., 6/9; 20-8-2¼in., 7/11.

AMPLIFIER CHASSIS, 16 s.w.g. aluminium, (undrilled) 12-8-2¼in., 7/11; 16-8-2¼in., 10/11; 20-8-2¼in., 13/6.

MISC. ITEMS. Ex-Govt. chokes 100 ma., 10 h., 100 ohms. Tropicalised, 3/11. Vol. Controls, 200 k., long spindle, 1/3 ea., 12/6 doz. Ex-Govt. R1124 Units, less valves, 10/9.

SELENIUM RECTIFIERS. Ex-new equipment. 120-0-120 v. 60 ma. 4/6; 230 v. 50 ma. H.W., 4/9; 250-500 v. 60 ma. H.W., 6/9; 680 v. 30 ma., 6/9; new 12-15 v. 1½ a. (Bridge F.W.), 7/11.

ELECTROLYTICS. Tubular 8 mfd. 350 v. 1/11, 8 mfd. 450 v. 2/3; Can 16 mfd. 450 v. 2/11; 8-16 mfd. 450 v., 4/6; 12-12 mfd., 350 v., 3/3; 16-16 mfd. 450 v., 5/3; 32mfd. 350 v., 4/3; 32 mfd. 450 v. 5/3; 32-32 mfd. 350 v., 6/6; 32-32 mfd. 450 v., 7/6.

FULL RANGE OF STANDARD COMPONENTS AVAILABLE AT KEEN PRICES. ALL GOODS GUARANTEED AND NEW, UNLESS OTHERWISE STATED. QUANTITY QUOTATIONS GIVEN FOR STANDARD TYPES OR SPECIAL MAINS TRANS. S.A.E. PLEASE WITH ALL ENQUIRIES. FULL STOCK LIST 4d. SPECIAL LIST FOR TRADE, 4d.

C. MARKS & CO.

SPECIAL THIS MONTH

WIREWOUND RESISTORS BY FAMOUS MANUFACTURER, CEMENT COVERED

6 x 8Ω ± 10% - 4 watt 3 KΩ ± 5% - 4 watt 1200Ω ± 5% - 5 watt
6 KΩ ± 5% - 4 watt 5 KΩ ± 5% - 5 watt 1000Ω ± 5% - 4 watt
3 KΩ ± 10% - 9 watt 5 KΩ ± 5% - 6 watt 750Ω ± 10% - 15 watt (Green vitreous)

1000Ω ± 10% - 2 watt (open wire type) 2000Ω ± 5% 4 watt 9.7Ω ± 10% - 3 watt - 10 KΩ ± 10% - 8 watt.

All at 1/- each. Specify price for quantities. These resistors are brand new and not Government surplus, but surplus to manufacturers requirements. Also 360Ω ± 10% 3 watt at 9 - doz.

KABOMOT LOADED EBONITE in the following sizes: —
1¾in. × 36in. × ¼in. thick at 15 - plus 3/6 carr. 1¾in. × 36in. × ⅛in. thick at 20 - plus 3/6 carr. 1¾in. × 36in. × ⅛in. thick at 25 - plus 3/6 carr. 1¾in. × 36in. × ⅛in. thick at 35 - plus 3/- carr. 1¾in. × 36in. × ¼in. thick at 40 - plus 3/- carr. Also Resin in the following sizes: ¼in. dia. × 20in. long (useful for extension spindles etc.) 4/6 doz. plus 1/- carr. ¼in. dia. × 20in. long 7/6 doz. plus 1/- carr. ⅜in. dia. × 40in. long 30 - doz. plus 1/6 carr. ⅜in. dia. × 40in. long 10 - each plus 4/- carr. ½in. dia. × 20in. long 6/6 each plus 3/- carr.

RECEIVER R3 ARK 2X. Command Type VHF Receiver covering 234 to 258 mc/s. 1st IF. on 6 spot freq. between 850 and 870 K/c.s. IF freq. 200 k/c.s. Includes BPO Thatcher 5-BAK3. 7-9001 and one 12A6 valves. Input 12 volt. Price £4 10 - plus 3/- carr.

931A PHOTO-ELECTRIC MULTIPLIER. R.C.A. in heavy circular case with built-in network. Suitable low intensity light working. Spectrum experiments etc. Complete with base, network and base 25 - each. Plus 1/6 post.

CONDENSERS BY FAMOUS MANUFACTURER. .25 mfd. 25 volt (micropack) at 1/6 each, 15 - doz. Starter capacitors 50 mfd. and 55 mfd. at 5 - each, plus 9d. carr. These condensers are brand new and not Government surplus.

KEY SWITCHES. 4 pole change over at 2/3 each. 2 pole change over at 1/9 each

FOX'S WIREWOUND POTENTIOMETERS. Toroidal wound. 3000Ω and 5000Ω at 3/6 each, plus 9d. post.

MIDGET PLUGS AND SOCKETS. Camera 2 pin type. Completely enclosed. 9d. per pair, plus 4d. post.

PYE COAXIAL PLUGS AND SOCKETS at 6 - doz. pairs.

AIR SPACED VARIABLE CONDENSERS. Trimmer type, silver plated. Screw-driver adjustment. 25, 50 and 100 mmfd. at 9 - per doz.

TRIMMERS. Postage stamp type. 50 mmf. at 3/6 per doz.

TELECOTHENE CABLE. 80 ohm Twin Suitable for T.V. etc. 3/6 per doz. yds.

COAXIAL CABLE. Semi Air Spaced at 1/3 per yd.

HIGH RESISTANCE HEADPHONES at 7/6 per pair.

INTERNATIONAL OCTAL VALVEHOLDERS (PAXOLIN) at 4/6 doz.

88 COMMERCIAL ST., NEWPORT, MON. Tele. 4711
also at **25 Wyndham Arcade, Cardiff**
All mail orders and enquiries to Newport branch please

RADIO EXCHANGE CO.

HIGH RESISTANCE HEADPHONES. Ericsson's first grade, 4,000 ohms per pair, brand new, in attractively coloured presentation boxes. ONLY 17/6

RECEIVER P40. Complete with valves, tuning 85-95 mc/s. these are ideal for Wrotham or "2" metre conversion. Housed in attractive robust grey cases these contain 4 EF54's (RF, mixer Xtal multipliers), EC32 (Xtal oscillator), 2 EF39's (2.9 mc/s IF's), EB34 (det), 6J5 and 6V6 (audio). In original cartons, complete with circuit. 69/6. (post 1/8). Circuit only 1/3.

RECEIVER 1225. Ideal for 2 metres, these are complete with 5 EF50's, 2 EF39's and EB34; the crystal controlled oscillator and RF's may be set to 4 pre-tuned frequencies. ONLY 39/6 (post 1/6)

TRANSMITTER 21. Sending CW, MCW or speech on 4.2—7.5 and 18—31 mc/s these are complete with valves, circuit, control box, key and front panel. Wire (not formers) from PA coils, and relays, have been stripped by the M.O.S. but may easily be replaced with the aid of our circuit and data. In excellent condition, 25/-.

POWER UNIT S441B. With separate individually controlled HT and LT transformers, jewelled indicator lights, attractive appearance and modest size (14 in. x 7¼in. x 7in.) these deliver 300 v. at 200 mA., fully smoothed, 12 v. at 3A. AC and 5 v. DC, from 200/250 v. 50 cps. In ORIGINAL CARTONS. Only 65/- (carr. 5/-).

VIBRATOR UNIT 21. 6 v. input, approx. 160 v. at 40 mA smoothed DC output; designed for the Tx/Rx/21. In new condition. ONLY 17/6.

BRAND NEW ACCUMULATORS in transparent, unspillable plastic cases. 7 A.H. 2 v., 6/6.

POWER UNIT S532. With 5Z4 rectifier, SU2150 (5 KV). EHT rectifier, choke, relay, condensers, transformers, etc., our conversion will produce a fine little HT or EHT unit for mains input, providing approx. 1,800 v. EHT or approx. 450 v. at 50 mA (unsmoothed). ONLY 17/6 (carr. 2/3).

NEW 1355 CONVERSION data for all 5 TV channels, 3/-.

MIDGET AMPLIFIERS with two 12SH7's, one 12SJ7, these measure 5in. x 3¼in. x 3in. OUR PRICE 15/-

H.T. BATTERIES. 60 v., 4/9; 2 for 8/11, plus 1/8 postage etc.

9 CAULDWELL STREET, BEDFORD
Phone: 5568.

G2AK *This Month's Bargains* G2AK

HEAVY DUTY ADJUSTABLE RHEOSTATS. 4 ohms, 25 amps. Beautifully made, 5/- each. Post and packing 1/6.

C.R. TUBES. Type 5CP1 brand new in cartons, 17/6 each, plus 1/6 postage.

T.V. TUBE MASKS. 12in. New Ratio, brand new, 15/- each, post free.

MOVING COIL HEADPHONES with moving coil microphone. Price 6/-. Post 1/-. Transformer to match 2/-. Balanced Armature L.R. Phones, 9/6 per pair.

TWIN RIBBON FEEDER. Heavy duty 300 ohm, 5d. per yd. Standard K.25 300 ohm ribbon, 9d. per yd. Co-ax. cable, ¼in. dia. 70 ohm., 8d. per yd.; ¼in. dia., 1/3 per yd. 7ft. length ¼in. dia. Co-ax. with Pye plug one end, 1/6, post free. All other Co-ax., and feeder, plus 1/6 post any length.

POTENTIOMETERS. 5 watt wire-wound 20 k., 25 k., 2/-. Carbon Type Potentiometers, 50 k., 100 k., 1 meg., 2 meg. 1/6.

TRANSMITTING TUBES. Type 807, 10/- ea. Type 813 New and Boxed £3 10 each. Type 866A, 17/6 each. Few only.

METERS. 2½in. Flush mounting M.C. 100 m.a., 500 m.a., and 20 m.a., 12/6 each. 2in. Flush M.C. 500 microamp., 10/-, 5 m.a., 7/6 0.5 amp. thermo., 5/-. Special offer 2½in. flush 0—1 m.a. Rectifier Meter, scaled 0—10 volts, 22/6 each. Few only.

CERAMIC 2-bank, 4-pole, 4-way Switches, 3/9 each. Post free.

CERAMIC COIL FORMERS. 5in. long by 2½in. diameter; threaded 24 grooves, 4/6 each, post free.

JONES PLUGS. 8-pin, male and female, 1/6 per pair, 12/- per dozen pairs.

Carriage paid on all orders over £1 except where stated. Please include small amount for orders under £1.

Please print your name and address.

CHAS. H. YOUNG, G2AK

All Callers to **110 DALE END, BIRMINGHAM**
'Phone: CENTRAL 1635.
Mail Orders to **102 HOLLOWAY HEAD, BIRMINGHAM**
'Phone: MIDLAND 3254.

'SCOPE UNIT in steel case 6in. x 6in. x 15in. Containing VCR138 ECR35. 3½in. C.R.T. with mu metal screen. 2-EF50's, 2-EB34's. Pots and the usual resistors and condensers. Can be modified as a standard scope in a few hours and only requires external power pack (cost £3) Price 70/-.

6-VOLT VIBRATOR UNITS. Complete in black steel case 7½in. x 5¾in. x 3¾in. Output 200 volts, 40 mA., Price 22/6.

2-VOLT BATTERY RECEIVERS—190-200 Mc/s. Complete with 2 valves. Unused, 14/-.

ARMY PRACTICE MORSE KEY AND BUZZER SETS. New and boxed. 6/6.

RF24 UNITS. Converted to 28 Mc/s Band. Variable tuned with 100-1 geared S.M. Dial. Complete with plug and leads for immediate use. £3.

MAINS TRANSFORMER. Input 200/240 v. Output 350-0-350 or 250-0-250 volt, 80 mA. 4 and 6.3 v. 4 a. and 4 and 5 v. 2 a. Price 22/6. Input 200/240 v. Output tapped 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 20, 24, 30 volts, 2 amps., 21/3. All with one years guarantee.

NEW MINIATURE VALVES. DL72, CK512AX 9/-; 6AG5 10/6; 9001, 9002 7/6; 9003 6/6.

D.P.D.T. RELAYS. Operate at 200/300 volts, D.C. 6 mA. 13/-.

EXIDE P.O.2 UNSPILLABLE ACCUMULATORS 11 a.h., 4¼in. x 3¼in. x 2¼in. 19/6.

TYPE 18 Tx. CHASSIS, partly dismantled but can be put into working order easily, less valves, 16/6.

All the above Post Paid from: Dept. W.W.,

The RADIO & ELECTRICAL MART

253B PORTOBELLO ROAD, LONDON, W.11
Phone: PARK 6026

OUR 17TH YEAR MONEY-SAVING OFFERS

G.E.C. Ex-GOVT. TRANSMITTER RECEIVER. M.R. Series. 10 valves: 1 Det. 19, 1 L63, 1 H63, 1 D63, 3 KTW63, 1 KT63, 2 RCA 954 (value of valves exceeds £10 at current prices), 2 westectors, etc. Grey enamel case size 10 x 8 x 7in., weight 22 lbs. All valves guaranteed. Operating frequency around 90 mcs. We regret we have no precise technical data on this instrument. Apparently designed for mobile work with crystal control (no crystals included). An outstanding bargain at **£3.19.6**, plus 5/- packing and carriage. Condition as new.

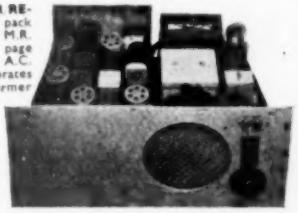

G.E.C. TRANSMITTER RECEIVER, with power pack. Same specification as M.R. series illustrated on this page with the addition of A.C. power pack. This incorporates heavy-duty mains transformer and choke, 5u4G rectifier valve, smoothing condensers, circuit breaker, 6in. P.M. speaker, H.T. switch, mains switch, jewel light, output attenuator. Front panel size 19 x 8in., grey enamel finish. Front to back width, 12½in., weight, 60 lbs. First-class condition. Bargain price **6 gns.**, plus part packing and carriage 12/6.

TELEVISION PRE-AMPLIFIER. Just the thing you have been looking for. This ex-Govt. 1-valve pre-amplifier is extremely sensitive and stable. It makes an amazing improvement in both vision and sound reception in all fringe areas. Available for London (type A), Birmingham (type B), Holme Moss (type H).
Very small dimensions. Length, 4in. Width, 3½in. Chassis depth 1¾in. Overall depth from top of valve, 4¼in. Fitted with EF50 valve. Ready for use. Power requirements 6.3 v. L.T. 200/275 v. H.T. Coax. Input and Output sockets. Unique value at the price of **15/-** (post paid).

EDDYSTONE 358J COMMUNICATIONS RECEIVER (4 only). Grey cabinet with chrome handles. Size L19, W13, D11, 7 valves. EF39 (4), ECH35, EL32, EBC33. Valve check meter switched to all valves. Controls, H.F. gain, H.T. on-off, 120 ohm and 2,000 ohm phone jacks, B.F.O. switch A.V.C. switch, L.F. Gain, B.F.O. Control, Tone, main tuning with micrometer indicator. Each set is complete with Eddystone 230 v. A.C. Power Unit incorporating 5Z4 rectifier with heavy duty smoothing chokes. Separate power switch. Grey case size 11½ x 6½ x 3½in. loudspeaker in grey enamel cabinet 8in. unit with high and low impedance connections. Nine Eddystone coils giving continuous coverage from 90kcs. to 31 mcs. Everything for a complete station. These ex-Govt. receivers have been used, but are in ex. cond. Really outstanding value at **£25** each carr. paid per pass. train.

R1224A 5-VALVE BATTERY RECEIVERS. A few only. These very scarce 3 waveband battery superhets, tune 30-300 metres. Valves: 2 VP23's, FC2A, HL2, PM2A included. IF 470 kcs. Has R.F. stage, Muirhead dials, 2 output jacks, Air Force grey cabinet. Requires 120 v. H.T. and 2 v. L.T. Outstanding performance. Price **£7/10/-** carr. paid.

CRYSTAL MULTIPLIERS for the ET4336 Transmitter. New condition. Less valves and M.A. meter. **30/-** each, carr. 3/6.

CAY TUNING UNITS 4715A. 800-1,500 kcs. Brand new in metal case with lid, 3 slow-motion dials, 4 switches. Many fine components, **15/-**, or without case, **10/-**, carriage 2/6.

SECTIONAL AERIAL MASTS. Approx. 30ft. Seasoned timber. 10 metal sleeved sections. Store soiled but absolutely sound, **30/-** each, carr. 5/-. Last few.

C.3 VOLTAGE CONTROL UNIT. Ref. No. 5U/1269. Contains on/off switch, pilot light, 6 bank fuse panel, 5 plus 3 mfd. Heavy duty fully filtered mains suppressor. Handsome case. Size 11 x 8 x 7½in., **10/-** each, carr. 2/6.

CONTROL UNIT 454A. Brand new in sealed packing. Size 8½ x 6½ x 3½. Fitted with 0-1 mA. meter, four 50k pots., 1 5k pot., 1 250k pot., 1 D.P. toggle switch, 3 jewel light jacks, 1 G.P.O. type 2-pole switch, 1 Yaxley 5-pole switch. Suitable as basis for a good test meter. Price **30/-**, carr. paid

PAMPHONIC P.A. SPEAKERS. 10in. high flux unit (not surplus). Handsome maroon cellulose metal cabinet 20 x 9 x 13in., impedance 3 ohms. New and unexpected delivery enables us to repeat this popular item. Price **55/-**, carr. 4/-.

Enquiries must be accompanied by 2½d. stamp.

SATISFACTION GUARANTEED AS ALWAYS
ITEMS OVER 16 lbs. IN WEIGHT CANNOT BE SENT C.O.D.

H.P. RADIO SERVICES LTD.
BRITAIN'S LEADING RADIO MAIL ORDER HOUSE
55 COUNTY RD., LIVERPOOL 4. Est. 1935. Tel. Aintree 1445

For Quality Bargains Always

-Best Buy at Britain's

EX-W.D. MAINS TRANSFORMERS.

PLATE TRANSFORMER. Potted. Primary tapped every 10 volts from 100 to 250 volts. Secondary 2000-0-2000 volts R.M.S. Rating 1 Kv.A. Ref. ZA11123. Weight 82 lbs. Brand new—**£10.10/-**, carriage paid. The size is 10in. x 10in. x 9½in.

MULTI-PURPOSE TRANSFORMER. Upright mounting, primary 230 volts, 50 cycles. Secondaries—(1) 500-0-500 volts 400 mA., (2) 300 v. 100 mA., (3) 4 v. 7 A., (4) 10 volts centre tapped 11 A., (5) 12 v. 1 A. centre tapped, (6) 6.3 v. 3 A. centre tapped. Size 6½in. x 6½in. x 7½in. Brand new **59/6**, plus 5/- carriage.

FILAMENT TRANSFORMER. Primary 230 volts 50 cycles. Secondary —4.2 v. 2.5 A., 4 v. 1 A. at 8 Kv. test. 6.3 volts at 7.7 A. Size 4½in. x 4½in. x 4in. Brand new. Price **17/6**, plus 1/6 post.

H.T. TRANSFORMER. Primary 230 volts 50 cycles. Secondary— 330-0-330 volts 150 mA., 4 v. 3 A. Size 4½in. x 4in. x 4in. Brand new at **22/6**, post 1/6 extra.

STANDARD TRANSFORMERS of current manufacture. Three types, all standard primaries. Universal mounting. (1) 350-0-350 volts 80 mA., 0-4-5 v. 2 A., 0-4-6.3 v. 4 A., (2) 250-0-250 volts 80 mA., 0-4-5 v. 2 A., 0-4-6.3 v. 4 A., (3) 30 v. 2 A. tapped at 3 v., 5 v., 6 v., 8 v. 9 v., 10 v., 12 v., 15 v., 18 v., 20 v., 24 v. All these transformers are brand new and boxed, fully guaranteed and priced at **18/6**, plus 9d. post.

EX-W.D. HEAVY DUTY CHOKES. 15 Henry at 275 mA. Upright mounting. Size 5in. x 4½in. x 6in. Brand new at **22/6**, plus 2/6 post. 30 Henry at 100 mA. Upright mounting. Size 3in. x 2½in. x 3in. Brand new at **12/6**, plus 1/- post.

METAL RECTIFIERS. 12 v. 2 A. full wave bridge, **12/6**, p.us 6d. post. Miniature H.T. rectifiers, type RM2—125 v. 100 mA., at **4/3** each, or 2 for **8/-**. RM3—125 v. 120 mA., at **5/-** each or two for **9/6**, plus 6d. postage on one or two. Selenium rectifiers 150 v. 40 mA. at three for **10/-**, post paid. 230 v. 60 mA. at two for **9/-**, post paid. 12 v. 5 A. full wave bridge rectifier at **17/6**, plus 6d. post.

HEAVY DUTY RECTIFIERS—Funnel cooled, full wave, 30volt 20 amp. Selenium. Each rectifier consists of 20 discs size 112 mm. Brand new and boxed at £4.10/-, plus 3/6 carriage.

SMALL 24 V. MOTOR AND GEAR BOX. A.C./D.C. operation. Will also work on 12 volts. About 140 to 1 double reduction worm drive, giving very high torque at slow speeds. Price **19/6**, plus 1/6 post.

SPECIAL PURPOSE VALVES. VT501(TT11), **5/-**, 954, **2/6**, VR136 (EF54), **6/6**, E1148, **2/6**, VR65a(SP41), **3/-**. Hundreds of other types in stock. Post 6d. extra for 1 to 4 valves.

EF50(VR91) Red American Sylvania types at **8/6** each. Brand new. British makes also available at **5/-** each, tested.

COMMUNICATION RECEIVER R1155. A few still available, absolutely brand new at £13.19.6, plus 10/6 carriage and packing in original transit case. Any set gladly demonstrated to callers. Full details of this fine set are given in the "Wireless World" reprint, which is supplied free with each set or will be sent for 1/3 post free.

R1155 POWER PACK AND OUTPUT STAGE. Enables this receiver to be operated direct from A.C. mains. Just plug in and connect low impedance speaker. (Note—speaker not supplied). Price **£4.10/-**, carriage paid. This unit is manufactured by ourselves from new components and valves, and assembled in a neat black A.M. case, size 8½in. x 6½in. x 4in. All the necessary leads and plugs are supplied and included in the price.

ERSKINE OSCILLOSCOPE TYPE 1A. We have just a few of these 'scopes left, as previously advertised. Price £10.10/-, plus 5/- carriage. Full illustrated details will be supplied on receipt of S.A.E.

ELECTROLYTIC CONDENSERS. 16 mF. 350 volt working, metal can type—type CE26L. Brand new at 4 for **10/6**, post paid. 12-12 mF. 350 volt working, type CE34LF, small tubular alily. can at 3 for **10/6**, post paid. 30 mF. 450 volt working plus 20 mF 25 volt working. Drilltic all., can, 2 for **11/6**, post paid. All well known make and brand new. Minimum quantities as stated.

We have a large range of units and components, some of which are in insufficiently large quantities to advertise. We suggest you pay us a visit to secure some real bargains. Many items are of interest to Schools, Laboratories, Manufacturers and others connected with the Electronic Industry.

CHARLES BRITAIN (Radio) Ltd.
11 UPPER SAINT MARTIN'S LANE
LONDON, W.C.2 *TEM 0545*

3 minutes from Leicester Square Station (up Cranbourn Street)
Shop Hours: 9—6 p.m. (9—1 p.m. Thursday). Open all day Saturday.

OUTSTANDING OFFERS FOR EXPORT ONLY

U.S.A. Radio & Radar Equipment
RCA TRANSMITTERS, Type ET-4336-B, H. K. L.
Westinghouse AIRCRAFT TRANSMITTERS, Model GO-9
TRANSMITTERS/RECEIVERS SCR-536.
TEST EQUIPMENT IE-46 (Signal Generators 1-196-B,
Frequency Meters BC-906-D, Radio Receivers
BC-1066-B).
AN/TRC EQUIPMENT.
Hallicrafters SCR-299, 399 and 499 (BC-610).
RADAR Mk.26 (Models 3 and 4).
INTERROGATORS-RESPONSORS BM-1 (and BN-1).
REPEATER-INDICATORS AN/APA-1.
RADAR INDICATING EQUIPMENT, Model VF.
AIRCRAFT RADAR EQUIPMENT APS-3, 4 and 6.
TEST UNITS AN/UPM.
GISHOLT-BALANCING METERING UNITS
AN/APN RADIO ALTIMETER EQUIPMENT

Spares (Radio & Radar—U.S.A.)
Full range of spares for AN/APN-3.
Spares for most models of U.S.A. Naval and Aircraft
RADAR UNITS.
Spares for most AMERICAN TRANSMITTERS.
Brand new Klystrons (RAYTHEON) 2 K-33.
CRYSTALS (for SCR-610, etc.)

Complete Operations Center AN/TTQ-1
(Full installation for Wing Filter or Operations Room, or Combined Filter-Fighter Control Area Operations Room.)

Power Units, Wavemeters, Motor Generators, Dynamotors and large quantities of various components.

Aircraft Instruments and Accessories
Large selection of Bendix Instruments.
Aircraft Generators and Motor Assemblies.

Individual Test Certificates and A.I.D. Certificates can be supplied upon request.

Enquiries to

BRITISH SAROZAL LTD.
(Export Branch)
1 BRISTOL HOUSE, SOUTHAMPTON ROW, LONDON, W.C.1
Telephone: HOLborn 6761/4/5 *Cables: Sarozal, London*

OVERSEAS BUYERS ARE CORDIALLY INVITED TO VISIT OUR WAREHOUSES, SHOWROOMS AND LABORATORY

1 KW TELEGRAPH TRANSMITTERS. Two MF 300's output. Operation 3.5 mc to 16 mc.

RCA TRANSMITTERS. Type ET-4336. Complete with matched speech amplifier, crystal multiplier and VFO units. Brand new.

LM-300 TRANSMITTERS (U.S.A.). 140 kc to 400 kc and 650 kc to 1 600 kc 300 watt output.

No. 12 TRANSMITTERS. With coupling units, remote control, etc.

AR.-77's, AR.-88's, NC200, NC45, HRO and others.

AUTOMATIC HIGH SPEED TELEGRAPH EQUIPMENT, "BOEHME" (U.S.A.). Up to 400 signs per minute on line and wireless.

NAVY MODEL TBY-8 TRANSMITTING-RECEIVING EQUIPMENT. Output 0.75 watts on M.C.W. telegraphy and 0.5 watts on telephony. Frequency range 28-80 mc.

All above items in excellent working condition.

Working demonstration upon request.

TX VALVES 803, 805, 807, 814, 861, 866A, DET-16 and many others.

Large stock of Tx condensers, crystals and other components. Alignment and repair of communication receivers and all other short-wave equipment undertaken.

P.C.A. RADIO

Transmitter Division :—
The Arches, Cambridge Grove, London, W.6. *Tel. RIV 3279*

Receiver Division :—
170 Goldhawk Road, London, W.12. *Tel. SHE 4946*

EXPORT AND WHOLESALE ONLY

VALVES RECEIVING VALVES TRANSMITTING
TUBES CATHODE RAY

- **Govt. Surplus & Regular Types**
- **Special purpose tubes**
- **No Dollar Expenditure**
- **Rapid Delivery from Ample Stocks**
- **One of the Largest in England**

Also large stocks of

- **P.M. Speakers 2½"—12"**
- **Mains Transformers**
- **Resistors :- ¼, ½ and 1 Watt**
- **Condensers :- Mica, Electrolytic, Oil, etc.**

SEND US YOUR REQUIREMENTS

V.E.S. WHOLESALE SERVICES LTD.,
11, GUNNERSBURY LANE, W. ACTON, W.3.
Telephone: ACOrn 5027 (3 lines).

A MINIATURE MAGNETIC LIGHTWEIGHT EARPHONE

The new Amplivox e.4 earphone has been primarily developed for use with office dictating machines, industrial equipments and hearing aids where a highly sensitive, lightweight, miniature receiver is needed.
Available in D.C. resistances 2-2000 ohms; frequency 100-4000 c.p.s.; diameter .835", depth .420"; weight ¼ oz.

AMPLIVOX LTD.
2 Bentinck Street, London, W.1

"ADCOLA" SOLDERING INSTRUMENTS
Reg. Trade Mark.

Reg. Design No. 881327

Designed for Wireless Assembly and Maintenance.
SUPPLIED FOR ALL VOLT RANGES FROM 6/7v. to 230/50v.
The three Adcola Models cover the requirements of the **Television, Telecommunication and Radar Engineers** and assure thorough jointing.
⅛in. dia. Bit Standard Model — 22/6
¼in. dia. Bit Standard Model — 25/-
⅛in. dia. Detachable Bit — — 30/-
Patented in England and Abroad.
Sole Manufacturers

ADCOLA PRODUCTS LIMITED
General Offices & Works: CRANMER COURT, CLAPHAM, HIGH STREET, LONDON, S.W.4. *Tel: MACaulay 4272.*

Wireless World Classified Advertisements

Rate 7 - for 2 lines or less and 3/6 for every additional line or part thereof, average lines 6 words. Box Numbers 2 words plus 1 -. (Address replies: Box 0000 c o " Wireless World " Dorset House, Stamford St., London, S.E.1.) Trade discount details available on application. Press Day March 1952 issue, Thursday, January 31st. No responsibility accepted for errors.

WARNING

Readers are warned that Government surplus components which may be offered for sale through our columns carry no manufacturers' guarantee. Many of these components will have been designed for special purposes making them unsuitable for civilian use, or may have deteriorated as a result of the conditions under which they have been stored. We cannot undertake to deal with any complaints regarding any such components purchased.

NEW RECEIVERS AND AMPLIFIERS

UNIVERSAL ELECTRONIC PRODUCTS, 36, Marylebone High St., London, W.1. Welbeck 4058. SPECIALISTS in the design and manufacture of high fidelity reproducing equipment from 5-100 watts for domestic or industrial purposes. Our new twin channel amplifier (type U.E.57), with independent bass and treble outputs, provides the most satisfying standard of reproduction we have yet experienced. It is now being demonstrated in our showrooms daily (we close Thursday 1 p.m., Saturday 4.30 p.m.), and we invite those who seek perfection from recorded music to hear this superb instrument. We also offer tuning units or complete chassis designed and constructed to individual requirements. [0064

12-watt high quality amplifiers, bass and treble boost; £12.15; lists.—Broadcast & Acoustic Equipment Co., Ltd., Tombland Norwich. [0065

MIDLAND RADIO COIL PRODUCTS offer a full service for the production of high quality amplifiers and radio equipment to specification; list of standard products is available; suppliers of audio and radio equipment to the Northamptonshire Education Authority.—Enquiries to 28, Winstanley Rd., Wellingborough. [6536

C.J.R. ELECTRICAL & ELECTRONIC DEVELOPMENT, Ltd., Bickford Rd., Witton, Birmingham, 6 (Eas. 0455), the Midlands specialist manufacturers of high fidelity sound reproduction equipment for the world-famous Williamson amplifier and associated accessories including tone control stages, loudspeaker crossover units, distortionless contrast expanders and radio feeders; send for details and prices. [0105

TELRAD ELECTRONICS, 70, Church Rd., Upper Norwood, London, S.E.19.—Designers and manufacturers of Telrad quality amplifiers; established as the most outstanding value in high-quality amplifiers, thanks to faithful reproduction at unrivalled price; these unique amplifiers are the first choice of the enthusiast; built to satisfy the discriminating ear; bass and treble independent controls, providing widest possible variation to suit all recordings and varying acoustic properties of one room with another; full details on request.—Write, call or 'phone Livingstone 4879.

RECEIVERS, AMPLIFIERS SURPLUS AND SECONDHAND

HALLICRAFTER Sky Champion S20R; £15.—Maida Vale 8401. [7979

R107, with handbook; £11.—Phillips, 89, London Rd., Hemel Hempstead, Herts. [7981

7-valve amplifier with tone control, Goodman's 20-watt axiom; £18.—Box 6133. [8021

R1155, with power unit and output stage, less aerial switching circuits, carriage paid; £6.—Box 6095. [7980

SOUND sales DX+1 feeder unit and TCI tone-control unit, both as new; offers.—Burgess, 166, North Way, Maghull, Liverpool. [8026

15 inch Baird T.9 television combined all-wave radio (just overhauled), beautiful cabinet, burr walnut; £50 (London).—Box 6105. [8004

HRO Rx's and coils in stock, also AR88, BC348R, CR100, etc.—Requirements please to R.T. & I. Service, 254, Grove Green Rd., London, E.11. Ley. 4986. [0055

A.C. 15watt amplifiers, £10; 12v amplifiers, 10watt £8, 25watt, £12; 50watt, £16; all less cabinets, like new.—Radiovox Sound System, 5, Oxford Place, Leeds, 1. [7897

HIGH-quality amplifier, push-pull PX4s, separate power pack, Connoisseur pick-up and Collaro motor in table cabinet, Mullard 12in C.R.T., good condition, offers.—Box 6099. [7991

Partridge News

FAMOUS "EXPORT ONLY"

CFB TRANSFORMER

now available

"AT HOME"!

From its inception a year ago the C.F.B. was acclaimed (by those fortunate enough to obtain them) the finest audio transformer yet produced. Hitherto this model has been for "export only"—and it literally swept the American continent. Now, an allocation is permitted for home users.

Those familiar with the performance of our WWFB series must raise a speculative eyebrow when we say that the CFB series is as far ahead of the WWFB as the latter was of ordinary output transformers. For instance, at 16 watts, 50 c.p.s., the WWFB has 0.5 per cent core harmonic distortion. The CFB has 0.05 per cent! The CFB shows as little as 10 m.h. series leakage inductance and has therefore more than twice the ratio of Primary Shunt L. to leakage series L. of the WWFB. This plus the ability to handle up to 60 watts with less than 1 per cent distortion and a 15 octave bandwidth, even without feedback, a low 88 ohm half-primary resistance but with a primary shunt inductance in excess of 120 Henries, extremely low phase angle at even the highest frequencies and many other features combine to make this the most outstanding output transformer available regardless of price. Its outstanding performance lies in the use of a grain oriented, strip wound C.I. core. The extraordinary characteristics made possible by this type of construction permit of a very considerable amount of feedback across several stages of triodes and it therefore becomes the very finest of output transformers for the Williamson circuit where only perfection of performance, and not price, is the consideration.

PARTRIDGE

TRANSFORMERS LTD

ROEBUCK ROAD, KINGSTON BY-PASS

TOLWORTH SURREY

Telephone ELMbridge 6737-8

NEW LOUDSPEAKERS

BARKER model 150 £18.18; Goodmans Axiom 150 £10.5.6; Wharfedale W10/CS £8.10; Golden CSB £5.7.6; Super 5 £4.12.6; E.M.I. 15-in elliptical £4.17.6; WB Concentric Duplex £6.15; illustrated loudspeaker cabinet leaflet available on request; all speakers despatched post free.
ROGERS DEVELOPMENTS Co. (M.O. Dept.), 116, Blackheath Rd., S.E.10. [7959

LOUDSPEAKERS SURPLUS AND SECONDHAND

WHARFEDALE W/S/CS, W/O/CSB and Crossover unit; offers.—Box 6132. [8019

PA 50in re-entrant metal horn speakers, 10watt; 6.5ohms, 90/-; P/A 50in straight metal horns, 55/-, like new.—Radiovox Sound System, 5, Oxford Place, Leeds, 1. [7898

BATTERIES

LEAD acid batteries, new, 2v, 14 amp hr, 20 amp hr and 90 amp hr.—H. B. Barnard & Sons, Ltd., Dudley Port, Tipton, Staffs. [7942

NEW DYNAMOS, MOTORS, ETC.

BATTERY chargers, 2-6-12volts, lamp, a.c. mains operated, ammeter fitted, guaranteed; 52/6 (despatch 2/6).—Thames Valley Products (W), 28, Camden Ave., Feltham. [7654

BATTERY chargers, 4 models, 2-6-12v, 1-2-4 amp D.C., any mains voltage; also larger types special transformers, chokes, test gear, interior car heaters, etc.—The Banner Electric Co., Ltd., Hoddesdon, Herts. [0122

ALL types of rotating electrical machinery up to 20kva available, including rotary converters, rotary transformers, motors, petrol and diesel-engined generating plants, alternators and d.c. generators. We are also in a position to quote for power transformers, as actual manufacturers we will be glad to quote for any quantity for home or export.
DIESEL Electric generating plants, 3kva, 230v with push-button remote control, starting equipment, ready for use; £275.
ROTARY transformers, input 20v d.c., outputs 6.5v d.c. and 500v d.c., permanent magnet field; 20/-, ditto, input 28v d.c. and 1,200v 70ma d.c. output; energised field, 35/-; ditto, input 12v d.c., output 500v, 90ma d.c., energised fields 35/-; reasonable delivery.
CHAS. F. WARD, Lordscroft Works, Haverhill, Suffolk. Tel. 255. [0039

DYNAMOS, MOTORS, ETC.—SURPLUS AND SECONDHAND

ROTAX rotary convertor, input 50 volts d.c., output 230 volts 50 cycles 100 watts, radio shielded and in perfect condition, new 1948; Box 6129. [8015

THE Pearce new model diesel alternator plant, on welded steel frame, 250/1/50 5kva, plus 52v 15a d.c., Petters latest AVA1, air-cooled diesel engine, belt-driven alternator, self-energised, automatic voltage control by winding on stator, at govern. speed 1,500rpm, d.c. output trickle charges or charges lighting and starter battery up to 15 amps, 24v lighting is used when plant is not in use, start and stop by remote control push-buttons, complete with main switch & fuses, battery cables, 24v 72 amp/h. batt, instruction book, spares, engine covered by Petters' unsupported 2 year guarantee; delivery 100 mls. London, where remote start and stop not required, but only push start on plant reduction of £6/10; a few from stock others quick delivery, if you collect, or we deliver battery is charged and a 10 cu. ft. concrete bed given free.
ALTERNATORS, type as fitted in above plant, 110/1/60, or 250/1/50, 5kva, wt. 240lb, £72 del.; also 110/1/60 or 250/1/50 6kva, wt. 400lb, £95 del.; 5kva, £77, 6kva, £102, f.o.b. Liverpool or London docks; please state direction of rotation at pulley end; fullest details of plant or alternators by return post; the above are not surplus but current products of British manufacture.
THIS month's genuine bargain, one only, lighting plant, Fowler twin-cylinder diesel engine water-cooled, 12hp at 1,200rpm, alternator, type as above, 6kva 250/1/50, plus 52v 15a d.c., auto voltage control, remote control, start and stop, etc., 24v 120 amp/h. battery, price a little over £500.
6V BATTS., 100-125 amp/h., £5 del.; rotary converters, 24v d.c. to 230v 50, 80-100 watts, switch, metal box, tested, £5/17/6 del.; shunt dynamos, 52v 9a, £6/5, used but good, 90/- del.; sliding res. Zenith 2(); 16a, 5() 10a 19/6 del.; 12 and 24v battery chargers, see "W.W." August, p. 74.
PLEASE see displayed advert, page 106, for S.T.C. selenium rectifiers; terms c.w.o., pro forma invoice, c.o.d. (post goods only).
T. W. PEARCE, 66, Great Percy St., W.C.1 (near Angel). [0014

TRANSMITTING EQUIPMENT

MAGSLIP transmitters from 10/-; ideal for remote control of radio apparatus, including Antenna direction indication; stamp for details.
ENGINEERING FACILITIES LTD., 29, Rea St., Birmingham, 5 [7907

VALVES

VALVES.—Large stock of non-current type valves at original prices; 24-hour service.
W. WATERS & SONS, Ltd., 52, Great North Rd., Hatfield, Herts. Tel. Hatfield 2255. [7902

MEASURED PROOF OF THE AMAZING PERFORMANCE OF THE 215 SPEAKER

While H. A. Hartley was in the U.S.A. he had an opportunity of getting some highly accurate measurements of the Hartley-Turner 215 speaker and the Boffle taken in one of the most up-to-date and most comprehensively equipped of the acoustical laboratories of America.

Apart from our resounding success at the New York Audio Fair, backed up by a pile of American testimonials, some of which are almost lyrical in their praise of the speaker, H.A.H. confessed to some nervousness as to what these measurements would show.

This was not due to any doubts in his mind that the speaker is a good one, but the cold impersonal results of pure scientific measurement have sometimes a damping effect not on a speaker but on its designer. However, he said "Go ahead and let us know the worst."

The results are astonishing, in some respects almost staggering. What we find are these :

1. Except for two extremely narrow valleys only a few cycles wide, the speaker comes within the usual limits of 10 dB from 60 c.p.s. to 18,000 c.p.s.

2. This performance INCLUDES the 18-inch cube Boffle.

3. The response is only 7 bB down at 20,000 c.p.s.

4. There is no bass resonance detectable down to 20 c.p.s.

5. Polar radiation curves show an almost perfect spherical radiation at 2,000 c.p.s. ; very good radiation at 4,000 c.p.s. ; 120 degrees at 13,000 c.p.s. and over 90 degrees at 20,000 c.p.s.

The full report is being sent to everyone who has asked for our catalogue and will be included in every future request (1½d. stamp).

In the past we have suggested the 215 will outperform any other speaker at any price, and the figures we quote now tend to prove that we were not just writing advertisingese. Yet the 215 really costs you very little.

Send for illustrated catalogue to-day

H. A. HARTLEY Co. Ltd.

152 HAMMERSMITH ROAD, LONDON, W.6

Phone : RIV. 7387

VALVES

VALVES.—Most new British types in stock; return-of post service.—City & Rural Radio, 101, High St., Swansea. [8050

NEW TEST EQUIPMENT

TOROIDAL cored coils—offer optimum performance at all frequencies. Technical advice offered.—BEL SOUND PRODUCTS, Co., Marlborough Yard, London, N.19. Arc 5078. [0186

TEST EQUIPMENT—SURPLUS AND SECONDHAND

COSSOR 339A double beam oscilloscope, brand new condition, £45. o.n.o.—Box 6101. [8000

FOR sale, general radio UHF signal generator, improved type 804-A.—Best offer to United Insulator Co., Oakcroft Rd., Tolworth, Surrey. [8029

SIGNAL generators, oscilloscopes, output meters, valve voltmeters, frequency meters, multi-range meters in stock; your enquiries are invited.—Requirements to R.T. & I. Service, 254, Grove Green Rd., London, E.11. Ley. 4986.

COSSOR 339 oscilloscope 343 Wobbulator, £55 the two; BC221 frequency meter (modulated), complete with mains unit, service manual, etc., new, one only, £40, callers preferred. T.M.C.'s condenser, microphone tester.—Haynsons, 14, St. Mary's, Bedford. Tel. 5568.

ADVANCE constant volt trans. 150w., £5/10; Advance B.3.C. generator, £15; Audio-R.C. gen. A.G. 20c-50k.c., £12; Fuckie A.C.T. base 5-valve, £2/10; Avo valve tester, 2-panel, £8; G.E.C. miniscope, £10; also others.—L. P. Dismore, 52c, Old Church Rd., Chingford, E.4. Tel. Sil. 4987, evenings. [8016

NEW GRAMOPHONE AND SOUND EQUIPMENT

FRITH RADIOCRAFT Ltd., offer from stock :—COLLARO 3-speed auto-changers; basic 3-RC-511 unit without pickup heads, £12/9/5. Acos GP-27 pickup heads in three types, standard, long-playing or dual-purpose, £5/2/4 each, complete unit with dual-purpose head, metal table cabinet, £18/15, ditto in de luxe walnut cabinet, £26/16/2.
COLLARO 3-speed single record players: basic 5-514 unit without pickup heads, £8/4/2. GP-27 heads as above.
COLLARO single-speed auto-changers RC-500, magnetic PU £11/16/9; crystal PU, £12/2/11.
COLLARO AC-514 single-speed r/p unit, mag PU, £6/13/5.
PESSEY multi-speed auto-changers to play 8-10 records 10in and 12in mixed at 33 or 78 rpm, or 8-10 records 7in only at 33 or 45 rpm; Acos dual sapphire head, £23/15.
CONNOISSEUR super de luxe 2-speed motors with 12in machined turntable, instant change from 33 to 78 rpm, £22/18/8; de luxe pickups with twin heads and sapphires, £10/0/8. Connoisseur Stroboscopes for 33 and 78 rpm at 25, 50 and 60 c/s, 5/11.
W. B. "Stentorian" speakers, 2½in 18/6, 3½in 19/6, 5in 21/-, 6in 32/6, 9in 56/9, 10in 44/6; dual concentric types 10in £6/15, 12in £17/17 or with transformers £7/15 and £8/18.
GOODMANS 12in speakers; Audiom 60, £8/12/6; Axiom 150, twin-cone, £10/5/6; Celestion P-44 speakers, 12in FLF, 5 ohms, £4/5. Ekco moulded plastic speaker grille 16½in×12in cream or gold, entirely free from resonance, 6/6 plus 1/3 post; sample on request; Escutcheon moulding, flexible cream plastic 5/16in D section, 1/6 per yard.
RESLO ribbon microphones type URA £7/10, moving coil type VMC £6.
ACOS crystal microphones MIC 21/1 or 22/2 for floor or desk stand fitting, £6/6; table stands, 25/-; 3-section folding floor stands, £3/7/6.
RECORDING tape EMI 65A, 65B or H60, 35/-; Scotch Boy (Durex), 35/-; Philips, £2; all 1,200ft reels, spare reels 4/-.
RECORDING motors, BSR SR-1, 32/-; SR-2, 25/-; FP-10 clockwise or anti-clockwise, 58/-; Collaro ditto, 42/-.
AMPLION multi-range meters, 1,800 ohms per volt, 9 ranges, £5; Pullin series 100 multi-range meters, 10,000 ohms per volt, 21 ranges, £11/11.
FRITH Radiocraft Ltd., 69-71 Church Gate, Leicester. Tel. 54927. [0024

TAPE recorder motors, 250v a.c., powerful, quiet, brand new, 15/11, post etc., 1/1.—K. W. Logan, Westalley, Hitchin, Herts. [6469

MAGNETIC tape, new high coercivity Emitape 35/- spool 1,200 feet tape decks, blank recording discs, 9in. 5/- from stock; full trade terms.
SOUND DISCS (SUPPLIES) LTD., 178 Bispham Rd., Southport, Lancs. Tel. 88153. [7765

MAKE your own m.c. pick-up, first-grade instrument, response to 14kc/1db, components supplied.—S.a.e. for details to Pollock, 31, Brooklawn Drive, Manchester 20. [7589

THREE speed record players, walnut finish (with 1d) fitted B.S.R. MU.14 motor at £11/5; complete with Chancery dual cartridge crystal pick-up £15/9/6; with Decca X.M/S magnetic pick-up £16/5; any make fitted to order; MU14 motor at new reduced price of £6/8/6 post free.
RECORD filing cabinets for the Connoisseur in hand French polished oak, walnut or mahogany from £15/15; sizes to hold 500 or 500 discs; specials to order.
SAND-FILLED corner speaker enclosures, non-resonant (as described by G. A. Briggs in his book "Sound Production") in walnut finish, from £15.
BASS-REFLEX cabinets suitable for any size speaker, solidly constructed from hardwoods, plywood and Weyroc; any type of cabinet made to customer's own specification.
DETAILS for 2½d stamp from—"Phase-In" Speakers, 99, Ash Bank, Bucknall, Stoke-on-Trent. [8005

FIDELIA *De luxe*

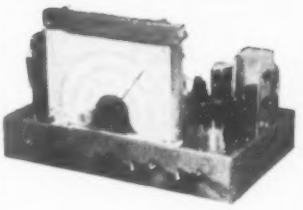

Luxury 9 valve Radiogram chassis with 20-20,000 cycles audio response and triode push-pull output stage. **£55/5/-.**
Our range of Fidelia chassis now includes a new 10 valve model—the Major. This model has increased R.F. sensitivity over our popular "de luxe" model. The Major is built in two sections, all controls being mounted on the R.F. section. The audio and mains components being rather heavy, are mounted on a separate chassis. The price is **£31/10/-.**

Our range also includes
Fidelia Standard 7 valve model, **£21.15/-.**
Fidelia Plus 8 valve model, **£24.5/-.**
Precision 5 valve model, **£13.13/-.**
Technical data sheets willingly sent on request.

Please note our new address below—our new home faces the main Brighton-Newhaven road, where we shall be very pleased to demonstrate any of our equipment by appointment.

ELECTRO Acoustic DEVELOPMENTS

9 Amherst Road, Telscombe Cliffs, Sussex

JEWEL NEEDLES

★ **SAPPHIRE 9/11** including tax.
GEMTIPT straight and trailer for crystal and magnetic pick-ups. SAPPHIRE STYLUS for light weight pick-ups.

★ **DIAMOND 7 gns. plus 62/11 tax.**
To fit most light weight pick-ups.
Pick-ups with removable armatures or fixed point, fitted at **£7.13.11** plus **55/11** tax; L.P. at **£8.14.11** plus **74/11** tax.

These unique needles are unimpaired by years of use. 90 times harder than sapphire and more shock-proof.

STARR NEEDLES are stocked by Webb's Radio, Keith Prowse, Qual-ty Mart and other good dealers. In cases of difficulty write direct.

STARR BRITISH PRODUCTS

8 DARTMOUTH PARK AVENUE, LONDON, N.W.5 Tel. GULliver 1131

Export Enquiries :

General & Overseas Trading Corp., Ltd.,
6 Duke Street, St. James's London, S.W.1

A WINDOW WORTH LOOKING INTO

Television Coil Formers. With iron dust cores, Polystyrene, 1in. x ¼in. with single hole fixing, 6 BA, **6d.** each, **5/6 per dozen.**

Television. 1 mfd. high-voltage condensers "Mansbridge" type, 5000 volt, "No Trouble," very limited number left. **2/-** each.

Television. EF50 (VR91) Boxed, brand new, **7/6** each.

Television. Diode Holders. **3d.** each; Cradle type, **6d.** each; Ditto, Polystrene, **8d.** each.

Television. Wire-Wound Pots 10k., 20k., 25k., 50k. All at **2/-** each.

Television Dural Aerial Masts. Telescopic from 15in.—7ft. 6in. long, ideal for making your own Television Aerial, **4/6** each.

Television Chassis, 4 stage, EF50 and diode holders mounted with coils and coupling condensers also resistors, each stage separately screened, wonderful bargain, **8/6** each.

Micro-Amp Meters, Brand New and Boxed, 0-100, 2½in. Scale, **39/6** each.

Special Offer. Condensers 16 x 16 x 16 Mfd. 450 working, brand new, **3/6** each.

Micro Switches. Several types available. Large stocks, please let us have your enquiries.

Switch. Suitable for the Williamson Amplifier. Single pole 6 way 5 bank, **3/6** each.

Ex-W.D. 2-Valve Battery Amplifiers. Complete with 2-volt driver and Q.P.P. output valve. Brand New. Ideal for mic. or gramophone, **12/6** each, valves alone are worth this.

Bendix Command. 12/14-volt input plug-in type Rotary Transformers, output 250 volt 60 M/a. Very limited number only, **29/6** each.

Moving Coil Headphone Microphone Sets. Ex-W.D., **10/6** per set. Limited number only available.

Rotary Convertors. 24 volt D.C. input, 230 volt A.C. 50 cycle output at 100 watts, **92/6** each.

Welding Transformers. Input 230 volt A.C., output 15 volts 80 amps, **82/6** each

Midget Wire-Wound Volume Controls. 20 ohm centre tapped, ¼in. diameter, ¼in. spindle, large number available **12/-** each.

Chokes. Ex-W.D. 30 Henry 100 M/a., will pass up to 150 M/a., wonderful bargain, **12/6** each.

Chokes. Ex-W.D. 5 Henry 200 M/a., resistance 100 ohms. **5/6** each.

B7G Button Base Holders. With bottom screen, large stocks available, **1/2** each.

Bendix Command Receivers, 6-9 Meg., brand new in sealed boxes, with valves and rotary transformer, absolute 100 per cent condition, **99/6** each.

Callers Only. No Post. 8 x 8 x 8 Mfd. electrolytic condensers, 450 volt. Special temptation price, **1/-** each.

Don't forget your postage.

Open all day Saturday.

G. W. SMITH & CO.
(RADIO) LTD.

3, LISLE STREET, LONDON, W.C.2
Telephone: GERrard 8204/9155.

NEW GRAMOPHONE AND SOUND EQUIPMENT

CONNOISSEUR super lightweight p.u. 33 and 78 heads, £10.6.8. Decca XMS p.u. 33 and 78 heads, £7; Acos GP20 standard p.u., £5.11.3; GP19 L.P. head £2.3.4. Connoisseur precision 2-speed motor, £22.18.8. Decca 3-speed motor £7.5.4, all pick-ups and motors despatched post free.—ROGERS DEVELOPMENTS Co. (M.O. Dept.), 116, Backheath Rd., S.E.10. [7960

CINE-VOX disc recording equipments ... C70 for high-quality recordings from existing ... also available as a complete channel inclusive of disc amplifier and playback equipment at 70gns. type C7 for highest quality professional requirements—recorder mechanism at 46gns. or complete channel at 110gns. demonstrations arranged in London.—PLEASE write for details to K.T.S., Ltd., 60, Aylward Rd., London, S.W.20. (Liberty 2426). Callers by appointment only. [0207

"MAGNETIC Tape Recorder Construction" (8/6) besides explaining the theory also gives full constructional data, sketches, instructions for aligning and testing a complete high-fidelity recorder; 7½in p.s. wow-free reproduction, fast rewind, low noise-level; kit of precision-made mechanical parts supplied which makes assembly of desk a simple matter of drilling and mounting.—GMGLS., 15, Corstorphine Hill Rd., Edinburgh. [7950

GRAMOPHONE AND SOUND EQUIPMENT —SURPLUS AND SECONDHAND

LANE tape deck, as new, £14; set Phildelity record/playback, erase heads, £5.—Watson, Eagle House, Sandhurst, Camberley. [7962

DISC recorder, B.S.R., DR33M and AR15C ribbon and m/coil mics.; stock of blanks, excellent condition, £110.—Box 6125. [8006

25 watt P.A. amplifier, mike and gram. inputs, tone control, push-pull, 615 output, first-class jobs, available, £15/15 each, also Williamson, £19/10.—Box 6097. [7988

NEW COMPONENTS

CRYSTAL microphone inserts (Cosmocord Mic-6) guaranteed brand new; 15/6 post free.—RADIO-AID, Ltd. (Retail Dept.), 29, Market St., Watford. [0056

TELEVISION—Coilsets—most channels, 16/6 to 25/-, as prev. advert., ¾in x 2in alloy canned, two-cored, tagged formers 2/- ea. Trade enquiries invited. On Govt. lists.—BEL SOUND PRODUCTS Co., Marlborough Yard, London, N.19. Arc. 5078. [0184

EVERYTHING for home constructor, chassis, condensers, coils, valves, resistors, gram units, speakers, test gear. Viewmaster kits, etc., cash or H.P.; stamp for lists, quick service, no Govt. surplus offered.—James H. Martin & Co., BCM/EDHWA, London, W.C.1. [7694

MINICOILS—Your popular choice of dependable midget radio tuning coils, superhet or TRF, all standard types, 5/6 each; also standard replacement pick-up bobbins, 7/6 each. Send for literature.—Manufactured by Cretton Radio, 549, Copnor Rd., Portsmouth. [7921

2/6 only for our new constructor's handbook containing 14 circuits and parts lists, full diagrams and constructional details for building our popular superhet coil packs, pages of useful information, etc., full catalogue with each handbook; send for your copy today.—SUPACOILS, 98, Greenway Ave., London, E.17. [0155

FOR really good results you can do no better than use Osmor coils and coilpacks, as anyone of experience! Send 5d (stamps) today for beautifully-drawn free circuits, our new coil-data leaflet, and latest lists of matched radio components; a speedy mail order department is at your service, and remember, all Osmor lines are guaranteed. (Trade enquiries invited). Dept. C.W.1.—OSMOR RADIO PRODUCTS, Ltd., Bridge View Works, Borough Hill, Croydon. Tel.: Croydon 5148/9. [0046

COMPONENTS SURPLUS AND SECONDHAND

C. J. EMMS Ltd.

RECTIFIERS full wave bridge type, as follows: 1 amp. 12 or 6v. 5/6; 3 amp. 12 or 6v. 12/6; 4 amp. 12 or 6v. 15/-; 5 amp. 12 or 6v. 17/6; 7 amp. 6 or 12v. 22/6; 24v 1 amp. 11/-; 24v 3 amp. 25/-; 24v 4 amp. 30/-.

NEW sliding resistance sets from 1 to 4 amp 14Ω to 12 amp 1Ω, 7 in all, 50/- per carton.—26a, Cochrane Mews, London, S.W.10. [7971

MAGSLIPS at 1/10 to 1/20 of list prices, huge stocks, please state requirements.—K. LOGAN, Westaway, Hitchin, Herts. [6569

ALMOST complete set of unused parts and circuit for Wearite tape recorder; £20.—Fountaine, 68, Dunstable St., Ampthill, Beds. [7940

0.1—500 5d., 4/- doz.; 1.2k 10w, 6d.; L.T. rects., 1/6; potmts., I.F.T., 1/-; VCR97 holders, 9d.; UX5 ceramic, small pfs, 3d.; post extra; s.a.e. lists; wanted 5-pin plugs, ZA25864.—ANNAKIN, 25, Ashfield Place, Otley, Yorks. [7999

ELECTROLYTIC conds. (not Govt. surplus) tub. wire end 500vw, 8mf 2/6, 16mf 3/6, 32mf 5/-, 25v 25mf 20/- doz.; Al. can 500vw 16-16mf 5/6; mica conds., moulded case, 0.1mf 1,500v dcw, 20/- doz.—Ward, 9, West Cliff, Dawlish, Devon. [0214

Come to Classic for

"The Classic Service"

Our Motto is: "Nothing is too much trouble"
We will ship to any part of the British Isles or abroad

TAPE RECORDING EQUIPMENT:	Delivery	Price
Simon Simphonic, Model IA	Soon	
Sound Mirror, Table model	Stock	£69 10 0
Sound Mirror, portable model	Stock	£79 10 0
Bradmaster Tape Desks	Stock	£42 10 0
Microphones	Stock	£6 16 6
Tapes from stock		£1 5 0

AMPLIFIERS AND HI-FI EQUIPMENT

Leak T12 Amplifiers, with control unit	Stock	£37 16 0
Williamson (Goodsell), with control unit	Stock	£40 15 0
Quad Amplifier with control unit	Stock	£35 0 0
Quad Radio Feeder Unit	Stock	£26 0 0
Leak Radio Feeder Unit	Stock	£37 2 4

MOTORS AND PICK-UPS

Connoisseur 2-speed Motor	Stock	£22 18 0
Connoisseur Super light-weight Pick-up	Stock	£4 10 5
Plessey Auto-changer Unit, 3-speed, 7in., 10in. and 12in. mixed	Stock	£23 13 0
Collaro Auto-changer Unit, 3-speed, 8-record	Stock	£18 14 1
Decca 2-speed Motor and Pick-up	Stock	£9 19 4
Decca dual Head Pick-up	Stock	£3 10 0
Leak Pick-ups, standard or L/P	Stock	£8 8 0
Trix Autogram 3-speed Garrard Unit	Stock	£44 0 0

QUALITY SPEAKERS, UNITS

Barker's 148A Unit	Stock	£15 15 0
Barker's 150 Unit	Stock	£18 18 0
W.B. 10in. Duo Concentric	Stock	£6 6 0
W.B. 12in. Series gap 15 watt	Stock	£8 10 0
Wharfedale Units, wide range	from	£4 14 6

QUALITY SPEAKERS, CABINET TYPE

Leak, 2 unit, 400 cyl. crossover, in walnut cabinet	Stock	£37 10 0
Decca, Corner Speaker, 3 or 15 ohms	Stock	£21 0 0
W.B. 10in. Duo Concentric Corner	Stock	£13 16 0

COMPONENT AND KITS

Williamson Amplifier Kits Comp.		£20 10 0
Viewmaster Tele. Kits	Stock	£27 10 0
Germanium Crystals	Stock	3 9
16ft. Portable Aer al		£1 12 6

Special line in surplus **Mains Transformers,** suitable for T.V Receivers **35/-.**

Northern readers send for full details of our special T.V offer.

All goods despatched by post or passenger train.
Please include carriage.
Send stamps for list. All enquiries to

The Classic Electrical Co. Ltd.

"THE HI-FI TELEVISION SPECIALISTS"
352/364 Lower Addiscombe Road, Croydon, Surrey. Telephone: Addiscombe 6061/2.

They're worth waiting for...

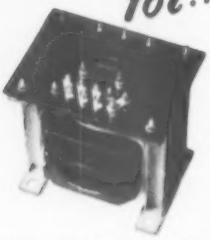

A lot more people than ever before have been ordering a lot more Savage Transformers than ever before. This, and the shortages of raw materials are extending deliveries more than somewhat. As one of our Welsh customers said, however, "Savage Transformers are worth waiting for."

SAVAGE TRANSFORMERS OF DEVIZES LIMITED

SAVAGE TRANSFORMERS LTD.
Nursteed Road, Devizes, Wilts.
Telephone: Devizes 538

COMPONENTS—SURPLUS AND SECONDHAND

HALLICRAFTER skyrider Model 23, perfect ...4, transmitter, communication receivers in stock. Hammarlund output, etc. R.S.G. senders C.R.100, A.R.88D, A.R.88LF., etc., all in perfect order; R.1155 receivers in new condition, your enquiries are invited for rotary convertors and electric motors, mos, sizes and types available from stock; special clearance of F.H.P. electric motors, 35/-, 110-250v a.c.

UNIVERSAL a.c./d.c. motors, suitable for sewing machines, 40/- each. 12v-15v a.c./d.c. motors with extended spindle, suitable for models, etc., 9-5, 20 watt P.A. rack mounting amplifier, new and complete, with heavy duty a.c. power pack, 200/250v, PX25 P.P. output, £5 10, less valves, new moving coil microphones, hand type, heavy duty and complete with 12yd screened cable, £3 15/-. 20ft telescopic tubular T.V. mast, 15/6 each; large selection of test equipment; multirange meters, valve testers, signal generators, oscilloscopes, bridge meggers and meggers, etc., all at unbelievable prices, hand gear for prismatic compasses, perfect, 45/- each; very large stocks of transmitting valves, Klystron, of all types, send us your requirements, special offer of new, but ex W.D. mains transformer, semi-shrouded 200-250v tapped primary, 250-0-250, 100ma, 5v 3amp, 6v 4amp, 21/6 each; large stocks of L.T. transformers, special sizes and ratings wound to specification, auto-record changers in stock from £15 2/6 to £15 10; switchboard mounting voltmeters, ammmeters, various ranges a.c. and d.c. available at cheap prices to clear, large stocks of enamelled wire, 14 and 20 s.w.g., D.S.C. No. 15 D.X. base, American valves available. Special offer, H.R.O. coils, 48-96 m/s and 180-450 c/s, 45/- each, quantity of 1ft2 and nickel chrome wire available, type 74 indicator units, complete with tube and valves, £6 each. Hallicrafter Super Skyrider SX28 in stock. Eversheds bridge megger, 500v 1½kw, e.d.c. rotary converter, 220 d.c./250 a.c., complete with Tarzan starter, £28. Large selection of American Pyranch high-voltage working condensers, 0.5 m.a meter rectifiers 6/3 ea.

HAMMERLUND B.C. 779B, perfect order, rack mounting, £42 10. Q-Max Q-5 10 receiver, new, £58, prices do not include postage.

SERVICE RADIO SPARES, 4, Lisle St., W.C.2. Gerrard 1734. [0188

V.H.F. receiver, type 1481, complete with valves, £7/10.

BENDIX frequency meters, type BC221.

THROAT microphones, 5/6 each.

LORD antivibration mountings, 8lbs ff. 10lbs, £8 per 1,000.

TELESCOPIC aerial for No. 19 set Mark II.

POWER unit for No. 19 set, U.S.A. and British Mark II, 25/-.

VOLTMETER MC DC 5,500 volts, 3½in projecting type, 45/- each.

EIMAC vacuum condensers, 100pfd, 20,000 volts; 15/- each.

MICA condensers, American types, bulk quantities only, types X, S, Sangamo, Solar A2 etc., 500v to 5kv, assorted resistors, American 40 ohms to 50,000 ohms wattages 25 50 75, 100, all at 4/- ea.

COMMAND receiver Bendix drives from 5in to 25ft long, 5in 5/- each, from 2ft to 8ft, 8/6 ea., from 15ft to 25ft, 16/- ea.

McELROY ADAMS MFG. GROUP, Ltd., 46, Greyhound Rd., Fulham, W.6. Tel.: Fulham 1158-9. Cables: Hallicraft London. [0196

G. A. RYALL, "Dhupia," Mayfield Rd., Herne Bay, Kent, offers post free bargains at reduced prices to clear, all new and unused. Paxolin panels, ⅛in, 12×8, 5/9 each or 35/6 doz. 4 new resistance panels with 50 ¼-½-1-2 watt colour coded best make carbon resistors, 5/-. condensers, mica, 0.01 550v, 6 1/6; 0.004mf 1,200v wkg, 6 1/6; 4mf mansbridge, 400v wkg, upright, terminals feet, 2/3; 1mf ditt 500v wkg 2 1/6, 25pf silver mica, 6 1/6, special note insulation of all condensers perfect, 18mf, that is 11×7mf 250v wkg non-inductive mansbridge type, large construction, heavy terminals at vide, 8/6 each, high resistance headphones with good type carbon microphone, padded double bands, sponge earpads, all wired into large 4-cleft plug, ex R.A.F., good condition, as new, 8/9 set. meters, 2in voltmeters, 0-500v with separate series (5ma) resistance, 6/9, best make open scale 2in 0-5ma, 6/9; good make 0-50ma 2½in, 6/9; and 2in circular 0-50ma, best make, 6/9; first two meters are square front, all front flange fixing, one type plug in meter, 2in circular, full size deflection 1.5ma, scaled 0-5 in 50 divisions, 12/6 each; 5 high stability vitreous resistors, 2in on Govt. grade paxolin panel with insert sockets and bolts for mtg, 2-25,000 ohms and 1-150 ohms, 15/- per panel; miniature red panel mtg lamp holders in brass with 12v bulb and can, 1/3 each complete, pairs of 25mf 50v electrolytics, 1/9; over 2 yards screened twin cable 1/3, 3 yards light twin circular 1/3, 5 yards light triple circular 1/3, 2-way plug and socket 1/3, triple plug and socket 1/3, Bakelite toggle, 250v 2p ST, 1/3, and 2p DT changeover, 1/9, 4-gang 0.0003 condensers straight type, 5/10, 5-gang 0.0005 type 6/10; switches, miniature instrument, SB 2p 6-way, 1/3; standard Yaxley type, 2p 5P 6-way, 1/3, smaller type 5b 2p 6-way, total 5 poles, 2/-; one type soldered tags, 5 poles 4-way, 1/3, all single hole fixing, standard Yaxley type SB 5P 9-way, 1/3 each, special offer control boxes, size 6×3×3 approx, contains Yaxley type switch, 5-pole 4-way, well finished 2½in pointer knob, Bakelite switch 2p ST and ditto 2p DT CO, both 250v, 5 4-way plugs, 8-180, 3/6 each post free, new and boxed. radio mains filters, four divisions, fully screened in metal cases with fixing feet, 5/9 each; metal boxes, black finish, 8½×7½, abt. 5in deep, with ¼in paxolin lid, feet for wall or bench, new, 6/9 complete. [0205

THE MODERN BOOK CO.

World Radio Handbook for Listeners. By Johansen. 1952 edition. Price **8s. 6d.** Postage 6d.

The Oscilloscope Book. By E. N. Bradley. Price **5s.** Postage 3d.

Theory and Design of Valve Oscillators. By H. A. Thomas, 2nd edn. revised. Price **36s.** Postage 9d.

Sound Reproduction. By G. A. Briggs. 2nd edn., revised. Price **10s. 6d.** Postage 6d.

Television Receiving Equipment. By W. T. Cocking. 3rd edition. Price **18s.** Postage 9d.

Cathode-Ray Oscillographs. By J. H. Reyner. 4th edition. Price **15s.** Postage 6d.

Radio Receiver Design. By K. R. Sturley. 2 vols. Price **28s.** Vol. I. Postage 6d. Price **30s.** Vol. 2. Postage 6d.

Radio Handbook. Ed. by R. L. Dawley. 13th edition. Price **48s.** Postage 1/-.

Advanced Theory of Waveguides. By L. Lewin. Price **30s.** Postage 6d.

Transmitting Valves. By J. P. Heyboer and P. Zuilstra. Price **35s.** Postage 9d.

Time Bases. By O. S. Puckle. 2nd edn., revised. Price **30s.** Postage 9d.

Encyclopaedia on Cathode-Ray Oscilloscopes and their Uses. By J. F. Rider and S. D. Uslan. Price **75s.** Postage free.

Radio Engineers' Handbook. By F. E. Terman. Price **50s.** Postage free.

Radio Engineering. By F. E. Terman. 3rd edition. Price **50s.** Postage free.

Radio Valve Data. Comp. by "Wireless World." 2nd edition. Price **3s. 6d.** Postage 3d.

We have the finest selection of British and American Radio books in the Country. Complete list on application.

19-23 PRAED STREET
(Dept. W.2)
LONDON, W.2
PADdington 4185

SURPLUS BARGAINS
MANUFACTURERS' & BANKRUPT STOCKS
LIMITED SUPPLIES ONLY

We can offer for immediate delivery

JUST PURCHASED!
LARGE CONSIGNMENT OF RESISTORS
ALL VALUES: ½, ¼, ½, 1, 2, and 3 WATT.

Low and High Resistance Headphones

EX. W.D. AERIALS—BRAND NEW—CAN ALSO BE USED AS FISHING RODS.

12 ft. Light Steel Aerials in 3—4 ft. sections screw-in or plug-in type

Electrolytic Condensers—All Types

Yaxley Type Switches, Matalotlige Condensers (Oil filled and Jelly), Burgoyne Solder coins, Tannoy Handbooks, Dinghy Transmitter Sets, Adhesive Tape, Coaxial Cable, Magnifying Lenses, Rubber Masks, Speakers, Coaxial Plugs and Sockets, etc., etc.

Your enquiries are invited

WHOLESALE AND EXPORT ONLY

For further bargains call at our Counter or write for NEW bulletin.

RADIO MERCHANDISE
COMPANY LIMITED
65, Farringdon Road, London, E.C.1
Telephone: HOLborn 4177 Cables: Ohms, London

"You can rely on us"

FOR CLEAN COMPONENTS AT COMPETITIVE PRICES

MIDGET I.F. TRANSFORMERS.
465 K.cs. Wearite M800 1¾16" square 1 13.16" high 10 6 each. Super midget, 13.16" square 1¼" high 10 6 each.

QUALITY OUTPUT P.PULL TRANSFORMERS.
MR 7, 10 watts, 12 ratios, fitted with Terminal Panel, 18 9.
MR 15, 18 watts, 11 ratios, secondary 1 to 30 ohms, primary 2,000 to 16,000 ohms. 41 6.
MR 30, 30 watts, 11 ratios, Max. Current 170 m/a., Primary and Sec., as MR 15. 48 6.
PX25L, 15 watts, 6L6 Class A, 4 ratio, Primary 5,000. 42/-.
PAX4L, 10 watts PX4, 4 ratio. 33/-.
All new transformers NOT surplus.

EXPERIMENTAL TRANSFORMERS.
Standard Primary 200/230 v., Secondary 3 v. to 30 v. at 2 a., 24/-.

COILS.
Wearite "P" Coils all ranges, 3/- each. Weymouth "H" coils 3/6. "K" coils 4 9. T.R.F. pair with reaction, MW/LW 7 6.

COILPACKS MW/LW/SW.
Bargain offer, superhet pack for 465 K.cs I.F., 25/- each.

LOUDSPEAKERS.
WB 5" 17 3, Plessey 8" T.V. Type 14 9, 6" TV Type, 15/-.

HIGH VOLTAGE CONDENSERS.
T.C.C. .001 mfd 6 Kv. 4 6, .001 mfd. 12.5 Kv. 7 6, .01 mfd. 6 Kv. 4 6, .1 mfd. 3 kv. 13 6. All new stock.

MISCELLANEOUS.
Full range of Morganite Type "I" Miniature resistors, max. rating 1 watt 6d. each, 3-piece polished aluminium nut, Octal Valve caps 1 6. Miniature Vol. Controls, with s.w. 5/-, less 3 6. Aladdin Formers and Cores ½" 10d., 1" 7d. New High Resistance Lightweight Headphones 12 6 pair. Rotary toggles, SP ST 2 6, DP ST 4 3. B Lee Co-Ax. Plugs 1 6. Sockets 1 6.

Stockists of :—
HAYNES, WEARITE, WEYMOUTH, VIEW-MASTER, B.V.A. Valves, ELSTONE Products.
Our 52-page Catalogue No. 10 6d.

RADIO SERVICING Co.
444 Wandsworth Road, London, S.W.8
Phone: MACaulay 4155.
77, 77A Bus; 28 Tram. Wandsworth Rd. S.R. Station. Open till 6.30 p.m.

ALEC Davis SUPPLIES Ltd.

DEPT. W.W. 18 TOTTENHAM CT. RD. LONDON, W.1. MUSeum 4539 2453

LANE TAPE TABLE complete with heavy duty motor, erase and playback heads, **£16 10** - plus 10 - carriage and packing.

OC 2 OSCILLATOR COIL. For use with high or low impedance heads. **10** - plus 6d. post.

SCOTCH BOY MC-I-III MAGNETIC TAPE. 1,200ft. coil, **£1 15** -.

LUSTRAPHONE DYNAMIC M-C MICROPHONES. Low impedance type **£3** -. High impedance type **£5 12 6** plus 1/- post.

5-VALVE 3-WAVE BAND SUPERHET CHASSIS in kit form, complete with 8in. speaker. A really first class kit. All new components. **£9 19 6** plus 2/6 carriage.

3-VALVE PLUS METAL RECTIFIER. 2-wave band T.R.F. kit, complete with speaker and cabinet. Nothing else to buy, **£6 15** - plus 2/6 carriage.

A.D.S. 4½W. QUALITY AMPLIFIER incorporating a pre-amplifier stage with bass boost. Also suitable for use with a radio feeder unit. Complete set of components for above amplifier including cabinet, **£7 15** -. Complete amplifier constructed and fully tested, **£9 17 6**.

A.D.S. 10W. PUSH-PULL AMPLIFIER. Low and high level inputs. 3, 5, 7, or 15 ohms output. Details on request, **£12 17 6** plus 2/6 carriage.

A.D.S. MEDIUM-WAVE RADIO FEEDER UNIT. EF36 R.F. Amplifier. EF36 Triode connected detector. This unit is ideal for quality reproduction of local transmissions. Power required 250 v. 15 mA. 6.3 v. 5 a. Complete in Black Crackle Cabinet **£6 12 6** plus 1/6 carriage.

SPEAKERS.

5in. 3 ohms W.B Stentorian	19 6
5in. 3 ohms ELAC	15 -
8in. 3 ohms Manufacturers surplus	17 6
10in. 3 ohms Manufacturers surplus	39 6

All plus 1/- Post.

"DENCO" ALIGNMENT OSCILLATOR D.A.O.I. This unit provides a modulated signal for the alignment of I.F. Amplifiers, etc. The two standard frequencies of 465 kc/s and 1.6 mc/s are selected by the turn of a switch. Price **47 6** plus 1/- post.

MANUFACTURERS SURPLUS. 465 kc/s I.F.T. at **7 6** a pair plus 9d. post.

10 MC/S I.F. TRANSFORMERS at **2** - each plus 6d. post.

RM2 SENTERCEL RECTIFIERS 125 v. 100 mA **4** - each.

OSMOR "Q" COILS. Aerial H.F. or OSC 13-2,000 M in 8 ranges **4** - a coil.

DENCO TYPE "C" T.R.F. COILS. Medium and Long Wave, **8** - a pair.

THE CHANCERY LONG PLAYING ATTACHMENT. Converts your 78 r.p.m. player to 33⅓ r.p.m., **£3 12 6** plus 1/- post.

2 GANG .0005 Midget Var Condenser, **7 6** plus 9d. post.

2 GANG .0005 Standard Var Condenser, **9** - plus 9d. post.

3 GANG .0005 Standard Var Condenser, **7 6** plus 9d. post.

MAINS TRANSFORMERS. (All upright mounting).

Pri. 200-240 v., sec. 3 v., 4 v., 5 v., 6 v., 8 v., 9 v., 10 v., 12 v., 15 v., 18 v., 20 v., 24 v., 30 v. at 2 amps., price **19 6** plus 1/- post.

Pri. 200-240 v., sec. 250-0-250 v. 60 mA., 6.3 v. 3 a., 5 v. 2 a., **21** - plus 1/- post.

Pri. 200-240 v., sec. 350-0-350 v. 80 mA., 6.3 v. 3 a., 5 v. 2 a., **27 6** plus 1/- post.

Pri. 200-240 v., sec. 350-0-350 v. 120 mA., 6.3 v. 5 a., 5 v. 3 a., **37 6** plus 1/- post.

Pri. 200-240 v., sec. 425-0-425 v. 150 mA., 6.3 v. 4 a., 5 v. 3 a., **52 6** plus 1/- post.

Pri. 200-240 v., sec. 12 v. tapped 6.3 v. 3 a., **21 9** plus 1/- post.

J.B. SL8 3 wave band Spin wheel dials and drive, **27 6**.

J.B. SL5 3 wave band Dial and drive, **26 6**.

J.B. Full vision 3 wave band dial and drive, **13** -. All post 1/-.

FULL MAIL ORDER FACILITIES

Shop Hours: Monday-Friday 9-5.30 p.m. Saturday 9-1.

COMPONENTS—SURPLUS AND SECONDHAND

RADIO CLEARANCE, Ltd., 27, Tottenham Court Rd., London, W.1.

CLEARANCE offer of electrolytic condensers, capacity, voltage, size, type of mounting, price post paid, in total orders: 500+500, 6v, 1in×2in, cup, 1/6; 8+8, 450v, 1in×2in, cup, 2/6; 8+8, 500v, 1in×2in, cup, 2/9; 8+16, 450v, 1in×2in, cup, 2/9; 8+32, 450v, 1in×2in, cup, 3/6; 16+16, 450v, 1in×2in, cup, 3/6; 16+32, 450v, 1in×2in, cup, 4/-; 32+32, 450v, 1in×2in, cup, 4/6; 50+50, 350v, 1in×2in, cup, 5/6; 32+32, 500v, 1in×2in, cup, 5/-; 100, 450v, 1in×2in, cup, 2/9; 16, 450v, 1in×2in, cup, 3/-; 32, 450v, 1in×2in, cup, 3/6; 50, 350v, 1in×2in, cup, 3/6; 32+32, 450v, 1in×2in, cup, 4/-; 16+8, 450v, 1in×2in, cup, 3/6; 16+16, 450v, 1in×3in, lug, 3/-; 24+12, 450v, 1in×2in, cup, 5/-; 40, 450v, 1in×3in, lug, 4/-; 60+100, 450v, 1in×4in, clip, 6/6; all are all cans, some with cardboard sleeves as voltages are wkg., all new stock; some limited quantities.

TELEVISION! Set of 5 components, comprising line output trans. with E.H.T. winding to give 7 kV. using EY51 (theater winding for EY51 also included), and fitted with width control scanning coils, low impedance line and frame, focus coil (res. 10,000Ω), current approx. 20 mA); the set of 5 for 42/-, plus 1/6 post, diagram of line trans. supplied.

PERSONAL receivers, 3 valve T.R.F., using 1T4s, contained in handsome bakelite case with lift-up lid, size 7×6½×5in with lid closed, plastic carrying handle. Tram AE in lid, these receivers cover the medium waveband and operate from self-contained dry batts., standard types, W1435 and U2, output to a pair of lightweight 'phones (H.R.) cobra-head, SSG tuning and reaction, opening lid switches on, supplied brand new, with valves, batteries, 'phones, an ideal set for invalids, hosp. patients, etc., these receivers are not Govt. surplus and are offered ready to play, carr. paid £4/4.

CHASSIS steel, 5½×5½×1¼in drilled 5 button base holes, 1/9, 5×9×1½ drilled 5 button base holes, 2/3, 4½×12×2½ drilled 7 int. octal and square, open ends 5/-, all 14½×10×2¾ drilled 10-B8A, 5 int. octal, ex. T.V., 4/3; primary 0-110-210-240v 50c/s, secs 300-0-300v 80ma, 4v 2a., 6.3v, 2.5a, 15/6; smoothing chokes, 5H 200ma, 100Ω, 8/6; 8H 250ma 50Ω ditto 4×5×5 potted 10/6 post paid; electrolytics 32mf 350v card 2/-, 32-350v can 2/6, 16-450v can 2/6, 8+4 275v 2/-, 2-450v 1/6, switches standard Yaxley type, 2p 4w 1lb with shorting wafer 2/-, superhet coils ⅝×1¾, formers M. wave H.F. AE, Osc. L. wave H.F., AE, Osc., 1/9 per coil; I.F. trans. 465kc/s 1¼×1¼×4in iron cored 8/- pair, meters 2in square bakelite case, 0.5ma 6/6 50ma 7/6, 0-500v d.c. with series res. 7/6, Rotary power units, type 104, p.m. rotary mounted on chassis with supp. input 12v d.c. output 250v 60ma, 6.5v 2.5a, d.c. type 87 24v input, 0-250v 150ma, 104, 6/6 post paid; plugs and sockets, bakelite with keyway, 5, 7, 1/6 pair; extension speaker controls, 10Ω wire wound, ¼in spindle, 9d.; "Pye Strips," the well-known 45mc/s s.w. ion strips, brand new less EF50s, with EA50, perfect condition, 39/6, plus 1/6 post; focus coils, low res., 200Ω, standard TV, 8/6, can be had as alternative with kit if required, 6/6 in base sockets, p.m. less 'phones, boxed, 12/6 post paid; Mansbridge conds., 4mf 1,000v wkg., 5/-; v.c. with sp switch, long spindle 25k, 50k, 100k, 2m, 4/-.

FRAME aerials for personal sets, etc., medium wave, rectangular winding, size 6½×4½×1in, wound round 4 wooden bobbins mounted at the corners of all ali. plate, tabs for connections, 2/6 post paid; output trans., 5,000-5,750, 2/11; valveholders, Amphenol type, octal 7d.

10IN loudspeakers with trans. (4,5000Ω), 34/-, small size 4P 3v switches, 1in spindle, 2/9.

RADIO CLEARANCE, Ltd., 27, Tottenham Court Rd., London, W.1. Tel. Museum 9188. [0015]

SUPREME RADIO, 746b, Romford Rd., Manor Park, London, E.12. Tel. Ilf. 1260. Est. 17 years.

LOOK!! 1952 bargains—New stocks of vol. controls, just arrived, standard size with long spindle and s/pole switch, 2 meg., 250K ohms, 100K ohms, 25K ohms, 10K ohms and 5K ohms 2/6 ea., also the following values less switch: 2 meg., 250K ohms, 100K ohms and 10K ohms, 1/6 ea.

WESTINGHOUSE type metal rectifiers, 250v R.M.S., 65ma, 5/6 ea.; standard size I.F.T.s, 465kc/s, 8/6 pair, flat type mains dropper, tapped 200-250v, 650 ohms at 0.2 amp, 1/6 ea.

VALVE holders, moulded B7G, 10d ea., int. octal, Amphinol types, 7d ea.; B9G (EF50), slate type, 6d ea.; 3-pole 3-way small spindle rotary switches, 1/3 ea.; 4-pole 3-way small rotary switches, with medium spindle, 2/11 ea.

GLASS dials 3½in×2½in, m.L.M.S. wave station name for the new wavelengths (pointer action is semi-circular), wave-bands in 3 colours, very attractive, 3/6 ea., metal escutcheon for same, 2/6 ea., pointer 10½d ea.

ELECTROLYTIC cond. 32+32mfd 350v, can type, 5/9 ea.; 16+32mfd 350v small can cond., 4/9 ea.; 32mfd 500v tub. cardboard wire-end cond., 5/6 ea.; bias cond. 50mfd 50v cardboard or 50mfd 12v metal tag end cond., 1/- ea.

MAINS trans., drop through type, primary 0-250v tapped on voltage panel, sec. 275-0-275v 80ma, 6.3v 5amp, 5v 2amp, with screen, 15/11 ea., 4B.A. brass n'plated terminals 2/3 doz.; 28 way tag strips, break it as required, 1/- ea.

MANY other bargain lines in stock; terms c.w.o., no c.o.d., send 6d. extra for postage orders under £5; 2½d. s.a.e. all enquiries and list. [0021]

SOUTHERN RADIO SUPPLY, Ltd., 11, Little Newport Street, London, W.C.2. See our displayed advertisement page 115. [0016]

Armstrong

THE CHASSIS PEOPLE

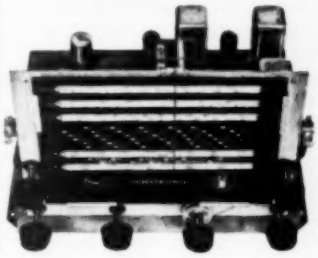

The prestige of Armstrong chassis is firmly based upon many years of constant endeavour to produce reliable and efficient receivers at an economical price. Our present range of chassis will even further advance the already high reputation enjoyed by our receivers. We are delighted to give demonstrations in our showroom and our illustrated catalogue will be sent on request.

MODEL EXP 125 3 14-VALVE ALL-WAVE RADIOGRAM CHASSIS

5 Wave Bands covering from 10.9 to 550m and 800 to 2,000m. R.F. Pre-Amplifier. Two I.F. Stages with Variable Selectivity. Bass and Treble Controls. 15-Watt Push-Pull Output. For A.C. Mains. **£36.15.0**, plus P.T.

MODEL RF 104 10-VALVE ALL-WAVE RADIO CHASSIS

4 Wave Bands. R.F. Pre-Amplifier. Two I.F. Stages with Variable Selectivity. 10-Watt Push-Pull Output. For A.C. Mains. **£24.0.0**, plus P.T.

MODEL EXP 73 8-STAGE ALL-WAVE RADIO CHASSIS

3 Wave Bands. Variable Selectivity. Fly-Wheel Tuning. 8-Watt Push-Pull Output with Negative Feed Back. For A.C. Mains. **£17.15.0**, plus P.T.

TELEVISION

The new ARMSTRONG TELEVISION CHASSIS, model TV.15, incorporating a 12" C.R.T., is now available for distribution.

PRICE: 53 GUINEAS

TAX PAID

Unfortunately, owing to the limited supply of material, the Chassis is at present available only for the London Service Area. Please send for full details.

ARMSTRONG WIRELESS & TELEVISION **CO. LTD.**

WARLTERS ROAD, HOLLOWAY, LONDON, N.7

Telephone: NORth 3213

THE
BRITISH NATIONAL
RADIO SCHOOL
ESTD. 1940

NOW IN OUR THIRTEENTH YEAR AND STILL

NO B.N.R.S. STUDENT HAS EVER FAILED

to pass his examination(s) after completing our appropriate study course.

NOTHING SUCCEEDS LIKE SUCCESS

and we have every reason to believe that we can help YOU to increase your PRODUCTIVITY, i.e. your EARNING POWER!

A.M.Brit.I.R.E. and
CITY and GUILDS Radio and Telecommunications Exams, etc., etc.

Please mention this advert. and send for free booklet to —

STUDIES DIRECTOR
BRITISH NATIONAL RADIO SCHOOL
66, ADDISCOMBE ROAD, CROYDON
Phone: Addiscombe 3341

SOLONS FOR ESSENTIAL JOBS!

Use SOLONS for the jobs that matter — this modern precision tool makes soldering speedier, simpler and more reliable. 5 models: 65 watt with oval tapered and round pencil bit; 125 watt with oval tapered and round pencil bit; 240 watt with oval tapered bit; each with 6 feet 3-core Henley flexible. Voltage ranges from 100 to 250.

W. T. HENLEY'S TELEGRAPH WORKS CO. LTD.
51-53 Hatton Garden, London, E.C.1

Write for Folder Y 10

HENLEY SOLON SOLDERING IRONS
FOR INDUSTRIAL USE

COMPONENTS, SURPLUS AND SECONDHAND

RADIO UNLIMITED, Elm Rd., London, E.17 offer speakers 4in 15 ohm 11/-, 5in 50 ohm 11/-, 8in 2.5 ohm 15/6, 5in 12/6, in 12/6, 8in 15/6, 10in 24/6; mains trans 500-0-500, 6v-4A, 5v-2A, 100ma 25/-; pend out trans tapped 3/9, V controls, L-sp., all values 2/9, W-sw 4/3, electr 450vw 4mf 1/6, 8 2/3, 16 3/-, A-x 16 4/-, 16+16 4/-, 32+32 5/9, 500vw 4mfd 5/-, 16 3/9, bias 25, 25 1/6, 50 50 2/3, part wired chassis with 5-gang, 465 i.fs, V & T controls, conds, resistors, etc., real value at 24/6 post free. [0062

WORK WANTED

LIGHT assembly work and chassis wiring by experienced craftsmen, single chassis or quantity.—Box 5679. [7925

PRECISION wave-winding; Govt. sub-contract work welcomed.—A. P. Crellon, 349, Copnor Rd., Portsmouth. Tel. No. 2175. [7922

SMALL manufacturer has capacity available for design and or assembly and wiring any type electronic equipment, prototype or production runs.—Box 6000. [7952

T.V. aerials erected, burglar alarms fitted, radio repairs undertaken; estimates free.—Rowes & Jupe, 46, Phipps Bridge Rd., Colliers Wood, S.W.19. Tel. Mitcham 4744. [7917a

DRAUGHTING, tracing and photoprinting services; estimates free; contractors to the Ministry of Supply and the Admiralty for drawing and tracing work to their requirements and specifications; sub-contracting work of this nature undertaken.
DRAWING & TRACING, Ltd., 456a, Ewell Rd., Tolworth, Surbiton. Tel. Elmbridge 7406. [5975

DESIGN and development drawings by competent designers and draughtsmen; existing schemes in the electro-mechanical fields developed or modified in accordance with customers' or Ministry specifications, whatever your draughting problems, ask for free estimate.
THE DESIGN & DRAUGHTING Co., 307, Malden Rd., New Malden, Surrey. Tel. Ma. 1979. [7912

WANTED, EXCHANGE, ETC

DURAL or alum tube 7in O.D.; large quantities.—Brit. 6651. [7852

VOIGT corner speaker only alternatively with modern P.M. unit.—Box 6002. [7954

LEAK, RC/PA/U, pre-amp quality tuner unit.—24, Meadow Bank, Manchester, 21. [7992

BM3A stabilising valves urgently required, any quantity purchased.—Apply Box 6003. [7958

BC939A and BC729 antenna tuning units, highest prices paid, state condition.—R.S. 6102. [8001

WANTED, dynamometer, a.c. test set, also oscilloscope type 339A, also L050A oscillator.
LESLIE DIXON & Co., 214, Queenstown Rd., Battersea, S.W.8. Macaulay 2159. [0176

DISC recording equipment of the highest quality, wanted urgently.—Flat 5, 169, George St., W.1. [7982

VALVES, unused surplus, any type, any quantity.—Details to City and Rural Radio, 101, High St., Swansea. [8051

WANTED, laboratory test equipment, including standard signal generator, watt meter, oscilloscope, bridges, recorders; send price and details to
HATFIELD INSTRUMENTS, 175, Uxbridge Rd., Hanwell, W.7. Tel. Ealing 0779. [0057

WANTED, HRO coils, Rxs, etc., A.R.88s, BC348s, S27s, etc.—Details to R.T. & I. Service, 254, Grove Green Rd., London, E.11. Ley. 4986. [0165

WANTED, set manufacturers' or ex-Government radio equipment, large or small quantities of valves, electrolytics, speakers, meters, also components.
LOWE BROS., 199, Mile End Rd., London, E.1. Ste. 2579. [6554

TRANSFORMER laminations and copper wire urgently wanted; top prices paid, or similar goods in exchange.—Porchester Electrical, 15-16, Gerrard St., London, W.1. [0211

VALVES, type 805, 807, 813, 832, 100th and 250th, urgently required; good prices paid.—Details Pype-Hayes Radio, 606, Kingsbury Rd., Birmingham, 24. Tel. Erdington 4942. [8025

WANTED, RCA speech amplifier type MI-11230 J or K and aerial tuning units BC939A.—Offers stating quantity and price to PCA Radio, The Arches, Cambridge Grove, W.6. [0080

WE pay highest price in the trade, modern test equipment, tape recorders, modern radio and television receivers, car radios, amplifiers, record-changers, etc., etc., call, write or send.
MILLER'S RADIO, 38a, Newport Court, Charing Cross Rd., near Leicester Sq. Tube. Ger. 4638. [7905

WANTED, BC-o/o Hallicrafter, RCA ET-4336 transmitter, SX-28 AR-88, S-27, HRO receiver and spare parts for above; best price.—Write Box 664, c/o Spiers Service, 82, Centurion Rd., Brighton, Sussex. [0081

THE "FLUXITE" QUINS AT WORK

"Our 'gram needs repairing I fear,
That auto-change acts pretty queer.
A touch of FLUXITE
Will soon stop the flight
Of these records that whizz past your ear!"

See that **FLUXITE** is always by you—in the house—garage—workshop—wherever speedy soldering is needed. Used for over 40 years in Government works and by leading engineers and manufacturers. Of all Ironmongers—in tins from 1/- upwards.

TO CYCLISTS! For stronger wheels that will remain round and true, here's a time tested tip. Tie the spokes where they cross with fine wire AND SOLDER. It's simple—with FLUXITE—but IMPORTANT.

The **FLUXITE GUN** puts **FLUXITE** where you want it by simple pressure. Price 2/6, or filled 3/6.

FLUXITE
SIMPLIFIES *ALL* SOLDERING

Write for Book on the Art of "SOFT" soldering and for leaflet on CASE-HARDENING STEEL and TEMPERING TOOLS with FLUXITE. Prices 1/- each.

FLUXITE LTD. (Dept. WW), BERMONDSEY STREET, LONDON, S.E.1.

PHILIPS
FOR SOUND INSTALLATIONS

PHILIPS

TRADE MARK,
PHILIPS ELECTRICAL LTD.

All enquiries to:

PHILIPS ELECTRICAL LTD.
DEPT. ELA AMPLIFIERS
Century House · Shaftesbury Ave.
London · W.C.2.

OR

C. W. CAMERON LTD.
(Sole Distributors for Scotland)
57, Oswald Street · Glasgow · C.1.

ARTO

ALPHA OFFERS

VOLUME CONTROLS. 100KΩ, ½ megΩ, ¼ megΩ, 1 megΩ, 2 megΩ, with S.P.S., 4/3 each. 25KΩ, 50KΩ, ½ megΩ, ¼ megΩ, 1 megΩ, 2 megΩ, with D.P.S., 5/- each. 50KΩ, ½ megΩ, ¼ megΩ, 1 megΩ, 1.5 megΩ, LESS switch, 2/3 each.

EX-GOVERNMENT SURPLUS—1KΩ, 2KΩ, 5KΩ, 20KΩ, 25KΩ, 50KΩ, 100KΩ, 120KΩ; ALL CARBON TRACK, 1/- each. 5Ω, 200Ω, 20KΩ, WIRE WOUND, 1/6 each.

STANDARD CAN CONDENSERS. 8 mfd., 450 V., 1/11 each. 16 mfd. 350 V., 2/9 each. 32 mfd. 350 V., 4/- each. 16 mfd. 500 V., 3/9 each. 24 mfd. 350 V., 4/9 each. 16 x 16 mfd. 450 V., 4/9 each.

SPEAKERS. 3in. 3Ω FOR PERSONAL SETS, 12/6 each, post 6d. Output Transformer to suit 15/4, 3/4, etc., 4/6 each. 5in. 3Ω lightweight, 12/6 each, post 9d. 8in. 3Ω lightweight, 14/6 each, post 1/-. 6½in. 3Ω with dust cover, 13/6 each, post 1/-. 10in. 3Ω robust job large magnet, 32/6, post 1/6. 6½in. 3Ω Mains energised 1500Ω field, 17/6 each, post 1/6. 8in. 3Ω Mains energised, 600Ω field, 15/9 each, post 1/6.

STANDARD 3 GANG. .0005 Mfd. Ceramic insulation ¼in. spindle, 7/- each.

HEAVY DUTY COOKER SWITCH. 4 Position Switch—Porcelain and Bakelite insulation, 4/- each, post 1/- ea.

CHOKES. Ex Government equipment, midget 15Ω 1H. 500 M.A. pitch dipped, 2/- each. Large type, 600 120 M.A., 5/- each.

MIDGET CHASSIS. Holes cut out for Valve Holders, Speakers, and Controls, etc., 1/- each. Post and Pkg. 1/-.

INDICATOR LAMPS. Single hole fixing, metal construction—as fitted on ex-Gov. telephone sets, etc., will take standard MES Bulb, 1/9 ea.

MICROPHONE INSERTS. Ex. Gov. by Truvox and Tannoy, 1/6 ea.

MOULDED MICA CONDENSERS. .0001, .0002, .0003, .0005, .0004, .00027, .01, .001, .002, .003, .005, .0008, .00005. All 5/6 doz.

METAL RECTIFIERS. 12 volt ½ amp., 1/- each. 2 volt ½ amp., 5/- each. 300 volt 80 M.A., 5/9 each. 280 volt 75 M.A., 5/6 each. 12 volt 3 amp., 18/6 each. 200 volt 60 M.A., 4/9 each.

CONDENSERS. .0001 mfd. 1,000 V., 4/6 doz. .01 mfd. 1,000 V., 7/- doz. .1 mfd. 350 V., 7/- doz., .01 mfd. 600 V., small type, 7/- doz. .02 mfd. 750 V., 7/- doz. 8 mfd. 450 V. D.C., 4/6 each.

MAINS TRANSFORMERS. Standard 3-way mounting suitable for 4 or 6 volts. 200-220-240 Primary. 350-0-350 V. 80 M.A. H.T. 0-4 V.-5 A., 6.3 V. 4A.-0-4 V.-5 V.-2 A., 16/- each. Post 1/6.

EX-GOVERNMENT WITH TAPPED PRIMARY. 350-0-350 V. 80 M.A. H.T. TWO 6.3 V. at 4 amps. 5 V. 3 A. Wax dipped, 25/6 each. Post 1/6.

HEADLAMP BULBS. 6-7 volts. 18 watts, 1/6 each.

BATTERY BUZZER. Brown Bakelite case, 1/6 each.

PLUG AND SOCKET. 5-pin 10H/254. Flexible plug, with chassis mounting socket, 2/- ea. 7-pin 10H/256. Flexible socket, with chassis mounting plug, 2/- ea. 2-pin 5C/591. Small flex connector 1/3 ea.

VIEW MASTER. Envelope for HOLME MOSS. All instructions. 5/- ea.

VALVE HOLDERS. AMPHENOL: B7G with base screen, 10/- doz.; International Octal, 7/- doz.; Mazda Octal, 4/- doz.; UX 5-pin, 2/6 doz. PAXOLIN: International Octal, 5/- doz.; 5-7 pin British, 5/- doz. B9G EF50 type, 6/- doz. Ceramic B9G, complete with retainer ring, 10/- doz.

Full range of condensers, resistors, etc., write for list (3d. stamp).

TERMS: Cash with order or C.O.D.

Please add 1/- postage under £1; 1/6 under £2.

ALPHA RADIO SUPPLY CO.

5/6 Vinces Chas., Victoria Square, LEEDS 1

WANTED, EXCHANGE, ETC.

COPPER wire and transformer laminations urgently wanted, top prices paid, or similar goods in exchange.—Porchester Electrical, 15-16, Gerrard St., London, W.1. [0212

DUMONT oscilloscope with double beam and 5BP1A tube; two or more wanted, any condition; money no object.—Please send details to Field, 68 Hurst St., B'ham, 5. [7989

WE purchase all types of domestic or ex-Government radio receivers and equipment, send full details of call and collect cash; large or small quantities.—Walton's Wireless Stores, 48, Stafford St., Wolverhampton. [0146

WANTED AN/APR-4 receiver, any units, any other good quality U.S. surplus radio and radar tubes, test sets, laboratory equipments, etc.; give condition and price in first letter.—Littell, Fairhills, Box 26, Dayton, 9, Ohio, U.S.A. [6546

WANTED, to buy or hire diagram and or service manual of U.S. Signal Corps receiver BC348N (not others); wanted, new meta. VT215 (6SR7) valve, wanted, Cossor Oscillator Mode 3343, good order essential.—Richardson, 11, Hillbrow Rd., Ashford, Kent. [7975

NOTICES

BRITISH SOUND RECORDING ASSOCIATION.
MEMBERSHIP of the Association is essential to all actively engaged or keenly interested in high quality sound recording and reproduction; the annual fee is most reasonable and within the reach of all; the 1951-2 lecture season is, as usual, very successful, and arrangements are also in progress to further increase our activities in the provinces; the publications of the association are extensive and include the journal, "Sound Recording and Reproduction", full information is given on list P.104, this also includes particulars and prices of our special and exclusive test records; membership of the association is world-wide and growing rapidly, particulars are given in the new brochure and this, with a membership application form and P.104, may be obtained from the membership secretary—Harrie J. King, 48, Mount View Rd., North Chingford, London, E.4, England. [0119

REPAIRS AND SERVICE

A SCOTTISH winding service.
ALL types of transformers, chokes, field coils, etc., rewound and manufactured to highest standards, write for details.—WILFLO PRODUCTS, 230-254, Brand St., Glasgow, S.W.1. Tel. No. Ibrox 0140. [7947

MAINS transformers rewound, new transformers to any specification.
MOTOR rewinds and complete overhauls; first-class workmanship, fully guaranteed.—F.M. ELECTRIC Co., Ltd., Potters Bldgs., Warser Gate, Nottingham. Est. 1917. Tel. 54555.

LOUDSPEAKERS repaired promptly.—Model Loudspeaker Service, 34a, Bullingdon Rd., Oxford. [6919

TELEVISION, trade servicing by highly skilled engineers.—F. H. Hellyar, Ltd., Riv. 5484-5. [8005

METROPOLITAN RADIO SERVICE regrets to advise that their transformer rewind service is temporarily suspended.—75, Kilburn Lane, London, W.10. [0150

MULLARD & Philips neg. feedback output trans., special rewind service, delivery by return, year guarantee.—A. McLuckie, 41, Lowther St., Carlisle. [7944

MAINS transformers rewound or constructed to any specification, prompt delivery.—Bede Transformer Co., Ltd., Bedeaway, Bede Trading Estate, Jarrow. [5198

REPAIRS.—E.H.T., mains and O.P. transformers, field coils and chokes, also armatures and motors; new transformers designed to any specification, all work fully guaranteed.—WILLESDEN TRANSFORMER Co., Ltd., 20a, Church Lane, Church Rd., N.W.10. Tel. Willesden 7095. [0076

ELECTRICAL measuring instruments of every make, multi or single range, repaired and standardised, prompt attention.—The Electrical Instrument Repair Service, 329, Kilburn Lane, London, W.9. Tel. Lad. 4162. [5715

BERNARD J. BROWN can supply individual designs and constructional data for radio/television amplifiers kits assembled or built to order; callers only by appointment.—33, Goldhawk Rd., Shepherds Bush, London, W.12. Tel. Riverside 3519. [0117

24-HOUR service, 6 months' guarantee, any transformer rewind, mains outputs and i.f.s., etc.; all types of new transf. etc., supplied to specification; business heading or service card for trade prices.—Majestic Winding Co., 180, Windham Rd., Bournemouth. [6520

A SERVICE with a smile, by F.R.I., great repair and winding service all speakers, output, f.f., coils, etc., mains, special trans and tele. rewinds all armature, fields, electric motor rewinds up to 1hp, engineering, electrical work, send it to F.R.I., they will help; outside television service, London and near; electrical contracting, experimental work.—79, Church Hill Rd., East Barnet. [0112

MISCELLANEOUS

OVER 500 copies "W.W." 1926-51, best offer secures.—Box 6127. [8008

GIVING YOU THE WORKS!

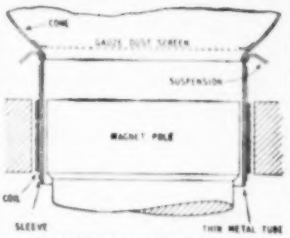

A "Wireless World" reader wrote to us recently and asked for more details of how our sound units work. He said that our monthly chat—and it is meant to be just that—interested him greatly but told him little! Of course our object is to create enough interest in your own mind to persuade you to seek the paper or postcard, fill your pen and write to us NOW for that extra information!

However, instead of our usual photo of a unit, here is a drawing of the famous dual drive with featherweight aluminium cylinder overwound with a skin of pure latex and the fine wire coil. This combination is unique; no other reproducer has it, and it is fully covered by patents here and abroad. The effect is threefold.

First, it forms a wide range dual drive with built-in crossover. Then second, the cylinder is a very low resistance closed circuit in the magnet field, thus acting effectively as a source of feedback and giving a remarkably flat impedance over the entire audio frequency range. Third, it imposes heavy critical damping on the whole system, so ironing out all resonances as well as making transients clean, clear and free from colouration.

The cone is also unique, being made by hand from special fabric, doped and pressed into shape with graded corrugations forming a smoothly varying compliance from near apex to rim. Its suspension is such as to give sufficient restoring force without flap, yet sufficient freedom for full bass without boom.

Magnets? More facts and figures? We've come to the end of our space, so what about sending us that card?

You can buy for cash or on H.P. from us or through a dealer.

BARKER NATURAL REPRODUCERS

3 Newman Yard, London, W.1

"GOODSELL of BRIGHTON"

offer

A COMPLETE
HIGH FIDELITY
EQUIPMENT
comprising

SA.8 Amplifier . . £15-15-0
PA.2 Tone Control £6-10-0
SP.1 Radio Tuner £10-10-0

TOTAL £32-15-0

Purchase Tax on Radio Tuner £5-5-0 extra

Sole Distributors:-
B.K. PARTNERS, Ltd.
229 REGENT STREET, LONDON, W.1.

"Quixo RADIO Coil Tester"

Accurate tests
High, Low and Grid
Bias Batteries.
Write for leaflet 30M

RUNBAKEN MANCHESTER 1

SAMSONS SURPLUS STORES

1951 AERIAL MASTS. R.A.F. Type 30. Complete kit consists of 9 tubular steel sections, length 45 ft., diameter 3in. Set of pickets. Top plate, guys and all fittings supplied brand new in canvas carrying bags. Ideal for T.V. Aerial Masts. **£8 10 -**. Carriage £4.

FIELD TELEPHONE. Type D.3. Complete with hand set. Single headphone. 2 1½ v. cells in perfect condition. **65 -**. Carriage 4/-.

FIELD TELEPHONE CABLE. Type D.3, on 1 mile drums. Unused **55 -**. Carriage 5/-.

MASTER VOLTMETER. 0-20 v. A.C. Moving iron 6in. mirrored scale by Meter Vickers. **25 -**. Carriage 3/6.

ALKALINE CELLS. 2.5 v. 11 A.H. **12 6**. Carr. 1/6. 2.5 v. 10 A.H. **10 6**. Carriage 1/-.

DESYNN TRIMMERS. 12 v. type No. 187. **10 6**. Carriage 1/-.

VARIOMETER INDUCTANCES. As used in the No. 19 set Variometer, **3/6**. Carriage 1/-.

CRYSTAL LAPEL MIKE INSERTS. Diameter 1¼in. **12 6**. Carriage 9d.

[69-171 Edgware Road London, W.2. Tel. Pad. 7851
125 Tottenham Court Road, W.1 Tel. EUS. 4982

All orders and enquiries to our Edgware Road branch, please. Open all day Saturday at the Edgware Road Branch.

MISCELLANEOUS

AUTOMATIC coil winder, reel carrier and wire tensioner, £35—Box 6150. [8017

METALWORK; all types cabinets, chassis, racks, etc., to your own specifications.—PHILPOTT'S METAL WORKS, Ltd. (G4BU), Chapman St., Loughborough. [0208

WALNUT radiogram cabinets, stamp leaflets.—Cabinetware, 1a, Heyes St., Blackburn.

WALNUT radiogram cabinet; stamp details.—E. Wisker, 501, Hale End Rd., Highams Park, E.4. [6942

BOUND volumes "W.W." 1920-1939, also many unbound. Q.S.T., offers.—Grove House, The Common, Gerrards Cross. [7916

WALNUT radiogram and television cabinets, soundly constructed, stamp details.—R. Shaw, 69, Fairlop Rd., Leytonstone, E.11.

QTY. 20 and 21 s.w.g. d.c.c. fine, also 46 s.w.g. enamelled, 28 s.w.g. paper on enamel, wires.—Champion, 45, Uplands Way, London, N.21. [0102

SELENIUM photo-electric cells, 40×22mm., 7/6, all standard photo-cells in stock, photo-electric exposure meter kits, 57/6 and 42/6. Neon indicator lamps, 110/250 v., 15/- per dozen.—G.R. PRODUCTS, 22, Runnymead Avenue, Bristol, 4. [7996

TV. cabinets, baffles, consoles, etc., to your own design measurements and finish; no enquiry too small or too large.—Write or 'phone, Ashdown, 98, Hertford Rd., N.9. Tot. 2621. [7984

ENGRAVING.—On all metals and plastics, name plates, panels, dials, instruction panels, advertising novelties, etc., etc., trade enquiries invited.—E. S. Reddish, 17, Standard St., New Kent Rd., S.E.1. Hop. 0505. [7949

ENGRAVING, amateurs and trade could take the opportunity of engraving problems in the future by getting in touch with A. G. Engraving 13a, Windmill Rd., London, S.W.18. Brass, bronze, erinoid, Perspex dials; one knob or repetition equally entertained. [0054

ALLSCREWS, Ltd., for B.A. screws, nuts, washers, studding, grub-screws, bolts, soldering tags, woodscrews, etc., plain or nickel or cadmium plated, one-gross packets or large quantities, stamp for lists.—270a, King St., Hammersmith, W.6. Riv. 7762. [5426

COPPER wires enamelled, tinned, Litz, cotton, silk covered, all gauges, B.A. screws, nuts, washers, soldering tags, eyelets, ebonite and laminated bakelite panels, tubes, coil formers, Tufnol rod, headphones, flexes, etc.; latest radio publications, full range available, list, s.a.e. Trade supplied.—Post Radio Supplies, 55, Bourne Gardens, London, E.4. [0138

TV-ITIS; a complaint suffered by many who have no black screen; our conversion kit will change your ordinary television set into a black screen set; price 9/6, post free, will fit any size of set from 12in. tube downwards, no suckers, no screws, no glue, and can be removed and replaced at any time; trade enquiries invited.—Unit Light Manufacturing Co., 19, Queen St., Blackpool. [7995

FLUORESCENT control ballast, wired, tested, ready for 5ft. 80v. tube, 250v. a.c., 49/5, 80w. brick choke, 22/6. Glow starter lamps, 5/5, battery chargers, 250v. will charge 6v. battery at 5 amps, meter, leads, 57/6, metal rects., 12v. 2amp full-wave, 8/9, dry battery chargers, 250 a.c., all types up to 3v. and 2v. accumulators, 16/6.—Malden Transformer Supplies, 202, Cambridge Rd., Kingston-on-Thames. [0058

SITUATIONS VACANT

ADMIRALTY.

APPLICATIONS are invited from engineering electrical and ship draughtsmen for temporary service in Admiralty Departments at Bath.

CANDIDATES must be British subjects of 21 years of age and upwards, who have had practical workshop and drawing office experience.

SALARY will be assessed according to age qualifications and experience within the range £520-£545 per annum.

APPLICATIONS, giving age and details of technical qualifications, apprenticeship (or equivalents), workshop and drawing office experience, should be sent to Admiralty (C.E. II, Room 081), Empire Hotel, Bath. Candidates required for interview will be advised within two weeks of receipt of application. [6952

RADIO Engineers

WE have vacancies for several good class radio engineers, must be able to drive car, permanent posts and good wages for the right men. APPLICANTS should apply in own handwriting, stating age and giving full particulars of training and experience to—JAMES McKENZIE, Ltd., 25, Oxton Rd., Birkenhead. [7942

RADIO and television.

WANTED.—Man with good experience of the technical side of television and radio, must be capable of doing repairs to all makes of television sets, this is a permanent pensionable post and offers good scope to a man with high technical knowledge.—Reply, stating age, experience, and wage required, to Box 6096. [7985

HARRODS, Knightsbridge, require an experienced television and radio engineer.—Apply to Staff Manager, 44, Hans Crescent, S.W.1. [7936

NEW S.T.C. SELENIUM RECTIFIERS. Largest L.T. range in Great Britain. Current products. NOT SURPLUS. E.H.T. N2/100 17/-; for "W.W." Televisor, for VR97 N2/50, 12/-; Post 6d. PRIORITY ORDERS ONLY.

NOTE REVISED PRICES 1st JUNE, 1951

HALF WAVE HEAVY DUTY 7¼in. SQUARE COOLING FINS. 16 v. 5 a., 26/-; 10 a., 29/-; 16 a. 53/-; 30 v. 5 a., 41 6; 8 a., 47/-; 40 v. 2.5 a., 31/-; 5 a. 56/-; 8 a., 65/-; all post 1/-.

BRIDGE CONNECTED FULL WAVE. 17 v. 1.25 a., 14 2; 1.7 a., 22 9; 2.5 a., 25/-; 3 a., 26/-; 4 a., 30/-; 5 a., 32 6; all post free. 33 v. 7 a. or 0.7 a. or 6.5 a., 21/-; 1 a., 24 3; 1.5 a., 39/-; 2 a., 44/-; 3 a., 45/-; 4 a., 54/-; 5 a., 58/-; all post 11d. 54 v. 1 a., 33 6; 1.5 a., 54/-; 2 a., 60/-; 3 a., 61/-; 5 a., 81/-; 72 v. 1.5 a., 68/-; 2 a., 79/-; 3 a., 80/-; 5 a., 106/-; 100 v. 1.5 a., 97/-; 2 a., 112/-; 5 a., 152/-; all post 1/-.

BRIDGE CONNECTED HEAVY DUTY 7¼in. SQUARE COOLING FINS. 17 v. 6 a., 43/-; 10 a., 49/-; post 1/6.

BRIDGE CONNECTED HEAVY DUTY Funnel Cooled, also **7¼in. SQUARE COOLING FINS.** Revised price, same both types. 17 v., 12 a., 88/-; 20 a., 102/-; 30 a., 142/-; 50 a., £11; 33 v. 6 a., 79/-; 10 a., 91/-; 12 a., 146/-; 20 a., 164/-; 54 v. 6 a., 104/-; 10 a., 124/-; 72 v 6 a., 134/-; 10 a. 154/-; 100 v. 6 a., 192/-; 10 a., £11; all post 1/8.

SOME G.E.C. & "WESTINGHOUSE" RECTS. NOW STOCKED. VERY SLOW DELIVERY OF MANY RECTS. WILL DO OUR BEST! HOSPITALS, RESEARCH LABS. AND GOVERNMENT CONTRACTS GIVEN PRIORITY.

Wholesale & Retail

T. W. PEARCE (Est. 20 yrs.)
66 GREAT PERCY STREET, LONDON, W.C.1
Off Pentonville Rd. Between King's Cross and Angel

LOCKWOOD
makers of
Fine Cabinets
and woodwork of every description for the Radio and allied trades

LOCKWOOD & COMPANY
Lowlands Rd., Harrow Middlesex. Byron 3704

WEST END RADIO LTD.
Estd. 20 YEARS
FOR RADIO BARGAINS

Electronic Stethoscopes as used for the detection of bomb fuses. Containing the following:—

2 crystal microphones on magnetic bases (one underwater type), 3 valve battery amplifier, 'phones, etc., packed in metal case. 11 x 7 x 5in.

Brand new, **59 6.**

0-250 v. A.C. Meters, 2½in., new, boxed, **25/-.**

0-500 Micro-amp Meters, 2in., scaled 0-10 volts, D.C., **7 6.** Brand new.

0-30 M A Meters, 2in. D.C. New, boxed **6 11.**

CR100 11-valve Communication Receivers ex-Navy for 200-250 v. A.C. operation. Send 6d. for illustrations. As new, **£39 10/-.**

Thousands of bargains for callers. Please enclose postage with order.

WEST END RADIO LTD.,
14, LISLE ST., LEICESTER SQUARE, LONDON, W.C.2. Phone GER 7341
OPEN ALL DAY SATURDAY.
NO LISTS AT PRESENT.

GALPINS
ELECTRICAL STORES

408 HIGH ST., LEWISHAM, LONDON, S.E.13

Tel.: Lee Green 6309 *Near: Lewisham Hospital*

TERMS: CASH WITH ORDER NO C.O.D.
All goods sent on 7 days' approval against cash.

EARLY CLOSING DAY THURSDAY

MAINS TRANSFORMERS (NEW), input 200/250 volts in steps of 10 volts output 350-0-350 volts 300 m/amps, 6.3 volts 8 amps twice, 4 volts 4 amps, 5 volts 4 amps **65/-** each, carriage 3/6, ditto, 450-0-450 volts 250 m/amps 6.3 volts 8 amps twice 4 volts 4 amps, 5 volts 4 amps **65/-** each carriage 3/6, another input as above, output, 500-0-500 volts 250 m/amps 6.3 volts 8 amps twice 6.3 volts 4 amps, 4 volts 4 amps, 5 volts 4 amps, **70/-** carriage 3/6. Another, wound to (electronic) specifications, 350-0-350 volts 250 m/amps 4 volts 8 amps, 4 volts 4 amps 6.3 volts 8 amps, 0-2-6.3 volts 2 amps **63/6** each carriage paid, another input as above output 500-350-0-350-500 volts 250 m/amps 6.3 volts 6 amps 0-2-6.3 volts 2 amps, 0-4-5 volts 4 amps twice, **67/6** each, carriage 3/6.

SWITCH-BOARD METERS, 4 inch scale moving coil (D.C.) only 0 to 14 amps **17/6** each, post 1/6. Ditto, A.C./D.C., **22/6** each, post 1/6, another 0 to 30 amps A.C./D.C. **25/-**, post 1/6.

MAINS TRANSFORMERS (NEW). Input 200/250 volts in steps of 10 volts, outputs, 350-0-350 volts 180 m/amps 4 volts 4 amps 5 volts 3 amps, 6.3 volts 4 amps **39/6** each, post 1/6, another 350-0-350 volts 180 m/amps 6.3 volts 8 amps, 0/4/5 volts 4 amps, **39/6** each, post 1/6, another 500-0-500 volts 150 m/a. 4 volts 4 amps C.T., 6.3 volts 4 amps, C.T., 5 volts 3 amps, **42/6** each, post 1/6, another 425-0-425 volts 160 m/amps 6.3 volts 4 amps, C.T. twice 5 volts 3 amps, **42/6** each, post 1/6.

DOUBLE WOUND VOLTAGE CHANGER TRANSFORMERS 3,000 watts, 110 to 240 volts or vice versa, weight 100 lbs. **£10/10/-** each carriage 10/-.

EX-RADAR MAINS TRANSFORMERS 230 volts input 50 cycles 1 phase, output 4500-5500 volts approx. 80 m/amps 6.3 volts 2 amps, 4 volts 1½ amps 2 volts 2 amps, these transformers are new immersed in oil, can be taken out of the oil and used as television transformers giving output of 10 m/amps, overall size of transformers separately 5½in. x 4¼in. x 4in. and 3in. x 3in. x 2½in., price **£3/10/-** each carriage paid.

ROTARY CONVERTERS. 24-28 volts D.C. input, 1,200 volts 70 m/amps D.C. output, **10/-** each, P.F.

MAINS TRANSFORMERS (NEW) suitable for spot welding, input 200/250 volts, in steps of 10 volts, output suitably tapped for a combination of either 2/4/6/8/10 or 12 volts 50/70 amps, **87/6** each, carriage 7/6.

AUTO-WOUND VOLTAGE CHANGER TRANSFORMERS, tapped 0/110/200/230 volts 350 watts, **48/6** each, post 1/6, as above but 500 watts 62/6 each carriage 3/6 as above 200 watts, **35/-** each post 1/6.

RECTIFIERS (NEW) D.C. output 36 volts 50 amps, complete with mains transformer 230 volts A.C. input 50 cycles 1 phase output to match the required voltage for the rectifier, **£15/-/-** per set, carriage 10/-.

EX-NAVAL ROTARY CONVERTERS, 110 volts D.C. input, output 230 volts A.C. 50 cycles, 1 phase, 250 watts capable of 50% overload, weight 10 lbs., price **£10/10/-** each, carriage forward.

ELECTRIC LIGHT QUARTERLY TYPE CHECK METERS, all for 200/250 volts A.C. 50 cycles 1 phase, 5 amp load, **17/6** each, post 1/6, 10 amp **21/-** each, post 1/6, 20 amp load, **25/-** each, post 1/6.

MAINS TRANSFORMERS (NEW), 200/250 volts input, in steps of 10 volts, outputs, 0, 6, 12, 24 volts 6 amps, **37/6** each, post 1/6. Another as above but 10-12 amps **48/6** each, post 1/6, another as above but 25/30 amps, **70/-** each, carriage 1/6, another input as above, output 0/18/30/36 volts, 6 amps **42/6** each, post 1/6.

EX-R.A.F. ROTARY CONVERTERS. 24 volts D.C., input 50 volts, 50 cycles, 1 phase at 450 watts output, complete with step-up transformer 50 to 230 volts, **£9/10/-** each, carriage 10/-.

EX-U.S.A. W.D. ROTARY TRANSFORMERS, 12 volts D.C. input, 500 volts, 50 m/amps, 275 volts 100 m/amps D.C. output. Complete with smoothing switches, fuses, etc., as new, **17/6** each, carriage 2/6, can be run on 6 volts giving half the stated output.

VARIABLE RESISTANCES, 9 ohms, 4 to 12 amps, **30/-** each.

SYNCHRONOUS F.H.P. MOTORS, complete with a large selection of gear wheels 200/250 v., A.C. mains, **14/6** each.

MAINS TRANSFORMERS, 230 v. input, 150-0-150 v., 200 m.a., 6.3 v. 8 amps, 5 v. 2 amps output, **21/-** each.

SITUATIONS VACANT

CROWN Agents for the Colonies.

RADIO officer required by the East Africa High Commission for the Directorate of Civil Aviation for one tour of 48 months in the first instance. Commencing salary according to age and experience in scale £550 rising to £715 a year. Cost of living allowance between £262 and £1,107 a year according to salary. Gratuity between £74 and £96 a year payable on the satisfactory completion of service. Outfit allowance £50. Free passages. Candidates, under 40, should hold a First-Class Certificate of Proficiency in Radio Telegraphy issued by the Ministry of Civil Aviation; or alternatively hold the Provisional Aircraft W/T Operator's Licence and have had not less than 1,000 hours' flying experience on civil aircraft.—Apply at once by letter, stating age, full names in block letters, and full particulars of qualifications and experience, and mentioning this paper to the Crown Agents for the Colonies, 4, Millbank, London, S.W.1, quoting on letter M.25107/B. The Crown Agents cannot undertake to acknowledge all applications and will communicate only with applicants selected for further consideration. [7978

TECHNICAL engineer, to take charge of layout and planning of special electronic products.
TECHNICAL manager to control transformer production.—Write details of experience to All-Power Transformers, Ltd., Chertsey Rd., Byfleet, Surrey. [7965

DIGITAL computors.—There are vacancies in the Computer Section of Ferranti, Ltd., for the following:—
(a) CIRCUIT engineer, experienced in pulse or radar circuits with an interest in the development of circuits associated with high speed mechanical devices; some mechanical engineering background is desirable but not essential.—Ref. D.C.C.
(b) MECHANICAL engineer with wide experience in design of precision high speed mechanical devices, an interest in electronics is preferred but not essential.—Ref. C. Mech.
(c) ENGINEER with wide experience of magnetic recording equipments required for interesting new project.—Ref. D.C. Mag.
SALARY for the above posts will be in accordance with experience and ability, in the range £520—£1,000 per annum; contributory pension scheme in operation.
FORMS of application from Mr. R. J. Hebbert, Staff Manager, Ferranti, Ltd., Hollinwood, Lancs. [7865

TRANSFORMER designer for design and quality control of transformers for electronic apparatus.—Box 6095 [7969

APPLICATIONS are invited for posts as lecturers at the R.E.M.E. Training Centre, Arborfield, under the War Department.
QUALIFICATIONS required:—A degree in electrical engineering or an equivalent qualification; experience in light current, radio or radar engineering is essential.
SALARIES will be in accordance with the Burnham Technical Scale for Assistants B and will allow for the special incrementis, etc., attaching to degree and other special qualifications; a special £75 non-pensionable allowance is also payable.
THE service will reckon as contributory under the Teachers Superannuation Acts.
FULL particulars and forms of application may be obtained from the Under-Secretary of State, The War Office (M.E.1), London, S.W.1. Closing date for applications, 11th February, 1952. [8024

ELECTRICAL and radio draughtsmen required.—Apply Employment Manager, Vickers-Armstrongs, Ltd. (Aircraft Section), Weybridge, Surrey. [7875

EXPERIENCED radio and television engineer required, permanent position, good wages.—Apply Maxwell & Sons, Ltd., 45, Hill Rd., Wimbledon. [7956

ROOTES Group distributors and Radiomobile accredited dealers in Newport, Mon. require mechanic to install and repair car radios in new and used vehicles.
APPLICANTS must be prepared to attend H.M.V. Course, conform to Radiomobile standards and be in charge of radio stores and equipment.
REPLY in writing to Secretary, F. N. Morgan & Co., Ltd., 57, Chepstow Rd., Newport, Mon. [7945

FIRST-CLASS Electronic Engineers of British nationality are invited to join a company located in country surroundings in the South West of—but close to—London.
THE company's operations which are on a considerable scale are solely concerned with pure research and development work in the fields of electronics, electricity and intricate mechanisms.
THE working conditions are ideal and the scientific equipment is plentiful and of high quality.
THE positions offered are permanent, the salary will be generous and there is a pension scheme.
APPLICATIONS in the first place will be seen by the managing director only and there need be no apprehension in the mind of any intending applicant of any breach of confidence.
APPLICATIONS should contain full personal particulars, details of education and all positions held subsequently and should be addressed to "the Box number given and marked "Managing Director."—Box 5676. [7917

COIL PACK
Model 320

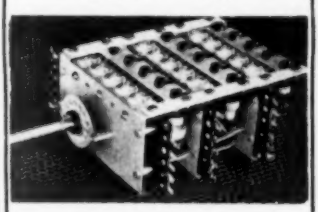

5-waveband coil unit.

A comprehensive pre-aligned assembly consisting of switch, complete set of aerial, H.F. and oscillator coils and all associated trimming and padding condensers for 5-waveband operation with tuned H.F. stage on all bands. All coils have dust iron cores for inductance adjustment. A six position switch is used with provision for pick up connections and H.F. muting on the sixth position. For use with any of the standard frequency changer valves (6K8, ECH35 etc.) and an I.F. frequency of 470 Kc.

Ranges: 1, 13—40. 2, 30—100. 3, 80—200. 4, 200—550. 5, 900—2000 metres.

Price £5.5.0 plus tax.

All parts for the above can be supplied separately if required (tax free).

Circuit diagram of this pack is available free.
Send S.A.E.

Circuit diagrams for complete receivers are in course of preparation together with calibrated glass scale and scale plan.

TELEVISION COMPONENTS

"*Electronic Engineering*"—
Focus Coil
Deflector Coils
Line Output Transformer

Deflector Coils and Line Output Transformers suitable for Viewmaster are also available.

I.F. TRANSFORMERS Iron Core Tuned 472 Kc. Per pair, **15/-**

ALLEN
COMPONENTS LTD

CROWN WORKS,
197, LOWER RICHMOND ROAD,
RICHMOND, SURREY.

'Phone: Prospect 4463

ELECTRADIX
for Satisfaction

PANORAMIC RADIO ADAPTORS. Navy Model R.B.W.8. CPN-55090-A Max Sweep Width 100 Kc/s. Input frequency 5.25 Mc/s. Power Source 115/230 volts A.C. 50/70 cycles Sweep Frequency adjustment 30 cycles, complete with Tubes and cathode ray Tube. **£55.** Ex. London Stores.

METERS. Ammeter D.C. moving coil 0-20 amps., with shunt 2in. panel **9/6.** 0-50 amps. 2in. panel **9/6.** 0-20 volts **7/6** 2in. panel. Postage 9d. Electrostatic Voltmeters, Everett Edg. 1500 volts 2½in. flush panel **65/-.**

A.C. Switchboard Meters 500 volts 5in. flush panel Crompton Parkinson with external Resistance **65/-.** G.E.C. 4½in. S.bd. 0-60 volts **55/-.**

RESISTANCES, var. sliders, 152 ohms 2 amps. **30/-**; 5 ohms 10 amps. **27/6**; 6½ ohms 5 amps. **25/-**; 300 ohms ½ amp. **18/-**; 1.2 ohms 15 amps. **12/6.**

ROTARY CONVERTERS, 100 watts 24 volts D.C. to 230 volts A.C. **75/-,** carr. 5/-. 200 watt 230 volts D.C. to 230 volts A.C. **£12 10/-.** 200 watts 110 volts D.C. to 230 volts A.C. **£10.** Carr. 10/-. 1 K.W. 220 volts D.C. to 230 volts A.C. **£25.** Carriage 10/-.

METAL RECTIFIER UNITS. Westinghouse. 50 volts 5 amps. **£9 10/-.** 50 volts 1½ amps. **£6.** 50 volt ½ amps. **£4 10/-,** all for 230 volts A.C. 50 cycle input. Battery chargers for all sizes made to specification.

Hewitic Type Rectifier by E.C.C. 365/440 volts 3-ph. 50 cycles input 110 volt 18.2 amps. 2 K.W. output ammeters, voltmeter, in ventil. metal case with new Hewitic type valve.

MOTORS. A.C. 50 c.s. 230 volt ¼ H.P. 1425 r.p.m. **£5 10/-**; ½ H.P. 230 volt 1425 r.p.m. **£8 10/-**; ¾ H.P. 110 volts A.E.G. 1400 r.p.m. **25/-**, carr. 2/-. ¼ H.P. 400 volt 3-ph. 1425 r.p.m. **£9** carriage extra at cost.

D.C. Motors 230 volt ¼ H.P. shunt wound 1425 r.p.m. **£4 10/-**, 24 volt starter Motors, new **25/-**; 12 volt ½ H.P. high speed **55/-**, carr. 5/-.

ELECTRADIX RADIOS

214 Queenstown Road, London, S.W.8

Telephone: MACaulay 2159

QUALITY TELEVISION COMPONENTS

HR

Scanning and Focus Coils
P.M. Focus Units
5/10 Kv. R.F. E.H.T. Units
E.H.T. and Output Transformers
Line fly-back E.H.T. Units
"TELEVISION CIRCUITS"
3rd Edition, 2/6

HAYNES RADIO Ltd.

Queensway Enfield Middlesex

THE *HAYES RG/135*
RADIOGRAM CHASSIS

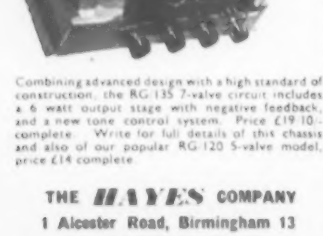

Combining advanced design with a high standard of construction, the RG.135 7-valve circuit includes a 6 watt output stage with negative feedback, and a new tone control system. Price £19 10/- complete. Write for full details of this chassis and also of our popular RG.120 5-valve model, price £14 complete.

THE *HAYES* COMPANY

1 Alcester Road, Birmingham 13

Telephone: South 0202

SITUATIONS VACANT

RADAR mechanics, ex-R.E.M.E. or others with experience of service radar.—Write details of experience to All-Power Transformers, Ltd., Chertsey Rd., Byfleet, Surrey. [7967

ELECTRONIC testers, for test and repair of special electronic equipments.—Write details of experience to All-Power Transformers, Ltd., Chertsey Rd., Byfleet, Surrey. [7968

TELEVISION and radio engineer required in Epsom/Ewell district, good wages and working conditions, able to drive, write full details of experience, etc., to—Box 5856. [7946

TRANSFORMER winding foreman to take complete charge of small shop.—Write details of experience to All-Power Transformers, Ltd., Chertsey Rd., Byfleet, Surrey. [7966

THERMIONIC technical assistant; must be keen on industrial electronics, some experience of audio equipment.—Please apply The Rover Co., Ltd., Lode Lane, Solihull. [7659

EXPERIENCED radio and television engineer required, permanent position, good salary and conditions.—Edwin P. Fox, Murphy Dealers, East Molesey, Surrey, Molesey 2721. [8014

JUNIOR electronic engineer required for development department of old-established company in Surrey.—Apply, giving details of age, experience and salary required, to Box 5855. [7957

SERVICE engineer required for Audio-frequency amplifier, preferable with some experience of sub-standard cine projectors.—Burgess Lane and Co., Sunleigh Works, Sunleigh Rd., Wembley 2578. [7994

E. K. COLE, Ltd. (Malmesbury Division), invite applications from electronic engineers for permanent posts in development laboratories, engaged on long-term projects involving the following techniques:—
1. Pulse Generations & Transmission.
2. Servo Mechanisms.
3. Centimetric & V.H.F. Systems.
4. Video & Feedback Amplifiers.
5. V.H.F. Transmission & Reception.
6. Electronics as applied to Atomic Physics.
THERE are vacancies in the senior engineer, engineer and junior grades. Candidates should have had at least three years' industrial experience in the above types of work, together with educational qualifications equivalent to A.M.I.E.E. examination standard. Commencing salary and status will be commensurate with qualifications and experience. Excellent opportunities for advancement are offered with entry into Pension Scheme after a period of service. Forms of application may be obtained from Personnel Manager, Ekco Works, Malmesbury, Wilts. [7822

YOUNG man, ex-National Service, required to assist in VHF radio installation work; excellent opportunity for an ambitious person keen to make a career in radio.—Write, giving full details and wage required, to Box 6094. [7976

TELEVISION/RADIO engineer required urgently, must be good, comfortable situation; very fine prospects, good wages, holidays and illness paid for.—Godwins (Stoke-on-Trent), Ltd., Liverpool Rd., Stoke-on-Trent. [8020

TELEVISION and radio engineers required for service department, able to drive service van, permanent positions with good working conditions, discount on store purchases. Write or call Staff Controller, Bentalls of Kingston. [7925

ADMIRALTY.—Vacancies exist for electrical and/or mechanical engineering draughtsmen in Admiralty Research and Development Establishments located in the vicinity of Weymouth, Portsmouth, Teddington (Middlesex) and Baldock, Herts.
DRAUGHTSMEN experienced in light current, electro-mechanical, precision mechanical and electronic equipment are particularly needed.
CANDIDATES must be British subjects of 21 years of age and upwards, who have had practical workshop experience (preferably an apprenticeship) together with Drawing Office experience.
APPOINTMENTS will be in an unestablished capacity, but opportunities will occur for qualified staff to compete for established posts.
THE salaries offered, depending on age, experience, ability and place of duty, will be within the range £520-£575 p.a.
HOSTEL accommodation is available at some establishments.
APPLICATIONS, stating age and details of technical qualifications, apprenticeship (or equivalents), workshop and drawing office experience, should be sent to Admiralty (C.E.11), Room 951, Empire Hotel, Bayswater, quoting DM.R.D. Personal testimonials should not be forwarded with application. Candidates required for interview will be advised within two weeks of receipt of application. [7858

MECHANICAL engineer, fully qualified, for N. London electronic factory; previous mass production exp. essential; salary up to £1,500 p.a.; interviews in London.—Applications, which should give fullest particulars, will be treated in confidence.—Write Box 5678. [7919

TELEVISION engineers required by E. London firm with all leading agencies; applicants should have extensive experience and initiative, and will work with 1st class team of engineers; salary according to ability.—Apply to "LB," Leytonia Radio, 828, High Rd., Leyton, E.10. [8022

The House for Quick Delivery

The following Goods Ex-Stock.

Cash with Order or C.O.D.

PLESSEY Multi-Speed Auto Record Changer. 10in.-12in. at 78 r.p.m. 10in.-12in. at 33⅓ r.p.m. 7in. at 33⅓ r.p.m. 7in. at 45 r.p.m. Virtually no needle changing. Simple design and construction, extremely easy to operate. Price including Tax, **£23/13/-.**

B.S.R. G.U.4. Three Speed Gramophone Unit complete with lightweight Pick Up, and High Fidelity crystal Head. Price including Tax, **£9/19/11.**

Limited number of G.E.C. Multi-Beam Loudspeakers. List Price **£35.** My Price **£18/10/-.** New, in original packing. Carriage extra.

DECCA 3 speed Motors with turntable ready for mounting, **£7/3/4.**

ACOS G.P. 20, complete with either Standard or L.P. Heads, **£3/11/5.**

ACOS Heads, Standard or L.P., **£2/3/4.**

GARRARD Standard Playing Unit with Pick-Up, **£6/3/2.**

COLLARO Standard Playing Unit with Pick-Up, **£6/10/4.**

LEAK TL.12 Watt "Point One" Feedback Amplifier, **£28/7/-.**

LEAK RC.PA.U. Remote Control Pre-Amplifier, **£9/9/-.**

LEAK V.S. Superhet Tuner Unit complete with Valves, **£37/2/4.**

Send me your order for all your:
Wharfedale Speakers. Test Meters—Avo, Taylor, Advance. Valves. Components.

Please note these prices are subject to any increase by the makers due to rise in costs.

A. ERNEST BUCHAN

(M.O. Dept.), 28 Belmont Street.

Aberdeen. Phone 23579.

J. C. LADD WHOLESALE

NEW BOXED VALVES. ALL GUARANTEED. LISTS FREE.

1R5	6B66	6Q7	50L6	EBC33	8D3
1S5	6D6	6R7	807	EF39	KT66
1T4	6F12	6V6	B36	EF50	MU14
3S4	6J5	6X5	DK91	EF55	SU2150
5U4	6J7	7S7	DAF91	EF92	8P61
5Z4	6K7	12K7	DF91	EL91	U50
6AG5	6K8	12K8	DL92	PW4/500	X61
6AM6	6L6	35L6	DL94	HVR2	Y63

Some types available in manufacturer's quantities. THO
J. C. LADD, 57 DAGNALL PARK, LONDON, S.E.25. 1665

G.E.C.

GERMANIUM CRYSTAL DIODES

LATEST, SMALLEST, SUPREME CRYSTAL DETECTOR
Midget Size, 5/16in. x 3/16in.
Wire Ends for Easy Fixing.
4/6 each, postage 2½d.

Technical Details and Selected Types available.
SILICON DIODES, 3/6. Postage 2½d.
Fixing Brackets, 3d. pair.

COPPER INSTRUMENT WIRE
ENAMELLED, TINNED, LITZ,
COTTON and SILK COVERED
Most gauges available.
B.A. SCREWS, NUTS, WASHERS,
soldering tags, eyelets and rivets.
EBONITE AND BAKELITE PANELS.
TUFNOL ROD, PAXOLIN TYPE COIL FORMERS AND TUBES, ALL DIAMETERS.
ERIE AND DUBILIER RESISTORS.
Latest Radio Publications.

SEND STAMP FOR LIST TRADE SUPPLIED

POST RADIO SUPPLIES

33 Bourne Gardens, London, E.4

GEE RADIO LTD.

931A PHOTO-ELECTRIC MULTIPLIERS. American **30/-** each.

C.M.G. 22 PHOTO-CELLS. Osram. **25/-** each.

50 OHM 40 WATT W.W. OR PORCELAIN POTENTIOMETERS. 3in. dia. **7/6** each.

10in. ELAC 3 OHM P.M. LOUDSPEAKERS. **25/-** each.

12in. P.M. TRUVOX 3 ohm speakers, **60/-** each.

3½in. C.R.T. VCR 138 (ECR35). Complete with mu-metal screen and base. **40/-**.

465 KC. I.F. TRANSFORMERS. (Wearite). Type S52 or semi-midget, ditto by Plessey, **10/6** per pair.

MAINS TRANSFORMERS. Primary 200-250 v. tapped Sec. 350-0-350 at 150 mA., 6.3 v. at 4 amp. 5 v. at 2.3 amp (Ex-E.M.I.). **25/-** each.

DITTO. 425-0-425 at 200 mA. L.T.'S 6.3 v at 2.3 amp. 6.3 v. 4.6 amp. or 4 v. at 2.3 amp. 5 v. at 2-3 amp. or 4 v. 3-6 amp. with connection instructions **65/-**.

METERS.
100 Micro-amp. 2½in. round flush mounting, s aled as 0-1500 yds. **25/-**.
2½in. round 0-20 amp. A.C. Moving iron flush mounting **12/6**.
2½in. round 0-15 v. A.C. Moving iron flush mounting **12/6**.

RECTIFIERS.
J.50 400 v. H/W at 2 mA. **6/9** each.
5 mA. meter rectifiers, **7/6** each.
280 v. H/W. 80 mA. **6/-** each.
12 v. 4 amp. F/Bridge, **18/6** each.
12 v. F/Bridge at 2 amps. **12/6** each.
24 v. F/Bridge at 1 amp. **15/-** each.
R.M.1. and 2.125 v. H/Wave at 60 and 80 mA. **4/-** each.
R.M.3. 125 v. H/Wave 100 mA. **5/-** each.

100 KC. R.C.A. OR BRILEY 3-PIN CRYSTALS, American **20/-** each.

9 HENRY 120 MA. SMOOTHING CHOKES, **10/6** each.

16 mm. BELL & HOWELL SOUND PROJECTORS, complete, reconditioned in good order. Utility model **£65.** Master Model **£98.** B.T.H. model as above **£105.**

COLLARO MOTORS for tape recorders. Clock or anti-clock rotation any type, **42/-** each.

12in. C.R.T. WHITE MASKS, slightly soiled **10/9**.

2 GANG .0003 TUNING CONDENSERS, with trimmers & spindle **3/9**.

R.1155 POWER SUPPLY UNIT. Complete with output stage. In good condition, **70/-**.

ALUMINIUM SHEET undrilled. 16 S.W.G. sizes available 12in. x 12in. 24in. x 12in. 24in. x 24in., 36in. x 24in., 36in. x 36in., **5/-** per square foot.

EXIDE 2 v. at 15 ampere Ex-Govt. Accumulators, **4/6** each.

The above are a few only of the many items available from stock. All goods offered are ex-manufacturers or ex-Govt., and in perfect condition unless otherwise stated.

Terms: C.W.O., C.O.D. or Pro-forma. Orders under 20/- plus 1/6 for P.P. British Isles only.

15 LITTLE NEWPORT ST., LONDON, W.C.2

GERrard 6794 1453

SITUATIONS VACANT

RADIO mechanic required for high priority electronic and light mechanical work in equipment laboratory, previous experience essential.—Apply Personnel Officer, United Insulator Co., Oakcroft Rd., Tolworth. [7961

TESTING assistants required for high frequency cables, with National Certificate or equivalent qualifications; previous experience not essential.—Siemens Brothers & Co., Ltd., Ref. 423, Woolwich, London, S.E.18. [7952

REQUIRED urgently, junior electronic engineer for development of radio interference suppressors and general test room duties. A.I.D. experience very desirable, single man under 30 having H.N.C. preferred.—Apply Aish & Co., Ltd., Vanguard Works, Poole. [7955

CALIBRATION Engineer required to supervise the maintenance of electrical test gear for valve and C.R.T. making plant, salary according to experience.—Applicants should apply in person or write to Personnel Department, E.M.I. Factories, Ltd., Hayes, Middx. [7920

INTERNATIONAL AERADIO, Ltd., require radar instructor in Army equipment, preferably staff officer experience, for senior post in Pakistan; good salary and pension scheme, passages provided. Write, quoting R1, Personnel Officer, 40, Park St., London, W.1. [8028

EXPERIENCED radio service engineer with some television experience required, first-class rates and excellent working conditions.—Write, stating age, qualifications, experience and salary required, to British Relay Wireless Ltd., Services Department, 397, Albany Rd., S.E.5. [7951

SITUATION vacant, good wages and prospects offered to sales engineer who can undertake job of dept. man, no academical knowledge required, but some theory together with practical experience is essential.—Write in first instance to E.P.E., 42-46, Windmill Hill, Ruislip. [7929

DRAUGHTSMAN required by firm of radio manufacturers for the design and development of domestic radio and television in all its aspects; must be a first-class man able to work with the minimum of supervision.—Box 105, Gordon House, Farringdon St., London, E.C.4. [7924

SERVICE engineer required for radio receiving station in Barnet, Herts; applicants must be fully conversant with communications type receivers and be prepared to work shift duties; ability to read morse an advantage; write, stating qualifications, experience, age, etc., to Box 6099. [7990

BUSINESS opportunity, established retail television and radio business with leading agencies has vacancy for a technical sales director and a service director; salary in each case £750 per annum, plus participation in profits; investment £5,000 in each case.—Box 6126. [8007

A VACANCY exists for a broadcast receiver engineer experienced in mechanical as well as electrical design in this field and capable of taking full responsibility for the design of individual radio receivers; salary in accordance with qualifications.—Apply in confidence to Box 5680. [7926

DETACHED house, modern, central position, all main services, plus good salary offered to efficient television and radio engineer; progressive town, 17 miles from Central London, main Green Line route and fast trains; please state experience, age, family, if able to drive, etc.—Box 5527. [7878

ELECTRICAL engineering tutors, opportunity for 2 qualified men (1) with telecommunications experience, (2) with experience in generation and transmission; pensionable appointments with eminent London correspondence college, no Sats.; canteen.—Details of age, experience, salary required, to Box 6001. [7953

WANTED, receiving and transmitting technicians experienced operations point-to-point radio stations also technicians experienced in maintenance Teletype, Creed, Wheatstone equipment; regular employment; state qualifications and experience.—RCA Communications Inc., Tangier, Morocco. [7941

A COST estimator is required by the industrial electronics department of a well-known Midland manufacturers; applicants should have good production experience in the radio industry and be capable of pre-production costing.—Write, giving full details of previous experience, quoting ref. IBC, to Box 5857. [7945

TELECOMMUNICATION engineer in early twenties required by large organization; minimum requirements Gd. 2 C/ & G. Telecom/radio; commencing salary £420; applicant must be keen to use the excellent opportunities for advancement which exist; pension scheme, etc., on establishment.—Write Box 5856. [7956

A NUMBER of senior and junior vacancies for radio, radar, electronic, television, etc. development, service engineers, draughtsmen, wiremen, testers, inspectors, etc.; urgently required 50 television service engineers.—Write in confidence, Technical Employment Agency, 179, Clapham Rd., S.W.9 (Brixton 3487.) [0105

INSPECTORS mechanical and electronic.—Good rates of pay plus staff appointments in cases of exceptional ability. Canteen facilities, social club and congenial working conditions.—Apply in writing or personally to Personnel Officer, Decca Radar Co., Ltd., Shannon Corner, Kingston-by-Pass, New Malden, Surrey. [7925

JOHN FARMER

336. CIRCUIT TESTING OHMMETERS, by Evershed & Vignoles. Scales 0-1000 and 100-200,000 ohms and inf. Test leads and prods. Leather case. **£5,** post 1/6. **271. POWER TRANSFORMERS.** 1 phase, 50 cycles, input tapped for 200-220-240 v. plus 10 v., bakelite panel attached, sec. leads to U17 and RZ1.150 valve bases, also neg. 700 v. pos. DC terminations. New, in wood cases, **35/-** each, carr. 3/6. **13. RADIO TRANSFORMERS,** Pri. 200-220-240 v., Sec. 350-0-350 v. at 80 m.A., 6.3 v. tapped at 4 v. at 5 a., 5 v. tapped at 4 v. at 2 a., screen, stout clamps with slots for chassis, etc., mounting. Overall size 4in. x 3¼in. x 2¼in. New, boxed, with termination data, **20/-** each, post 1/3. **18. MULTIPLE LT TRANSFORMERS,** input 200-220-240 v., 50 c.s., 1 phase. Output 2-4-5-6-8-9-10-12-15-18-20-24 and 30 v. at 2 amps. These transformers have a 101 uses—see items 19 and 132 for instance. Brand new, boxed, **22/6** each, post 1/3. **19. WESTINGHOUSE RECTIFIERS,** selenium full-wave bridge, DC output 12 v. at 2 a. from input of 15 v. AC. To charge 6 v. battery, AC input is 8 v., to charge 2 v. accumulator, AC input 4 v. Ideal for use with item 18 above. New, unused, with fixing brackets, **15/-** each, post 8d. **132. SMALL MOTOR BLOWERS,** 24 v. AC/DC. Size overall 4¼in. long, motor 2¼in. dia., blower casing approx. 3in. dia. New, unused, **10/-** each, post 10d. **323. UNITS FOR STRIPPING,** a nice bargain here for all radio constructors. Contain 12 octal valve holders, 1 ganging switch, 6 trimmers and about 100 misc. condensers, resistors, etc., **2/9** each, post 1/3. **223. VARIABLE RHEOSTATS, "ZENITH,"** 0.4 ohms., 25 amps., helical screw traverse, laminated contacts, wire wound, vitreous steel former. Base mountings and brackets, unused condition, **7/6** each, post 1/6. **285. SIEMENS HIGH SPEED RELAYS,** micrometer blade and gap adjustments, single pole change-over platinium contacts, slide-on cover, size 3in. x 1¼in. x 1in. 3 types: (a) twin coil, each 1,000 ohms. (b) twin coil, each 500 ohms. (c) single coil 145 ohms. New, unused, **10/-** each, post 4d. **272. "RECORD" BOND TESTERS,** 2½in. scale, 0 to 0.1 ohms, battery compartment, in bakelite cases with shoulder straps. New, unused, **20/-** each, post 1/6. **134. VOLTMETERS,** 0-100 v. AC, moving coil, internal rectifier, 1 mA. scaled, in 1/10th subdivisions, 0-20-40-60-80-100. 2½in. scale, flush panel mounting. New, boxes, **20/-** each, post 6d. **24. AMMETERS,** hot wire, 0-9 amps, AC/DC. 3½in. dia., 2½in. scale, fit 2½in. dia. hole, flush panel mounting. Brand new, boxed, **10/-** each, post 6d. **138. "PYE" 45 MCS I.F. STRIPS,** new, unused, with 7 valves, 6 EF50's and 1 EA50, **60/-** each, post 1/6. **184. FLEXIBLE DRIVES.** Will fit tuning controls on "Command" receivers, 13in. long, one end serrated push-on with screw lock-nut, other end 5/16in. dia. shaft for control knob. New, unused, **2/6** each, post 6d. **192. POTENTIOMETERS,** wire wound on ceramic formers, 500 ohms, 10 watts, single hole panel mounting, ¼in. shafts, new, unused, **7/6** each, post 4d. **199. UNITS,** U.S.A., contain eleven 1 and ½ watt 5% resistors (10-10-10-10-15-15-39-56-100-910-910 ohms), new, unused, **1/6** each, post 3d. **233. CLAROSTAT VARIABLE RESISTORS,** wire wound, semi-circular formers, ¼in. shafts, 2 types. (a) 0.5 ohms, **9d.** each, post 3d.; **7/6** doz., post 7d. (b) 50 ohms, 1/- each, post 3d.; **10/-** per doz., post 7d. **307. INTERVALVE TRANSFORMERS.** (a) 10K.9625. HT and plate 1000 ohms, G-GB-G., 2 separate windings 7000 and 7000 ohms, weight 2½ lbs., **7/6** each, post 11d. (b) 10K.9627, Pri. 350 ohms Sec. c.t., Sec. 500 ohms, weight 3½ lbs., **7/6** each, post 1/-. (c) 10K.9637, Pri. 200 ohms, Sec. 3000 ohms, weight 21 ozs., **3/6** each, post 8d. (d) 10K.8539, Pri. 5 ohms, Sec. 2000 ohms, weight 17 ozs., **2/6** each, post 7d.

The above are a few items taken from our latest lists. Send for your copy to:—

JOHN FARMER (DEPT. A.1.), 194 HARBORNE PARK RD., HARBORNE, B'HAM, 17

Tel.: HARborne 1309.

A REMARKABLE ACHIEVEMENT IN FILTER DESIGN

Pat. Applied For

E.M.G.
STEEP-CUTTING
INFINITELY VARIABLE FILTER

- Cuts at any selected frequency between 4,000 and 8,000 c.p.s.
- Average steepness of cut 20 db. per octave.
- Connects between secondary of output transformer and speaker 15 ohms, rated impedance.
- Specially valuable for use with new microgroove records.
- Greatly reduces needle-hiss on ordinary records with minimum high note loss and suppresses high pitched interferences on radio.
- No distortion, and no appreciable loss of volume.
- Leaflet available from the manufacturers.
- *Need crystal pickup pending.*

£4 - 10 - 0

Trade Enquiries Invited

E.M.G. HANDMADE GRAMOPHONES LTD
Newman St., Oxford St., W.1
Telephone: Museum 9971-2-3

TELECRAFT

AERIALS ENSURE THE
BEST TELEVISION

TRY ONE AND SEE FOR YOURSELF

LYONS RADIO Ltd.

M.C.R.1. POWER PACKS. Neat little power units especially useful for the operation of receivers where the 1T4, 1R5, 1S5 etc., series of valves are employed. Size: 8 x 3½ x 4½in. INPUT A.C. or D.C. 90 to 250 volts—with fully smoothed output of 90 v. D.C. at 15 mA. and 7.5 v. at 150 mA. Originally designed to operate the M.C.R.1 miniature Rx. **PRICE 35/-.**

POWER UNITS TYPE 87. Rotary converter units for 24 v. D.C. input and having a twin output of 250 v. D.C. at 50 mA. and 6.3 v. D.C. at 3.5 A. Can be operated in reverse (long 10/- parts) or S.v.c. Totally enclosed in an oil metal case 8½ x 9½ x 4½in. In good condition and working order. **PRICE 9/6.** Post 2/-.

SUB-STANDARD VARIABLE CONDENSERS. Fitted in glass cut cases with heavy brass rams. Calibrated (0.3 to 0.30). Approx. size 7 x 7 x 8½. Front panel fitted with brass terminals and shorting switch. In good condition. **PRICE 25/-,** or with glass container cracked or broken, 15/-. Postage 3/-.

POWER UNITS. TYPE 46. These units incorporate metal rectifiers. Input is 200 to 250 v. A.C. 50 cps. Smoothed outputs are 250 v. D.C. at 110 mA. and 6.3 v. D.C. at 11 A. Totally enclosed in metal, ventilated case 17in. high x 10 x 12in., weight about 100lb. Fuse holders on outside of case may be broken but can easily be replaced otherwise the units are in first-class order. **PRICE £8 7 6.** (Carriage 15/-).

MILLIAMMETERS. First grade moving coil 0-3 milli-amps. Bakelite case 3in. panel mounting overall dia. 4in. Brand new. **PRICE 15/-.**

3 GOLDHAWK ROAD, (Dept. M.W.)
SHEPHERDS BUSH, LONDON, W.12
Telephone: **Shepherds Bush 1729**

SITUATIONS VACANT

A NEW defence project of National importance being undertaken by a well-known aircraft company located in the northern outskirts of London, offers highly paid and interesting posts for suitably qualified applicants; vacancies exist in senior (salaried grades) and for junior engineers in various categories:—

(a) PHYSICISTS with experience in electronic problems.

(b) PHYSICISTS with experience in optical work.

(c) ELECTRONIC engineers with servo-mechanism experience.

(d) ELECTRONIC engineers with experience of low frequency work and measuring systems.

(e) ELECTRICAL engineers with experience in small motor design and development.

APPLICANTS for senior posts should possess a good University degree and preferably should have some industrial experience.

APPLICANTS for junior posts should have a good industrial experience, be qualified either by City & Guilds Certificate or by Inter B.Sc.

WRITE full details, qualifications, experience, age, salary sought, to—Box A.C.65488, Samson Clarks, 57/61, Mortimer St., W.1. [7940

TECHNICAL assistants required for interesting laboratory and field work connected with guided missiles project; applicants to be between 20 and 35 years of age, with at least National Certificate (Electrical) or equivalent; experience of R.F. technique up to 500mc would be an advantage.—Full particulars to Box 4522. [7940

DRAUGHTSMEN (senior and junior) required in research department for design and detail work on special radar and electro-mechanical equipment; West London area.—Write, giving full particulars of experience, age and salary required, to Box A.F. 694, Gerrard News, Ltd., 17, Moorgate, London, E.C.2. [7959

TELEVISION service engineers required for (customers' residence service (no sales), able to drive car; a driving course, part permanent, well-paid position for men with initiative and personality; vacancies in Worcester, Stoke-on-Trent and other districts.—Write for interview to Belcher, Ltd., 57, Windsor Rd., Slough. [7955

MANCHESTER area, first-class radio mechanic required by progressive hearing-aid manufacturer, for inspection and deputy works managers duties; state full details, past experience, references and salary required.—Apply, in writing, Alfred Bates & Son, Ltd., Advertising Agents, Old Exchange Chambers, King St., Manchester, 2. [7965

MANCHESTER firm of electronic engineers requires outside representative to cover Manchester and surrounding counties; must have previous successful sales record and be accustomed to electronic instruments and similar apparatus; car an advantage; reply giving full details of past and present employment, age and salary required.—F. C. ROBINSON & PARTNERS Ltd., 287, Deansgate, Manchester, 3. [7997

ASSISTANT manager required for radio, electrical, piano, music and record business in market town in East Anglia; must have had some practical experience in radio servicing, control of staff and costing; good opportunity for the right man.—Apply, giving full particulars of past experience together with references and qualifications, to Box 6157. [8052

A LABORATORY assistant required, capable of taking charge of electrical and electronic equipment for a guided missiles project; duties will include calibration and minor repairs of instruments; applicant with the necessary experience will also control sub-standard room and undertake design of laboratory equipment.—Full particulars to Box 4521. [7536

ASST. chief inspector reqd. with not less than five years' exp. on the inspection of electronic apparatus to Ministry requirements; should preferably possess a degree or Associate Membership of the Institute of Electrical Engineers; this post is permanent and pensionable; excellent salary to suitable applicant; N. London area.—Write fullest particulars to Box 5677. [7916

APPLICATIONS are invited by the Ministry of Supply for vacancies in the experimental officer class at the Atomic Energy Research Establishment, Harwell, Berks, for work in the following fields:—Physics, electronics and scientific computing (Ref. A 509/51/A); and chemistry (other than organic chemistry), chemical engineering and metallurgy (Ref. F 727/51/A).

THESE posts offer a wide variety of experimental work in connection with the development of atomic energy and the opportunity for a career in an increasingly important branch of science; candidates should possess at least Higher School Certificate or Higher National Certificate in a relevant scientific subject, or mathematics or equivalent qualifications; higher qualifications will be an advantage; appointments will be made according to qualifications, experience and age within the following salary ranges—experimental officer (male) £545—£695 per annum, assistant experimental officer (male) £240 (at age 18)—£505 per annum; rates for women somewhat lower.

APPLICATION forms obtainable from Ministry of Labour and National Service, Technical and Scientific Register (K), Almack House, 26, King St., London, S.W.1, quoting the appropriate Ref. No. [7970

CABINETS & CHASSIS

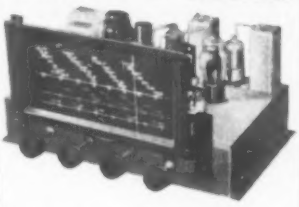

A.C. 5 valve 3 W.B. Superhet Radiogram chassis. Absolutely complete kit of parts including detailed wiring diagram **£10 15 0**
Or fully wired and tested **£12 10 0**

CABINETS OF DISTINCTION

Send 6d. for our new illustrated cabinet catalogue.

AMPLIFIERS:

4 to 15 watts . . . from **£3 19 6**

Full details from:—

LEWIS RADIO CO.
(Dept. 252)
322 HIGH RD., WOOD GREEN, LONDON, N.22.

Callers to:—
120 GREEN LANES, PALMERS GREEN LONDON, N.13
(near Bowes Road)
Phone: Bowes Park 6064

ELECTRONICS
DUPLEY
LTD.
CRANMER AV. EALING. W.13.

Transformer and Coil Manufacturers to the Trade
Telephone: EALing 3688

ODDIE FASTENERS

PAT. 507249

THE FASTENER WITH ENDLESS APPLICATIONS—SIMPLE—POSITIVE SELF-LOCKING. MADE IN A VARIETY OF TYPES AND SIZES.

SPECIAL FASTENERS TO SUIT CUSTOMERS REQUIREMENTS.

WIDELY USED IN THE RADIO INDUSTRY.

Illustrated brochures and other information will be gladly sent on request.

DEPT. "W.W."
Oddie, Bradbury & Cull Ltd., Southampton
Tel.: 55883 Cables: Fasteners, Southampton

NUSOUND PRODUCTS

136 WARDOUR STREET, LONDON, W.1

(Oxford Street End)

Tel: GERrard 8845

NUSOUND FIDELITY-TEN. The latest super quality Amplifier. All Triode line up P-Pull PX4 output. Frequency response 20-25 kcs. ± .6 d.b. and continuing up to 50 kcs. ± 9 d.b. Sensitivity 120 mv for max 10 w output. Total harmonic distortion 1 per cent. at 1,000 c.p.s. at 6 watts. 20 d.b. neg. feedback. Independent Treble and Bass controls. Chassis size: 14 x 9 x 7½in. high. A.C. model only. **£36.**

A NEW FEEDER UNIT. This is our latest addition to our range, and employs a t.h.e.t. with two I.F. stages and variable selectivity controls giving bandwidths of 7-10 and 14 kcs. The unit covers the medium-long and short wavebands and has a large illuminated dial. Price **17 gns.** inc.

RETAIL TRADE ENQ. ON ABOVE ITEMS. PLEASE SEND STAMP FOR LEAFLETS.

NUSOUND QUALITY AMPLIFIERS. 8½-WATT OUTPUT.—PP 6V6s—independent bass and treble boost and cut—switch for L.P. records—neg. feedback—provision for radio feeder unit—freq. response 25 to 20,000 c.p.s. ± ½ d.b.—hum 80 d.b. down at 6.5 watts—feedback 14 d.b.—sensitivity .05 volt. Price only **£15 17 6.** Also available with remote control unit. Price **£17 10 -.**

NUSOUND REFLEX CABINETS.—For Wharfedale speakers—10in., **£9 9 -**; 12in., **£10 10 -.** Veneered polish finish mahogany, elk or walnut.

Please send stamp for list of all our products. Our other products inc. 4½ watt Amp.—A.C. Model **£11 10 -**; A.C./D.C. **£12**; T.R.F. Preset Feeder, 3 station, **£7 12 6**; 3 station Preset S/Het, **£8 18 -**; two-band variably tuned S/Het, **£11 5 -.** Remote control pre-amp. Unit, inc. tone controls, **£5 7 6.**

GRAMOPHONE EQUIPMENT

Decca 33 or 78 r.p.m. motor, **£3 14 4**, inc. Connoisseur P/ups. Stnd. L. weight, **£4 11 8.** Trans. 13 -. Super L. weight, one head, **£6 9 -.** LP Head 71 8. Trans. 15 -. Fibre P/up **£4 3 2.** Trans. 25 -. Two-speed Stroboscope 3 11. Garrard Heads: Standard 25 3. Miniature 50 11. HiFi 56 -. Type A Adaptor 7 7. Decca Mag. Heads 59 2. Decca XMS P/up **£7** complete. Chancery Attachment 72 6. Decca 3-speed motor **£7 3 4.** Connoisseur 2-speed motor **£22 10 8.** Chancery Xtal P/up (LP20 insert) 53 -. Spare insert, LP 31 6. Garrard AC6 motor, speed controlled, 12in. table **£6 15 10.** Collaro A.C. 514MB motor and P/up **£6 10 5.** Collaro A.C./D.C. motor, 12in. table **£12 2 7.**

(We stock a full range of Wharfedale & Goodmans speakers and accessories.) TV and Gram. list 4d. (Please Add Postage.)

B. & H. RADIO

EAST STREET, DARLINGTON

BASS & TREBLE SEPARATOR

Enables the use of separate speakers for Bass and Treble. Permits adjustment of treble and matches up speakers of different impedance. Kit of Parts **£1 13 6**

SCRATCH FILTER

Easily fitted to pick-up and gives marked reduction of scratch **17 6**

WHISTLE FILTER

is very simply inserted in speaker wiring and completely eliminates 9 Kc's. whistle **£1 15 0**

A.F. and R.F. COILS rewound or wound to specification.

SITUATIONS VACANT

ALWYN SHERWOOD Ltd. require T.V. engineers for bench and field service. If you want good pay with prospects under ideal operating conditions, and you are master of your craft, contact the Service Manager, Alwyn Sherwood, Ltd., 91/95, Westgate, Wakefield. Tel. 3196/7. Expenses will be paid for all applicants selected for interview. [7817

LEADING capacitor manufacturers require technical sales engineer over 30; salaried position, pension scheme, vacancies—London, Midlands and North England areas; car or car allowance as necessary; also internal vacancies for younger men in London, electronic-electrical experience essential; write giving details of experience and salary required to—Box 6128. [8012

ENGINEER with extensive experience required for liaison between development groups engaged on the design of electronic equipment; applicants should have a degree or similar qualification with some general experience in electronics.—Apply giving full details of experience, salary required, etc., to Personnel Department (ED.64), E.M.I. Engineering Development, Ltd., Hayes, Middx. [7934

ELECTRONIC development engineer required to join staff of expanding laboratory team working on Government and industrial contracts; experience of video techniques essential, experience of waveguide techniques desirable; salary £700 p.a.; good opportunity for energetic man; write stating experience to—Technical Director, Winston Electronics, Ltd., 1 Park Rd., Hampton Hill, Middlesex. [7899

DRAUGHTSMAN required for an experimental office machinery project; applicants should have experience in the design of assemblies, using gears and light alloy castings, and should preferably have some electrical knowledge; the work on the project will run for at least one year and will be in the London and/or Croydon district.—Write, stating age, experience, salary required, to Box 6006. [7975

A VACANCY exists for a senior radio engineer with mechanical as well as electrical design experience to take charge of the broadcast receiver design group of a leading radio manufacturer; applicants will be required to produce evidence of responsible experience and successful development work in this field; a salary will be paid in keeping with the importance of the appointment.—Apply in confidence to Box 5681. [7927

EXPERIENCED radio mechanics required for the wiring of electronic gadgets; must be able to work to circuit diagrams, experience in transformer winding would be an advantage; permanent staff position.—Apply in writing giving full details of age, experience and qualifications to the Staff Manager (Ref. GBLC/G.92), Research Laboratories of the General Electric Co., Ltd., The Grove, Stanmore, Middx. [7951

WAYNE KERR require several draughtsmen for design and development work on high priority electronic test equipment; the work is interesting and offers considerable scope for men with initiative and design ability; attractive salaries in excess of the revised A.E.S.D. rates will be offered to suitable applicants; write giving details of past experience to—Wayne Kerr Laboratories, Ltd., Sycamore Grove, New Malden, Surrey. [8025

SENIOR and junior laboratory engineers required for electro-acoustic laboratory in High Wycombe; must have had experience on miniaturization and be theoretically qualified to National Certificate for junior position, and Higher National for senior position. 5-day week, canteen and usual welfare facilities.—Write, giving full resumé of experience and salary expected, to Box M.5207, Haddons, Salisbury Sq., London, E.C.4. [7964

JUNIOR radio engineer required for installation and testing of aircraft radio equipment; duties will involve test flying; current M.C.A. operator's licence an advantage, but consideration will be given to suitable applicants prepared to obtain licence during probationary period.—Application should be made in writing, giving details of experience and salary required, to the Personnel Manager, The de Havilland Aircraft Co., Ltd., Hatfield. [7600

ENGLISH ELECTRIC VALVE Co., Ltd., Chelmsford, have vacancies for young engineers to work on radio valve design and development; applicants should be of degree standard; while experience of this type of work is desirable it is not essential and otherwise suitable candidates will be considered.—Write giving full details quoting Ref. 497D, to Central Personnel Services, English Electric Co., Ltd., 24-30, Gillingham St., London, S.W.1. [7855

REQUIRED by an old-established firm at their research laboratories, Borehamwood, senior draughtsman for design of specialised electronic equipment or mechanical and electrical precision devices; sound general engineering and practical experience. Higher National Certificate standard preferred; must be capable of undertaking design work calling for originality and initiative; salary up to £625; five-day week of 39½ hours. Apply—Box 4185. [7443

BELLING & LEE, Ltd. Cambridge Arteria Rd., Enfield, Middlesex, require research assistants in connection with work on electronic components, fuses, interference suppressors and television aerials; applicants must be graduates of the I.E.E. or possess equivalent qualifications together with similar laboratory experience; salary will be commensurate with previous experience; applications must be detailed and concise, and will be treated as confidential.

SUPACOILS

PROUDLY PRESENT THEIR

NEW CONSTRUCTOR'S HANDBOOK

Get your copy today it costs 2'6 only and Contents include:—

(a) Circuits of these sets
- (1) 2-wave plus Gram. Superhet.
- (2) Fixed Station T.R.F. Transportable.
- (3) 2-wave plus Gram. T.R.F. Set.
- (4) 3-wave Superhet Feeder Unit.
- (5) 3-wave Superhet Feeder Unit with H.F. Stage and incorporating Gram. and Quality switching.
- (6) 5 v. A.C. all-wave Superhet.
- (7) 5 v. A.C./D.C. all-wave Superhet.
- (8) Feeder Unit Amplifier and Power Pack.
- (9) 6 v. A.C. all-wave Superhet.
- (10) 6 v. A.C./D.C. all-wave Superhet.
- (11) Signal Tracer.
- (12) 4 v. Battery Superhet.
- (13) 5-watt Amplifier.
- (14) 10-watt Quality Amplifier.

(b) Full constructional details of our very popular 2-wave plus gram. Superhet Coil Pack (extremely simple point-to-point wiring given in detail).

(c) Illustrations of many Receivers you can build with no previous experience.

(d) Complete Technical and Descriptive details of all our products.

(e) Pages of Constructional and Servicing hints.

(f) Many simple formulae in constant use.

(g) Complete Resistance Colour Code.

(h) Catalogue of our extensive Radio Stock forwarded with each Handbook.

This is a book you cannot afford to be without. **It will save you pounds.**

Send 2/6 **now** for your copy to

SUPACOILS MAIL ORDER OFFICE

98, Greenway Ave., London, E.17

YOUR METER DAMAGED?

Leading Electrical Instrument Repairers to the Industry

Contractors to The Ministry of Supply.

Repairs by skilled craftsmen of all makes and types of Voltmeters, Ammeters, Microammeters, Multirange Testmeters, Electrical Thermometers, Recording Instruments, Synchronous Clocks, etc. Quick deliveries—for speedy estimate send defective instrument by registered post to:—

L. GLASER

Electrical Instrument Repairers

341 CITY ROAD, E.C.1

Tel. Terminus 2489

"AUTOMAT" HOME CHARGERS, SELENIUM RECTIFIERS, CHARGER KITS

All New Goods with Full Guarantee

"AUTOMAT" HEAVY DUTY HOME CHARGER, for car or radio cells. Virtually unbreakable. Selenium rectification. Impregnated transformer of large size. Fine workmanship and appearance. 12 months' guarantee. For A.C. mains only. Standard model 6 v. 1.2 v. 2 amp. output, 4lb. wt. **59 6**, post 2/-. Minor model for 6 v. only at 2 amp. 54/-, post 2/-.

ELIMINATOR KIT. Transformer, selenium h.t. rect., 6 v. rect., 2 v. 15 tubes, tone-control, for 120 v. 20-30 mA eliminator with 2 amp. trickle charger **35/-**, or with handsome steel case **43/-**, post 1/2.

FOOLPROOF CHARGER KITS, standard model to suit trans., triple tapped, large 12 v. 2 amp. selenium rectifier, ballast indicator bulb for 2 v., 6 v., 12 v. charges, simple and foolproof. **38 6**, post 1/-; with handsome steel case, screws grommets **52 6**. 100/130 kit, but 60 watt trans. and 12 v. 3 amp. rectifier, **46/-**, weight 8 lb. or with case **58/-**. Junior kit, 6 v. 1.5 a. rect., 40 w. trans., ballast bulb, case, screws, for 6 v. 1.5 a. charge **42/-**, wt. 7 lb. Senior model kit, 12 v. 4 amp. S.T.C. rectifier 4in. diam. 70 watt transformer, ballast bulb for 6 v., 12 v. charges, **55/-**, post 1/6, smoother **12 6** extra (not essential). 2 v. trickle rectifier, 1 amp., with high-grade layer wound transformer **12 6**. 400w. but for flash gun charger, 4 v. 1 amp. **16 6**.

SELENIUM RECTIFIERS. New stock not surplus. 12/15 v. 2 amp. **15 6**, 6 v. 2 amp. **9/-**, post 9d. 12 v. 1 amp. half wave, **9/-**; 12 v. 3 amp. **16 6**, post 9d., 6 v. 4 amp. **16 6**, 12/15 v. 3 amp. **27/-**, post 9d. Tinned finned type, 12 v. 6 amp. **35/-**, post 1/-. 24 v. 4 amp. **54 6**, 24 v. 6 amp. **67/-**, 24 v. 7 amp. **29 6**, small-space H.T. rectifiers, selenium, 250 v. 60 m.a. **7 6**, 350 v. 120 v. 60 m.a. **6 6** (700 v. 100 m.a. bridge, **14 6**. All 6d. extra postage. (250 v. 200 m.a. bridge or half-wave 18 m.a.) **22 6**.

"REWEBAT." battery desulphator and conditioner **1 9**, post 3d. Car size, **3/-**, post 4d.

CHAMPION PRODUCTS

63 Uplands Way, London, N.21. Phone: LAB 4467

Dits and Dahs!!

THIS IS THE LANGUAGE OF THE AIR THAT EVERY RADIO AMATEUR, PILOT, SHIP'S OPERATOR, ETC., MUST BE ABLE TO READ AND SEND. IT IS EASILY AND QUICKLY LEARNED BY THOSE WHO TAKE UP A

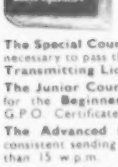

CANDLER CODE COURSE

THE CANDLER SYSTEM not only teaches you the **right way** to send but the **right way** to *read* code sound just as easily as you read print by sight.

The Special Course covers all the Code training necessary to pass the G.P.O. test for an **Amateur Transmitting Licence.**

The Junior Course is a complete Code Course for the **Beginner** who desires to secure the G.P.O. Certificate in which he is interested.

The Advanced Course is for those with a consistent sending and receiving speed of not less than 15 w.p.m.

Touch Typing Course. A series of interesting and easily followed lessons which enable one to record messages at high speeds.

Courses supplied on Cash or Monthly Payment Terms.

You are invited to send for a copy of the CANDLER "BOOK OF FACTS." It gives full details of the above training.

THE CANDLER SYSTEM CO.,

(55W) 52b, ABINGDON RD., LONDON, W.8

Candler System Company, Denver, Colorado, U.S.A.

SITUATIONS VACANT

VACANCIES exist in the development laboratories for junior and senior engineers experienced in the design of electronic test equipment (including valve voltmeters, C.R.O. oscillators, etc.); applicants will be responsible for the development of research models to the production stage and must have a good fundamental knowledge of electrical theory and practical experience of design; salary according to qualifications and experience; please quote reference J.EN.

ENGINEERS are required for the development of high grade test equipment in connection with the manufacture of automatic pilots and aircraft instruments; this work involves the application of electronic techniques over a frequency range from zero to approximately 100 Kc/s p.s. together with light electrical and mechanical engineering; applicants having experience of applied measurements in one or more of the above-mentioned engineering fields will naturally be preferred but the foremost qualification is a sound appreciation of fundamental engineering principles; salary according to qualifications and experience; please quote reference J.EN.

WRITE Personnel Manager, S. Smith & Sons (England), Ltd., Bishops Cleeve, nr. Cheltenham, Glos. [7955

LABORATORY assistant required for instrument section; previous experience in repairing, adjusting and calibrating both indicating and electronic instruments and test gear is essential. Higher National Certificate or equivalent qualification would be an advantage, but is not essential.—Apply in writing giving full details of training and experience to the Staff Manager (Ref. GBLC/G.219), Research Laboratories of the General Electric Co., Ltd., North Wembley, Middx. [8002

SEVERAL electronic engineers or physicists are required who have graduated in physics or telecommunications and have two or three years' radar experience in charge of the development of particular sections of a project involving radar. The work includes design of pulse generators, timing wave form oscillators, electronic computers, transmitters and radio receivers and servo systems. In addition technical assistants are needed with H.N.C. or equivalent qualifications.

ALL the positions available are for work of high interest in rapidly expanding field.

APPLICATIONS, which will receive prompt attention, should give the fullest details of education and professional experience with appropriate dates.

APPLY Employment Manager, Vickers-Armstrongs, Ltd. (Aircraft Section), Weybridge. [7752

AN instrument mechanic is required for duties in the Electronics Section of the Research and Experimental Department; applicants should possess a high degree of mechanical skill, and be able to participate intelligently in both design and manufacture of small electro-mechanical devices; experience in a similar capacity, whilst desirable, is not essential.—Write, stating age, experience, and salary expected to the Personnel Officer, Saunders-Roe, Ltd., East Cowes, I.O.W. [7921

SENIOR draughtsmen, Metropolitan-Vickers Electrical Co., Ltd., require for their Trafford Park works a number of senior draughtsmen preferably with experience in radio and radar equipment; for qualified men these jobs are permanent, five-day week under good conditions.—Apply in writing stating age, experience, qualifications, salary required, etc., marking envelopes "Radio D.O." to Personnel Manager, Metropolitan-Vickers Electrical Co., Ltd., Trafford Park, Manchester, 17. [7424

APPLICATIONS are invited for several important posts in large radio organisation (Pye) now expanding in marine field; two service managers with sales ability and one salesman with knowledge of sound reproduction equipment required now, as well as service engineers with V.H.F. knowledge; applicants, who must have ability and enthusiasm for advancement and who are willing to serve at any U.K. port should send full details, with references, to—Rees Mace Marine, Ltd., 11, Hinde St., London, W.1. [7948

SENIOR television development engineer required by well-known radio and television manufacturer in London area; applicant must have a wide experience in development for mass production of modern commercial radio and television receivers; a good salary will be paid to a person possessing drive and organizing ability and capable of carrying through projects from development to production stages, under the supervision of the chief engineer.—Kindly state full particulars of technical qualification and experience to Box 6007. [7977

£50 a year tax free is bounty paid to electronic artificers joining special section of the Supplementary Reserve. Men with City Guilds Final Certificate in Telecommunications and Radio and up-to-date experience in current electronic engineering practice will be needed to maintain electronic instruments controlling fire of anti-aircraft guns which protect vital centres of Great Britain should war break out. By joining the S.R. a man will not only be playing a vital part in the defence of this country but will also know his exact role in the event of war. Minimum rank Staff Sergeant. Minimum of 15 days' training per year with Regular Army rates of pay in addition to bounty.—Further details from D.D.M.E., A.A. Command, "Glenthorn," Stanmore, Middx., or the War Office (A.G.10) (B), London, S.W.1. [7928

EX GOVERNMENT BARGAINS

New and used equipment

T.R. No. 19 Chassis. As stripped by B.O.T., of meter, cells and relays, but containing dozens of condensers, resistances, etc., 0005 4-gang, 1-gang, and split stator condensers, 12 valve holders, 3 465 kc/s. IFTs, 6 mc/s. inter-valve and output transformers, switches, potentiometers, etc. **15/6**, carriage 7/-.

1196 Transmitter Chassis. Part stripped by B.O.T., but containing a host of useful components, etc., **3/-**, post 1/9.

Uniselector Switches. 5 banks of 25 contacts per bank new condition, **21 6**, post 1/3.

24 Volt Pumps. Submersible type, 120 G.P.H. 20ft. head, **45/-**, post 1/6.

Speaker Cases. Black bakelite to take 2in. speaker, or would make good case for multi-meter, **2 11**, post 6d.

Modulation Indicators. Containing 3in. 0-500 μA meter, meter rectifier, tuning unit, search coil, battery box, etc., all contained in die-cast metal box 6½in. x 11½in. x 7in., with detachable lid, new condition, **30/-**, post 2/6.

Jones Plugs and Sockets. Sets of three for B1155, **5 6** set, post 9d.

Relays. Miniature American type 250 ohm 8 P.C.O., ditto, 600 ohm D.P.C.O., **3/-** each, post 6d.

Transformers. 200/250 volts 50 cycles, output 150-0-150 volts at 1 amp. and 40 volts at 8 amp. **30/-**, post 4/6.

Selsyn Motors, Type 60. 10KB 440 heavy duty 11 6 spindle. **50/-**, post 2/-.

Instrument Rectifiers, type MRH. **2 6**, post 6d.

Condensers, large block type 1.5 M.F. 4,000 volt working, **1 9**, post 1/3.

Terminal Strips. 3 x 13in., containing 22 brass terminals, **3/-**, post 9d.

Scanners Type 83 for 3 cm., containing antenna, 12in. reflector covered by perspex dome, 24-volt drive motor, position transmitter suppressor gear, relay, etc., would convert for rotating beam, brand new in crate, **70/-**; used, less perspex dome, **35/-**, carriage 10/-.

Our New List No. 7, containing 300 ex Government items is now available, price **6d.** inland, **1/-** overseas Air Mail.

A. T. SALLIS

93, North Road, Brighton, Sussex

Phone: Brighton 25806

The VOIGT Loudspeaker is still ahead of all others. P.M. Unit with 33,000 line gap thus **£40** ex works. Corner Horns (in the white) **£19.10.0** or **£47.10.0** ex works.

Demonstrations in Toronto, Canada, by arrangement with Mr. Voigt.

VOIGT PATENTS LTD.

Sydenham, S.E.26 SYD 6666

Sole makers of VOIGT Products

WANTED

VISUAL INDICATORS TYPE 1

Large or Small Quantities

Box No. 5792, c/o "Wireless World."

CRYSTALS

Type "G"

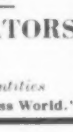

Frequency ranges: 100kc/s to 500 kc/s; 3 mc/s to 20 mc/s. Evacuated glass envelope having B7G valve base, with crystal connected across pins Nos. 3 and 7.

of world repute

BROOKES CRYSTALS LTD.

10, Beckwell St., Greenwich, London, S.E.10.

Phone: GREenwich 1828. Cables: Xtals London. Grams: Xtals Green London.

KOLECTRIC

ARMATURE WINDING HEAD

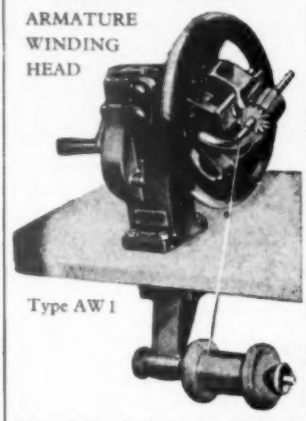

Type AW 1

This winding head has been primarily designed for use with the "Kolectric" Model H.1 hand coil winding machine, but it can be used on other makes of machines and can also be motorised if desired.

Please write for illustrated leaflets

KOLECTRIC LTD

73 UXBRIDGE RD., EALING, LONDON, W.5

Telephone: EALing 9096

SOUTHERN RADIO'S WIRELESS BARGAINS

WALKIE-TALKIE (TRANSMITTER-RECEIVER). Type 38 Mark II. Complete with 5 valves, Throat Microphone, Headphones and Aerial. 7 mc/s Amateur Band suitable for field use. Powerful Superhet Receiver. Modulated Transmitter. Guaranteed ready for the Air, less batteries, **£3/10/-.**

R.3515 TELEVISION UNITS. Complete with 21 valves. 6 Stage 14 mc/s I.F. Strip. Ideal for T.V. Conversion. Brand new in original wooden cases, **£3/10/-.**

G.E.C. "MINISCOPE" M861B. MINIATURE CATHODE RAY OSCILLOSCOPES 1½" Tube. Time Base etc., etc. Brand New in Makers Sealed Cartons with Leatherette Carrying Case—**£15/10/0** plus 5/- carriage.

LUFBRA HOLE CUTTERS. Adjustable from ⅜in. to 3½in. for use on Wood, Metal, Plastic, etc., 5/9. LUFBRA FLY CUTTERS, 1/4/6.

LIONEL "BUG" KEYS. Genuine U.S.A. Automatic Morse Key, Type J36. Few only, **£3/7/6.**

THROAT MICROPHONES. Magnetic type complete with long lead and plug, 4/6.

HAND GENERATORS. 6 volts at 5 amps. With Crank, 21/-.

PLASTIC TRANSPARENT MAP CASES, 14 inches by 10½ inches. Ideal for Maps, Charts, Display, Photographs, etc., **5/6.**

STAR IDENTIFIERS. With Hydrographic Office Modifications A-N Type 1. Complete in case, **5/6.**

MOVING COIL D.C. METERS. Brand new. 2in. 0-2 mA., 0-5 mA., 0-30 mA., 0-20 volts, **9/6 ea.**

WESTECTORS. Type WX6 and W112, 1/- ea., 11/-doz.

MARCONI AERIAL FILTER UNITS. Type "916" in conformity with P.O. Specification. Full instructions for fixing, 4/-.

CONTACTOR TIME SWITCHES. 10-hour movement, 2 impulses per second. Thermostatic Control in soundproof Cases, **11/6.**

VISUAL INDICATOR UNIT Type 3 (10Q/4). Contains two Moving Coil movements, two Neons, etc. Easily convertible to very efficient M.C. Meters, 11/-. Conversion fully described in "W.W." Sept. 1951.

Full list of Radio Publications, 2½d.

SOUTHERN RADIO SUPPLY LTD.,
11 LITTLE NEWPORT STREET, LONDON W.C.2. *GERrard 6653.*

SITUATIONS VACANT

EXCEPTIONAL opportunities exist in large progressive lighting organisation having vacancies on its technical staffs in fluorescent and incandescent lamp factories; applicants should be between 20 and 30 years old and have Ordinary or Higher National Certificates or equivalent qualifications; some industrial experience is essential, previous lamp making experience would be to the applicant's advantage; salary commensurate with qualifications and experience; applications regarded as strictly confidential and should contain fullest details.—Replies to Box 6004. [7972

H.F. heating engineers are required by the English Electric Company for their industrial electronics department; these vacancies are for junior and senior engineers with good experience of valve-type H.F. heaters; these are permanent and progressive appointments offering excellent opportunities for qualified engineers or those with sound practical experience of this class of work; interviews can be arranged for Saturday mornings.—Write, giving full details and quoting Ref. 357c, to Central Personnel Services, English Electric Co., 24/30, Gillingham St., London, S.W.1. [7971

RADIO wiremen are required for work at the G.E.C. Stanmore Laboratories; the work involves assembly and wiring of special airborne radio and radar equipment; laboratory test equipment, etc.; knowledge of techniques used in manufacture of miniature or similar assemblies, including ability to make and instal cable forms is essential; there are progressive staff positions with five-day week and good working conditions; write giving full details of age and experience to the Staff Manager (Ref. GBLC/G/9) Research Laboratories of the General Electric Company Ltd., Stanmore Common, Stanmore, Middx. [8010

OLD-ESTABLISHED British firm in Bangkok require sales and service engineer for their radio department; principals handle the distribution throughout Thailand of a well-known American range of domestic radio receivers, commercial and broadcast transmitters and allied equipment; applicants will be required to take charge of the department and must be fully conversant with the entire range of broadcasting equipment; a knowledge of television, both transmitting and receiving, will be to the applicant's advantage; applicants up to 35 years of age will be considered.—Write with full particulars to Box "JA/7," c/o 95, Bishopsgate, London, E.C.2. [8013

THE GENERAL ELECTRIC Co., Ltd., Brown's Lane, Coventry, have vacancies for development engineers, senior development engineers, mechanical and electronic for their development laboratories on work of national importance; fields include microwave and pulse applications; salary range £400-£1,250 per annum; vacancies also exist for specialist engineers in component design, valve applications, electro-mechanical devices and small mechanisms; the Company's laboratories provide excellent working conditions with social and welfare facilities; superannuation scheme; assistance with housing in special cases; apply by letter stating age and experience to—The Personnel Manager (Ref. CHC/) [7705

TECHNICAL grades II and III required for Ministry of Supply Establishment at Malvern, Worcestershire. Qualifications: British, of British parentage; apprenticeship in radio or electrical engineering, with knowledge of use or maintenance of electronic or light electrical equipment; be familiar with engineering drawings and drawing office procedure. Possession of Higher National Certificate (Ordinary National Certificate for Grade III) or equivalent qualification desirable. Duties: Preparation of radio equipment schedules, including spares and servicing recommendations for new radar installations and associated electrical equipment. Additionally, for Grade II, the preparation of technical information on modifications. Salary: Grade II £540 (linked to age 30)-£645 p.a. Grade III £457 (linked to age 26)-£545 p.a. (rates for women slightly lower). Not established; opportunities for established pensionable posts may arise.—Application forms from Ministry of Labour and National Service, Technical and Scientific Register (K), Almack House 26, King St., London, S.W.1. Quoting Ref. No. D565/51-A. [7957

ASSISTANT Technical Costs Officers required by Ministry of Supply for London; qualifications: British, of British parentage; regular engineering apprenticeship; good experience of rate-fixing, planning and prime cost estimating in works manufacturing high class engineering products; possession of O.N.C. (Engineering), or equivalent, an advantage; experience of fire control aircraft, aero-engines, or radio/radar production additional advantages; duties include preparing detailed estimates of prime cost manufacture of engineering products for establishment contracts; successful candidates must be prepared to travel; candidates selected for interview may be required to carry out blue print test of ability to perform duties; salary £370 (linked to age 30 to £675 p.a., women slightly lower; not established, opportunities for established pensionable posts may arise; written applications, giving date of birth and education, full details of qualifications and experience of posts held (including dates) should be addressed to Appointments Officer, Ministry of Labour and National Service, 1-6, Tavistock Square, W.C.1, quoting reference number K.F. 428, within 14 days of appearance of this advertisement. In no circumstances should original testimonials be forwarded. Only candidates selected for interview will be advised. [7987

OUTSTANDING VALUE IN BRAND NEW EQUIPMENT

COLLARO AUTOCHANGERS, model RC511, new single speed model with interchangeable plug-in pickup head, plays nine records, reject mechanism, beautifully finished unit plate, A.C. operation. Price with magnetic head **£11/16/9,** or with Acos GP27 crystal head, **£13/2/6,** carr. 5/-.

COLLARO 3-SPEED AUTOCHANGERS, model 3RC511, as above but for 33⅓, 45 and 78 r.p.m. Price with one dual purpose Acos GP27 head, **£15/10/6,** or with two separate GP27 heads for Std. and L.P. **£18/15/-,** carr. and pack. 5/-.

TABLE CABINETS to house above, stained and polished, **£6,** carr. pd.

COLLARO 3-SPEED GRAM. UNIT, model AC3/514, with pickup and autostop. Price with dual-purpose GP27 plug-in head, **£11/8/9;** with two sep. GP27's, **£14/8/9,** carriage and pack. 3/6.

RECORD PLAYER CASES, well made, measure 15½in. x 13½in. x 7in., beautifully covered in brown Rexine, fitted hinged lid, clasps and sprung carrying handle. Price complete with uncut motor board, **57/6.** Post 2/6.

SYMPHONY No. 1 (AMPLIFIER) by N.R.S. The most versatile domestic Audio Amplifier on the market to-day. Independent control of Bass, Middle and Top, separate Scratch Cut, negative feedback. For A.C. 200-250 v., input for magnetic, crystal and hi-fi pick-ups and Tuner. 5-watts output. Price: 3 ohm model, **9½ gns.**; 15 ohm model, **£10/7/6,** carriage 5/-.

SYMPHONY No. 2 MARK II. New model with 10 watts push-pull triode output, breathtaking realism, hum level negligible—90 db down. Woden main transformer, choke and output transformer for 3, 7.5 and 15 ohms. Input for ordinary and hi-fidelity pick-ups. Tone control system same as No. 1. A truly magnificent instrument for only **15 gns.,** carriage 5/-.

No. 2 PUBLIC ADDRESS AMPLIFIER. Same chassis and power parts as No. 1 Symphony but simple one knob tone control. 15 watts push-pull output, 2 inputs with separate volume controls for fading mike and gram. Complete kit **10 gns.** Ready built, **£11/19/6.**

BASS-REFLEX CABINET KITS give superb bass response and top (⅜in. patent timber). Full instructions supplied. 8in. speaker model 2ft. 6in. high x 1ft. 3in. x 1ft. deep. Price **85/-**; 10in. speaker model, 30in. x 16in. x 13½in., **97/6**; 12in. speaker model, 30in. x 17½in. x 16in., **107/6.** Any of above ready built for 7/6 extra. Carr. in any case, 7/6.

FOR CALLERS ONLY. Above B.R. Cabinets also now available, finished in high class veneers to match customers' individual furnishing schemes. Examples on view.

G.P.20 PICK-UPS with standard or L.P. head, **£3/11/5,** post 1/6, separate heads (Std. or L.P.), **£2/3/4,** post 8d.

WODEN OUTPUT TRANSFORMERS, high-grade, input to match two 6V6's or two 6L6's, output tapped 3, 7.5 and 15 ohms. **25/6,** post paid.

NORTHERN RADIO SERVICES
16 Kings College Road, London, N.W.3
Phone: PRImrose 8314

TAMSA

TAPE & WIRE RECORDING

We supply ALL RECORDING COMPONENTS. Write for Latest Price List of:—

TAPE MECHANISMS, TAPES, WIRES and SPOOLS, HEADS, AMPLIFIERS, OSCILLATOR COILS and UNITS.

NOW AVAILABLE—HIGH COERCIVITY TYPE H60 EMITAPE.

TOPHET M, High quality Recording Wire.

Constructors' Envelopes. Books on Tape Rec'd'g, Manufactured by

AUDIGRAPH LTD.

Dept. MR3, 74 Great Hampton Street, HOCKLEY, BIRMINGHAM, 18.

THE **VENTEX**
COLUMN REPRODUCER
• • •
A loudspeaker with all the qualities required for WIDE RANGE reproduction in the home.
- 1 sq. ft. FLOOR SPACE.
- 360° HIGH NOTE RADIATION.
- BUILT-IN DIFFUSER.
- RESPONSE 25-22,000 c.p.s.

Complete with TANNOY DUAL-CONCENTRIC UNIT
Price 45 gns. ex. works
C. T. CHAPMAN
(Reproducers) LTD. Pats. Pend.
RILEY WKS., RILEY ST., CHELSEA, S.W.10
FLAxman 4577/8
Demonstration at **Webb's Radio**, London.
Distributors for S. Wales :—
Snell & Haines, Ltd., 132, Western St., Swansea

TRANSFORMERS & COILS TO SPECIFICATION.
MANUFACTURED OR REWOUND
Filter Coils : a Speciality.
JOHN FACTOR LTD.
9-11 EAST STREET, TORQUAY, DEVON
'Phone : Torquay 2162

Special offer of **Electric Meters**, 2½in. scale, max. dia. 3¼in. **Milliammeters**, moving coil, 0-200 m.A. **Another**, 0-300 m.A., panel mounting. **Thermocouple R.F. Meters**, 0-6 amps. **Hot Wire Ammeters**, 0-9 amps. All the above **price 7/6**, post 9d.
D.C. Ammeters, moving iron, smaller, centre zero, 20-0-20 amps., bar mounting, suitable cars, chargers, etc., **7/6**, post 9d.
A.C. Voltmeters (will read D.C.), moving iron, 0-15 volts. **Price 9/6**, post 9d.
L. C. NORTHALL
14 Holly Road, Quinton, Birmingham, 32
Retail: 416 High Street, Smethwick. Phone: WOO 2106

"SENSITIVE TRF RECEIVER"
(Amos & Johnstone, November Issue)
SMITH'S
OF
EDGWARE ROAD
The Component Specialists
can supply ALL the parts, as used by the designers, for this amazing receiver.
Total cost about £7
Send for complete, priced, list of parts.
H. L. SMITH & CO. LTD.
287-9, EDGWARE ROAD, LONDON, W.2
Tel. Paddington 5891. Hours 9 to 6 (Thursday 1 o'clock)
Near Edgware Road Stations, Metropolitan and Bakerloo

SITUATIONS VACANT

A WELL-KNOWN progressive company has a vacancy in a rapidly expanding commercial department for a technical sales executive for radio and radar apparatus; candidates should have a good university degree together with industrial and/or Government experience, a methodical nature with a flair for organization, and a genuine interest in the varied types of work undertaken by sales engineers; importance will be attached to the adaptability of applicants and to their suitability to handle both technically and commercially a variety of equipments and to deal with customers at all levels; the post is permanent and has very good prospects for advancement; applications will be treated in strict confidence. Please forward detailed personal information and salary required to Box 6005. [4974

LIGHT electrical and electronic engineers required by Ministry of Supply in London and the provinces for the design, development, production and inspection of light and medium weight electrical, electro-mechanical, radio, radar and electronic equipment; airborne and portable, including servo systems and mechanisms, power supply (rotary and vibratory), radio communication, telemetry, circuit design (electronic), electronic valves and ammunition fuzes; qualifications: British, completion of apprenticeship and either be corporate members of one of the Institutions of Civil, Mechanical or Electrical Engineers or exempting qualifications, with appropriate experience in any of the above fields; an extensive knowledge of physics is essential for research and development in electronics; salary within the range £600-£1,450 p.a. (London) dependent on age, qualifications and experience; rates in provinces and for women slightly lower; not established, periodical competitions for established pensionable posts; paid sick leave, annual leave initially 25 days (30 in London) plus public holidays; normal working week 44 hours; application forms from Ministry of Labour and National Service, Technical and Scientific Register (K), Almack House, 26-28, King St., London, S.W.1, quoting D 408/51-A. [7986

VACANCIES exist for Production Inspectors at a number of Admiralty Establishments and in shipbuilding and industrial centres in various parts of the country. The duties involve work in connection with the manufacture, inspection, test and installation of a wide variety of mechanical, electrical and electronic equipment for H.M. ships. Candidates, who must be at least 25, should have served a recognisable engineering apprenticeship or have had equivalent training, followed by at least three years' relevant experience in industry or Government service. They should preferably be in possession of Higher National Certificate or equivalent; a lower qualification such as Ordinary National Certificate might, however, be considered. Ex-Service personnel with appropriate training and experience are eligible to apply. Appointments will be unestablished, but successful candidates will have opportunities at a later date of competing for permanent posts. The salary scale is £570 - £20 - £670 per annum and entry will be at the minimum, subject to a deduction of £20 for each year by which the age at entry falls short of 30. Rates outside London are a little lower. Write, quoting D.35/51-A, to the Ministry of Labour and National Service, Technical and Scientific Register (K), Almack House, 26, King St., S.W.1, for application form which must be returned completed by February 12, 1952. [7985

APPLICATIONS are invited by the Ministry of Supply for the following posts in the Experimental Officer class in the radio department of the Royal Aircraft Establishment, Farnborough: (1) Senior Experimental Officer to work on development of air and ground transmitters on V.H.F. and decimetre wavelengths and of various power levels; sound electrical and mechanical design ability is required in this field with thorough theoretical background, together with considerable experience of active development work on radio or electronics equipment; ref. A405/51-A. (2) Experimental Officer for work on the development of radio control and telemetering equipment and for supervision of relevant development contracts with industry; a sound knowledge of radio and light electrical engineering is essential and R/cos edge of telephone techniques (e.g. filters, relays, etc.) would be an advantage; ref. D579/51-A. (3) Assistant Experimental Officer for control tower work; candidates must have a sound knowledge of the basic principles of radio and radar, and practical experience of ground based radio communications equipment; radio navigation equipment and radar equipment, including planning of airfield radio installations, would be an advantage; ref. D580/51-A. (4) Assistant Experimental Officers for laboratory work on aeronautical radio communication, navigation and electronic equipment; duties are likely to include field investigations and observations in flight; ref. A406/51-A. Acceptable qualifications include Higher School Certificate with physics and mathematics as principal subjects, Grad. I.E.E. and Higher National Certificate in Radio or Electrical Engineering; a degree in physics or electrical engineering would be an advantage for some posts; salary will be assessed according to age, qualifications and experience within the ranges: Senior Experimental Officer (minimum age 35): £742 - £960; Experimental Officer (minimum age 28): £545—£695; Assistant Experimental Officer, £240 (at age 18)—£505; rates for women somewhat lower; the posts are unestablished.—Application forms obtainable from Technical and Scientific Register (K), Almack House, 26, King St., S.W.1, quoting appropriate reference no.; closing date 12th February, 1952. [7990

100 kcs. QUARTZ CRYSTAL UNIT *Type Q5/100*

for Secondary Frequency Standards
★ Accuracy better than 0.01%. ★ Temperature coefficient 2 parts in a million per degree Centigrade temperature change. ★ Gold electrodes applied by cathodic sputtering direct to the faces of the crystal, giving permanence of calibration. ★ Simple single valve circuit gives strong harmonics at 100 kcs. intervals up to 20 Mcs. ★ Octal based mount of compact dimensions. PRICE 45/- *Post Free*
Full details of the Q5/100 including circuit are contained in our leaflet Q1. Send stamp to-day for your copy.
THE QUARTZ CRYSTAL Co. Ltd.
63-71 Kingston Road
NEW MALDEN, SURREY
Telephone : MALden 0334

R. C. S.
Send stamp for new Catalogue giving range of prominent makers' components including
Coils, air spaced, all ranges. Coils, dust cored, all ranges. Coil Packs, I.F.'s, T.R.F. Coils, Chokes, Transformers, Speakers, Condensers, Resistors, Chassis, Dials etc. to
RADIO COMPONENT SERVICE,
68 Chesterfield Road, Leyton, E.10.

EXCEL SOUND SERVICES LTD.
are pleased to announce that they are now accepting orders for their Tape Recorders.
Trade enquiries invited
49, BRADFORD ROAD, SHIPLEY, YORKS.
Telephone: Shipley 55779 & 51291

Convert that old **Gramophone** OR OBSOLETE RADIOGRAM *into a* **MODERN All-WAVE RADIOGRAM** OR **POWERFUL RECORD PLAYER**

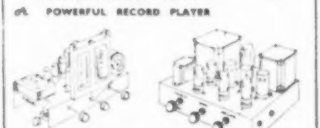

Our "Skyway" 9 **2/6** POST FREE

DESIGNS Book gives full details on how to build FOUR first-class Amplifiers and Radiogram chassis. No radio experience is required to understand the clear circuit diagrams and stage by stage wiring plans.

All parts and materials are easily obtainable, mostly without purchase tax. Performance equal to radiograms costing over £100

only from **Britch RADIOCRAFT Ltd** 69-71 CHURCH GATE LEICESTER PHONE 54971

OPPORTUNITIES IN RADIO

Get this FREE Book!

ENGINEERING OPPORTUNITIES' reveals how you can become technically qualified at home for a highly paid key-appointment in the vast Radio and Television Industry. In 144 pages of intensely interesting matter, it includes full details of our up-to-the-minute home study courses in all branches of **TELEVISION and RADIO, A.M. Brit. I.R.E., City & Guilds, Special Television, Servicing, Sound Film Projection, Short Wave, High Frequency, and General Wireless Courses.**

We definitely Guarantee

"NO PASS—NO FEE"

If you're earning less than £14 a week this enlightening book is for you. Write for your copy today. It will be sent **FREE** and without obligation.

BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY
Dept. 78A, ALEXANDRA HOUSE, 17-19 STRATFORD PLACE, LONDON, W.1

BIET

WILCO ELECTRONICS

TRANSMITTING UNIT.—AP.Q9, less Amplifier. A useful chassis for the Ham, **£3.** Carriage 7/6.

METAL RECTIFIERS.—12 v. 1 amp., **12/6**; 6 v. 1 amp., **10/6**; 48 v. 150 m.a., **10/-**; All Bridge type. Post 1/-.

ACCUMULATOR CHARGERS in black crackle case with fuses and meter. 6 and 12 volts at 4 amps. Bargain Price, **£4 19/6.** Pkg. and carr., **5/-.**

SLOW-MOTION DIALS, 6in. Scaled 0-100, reduction 200 to 1 or direct, ideal for wavemeters, signal generators, etc. Our price, while they last, **5/6** each, post 1/-.

"ELP" CIRCUIT BREAKER. 220 volts 2 amps., size 3 inches round, **10/6**, post 1/-.

KLAXON GEARED MOTORS No. IK55B3-W7. Torque 15 lbs. in., r.p.m. 175. Motor r.p.m. 1,400 at 230 v. A.C. Split phase induction type, **£10** each.

KLAXON CAPACITOR INDUCTION MOTORS with 4in. fan, 1/40 h.p. 200/240 v. A.C., 2,700 r.p.m. No. EM5CB2 with condenser, **55/-** each.

CUTTER HEADS.—"Recording" high impedance. Amazing bargain, **35/-** ea. Post 1/-.

CUTTERS STYLI, **6/-** per doz., large quantity available at special rates.

AIRCRAFT CLOCKS with splendid 8-day jewelled movement. Flange type, made to stringent Govt. specification. Brand new, guaranteed. Ideal for car, study, bedroom, etc. Special offer, **65/-** each. Post free.

P.M. SPEAKERS.—6½in. Rola in case with transformer and volume control, **40/-**. Post 1/6. Also 5in. Rola in wood cabinet, **17/6**. Post 1/6.

VOLTMETERS.—0-300 M.I. 3½in. flush or surface type, **22/6**. Post 1/6.

HAND MICROPHONES.—No. 3 with switch, flex and plug, **5/6**. Pos 1/-.

AERIAL RODS. 12" long, ¼" diameter. Any number of sections can be fitted together. **2/6** dozen; **6/-** for 3 dozen; **10/-** half gross; **20/-** gross.

204 LOWER ADDISCOMBE ROAD, CROYDON.

SITUATIONS WANTED

LIBRARIAN, retired 60, abstracting, classifying, patent work, seeks suitable post.—Box 6100. [7995

PRODUCTION manager, A.M.I.P.E., M.I.Ec.E., wide experience radio, television, radar, electronics, domestic appliances, requires responsible position London, car owner.—Box 6144. [8027

ELECTRONIC engineer (29), H.N.C., grad. I.E.E., desires responsible post in Home Counties, development experience on V.H.F. equipment, television and radar; present salary £550.—Box 6151. [8018

PATENTS

THE proprietor of British Patent No. 573315, entitled "Multiple Section Electronic Tube and Method of Making it," offers same for license or otherwise to ensure practical working in Great Britain.—Inquiries to Singer, Stern & Carlberg, 14, East Jackson Boulevard, Chicago 4, Illinois, U.S.A. [7950

THE proprietor of British Patent No. 609228, entitled "Improvements in arrangement for the remote control of a radio apparatus," offers same for license or otherwise to ensure its practical working in Great Britain.—Enquiries to Singer, Stern & Carlberg, Chrysler Building, New York 17, N.Y., U.S.A. [7713

THE proprietor of British Patents Nos. 613624, entitled "Improvements in transmitter-receiver combination," and No. 613217, entitled "Improvements in Radio Transmitting Receiving System," offers same for license or otherwise to ensure their practical working in Great Britain.—Inquiries to Singer, Stern & Carlberg, Chrysler Building, New York 17, N.Y., U.S.A. [8011

PAINTS, CELLULOSE, ETC.

PAINT spraying handbook 5/6, post free; cellulose and synthetic paints and all spraying requisites supplied; catalogue free.—Leonard Brooks, 55, Harold Wood, Romford. [0207

TECHNICAL TRAINING

CITY & Guilds (Electrical, etc.) on "no pass —no fee" terms; over 95% successes; for full details of modern courses in all branches of electrical technology send for our 144-page handbook—free and post free.—B.I.E.T. (Dept. 588A), 17, Stratford Place, London, W.1. [0117

INDUSTRY needs trained men, send for free brochure giving details of our Home Study Courses in radio, television and all branches of electronics; we prepare students for the A.M.Brit.I.R.E., City and Guilds Telecommunications, R.T.E.B., and other professional examinations. Train with the college backed by Britain's largest electronic industry.—Write to E.M.I. Institutes, Postal Division, Dept. WW33, 43, Grove Park Rd., London, W.4 (Associated with H.M.V.). [0179

TUITION

RADIO training.—P.M.G. exams. and I.E.E. Diploma; prospectus free.—Technical College, Hull. [0111

WIRELESS operating; attendance and postal courses.—Stamp for reply to Manager, The Wireless School, Manor Gdns., London, N.7.

NOTHING succeeds like success! What we have done a thousand times we can do again for you.—See the B.N.R.S. advt., page 104.

SEE the world. 600 Radio Officers required; send 2d stamp for prospectus to Britain's leading college; we train you in shortest period, at lowest cost.—Wireless College, Colwyn Bay.

A.M.I.Mech.E., A.M.Brit.I.R.E., City and Guilds etc. on "no pass—no fee" terms; over 95% successes; for details of exams. and courses in all branches of engineering, building, etc., write for 144-page handbook—free.—B.I.E.T. (Dept. 587B), 17, Stratford Place, London, W.1. [0118

TELEVISION postal course for radio trades Examination Board's diploma; also postal courses for P.M.G. 2nd and 1st class Certificates and Amateur Radio Transmitting licence.—Apply British School of Telegraphy, Ltd., 179, Clapham Rd., London, S.W.9. [40 years experience in coaching students in wireless telegraphy and allied subjects.] [0124

THE Institute of Practical Radio Engineers have available home study courses in every phase of radio and television engineering, specialising in the practical training of apprentices in the retail trade; enrolments limited; fees moderate.—The Syllabus of Instructional Text may be obtained post free from the Secretary, I.P.R.E., Fairfield House, 20, Fairfield Rd., Crouch End, London, N.8. [0088

FREE! Brochure giving details of home study training in radio, television and all branches of electronics; courses for the hobby enthusiast or for those aiming at the A.M.Brit.I.R.E., City and Guilds, Telecommunications, R.T.E.B., and other professional examinations; train with the college operated by Britain's largest electronic organization; moderate fees.—Write to E.M.I. Institutes, Postal Division, Dept. WW26, 43, Grove Park Rd., London, W.4. Chiswick 4417 (Associated with H.M.V.). [0001

PERSONAL

OPENING for active directorship in the company of Plomer & Wilkinson, Ltd., electrical engineers, 12/s, Charminster Rd., Bournemouth; first-class radio engineering, together with high-class business experience; fullest particulars and proposals to Company Secretary. [0009

What's our Line?

High Fidelity Equipment by,

LEAK. Tl/2 Amplifier with T.C. Unit	£37 16 0
V.-v. Radio Tuner Unit	£37 2 4
SOUND SALES. A.Z. Amplifier and Tone Colour Unit	£32 10 0
Tonemaster Amplifier and T.C. Unit	£25 0 0
D.S. Plus One Radio Tuner Unit	£22 14 7
ACOUSTICAL. Q.U.A.D. Amplifier and T.C. Unit	£35 0 0
Pre-set Radio Tuner	£26 0 0
ROGERS DEVELOPMENTS. Williamson Amplifier	£29 0 0
Baby De Luxe Amplifier with T.C. Unit	£25 10 0
B.D. Junior De Luxe with T.C. Unit	£17 10 0
GOODSELL. S.A.S. Amplifier	£15 15 0
Tone Control Unit	£6 10 0
V.-v. Radio Tuner	£19 10 0
ARMSTRONG. 7-valve Radiogram Chassis	£35 12 4
10-valve All wave Radiogram Chassis	£34 12 10
GOODMANS. Axiom 150 12in. Speaker Units	£10 5 6
Axiom 80, 12in. Units	£8 12 6
WHARFEDALE. W12/C.S. Speaker Units	£9 0 0
Super 12/C.S.A.L. Speaker Units	£15 0 0
TANNOY. 12in. Dual Concentric Speaker Unit	£27 10 0
BARKER. 150 12in. Loudspeaker Unit	£18 18 0
VOIGT. Domestic Corner Horn in whiter	£47 10 0
F.M. Unit with 25 k. line gap flux	£40 0 0
LEAK. Moving Coil Pick-up	£14 10 0
DECCA. X.M.S. Pick-up with 78 and L.P. Heads	£7 0 0
CONNOISSEUR. Super Lightweight pick-up	£6 9 0
ACOS. G.P./20 Super lightweight Crystal pick-up	£3 11 5
CONNOISSEUR. 2-speed A.C. Motors	£22 18 6
COLLARO. 3-speed Autochangers from	£11 16 9
RADIOGRAM CABINETS from	£12 12 0
CORNER SPEAKER CABINETS from	£7 10 0
GOLDRING. Three-way Lightweight Pickup.	
DECCA. G.U.4 Transcription type Player Units.	

Daily demonstrations of above equipment, hours 9.30 a.m.—6 p.m.; 9.30—1 p.m. Thursday at—

HOLLEY'S RADIO STORES,

285 CAMBERWELL ROAD, S.E.5.

Open all day Saturday. Callers only.

Phone: RODney 4988.

DUKE & CO.

SALVAGE RADIO-GRAM CHASSIS. Price **£9 17 6.** A.C. and Universal radio-gram chassis. Latest all wave 1952 models with pin-type Midget valves. Satisfaction guaranteed or money returned. Line up of valves and full particulars send without obligation. An opportunity to obtain a first-class set, made to sell at three times this price, which can be built into your own cabinet.

COLOURED FILTERS FOR TELEVISION SCREENS. A colour filter to suit the colour viewing pleasure. Gives beautiful colour tints to the picture, graduating from blue at the top, red in centre, to green at bottom. For 10in. screens, **10/6** ea., for 12in. screens, **12/6** ea.; for 15in. screens, **15/6**. When your friends see yours they will all want one.

BEDSIDE RADIO. Price **£5 12 6.** Our 4-valve T.R.F. Midget receiver which you can build yourself with the aid of our complete instructions, including point-to-point wiring. For A.C. or Universal. New and improved circuit. Choice of green, walnut or ivory plastic cabinet. At to-day's prices this is a real bargain. Postage and packing 2/6.

CONDENSERS. Electrolytic, 16 x 16 mfd. 500 v. D.C. **3/6** ea.; 12 + 12 mfd. 500 v. D.C., **4/9** ea.; 8 + 8 mfd. 350 v. D.C., **3/9** ea.; 8 mfd. 350 v. D.C., **2/9** ea.; 0.01 and 0.1 mfd., **20/-** per 100. Reas. 50 mfd. 12 v. D.C. **9d.** ea. Postage extra.

EARPHONES. Type D.L.R. 2 and D.L.R. 5, price **8/9** ea. A super-balanced sound-powered 'phone which is so sensitive that it can be used as a telephone without any batteries. We have a limited stock of these X.W.D. units in excellent condition. Postage 1/- per set.

WIRE-WOUND RESISTORS. Price **1/9** ea. Made by the International Resistance Company, Philadelphia. 1 watt, 1 per cent. accuracy. A precision job, wound on ceramic former, size 1¼in. long by 1in. dia. Postage 3d.

MIDGET SMOOTHING CHOKES. Price **1/6** ea., postage 6d. Made by well-known manufacturers tested and guaranteed.

RADIO CONTROL UNIT. Price **12/6**, postage 2/-. This unit which could be modified into a receiver or amplifier, has a chassis which fits into a metal cabinet of pleasing appearance, and includes a 3½in. tweeter speaker, 25 resistances, I.F. trans., 2 mst. type fuses, 7 v. holders (ceramic), 2 acorns (ceramic), 7 v. controls, relay, 2 on-ex. conn., partly wired, in clean condition.

BARGAINS IN WIRE. Nickel-chrome and spring steel wire—sizes .014in. and .022in. in 50-yd. and 30-yd. reels respectively. Spring steel wire, **1/-** per reel, 3 reels for **4/-**. Nickel chrome wire, **4/6** per reel. Postage 1/- per reel. Practically unobtainable to-day at these prices.

Mail orders: 621 Romford Road, Manor Park, London, E.12. GRA. 6477
Re all Sales: 219 ILFORD LANE, ILFORD, ESSEX. ILF. 0295

TRANSFORMERS

FOR ALL PURPOSES

SINGLY OR IN QUANTITIES
FROM OUR STANDARD RANGE
OR TO YOUR SPECIFICATIONS

GOOD DELIVERIES
REASONABLE PRICES

We have also a department for rewinds giving you a 24-hour service and a better job. Please label all burnt-outs with your name and address when despatching.

P. HOWORTH
51 POLLARD LANE · BRADFORD
Tel.: 37030

CABINETS FOR RADIOGRAMS
T.V. CONSOLES, REFLEX, ETC., ETC.

Send sketch for quotation for making to your requirements.
Ready made Radiogram cabinets from £15.0.0. in stock or early delivery

THE CHAFFEY CABINET CO.
6, SEFTON RD., PETTS WOOD, KENT
Telephone: Orpington 3559

YOU READ MUSIC ?

Then how about making yourself an electronic organ? Constructional data available—full circuits, drawings and notes. It has 5 octaves, 2 manuals and pedals with 24 stops—uses 43 valves. With its variable attack you can play Classics and Swing.

Write now for free booklet to: **C. S. Co.,**
10 Duke Street, Darlington, Durham.

FRENCH IMPORTER

disposing numerous licences, wants all British or American made radio-electrical equipment from Surplus Stocks: Transmitters and Receivers, Measuring Instruments, Valves, sundry Spare Parts, etc. Send offers to:

CIRQUE-RADIO
24 Boulevard des Filles-du-Calvaire, PARIS XI^e.
Telephone VOLTAIRE 22-76 and 22-77.

BOOKS, INSTRUCTIONS, ETC.

"RADIO Servicing." by Abraham Marcus. A practical guide to the methods of finding faults together with a concise technical background of theory and practice. 56/- (post free). —Write to Allen & Unwin, 40, Museum St., W.C.1, for descriptive leaflet. [7775

I.P.R.E. Technical Publications: 5,000 alignment peaks for superheterodynes, 4/9 post free. The Practical Radio Engineer, quarterly publication of the Institute: sample copy 2/- post free; membership and examination data 1/- post free.—Secretary, I.P.R.E., 20, Fairfield Rd., London, N.8. [0089

"PHOTOGRAPHIC Enlarging." By David Charles, F.R.P.S. 2nd Edition. The different types of enlargers are described and illustrated and the amateur is shown simply and clearly how to use them. 100 pp., 7½in x 5in. 4/6 net. By post 4/9 from all booksellers or The Publishing Dept., Dorset House, Stamford St., London, S.E.1. [F005

"PHOTOGRAPHIC Skies: How to Collect, Store and Use Them." By David Charles, F.R.P.S. Explains the technique by which the photographer can double-print cloud studies with other subjects to obtain attractive effects. 7½in x 5in., 120 pp., 5/- net. By post 5/5 from all booksellers or The Publishing Dept., Dorset House, Stamford St., London, S.E.1. [F004

BRASS, COPPER, DURAL, ALUMINIUM, BRONZE
ROD, BAR, SHEET, TUBE, STRIP, WIRE,
3,000 STANDARD STOCK SIZES
No Quantity too Small. List on application.
London: H. ROLLET & Co. Ltd. Liverp^l: 6, Chesham Place, S.W.1. Kirby Estate.
SLOane 3463 SIMONSWOOD 3271/3

AUTOMATIC SWITCHES
(RECONDITIONED)

ELECTRIC 1 to 100 AMPS. **CLOCKWORK** 7 to 35 DAYS

From **35/-** EACH

All guaranteed for a year.
Write for illustrated lists.

DONOHOE'S (Timers), 6, GEORGE ST., NORTH SHIELDS, NORTHUMBERLAND.

RADIO G200 OFFERS
Govt. Surplus Components, Special Purpose Transmitting, Obsolete Receiving Valves.
FG27a, 878a, 2A3, 803, WL2132 magnetron, HK304H, CV2, 725A, etc., available from Stock.
EXPORT—IMPORT. Enquiries also invited.
ARTHUR HOILE 56 UNION STREET, MAIDSTONE, KENT Telephone 2412, 2496

TANNOY
PRODUCTS
SOUND EQUIPMENT
clearly the best for all occasions
WEST NORWOOD S.E. 27

Radiospares' Quality Parts

THE SERVICE ENGINEER'S FIRST CHOICE

TOROIDAL WINDING CAPACITY AVAILABLE

BEL SOUND PRODUCTS CO.
Marlborough Yard, London, N.19
Tel: ARChway 5078

TESTOSCOPE *Mains Tester*

For high & low voltage testing:—
130 & 100/850 volts A.C. or D.C. Write for interesting leaflet 30F.

RUNBAKEN · MANCHESTER 1

ENGINEERS!

Whatever your age or experience, you must read "ENGINEERING OPPORTUNITIES." Full details of the quickest way to pass A.M.I.Mech.E., A.M.I.C.E., C. & G. (Electrical, etc.) General Cert., etc., on "NO PASS—NO FEE" terms and details of Courses in all branches of Engineering — Mechanical, Electrical, Civil, Auto., Aero., Radio, etc., Building, etc. If you're earning less than £14 a week, tell us what interests you and write for your copy of "ENGINEERING OPPORTUNITIES" today—FREE.

144 PAGES *Free!*

B.I.E.T.
387 Shakespeare Hse., 17-19 Stratford Place, London, W.1
BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

WALTON'S OF WOLVERHAMPTON

60 VOLT STANDARD H.T. BATTERIES. 6/-, post 1/-. 2 for 11/-, post 1/6. **72 VOLT** = 1½ **VOLT.** Layer Type. 6/-, post 9d.
2 WAY TELEPHONE SETS. Consisting of 2 Telemicrophones and approximately 12 yds. of twin cable. **10/6** each, post 1/6.
A.F.3. INTERVALVE TRANSFORMERS. 3/6 each, post 9d.
25 WATT "COLLINS" MODULATION TRANSFORMERS. Ratio 1-1. Impedance 6,000. New, boxed. **15/-** each, post 1/-.
4,000 OHM SUPER SENSITIVE PHONES. By S. G. Brown, complete with special ear-pads, lead, and plug. Brand new in boxes. **15/-** each, post 1/-.
POWERFUL 24 VOLT CAMERA MOTOR. A.C. or D.C. **15/-** each, post 1/6.
HEAVY DUTY 8in. EXTENSION SPEAKERS, 25/- each p. 1/-
2 VOLT ACCUMULATORS. Approx. 14 A.H. **5/-** each, post 1/6.
AERIAL RODS. 3 Tapered rods, screwed joints, assembled length 12ft., complete in fibre case. The finest rods made. **10/6** each, passenger train, **2/6.**

SEND S.A.E. and 3d. FOR SPECIAL LIST.

WALTON'S WIRELESS STORES, 48, STAFFORD STREET, WOLVERHAMPTON.

TRANSFORMERS
COILS
CHOKES

TRADE ENQUIRIES INVITED

SPECIALISTS IN
FINE WIRE WINDINGS
MINIATURE DEAF AID TRANSFORMERS, PICK-UP
CLOCK AND INSTRUMENT COILS, ETC

RADIOMENDERS LTD.
123-5-7 PARCHMORE ROAD, THORNTON HEATH, SURREY
LIVINGSTONE 2261 EST. 1933

RELAYS AND KEY SWITCHES

LARGEST EX-GOVT. STOCK IN GT. BRITAIN

Types 600-3000 Relays—Siemens High Speed
Also A.C. 400 volts 50 cycles

Uniselector Switches, Telephone Switch-boards, Telephone Components-Plugs, Jacks, Handsets — **Government Contractors.**

JACK DAVIS (RELAYS) LTD. (DEPT. W.)
36 PERCY STREET, LONDON, W.1
Phones : MUSeum 7960 LANgham 4821

PRATTS RADIO
1070 Harrow Road, London, N.W.10
(Nr. 'SCRUBBS LANE) Tel. LADbroke 1734

MODEL AC10E £9 18 6

AMPLIFIERS. College general purpose units. **MODEL AC10E**, 4 valve 10 watt. Neg feedback. **£9 18 6. MODEL AC15E**, 6 valve: 15 watt P.P output. Feedback over 3 stages. **£14 14 -. MODEL AC25E**, 25 watt: P.P output. Feedback over 3 stages. **£18 18 -. MODEL U10E**, for 100 AC mains, 6 valve 10 watt P.P output. Feedback over 3 stages. **£12 12 -.** All are complete with cases and chrome handles. They have a separate microphone stage. Separate inputs for mike and gram., allowing individual mixing, etc. Outputs match 3, 5 or 15 ohms speakers. Max. input volts required for full stated output average Mike .005, Gram. 3 v. **MODEL AC8C**, 5 valve P.P 8-10 watt unit for records, radio, etc. Feedback over 3 stages. Output to 3, 5, 15 ohms. **£9 18 6. MODEL AC4C**, 3 valve record/radio amplifier. 4 watts to 3 ohms. **£5 9 6.** Ditto U4C for 100 AC mains. **£5 9 6.** Stamp for list. Full range of accessories available including : Rothermel Crystal Mikes, **105 -**; Goodmans 12in. P.M. speaker, **£8 12 6** ; Collaro A.C. Record Players, rim drive, magnetic model, **£6 9 -**. Crystal, **£6 15 -**. Jack plugs **1 6** each extra.

All amplifiers are complete and ready for use.

CONDENSERS	Silver Mica · Tubular · Mansbridge
CRYSTALS	American · British
HEADPHONES	High and Low Impedance
METERS	Thermo·Moving Coil·Moving Iron
PLUG & SOCKETS	All Types
RESISTORS	Carbon and wire wound
VOLUME CONTROLS	Carbon and wire wound

We hold large and comprehensive stocks of new components and units, both Government and Manufacturers' Surplus

No. 19 Set, Equipment Available.

Wholesale and Export Only.

ANDERS RADIO LTD.
167 HAMPSTEAD ROAD, LONDON, N.W.1
EUS. : 1639 EST. 1928

TELEVISION

for "Fringe" and "Long distance" viewers is vastly improved with the SPENCER-WEST type AC/3 Pre-Amplifier. The specification includes a first stage neutralised triode cathode coupled to a grounded grid triode. The optimum arrangement for best "noise factor." Self-contained power supply unit complete with correctly adjusted interference filter. Price complete, **10 gns.**, from your Dealer or direct. Leaflets, etc., on request.

Conversion units type AC/4 for Holme Moss/London, or Sutton Coldfield or Sutton Coldfield/London, etc. Double oscillator mixer stage and R.F. stage for correct reception with absence of mixer noise and radiation to other receivers. Price complete with 5 valves and self-contained power supply unit, **15 gns.** Leaflets on request.

SPENCER - WEST
QUAY WORKS, GT. YARMOUTH
'Phone : Gt. Yarmouth 3009

POLYTHENE
H. F. EQUIPMENT
(AMBYTHENE BRAND)

COIL FORMERS
CHOKES
STAND-OFFS
FEED-THROUGHS

Send for Particulars and Samples

AMPLEX APPLIANCES (KENT) LTD.
19 DARTMOUTH ROAD, HAYES, BROMLEY, KENT
(RAVensbourne 5531)

WILKINSON'S of CROYDON

PHOTOMULTIPLIER No. 931A. Ideal for film scanning, spectography, Alpha counting, colorimetric measurement, etc., supplied complete in lightproof chamber with lamp, and wired with the complete resistor network, **90 -** post free.
SIGNAL AND NOISE GENERATOR. For Television frequencies 20-88 Mc/s in 4 Bands. Crystal controlled. Leaflet available on request. Price **£14 10 -.**
AUTO TRANSFORMER. 230/115 volts 500 watts 50 cycles, fully shrouded, new. Made by Met. Vic. **£4 10 -** each.
RECTIFIERS SELENIUM. ½ wave 12 v. 200 m.A., **2 6** each ; 240 v. 150 m.A., **12 2** each ; 336v. 75m.A., **9 9** each ; 444 v. 40 m.A., **9 3** each ; Voltage Doubler, 168 v. 40 m.A., **7 6** each ; 24 v. 2.5 amp. Funnel cooled, **87 -** ; Bridge type 24 v. 75 m.A., **3 4** each ; 36 v. 2.5 amp., **27 -** each ; 48 v. 75 m.A., **5 7** each ; 48 v. 150 m.A., **6 10** each 96 v 600 m.A., **31 -** each ; 96 v. 2.5 amp. **66 -** each.
TEST SET 205. Wavemeter range, 3.05 to 3.35 centimetres, built-in oscillator with 9 valves including Klystron type CV 129, etc., in good condition, **£20.**
We hold very large stocks of RELAYS, CONDENSERS, RACKS FOR 19in. PANELS, SLYDLOK FUSES, SANTON AND ARROW SWITCHES
19 LANSDOWNE ROAD, CROYDON CRO 0839

COILS • COILS • COILS

T.R.F. • SUPERHET • FILTERS • PACKS
TELEVISION COILS • I.F. TRANSFORMERS

FOR DEPENDABLE COMPONENTS CONTACT

OLYMPIC RADIO COMPONENTS

COIL WINDING SPECIALISTS & MANUFACTURERS
224, HORNSEY RD., N.7. **NORTH 2914**

ALL SECTIONS OF THE ELECTRONIC INDUSTRY IN THE U.K. AND OVERSEAS ARE INVITED

To send for our 1952 Wholesale Price List, giving full details of A.W.F. Loudspeaker replacement Cone assemblies, for quick, cheap, repairs in your own N'shops. A.W.F. Chokes and Transformers for all Electronic replacements. A.W.F. Repairs to Speakers, Transformers, Vac. motors, Gram motors, etc., Current stocks of Tungsram and other valves. T.C.C. and Dubilier capacitors, Erie Resistors and Pots. Brass B.A. Screws and nuts. Tallon Cabinets and all the specified components for View Master and Electronic Engineering Televisors, and hundreds of bargain lines. Viewmaster envelopes, etc., for Kirk O' Shotts now available. We specialise in giving overseas dealers rapid service, and have full experience of all export packings.

SEND YOUR TRADE CARD (Trade Only Supplied), with 3d. Inland U.K. or 2/- Overseas Air Mail (stamps or P.O.).

A.W.F. RADIO PRODUCTS
TATLER CHAMBERS THORNTON ROAD
BRADFORD YORKS
TEL. 24008 GRAMS & CABLES "TESTUBE"

INDEX TO ADVERTISERS

	PAGE
Acoustical Mfg. Co., Ltd.	29
Advance Products, Ltd.	96
Advance Components, Ltd.	51
Arrlaite, Ltd.	20
Allan, Richard, Radio, Ltd.	50
Allen Components, Ltd.	107
All-Power Transformers, Ltd.	46
Alpha Radio Supply Co., The	105
Altham Radio Co.	92
Ambassador Radio	28
Ampiex Appliances (Kent), Ltd.	117
Amplivox, Ltd.	98
Anders Radio, Ltd.	117
Antiference, Ltd.	12
Armstrong Wireless & Television Co., Ltd.	105
Ashworth, H.	90
Audigraph, Ltd.	115
Audio-Acoustic Diffusers, Ltd.	56
Automatic Coil Winder & Electrical Equipment Co., Ltd., The	1
Automatic Telephone & Electric Co., Ltd.	19
A.W.F. Radio Products	117
Bakers "Selhurst" Radio	50
B. & H. Radio	111
Barker Natural Reproducers	105
Bel Sound Products, Ltd.	116
Belling & Lee, Ltd.	69
Bennett College, Ltd., The	26
Berry's (Short Wave), Ltd.	50
Bird, B. S., & Sons, Ltd.	52
Birmingham Sound Reproducers, Ltd.	64
Bradmatic, Ltd.	56
Brandenoers Designs, Ltd.	90
Britain, Chas. (Radio), Ltd.	97
British Communications Corpn., Ltd.	58
British Institute of Engineering Technology	115, 116
British Insulated Callender's Cables, Ltd.	Cover ii
British National Radio School	104
British Physical Laboratories	14, 54
British Sarosa, Ltd.	96
Broadcaster Radio Supplies, Ltd.	18
Brookes Crystals, Ltd.	112
Brown, S. G., Ltd.	56
Buchan, A. E.	108
Bulgin, A. F., & Co., Ltd.	Edit. 81, 118
Bull, J., & Sons	24
Bullers, Ltd.	10
Candler System Co.	112
Caxton Publishing Co., Ltd.	76
Chaffey Cabinet Co., The	116
Champion Products	112
Chapman, C. T. (Reproducers), Ltd.	114
Charles Cook's Furnishing Stores, Ltd.	94
Cinema-Television, Ltd.	51
Cirque-Radio	116
Classic Electrical Co., Ltd.	101
Clydesdale Supply Co.	82
Cohen, D.	91
Cosmocord, Ltd.	60
Cossor, A. C., Ltd.	75
C.S. Company	116
Davis, Alec, Supplies, Ltd.	92, 105
Davis, Jack (Belavel), Ltd.	117
Day, Will, Ltd.	60
Donohoe's (Timers)	116
Dubilier Condenser Co. (1925), Ltd.	45
Duke & Co.	115
Dupley Electronics, Ltd.	110
Edison Swan Electric Co., Ltd.	39
Egen Electric, Ltd.	59
Electradix Radios	108
Electro Acoustic Developments	100
Electro Acoustic Industries, Ltd.	65
Electronic Precision Equipment	78, 79, 80, 81
Elm Electric Co.	48
E.M.G. Handmade Gramophones, Ltd.	110
E.M.I. Institutes	48, 62, 76
Enthoven, H. J., & Sons, Ltd.	12
Excel Sound Services, Ltd.	114
Factor, J., Ltd.	114
Farmer, John	109
Ferranti, Ltd.	15
Fielden (Electronics), Ltd.	65
Fluxite, Ltd.	104
Foyle, W. & G., Ltd.	118
Frith Radiocraft, Ltd.	80, 114
Galpins	107
Garland Bros.	88, 89
Gee Bros. Radio, Ltd.	109
General Electric Co., Ltd.	55
Glaser, L. F.	111
Goodmans Industries, Ltd.	13
Goodsell, Ltd.	106
Grampian Reproducers, Ltd.	54
Gray, Arthur, Ltd.	40
Hall Electric, Ltd.	55
Hallam, Sleigh & Cheston, Ltd.	44
Hanney, L. F.	58
Hartley, H. A., Co., Ltd.	100
Hayes Co., Ltd.	106
Haynes Radio, Ltd.	108
Henley's, W. T., Telegraph Works Co., Ltd.	104
Henry's	93
Hivac, Ltd.	91
Hogg, F. Livingston	26
Holle, Arthur	116
Holley's Radio Stores	115
Homelab Instruments, Ltd.	42
Howorth, P.	116
H.P. Radio Services, Ltd.	97
Hunt, A. H., Ltd.	17
Hyde, J. B., & Co., Ltd.	56
Iliffe & Sons, Ltd.	22
International Correspondence Schools	52
Kolestric, Ltd.	113
Ladd, J. C., Wholesale	108
Lasay's Radio	83, 84, 85
Leak, H. J., & Co., Ltd.	77
Lewis Radio Co.	110
Lockwood, & Co.	106
London Central Radio Stores	59
Lowther Mfg. Co.	24
L.R. Supply Co., Ltd.	61
Lyons Radio	110
Mail Order Supply Co.	8, 9
Marconi Instruments, Ltd.	57
Marconi's Wireless Telegraph Co., Ltd.	53, 70, 73
Marks, C., & Co.	96
Masteradio, Ltd.	40
McElroy-Adams Mfg. Group, Ltd.	94
McMurdo Instruments Co., Ltd.	10
Measuring Instruments (Pullin), Ltd.	98
Miers, N., & Co., Ltd.	54
Minnesota Mining & Mfg. Co., Ltd.	49
Modern Book Co.	102
Modern Electrics, Ltd.	58
M.R. Supplies, Ltd.	28
M.S.S. Recording Co., Ltd.	27
Mullard, Ltd.	3, 56, 66
Multicore Solders, Ltd.	Cover iv
Murex, Ltd.	34
Newman, J., & S., Ltd.	20
Northall, L. C.	112
Northern Radio Services	113
Nusound Products	111
Oddie, Bradbury & Cull, Ltd.	110
Olympic Radio Components	117
Osmor Radio Products, Ltd.	46
Park Radio, Ltd.	54
Partridge Transformers, Ltd.	99
P.C.A. Radio	98
Pearce, T. W.	106
Philips Electrical, Ltd.	22, 103
Post Radio Supplies	44, 108
Pratts Radio	117
Premier Radio Co.	5, 6, 7
Pye Telecommunications, Ltd.	25
Quartz Crystal Co., Ltd.	114
Radio Component Service	114
Radio & Electrical Mart, The	96
Radio Exchange Co.	96
Radiomenders, Ltd.	116
Radio Merchandise Co., Ltd.	102
Radio Servicing Co.	102
Radiospares, Ltd.	116
Radio Supply Co.	95
Radio Traders, Ltd.	94
Record Electrical Co., Ltd., The	54
Redfon, Ltd.	14
Reproducers and Amplifiers, Ltd.	46
Roding Laboratories	62
Rogers Developments Co.	58
Rola Celestion, Ltd.	52
Rollet, H., & Co., Ltd.	116
Royal Air Force, The	4
Rubber Bonders, Ltd.	21
Rumbaken Electrical Products	106, 116
Salford Electrical Instruments, Ltd.	41
Sallis, A. T.	112
Salway Morgan & Co., Ltd.	28
Samsons Surplus Stores	106
Sangamo Weston, Ltd.	74
Savage Transformers, Ltd.	102
Scharf, Erwin	60
Sifam Electrical Instruments Co., Ltd.	18
Simmonds Aerocessories, Ltd.	25
Simon Sound Service	11
Smith, G. W. (Radio), Ltd.	101
Smith, H. L., & Co., Ltd.	114
Sound Sales, Ltd.	74
Southern Radio Supply, Ltd.	113
Spencer-West	117
Sphere Radio, Ltd.	24
Stability Radio Components, Ltd.	30
Standard Telephones & Cables, Ltd.	47, 67, 72
Starr British Products	100
Steatite & Porcelain Products, Ltd.	45
Stern Radio, Ltd.	86, 87
Sugden, A. R. & Co. (Engineers), Ltd.	42
Supacoils	111
Szymanski, S.	95
Tannoy Rentals, Ltd.	116
Taylor Electrical Instruments, Ltd.	57
Telecraft, Ltd.	16, 110
Telegraph Condenser Co., Ltd.	Cover iii
Telegraph Construction & Maintenance Co., Ltd., The	60
Tele-Radio (1943), Ltd.	58
Telerection, Ltd.	32
Thermionic Products, Ltd.	40
Trix Electrical Co., Ltd.	Edit. 79
Uncles, Bliss & Co., Ltd.	42
University Electrical Instruments Corpn.	90
University Radio, Ltd.	92
Valradio, Ltd.	26
Venner Accumulators, Ltd.	2
V.E.S. Wholesale Services, Ltd.	98
Vitavox, Ltd.	48
Voigt Patents, Ltd.	112
Vortexion, Ltd.	71
Walton's Wireless Stores	116
Wayne Kerr Laboratories, Ltd., The	52
West End Radio, Ltd.	106
Westinghouse Brake & Signal Co., Ltd.	62
Wharfedale Wireless Works	44, 54
Whiteley Electrical Radio Co., Ltd.	33
Wilco Electronics	115
Wilkinson, L.	117
Wolf Electric Tools, Ltd.	16
Wright & Weaire, Ltd.	76
Young, C. H.	96

THE WORLD'S GREATEST BOOKSHOP

FOYLES

FOR BOOKS

Stock of over 3 million volumes

New, secondhand and rare books on every subject. Large Technical department.

Subscriptions taken for magazines.

119-125 CHARING CROSS ROAD LONDON W.C.2

Gerrard 5660 (16 lines) ★ Open 9-6 (inc. Sats.)

Printed in Great Britain for the Publishers, ILIFFE & SONS LTD., Dorset House, Stamford St., London, S.E.1, by CORNWALL PRESS LTD., Paris Gardens, London, S.E.1. *Wireless World* can be obtained abroad from the following: AUSTRALIA AND NEW ZEALAND: Gordon & Gotch, Ltd. INDIA: A. H. Wheeler & Co. CANADA: The Wm Dawson Subscription Service Ltd. SOUTH AFRICA: Central News Agency, Ltd. UNITED STATES: The International News Co.

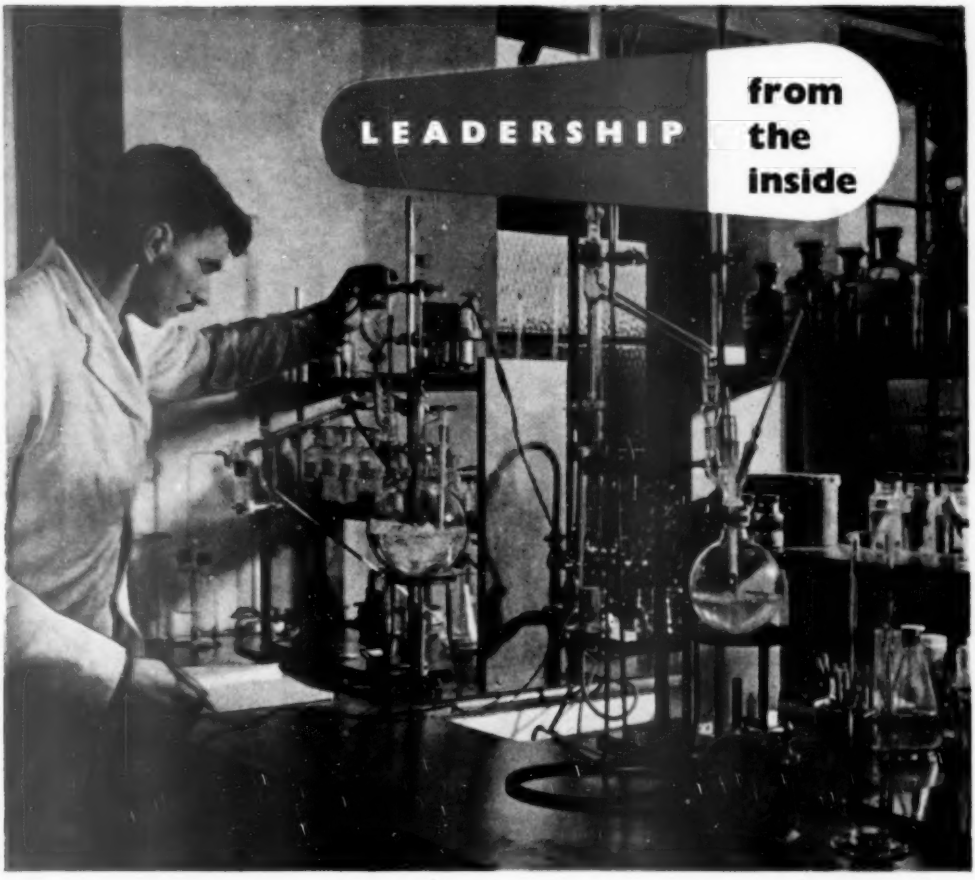

Quest and Test—symbols of Condenser Perfection

The task of the laboratory worker is often dull: only occasionally do the results of some original work assume proportions sufficient to glorify his monotonous routine.

We test all raw materials before approving them for use, and test to destruction all new types developed by the designs department. These are everyday tasks, but our chemists also carry out research on new materials which may result in the adoption of an entirely new manufacturing technique.

Research can never reach finality: it must keep abreast — and indeed ahead — of changing conditions and fresh applications.

SPECIALISTS IN CONDENSERS SINCE 1906

THE TELEGRAPH CONDENSER CO. LTD · *RADIO DIVISION* · LONDON W.3 · Tel: ACORN 0061 (9 lines)

Wherever dependable soldering is essential

Ersin Multicore is the solder used

Just *one* dry joint can seriously affect the reception of a radio or television set or impair the efficiency of other electrical equipment. Leading manufacturers all over the world, knowing they cannot risk injury to their reputation, eliminate the possibility of faulty connections by using Ersin Multicore—the finest cored solder ever made.

Ersin Multicore is the only solder containing three cores of exclusive, extra-active, non-corrosive Ersin Flux, which ensures instantaneous melting, guaranteed flux continuity and complete freedom from "dry" or H.R. joints. Ersin Multicore not only removes surface oxides but also prevents oxidation during soldering.

RADIO. An operative using Ersin Multicore Solder in the factory of Bang & Olufsen, Struer—one of Denmark's largest radio manufacturers.

TELEVISION. This single unit of the famous Pye Portable Television Transmitting Equipment has more than 3,000 Ersin Multicore soldered joints.

ELECTRONIC COMPONENTS. Ersin Multicore is used in large quantities by H. Karayannis & Co., Athens, the leading electronic distributors in Greece.

ELECTRIC MOTORS. At the Normand Electrical factory, London, an operative using Ersin Multicore to solder connections to commutator bars on lap-wound armatures for Neco fractional horse-power motors.

TELEPHONE EQUIPMENT. Ersin Multicore being used to solder switchboard apparatus at Autelca Mediterranea, S.A.T.A.P.—one of Italy's largest manufacturers of telephone equipment.

ELECTRIC LAMPS. The Johannesburg factory of African Lamps Ltd., where Ersin Multicore is used for soldering the cap connections by hand.

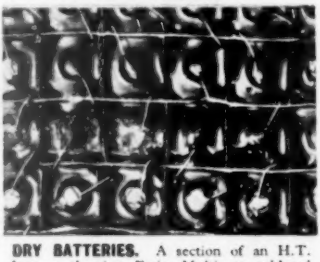

DRY BATTERIES. A section of an H.T. battery showing Ersin Multicore soldered joints on the top of the cells. In addition, each wire is soldered to the side of each battery can.

We will be pleased to send to manufacturers, free of charge, new technical literature and bulk prices. Service engineers, radio and television enthusiasts can obtain Size 1 cartons from most radio and electrical shops.

SIZE 1 CARTONS—5/- RETAIL

Catalogue Ref. No.	Alloy Tin/Lead	S.W.G.	Approx. Length per Carton
C 16014	60/40	14	13 feet
C 16018	60/40	18	37 feet
C 14013	40/60	13	13 feet
C 14016	40/60	16	26 feet

Ersin Multicore Solder

The Finest Cored Solder in the World

MULTICORE SOLDERS LTD., MELLIER HOUSE, ALBEMARLE ST., LONDON, W.1. • TEL. REGent 1611